

EE434

ASIC and Digital Systems

Midterm Exam 2

Mar. 31, 2017. (4:10pm – 5pm)

Instructor: Dae Hyun Kim (daehyun@eecs.wsu.edu)

Name:

WSU ID:



Problem	Points	
1	10	
2	10	
3	10	
4	10	
5	10	
Total	50	

* Allowed: Textbooks, cheat sheets, class notes, notebooks, calculators, watches

* Not allowed: Electronic devices (smart phones, tablet PCs, laptops, etc.) except calculators and watches

  Problem #1 (Layout, 10 points).


Represent *Out* as a Boolean function of *A, B, C, D, E, F*.




$$Y = \overline{(A + B + C)} \cdot (D + E + F)$$

 Problem #2 (DC Characteristics, 10 points).


An infinite chain of inverters is defined as follows:



 All the inverters are identical, i.e., have the same characteristics. The above chain is modeled as a block diagram as follows:



 where $Noise\ k$ is the k -th noise and $Source$ is a signal generator and $V_{Source} = V_{DD} \cdot u(t)$ (i.e., 0 if $t < 0$ and V_{DD} if $t \geq 0$). $V_{DD} = 1V$. The DC characteristic of an inverter is approximated using three segments as follows (If $V_{in} \geq V_{DD}$, $V_{out} = 0$. If $V_{in} \leq 0$, $V_{out} = V_{DD}$):



- 1) $V_{out} = \frac{V_{OH} - V_{DD}}{V_{IL}} \cdot V_{in} + V_{DD}$
- 2) $V_{out} = \frac{V_{OL} - V_{OH}}{V_{IH} - V_{IL}} \cdot (V_{in} - V_{IH}) + V_{OL}$
- 3) $V_{out} = -\frac{V_{OL}}{V_{DD} - V_{IH}} \cdot (V_{in} - V_{DD})$

Each noise source is an independent voltage signal and its range is as follows ($V_N > 0$):

- $|V_{noise}| \leq V_N$

Compute the max. value of V_N that does not cause signal inversion for the following two cases (Note: Signal inversion occurs if a signal reaches 0.5V when it should be 0 or 1):

- Case 1) $V_{OL} = 0V, V_{OH} = 1V, V_{IL} = 0.4V, V_{IH} = 0.6V$
- Case 2) $V_{OL} = 0V, V_{OH} = 1V, V_{IL} = 0.4V, V_{IH} = 0.8V$


Case 1) In this case, $y = -5x + 3$ in Region 2. The high noise margin is $0.4V$, so is the low noise margin. Suppose V_N is $(0.4 + \delta)V$ where $\delta > 0$. Let's take a look at the worst cases.

- Input of inverter m: $1V$
- Output of inverter m: $0V$
- Input of inverter (m+1): $(0.4 + \delta)V // a(n) = 0.4 + b(n)$
- Output of inverter (m+1): $(1.0 - 5\delta)V // -5a(n) + 3 = 1 - 5b(n)$
- Input of inverter (m+2): $(0.6 - 6\delta)V // -5a(n) + 2.6 - \delta = 0.6 - 5b(n) - \delta$
- Output of inverter (m+2): $(30\delta)V // 25a(n) - 10 + 5\delta = 25b(n) + 5\delta$
- Input of inverter (m+3): $(0.4 + 31\delta)V // a(n+1) = 25a(n) - 9.6 + 6\delta = 0.4 + 25b(n) + 6\delta \rightarrow b(n+1) = 25b(n) + 6\delta, a(n+1) = 0.4 + b(n+1)$
- ...

$a(n+1) = 0.4 + b(n+1)$ and $b(n+1) = 25b(n) + 6\delta$. Since $b(n)$ goes to infinity as n increases, so signal inversion happens.

If V_N is $0.4V$

 
- Input of inverter m: $1V$
- Output of inverter m: $0V$
- Input of inverter (m+1): $0.4V$
- Output of inverter (m+1): $1V$
- Input of inverter (m+2): $0.6V$
- Output of inverter (m+2): $0V$
- Input of inverter (m+3): $0.4V$
- ...



Thus, if $\delta > 0$, signal inversion will eventually occur no matter how small δ is. Thus, the maximum V_N is $0.4V$ in this case.

Case 2) In this case, $y = -2.5x + 2$ in Region 2. When the output is 0.4V, the input voltage is 0.64V. Suppose V_N is $X(V)$ where X is between 0.2V and 0.4V. Let's take a look at the worst cases.

 - Input of inverter m: 1V
- Output of inverter m: 0V
- Input of inverter (m+1): $X(V)$
- Output of inverter (m+1): 1V
- Input of inverter (m+2): $(1 - X)V$
- Output of inverter (m+2): $(-0.5 + 2.5X)V$
- Input of inverter (m+3): $(-0.5 + 3.5X)V$



If $(-0.5 + 3.5X)V$ is greater than 0.4V, the output voltage is less than 1V, then a positive feedback loop is formed, so we solve the following inequality:


$$(-0.5 + 3.5X)V \leq 0.4V$$

Thus, $V_N \approx 0.257V$.

 Problem #3 (Elmore Delay, 10 points).

The RC tree shown below has two delay constraints as follows:

- The delay from the driver to V_{L1} should be less than or equal to $900ps$.
- The delay from the driver to V_{L2} should be less than or equal to $6823ps$.




Currently, the delay at V_{L1} is $1k * 11f + 1k * 12f + \dots + 1k * 29f + 1k * 59f + 1k * 60f + \dots + 1k * 79f = 1829ps$, so is the delay at V_{L2} .

You are supposed to insert only one buffer in the RC tree to satisfy the delay constraints at both V_{L1} and V_{L2} . You can insert the buffer only into one of the designated nodes ($n1 \sim n60$). The buffer has the following characteristics:

- Input capacitance: $10fF$
- Internal delay: $20ps$
- Output resistance: $1k\Omega$

 When you insert a buffer into a node, the RC tree before and after the buffer are separated as follows (assuming the buffer is inserted into $n2$ in the figure above):



In this case (inserting a buffer into n2), the delay at V_{L1} is $[1k * 11f + 1k * 12f + \dots + 1k * 29f + 1k * 59f + 1k * 60f + \dots + 1k * 77f + 1k * 77f] + [20ps] + [1k * 11f + 1k * 12f] = (1749 + 20 + 23)ps = 1792ps$, so is the delay at V_{L2} . As you see, the delay is reduced from $1829ps$ to $1792ps$.

Insert a buffer into one of the nodes (n1 ~ n60) so that it satisfies the delay constraints at both V_{L1} and V_{L2} . Then, compute the Elmore delay at V_{L1} .

(Help: The sum of $a, a + 1, a + 2, \dots, n$ is $\frac{(n+a)(n-a+1)}{2}$. For example, $5 + 6 + \dots + 10 = \frac{(10+5)(10-5+1)}{2} = 45$.)

If I insert a buffer into node n21, the delay at V_{L1} is

$$\begin{aligned} & (1k * 11f + 1k * 12f + \dots + 1k * 29f + 1k * 29f) + (20ps) \\ & + (1k * 40f + 1k * 41f + \dots + 1k * 60f) \\ & = (380ps + 29ps) + (20ps) + (1050ps) = 1479ps \end{aligned}$$

If I insert a buffer into node n41, the delay at V_{L1} is

$$\begin{aligned} & (1k * 11f + 1k * 12f + \dots + 1k * 29f) + (1k * 40f + 1k * 41f + \dots + 1k * 60f) \\ & = (380ps) + (1050ps) = 1430ps \end{aligned}$$

If I insert a buffer into node n20, the delay at V_{L1} is

$$\begin{aligned} & (1k * 11f + 1k * 12f + \dots + 1k * 29f) + (1k * 59f) + (1k * 59f) + (20ps) \\ & + (1k * 11f + 1k * 12f + \dots + 1k * 30f) \\ & = (380ps) + (59ps) + (59ps) + (20ps) + (410ps) = \mathbf{869ps} \end{aligned}$$

If I insert a buffer into node n19, the delay at V_{L1} is

$$\begin{aligned} & (1k * 11f + 1k * 12f + \dots + 1k * 29f) + (1k * 59f) + (1k * 60f) + (1k * 60f) + (20ps) \\ & + (1k * 11f + 1k * 12f + \dots + 1k * 29f) \\ & = (380ps) + (59ps) + (60ps) + (20ps) + (380ps) = \mathbf{899ps} \end{aligned}$$

Node: n20 or n19

Elmore delay at V_{L1} : 869ps or 899ps

Problem #4 (Pseudo-nMOS, 10 points).

Draw a pseudo-nMOS schematic for $Y = \overline{A \cdot B \cdot C + (D + E) \cdot F}$ and properly size the nFETs to achieve the following output level for logic output 0:

- $V_{out} \leq 0.1V_{DD}$

Use the following parameters:

- Resistance of a $1 \times$ nFET = Resistance of a $2 \times$ pFET
- The size of the pFET: $4 \times$
- Do not use the transistor-mode-based computation for sizing. You can just use the resistance values for sizing.
- Do not oversize the nFETs.


The resistance of the pFET is $R_n/2$ where the resistance of a $1X$ nFET is R_n . Suppose the resistance of an nFET path is R_k . Then, $\frac{R_k}{(\frac{R_n}{2} + R_k)} \leq 0.1$, so $R_k \leq \frac{1}{18}R_n$.

For $A=B=C=1$:

$$3 \cdot R = \frac{1}{18}R_n \Rightarrow R = \frac{1}{54}R_n \Rightarrow A = B = C = 54 \times$$


For $F=1$ and $(D \text{ or } E=1)$:
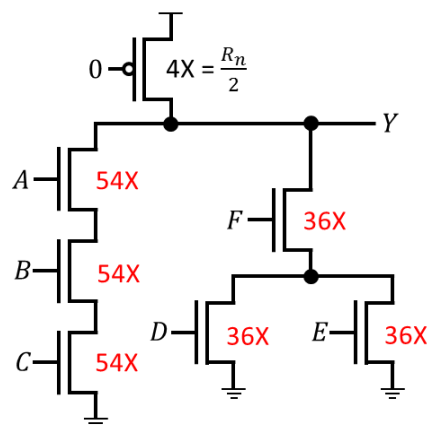
$$2 \cdot R = \frac{1}{18}R_n \Rightarrow R = \frac{1}{36}R_n \Rightarrow D = E = F = 36 \times$$



 Problem #5 (Capacitive Coupling, 10 points).

The following figure models the coupling effect between two adjacent wires.



$V_1(t)$ is an aggressor and $V_2(t)$ is a victim. $V_2(t)$ is as follows:

$$V_2(t) = \frac{V_{DD}}{2} \left[e^{-\frac{t}{\tau_1}} - e^{-\frac{t}{\tau_2}} \right] u(t)$$

where

- $\tau_1 = R(C + C_L + 2C_C)$
- $\tau_2 = R(C + C_L)$

In this case, the max. value of $V_2(t)$ is found by differentiating $V_2(t)$ with respect to t . The max. value occurs when t is

$$t_{max} = \frac{R(C + C_L)(C + C_L + 2C_C)}{2} \cdot \ln \frac{C + C_L + 2C_C}{C + C_L}$$

and the max. value of $V_2(t)$ is

$$V_{2,max} = \frac{V_{DD}}{2} \cdot \left(1 - \frac{\tau_2}{\tau_1} \right) \cdot \left(\frac{\tau_2}{\tau_1} \right)^{\frac{\tau_2}{2RC_C}}$$

Answer the following questions (Hint: Use the above formula or your intuition to solve this problem):

- If C_C increases, $V_{2,max}$ increases. (True/False)
- If C increases, $V_{2,max}$ increases. (True/False)
- If C_L increases, $V_{2,max}$ increases. (True/False)
- If R increases, $V_{2,max}$ increases. (True/False)
- The max. value of $V_2(t)$ can be greater than $V_{DD}/2$. (True/False)

(Hint: $\lim_{x \rightarrow \infty} \left(\frac{1}{x}\right)^{\frac{1}{x}} = 1$. $\lim_{x \rightarrow \infty} \left(\frac{x}{x+c}\right)^{\frac{x}{c}} = e$. $\left(\frac{x}{x+c}\right)^{\frac{x}{c}} > 1$. (when $c > 0$))

$$V_{2,max} = \frac{V_{DD}}{2} \cdot \left(1 - \frac{C + C_L}{C + C_L + 2C_C}\right) \cdot \left(\frac{C + C_L}{C + C_L + 2C_C}\right)^{\frac{C+C_L}{2C_C}}$$

$$\left(1 - \frac{C+C_L}{C+C_L+2C_C}\right) = a, \quad \frac{C+C_L}{C+C_L+2C_C} = b, \quad \text{and} \quad \frac{C+C_L}{2C_C} = d.$$

- If C_C increases, a approaches 1 and b and d approach 0, so b^d approaches 1. Thus, $V_{2,max}$ increases (approaches $\frac{V_{DD}}{2}$).
- If C increases, a approaches 0 and b^d approaches e , so $V_{2,max}$ decreases (approaches 0).
- C_L and C are interchangeable, so if C_L increases, $V_{2,max}$ decreases (approaches 0).
- $V_{2,max}$ does not include R , so it does not increase even if R increases.
- a is less than 1. b^d is less than 1. Thus, $V_{2,max}$ is less than $V_{DD}/2$.