
EE434
ASIC & Digital Systems

Testing for Single-Stuck Faults

Spring 2016
Dae Hyun Kim
daehyun@eecs.wsu.edu

Definition of Automatic Test-Pattern Generator (ATPG)

- **Operations on digital hardware:**
 - Inject fault into circuit modeled in computer
 - Use various ways to activate and propagate fault effect through hardware to circuit output
 - Output flips from expected to faulty signal
- ***Electron-beam (E-beam) test*** observes internal signals – “picture” of nodes charged to 0 and 1 in different colors
 - Too expensive
- ***Scan design*** – add test hardware to all flip-flops to make them a giant shift register in test mode
 - Can shift state in, scan state out
 - Widely used – makes sequential test combinational
 - Costs: 5 to 20% chip area, circuit delay, extra pin, longer test sequence

Test Generation

- Controlling value c
 - determines the value of the gate output regardless of the values of the other inputs.
 - A control value on an input of a gate blocks propagation of faults from other inputs.
- Inversion i
 - Inversion value of a gate is 0 if no inversion is done (otherwise 1).
 - The output value is $c \oplus i$.

	c	i
AND	0	0
OR	1	0
NAND	0	1
NOR	1	1

Test Generation

- Composite logic values & 5-valued operations

v/v_f	
0/0	0
1/1	1
1/0	D
0/1	\bar{D}

AND	0	1	D	\bar{D}	x
0	0	0	0	0	0
1	0	1	D	\bar{D}	x
D	0	D	D	0	x
\bar{D}	0	\bar{D}	0	\bar{D}	x
x	0	x	x	x	x

Test Generation

- Composite logic values & 5-valued operations

v/v_f	
0/0	0
1/1	1
1/0	D
0/1	\bar{D}

OR	0	1	D	\bar{D}	x
0	0	1	D	\bar{D}	x
1	1	1	1	1	1
D	D	1	D	1	x
\bar{D}	\bar{D}	1	1	\bar{D}	x
x	x	1	x	x	x

Test Generation

- Generate a test for l s-a- v .

set all values to x

Justify (l, \bar{v})

if $v = 0$, **then**

Propagate (l, D)

else

Propagate (l, \bar{D})

Justify (l, v)

set l to v

if l is a PI, **then return**

// now l is a gate (output)

c = controlling value of l

i = inversion of l

$inval = v \oplus i$

if $inval = \bar{c}$, **then**

for every input j of l

Justify ($j, inval$)

else

 select one input (j) of l

Justify ($j, inval$)

Propagate (l, err)

set l to err

if l is a PO, **then return**

k = the fanout of l

c = controlling value of k

i = inversion of k


for every input j of k other than l

Justify (j, \bar{c})

Propagate ($k, err \oplus i$)


Test Generation

- Example

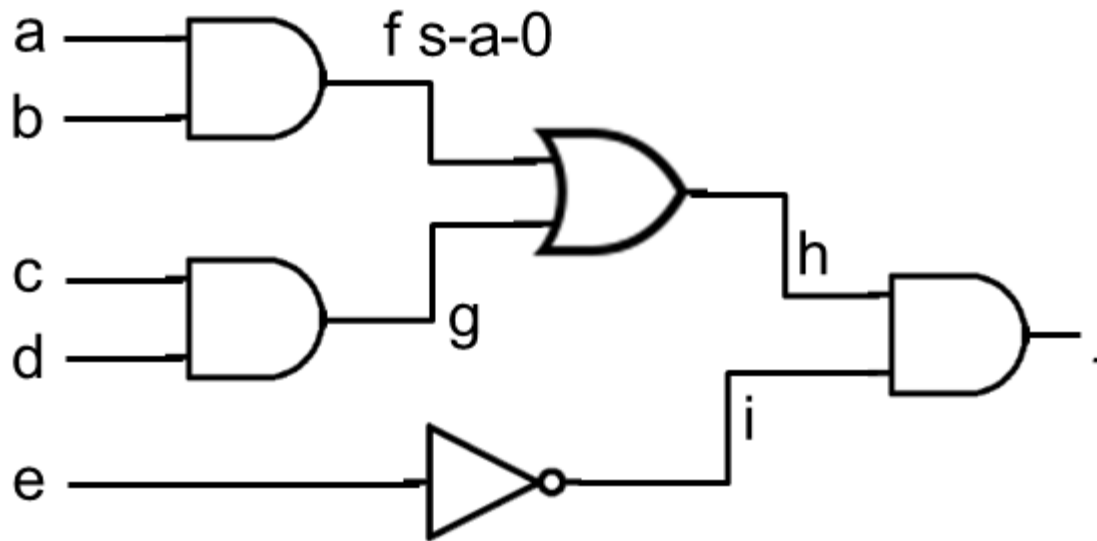

Test Generation

• Example

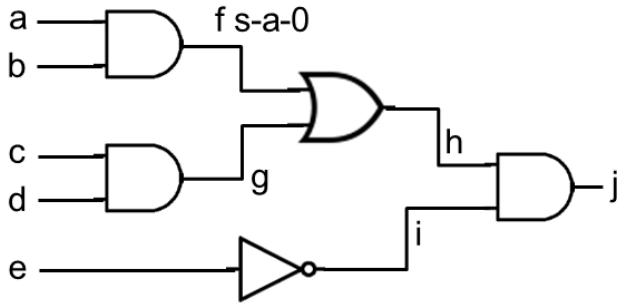


set all values to x $Justify(l, \bar{v})$ if $v = 0$, then $Propagate(l, D)$ else $Propagate(l, \bar{D})$	Justify(l, v) set l to v if l is a PI, then return $c =$ controlling value of l $i =$ inversion of l $inval = v \oplus i$ if $inval = \bar{c}$, then for every input j of l $Justify(j, inval)$ else select one input (j) of l $Justify(j, inval)$	Propagate(l, err) set l to err if l is a PO, then return $k =$ the fanout of l $c =$ controlling value of k $i =$ inversion of k for every input j of k ($\neq l$) $Justify(j, \bar{c})$ $Propagate(k, err \oplus i)$
--	--	--

1. $l = f, v = 0$
Justify($f, 1$)
Propagate(f, D)
2. Justify($f, 1$)
 $f = 1$
 $c = 0$
 $i = 0$
3. Justify($a, 1$)
 $a = 1$
4. Justify($b, 1$)
 $b = 1$
5. Propagate(f, D)
 $f = D$
 $k =$ the OR gate
 $c = 1$
 $i = 0$
6. Justify($g, 0$)
 $g = 0$
 $c = 0$
 $i = 0$
 $inval = 0 \oplus 0 = 0$
Justify($c, 0$)
7. Justify($c, 0$)
 $c = 0$

Test Generation

• Example

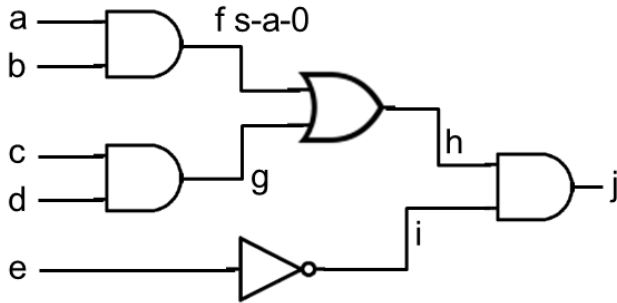

8. Propagate (h, D)
 $h = D$
 $k = j$
 $c = 0$
 $i = 0$
 Justify ($i, 1$)
 Propagate (j, D)
9. Justify ($i, 1$)
 $i = 1$
 $\Rightarrow e = 0$
10. Propagate (j, D)
 $j = D$

set all values to x
 Justify (l, \bar{v})
if $v = 0$, **then**
 Propagate (l, D)
else
 Propagate (l, \bar{D})

Justify (l, v)
 set l to v
if l is a PI, **then return**
 $c =$ controlling value of l
 $i =$ inversion of l
 $inval = v \oplus i$
if $inval = \bar{c}$, **then**
 for every input j of l
 Justify ($j, inval$)
else
 select one input (j) of l
 Justify ($j, inval$)

Propagate (l, err)
 set l to err
if l is a PO, **then return**
 $k =$ the fanout of l
 $c =$ controlling value of k
 $i =$ inversion of k
for every input j of k ($\neq l$)
 Justify (j, \bar{c})
 Propagate ($k, err \oplus i$)

$\Rightarrow abcde = 110x0$

$$Z = (ab + cd)\bar{e}$$

$$Z \oplus Z_f = \{(ab + cd)\bar{e}\} \oplus \{cd\bar{e}\} \Rightarrow abcde = 110x0 \text{ or } abcde = 11x00$$