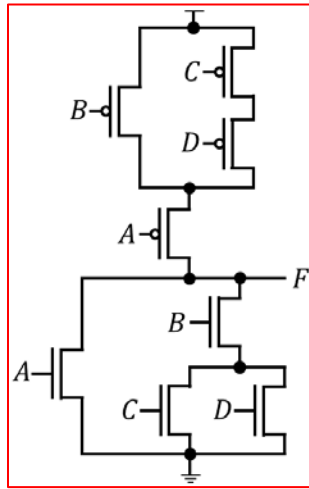


Homework Assignment 1 (Due Jan. 30th at the beginning of the class)

- (1) [Static CMOS Gates, 10 points] Draw a transistor-level schematic for the following function. Use 4 nFETs and 4 pFETs. Available inputs: A, B, C, D .


$$F = \overline{A + B \cdot (C + D)}$$



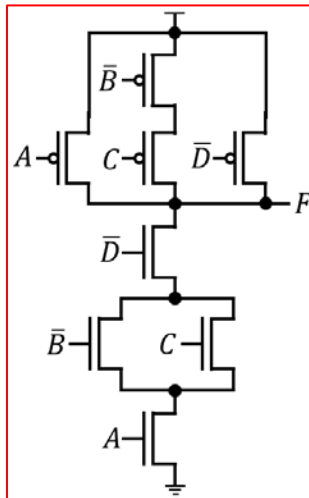- (2) [Static CMOS Gates, 10 points] Draw a transistor-level schematic for the following function. Try to minimize the total # transistors. Available inputs: $A, \bar{A}, B, \bar{B}, C, \bar{C}, D, \bar{D}$.

$$F = \bar{A} + B \cdot \bar{C} + D$$

$$F = \overline{\overline{\bar{A} + B \cdot \bar{C} + D}} = \overline{A \cdot (B + C) \cdot \bar{D}}$$



- (3) [Static CMOS Gates, 10 points] Draw a transistor-level schematic for the following function. Try to minimize the total # transistors. Available inputs: A, \bar{A}, B, \bar{B} .

$$F = A \oplus \bar{B} + \bar{A} \oplus B$$

$$F = \overline{A \oplus B}$$

