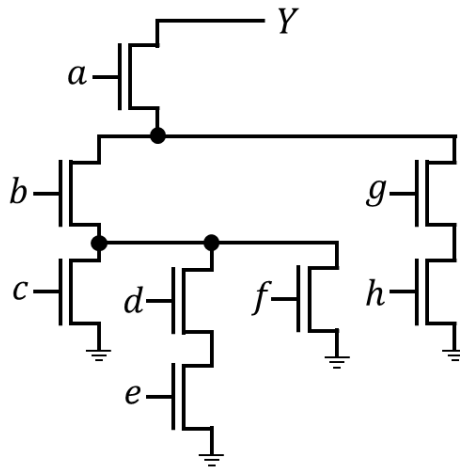


**Homework Assignment 2**  
**(Due Feb. 1st at the beginning of the class)**

- (1) [Static CMOS Gates, 10 points]  $Y$  is a Boolean function of eight variables ( $a, b, c, d, e, f, g, h$ ). The nFET network of  $Y$  is shown below. Express  $Y$  as a function of the variables. Available inputs:  $a, b, c, d, e, f, g, h$ .



- (2) [Static CMOS Gates, 10 points] Draw a transistor-level schematic for the pFET network of  $Y$  shown in Problem 1. Available inputs:  $a, b, c, d, e, f, g, h$ .
- (3) [Static CMOS Gates, 10 points] Draw a *gate-level* schematic for a ten-input AND gate using only two-input NAND and two-input NOR gates. Available inputs:  $x_1, x_2, \dots, x_{10}$ .