 



Homework Assignment 4 (Due Feb. 17th at the beginning of the class)

- R_n is the resistance of a 1X nFET.
- $\mu_n = 2\mu_p$.
- C_L is the load capacitance connected to the output.
- Target time constant: $R_n C_L$

(1) [FET Sizing, 10 points] Size the transistors in the following gate to satisfy the time constant. You should **minimize** the total width of the transistors.



 
(2) [FET Sizing, 10 points] Size the transistors in the following pFET network to satisfy the time constant. **Try to minimize** the total width of the transistors.




(3) [FET Sizing, 10 points] We are going to design the following logic:

$$F = (a + b) \cdot (c + d)$$

We can design this logic as follows:

 

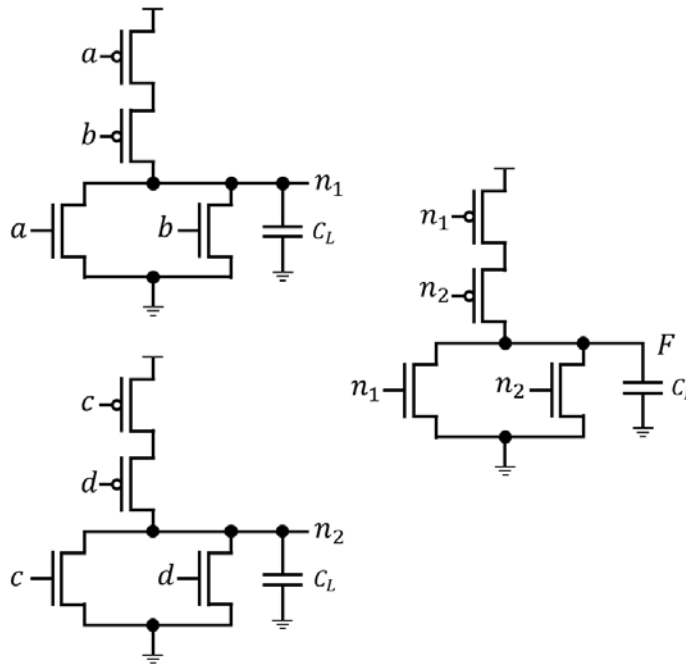The schematic shown above can be modeled as follows to compute the delay from the inputs to the output:



To simplify the problem, we assume that the delay from an input to the output is computed by $\tau_1 + \tau_2$ where τ_1 and τ_2 are the time constants for charging or discharging the first and the second NOR gates, respectively. The target time constant is still $R_n C_L$. Size all the transistors in the three NOR gates to satisfy the target time constant. **Minimize** the total width of the transistors.