 


## Homework Assignment 4 (Due Feb. 17th at the beginning of the class)

- $R_n$  is the resistance of a 1X nFET.
- $\mu_n = 2\mu_p$ .
- $C_L$  is the load capacitance connected to the output.
- Target time constant:  $R_n C_L$

(1) [FET Sizing, 10 points] Size the transistors in the following gate to satisfy the time constant. **Try to minimize** the total width of the transistors.




Total width =  $7 + 21 = 28X$

The best solution is as follows:

- For the nFET network,  $B=bX$ ,  $C=D=cX$ . Then,  $\frac{R_n}{b} + \frac{R_n}{c} = R_n$ , which is  $\frac{1}{b} + \frac{1}{c} = 1$ . Minimize  $b + 2c$ .  $c = \frac{b}{b-1}$ .  $f(b, c) = b + 2c = f(b) = b + \frac{2b}{b-1}$ .  $f'(b) = 1 + \frac{2(b-1)-2b}{(b-1)^2} = 1 - \frac{2}{(b-1)^2} = 0 \Rightarrow b = 1 + \sqrt{2}$ ,  $c = 1 + \frac{1}{\sqrt{2}}$
- For the pFET network,  $B=bX$ ,  $C=D=2bX$ ,  $A=cX$ . Then,  $\frac{2R_n}{b} + \frac{2R_n}{c} = R_n$ , which is  $\frac{1}{b} + \frac{1}{c} = \frac{1}{2}$ . Minimize  $5b + c$ .  $c = \frac{2b}{b-2}$ .  $f(b, c) = 5b + c = f(b) = 5b + \frac{2b}{b-2}$ .  $f'(b) = 5 + \frac{2(b-2)-2b}{(b-2)^2} = 5 - \frac{4}{(b-2)^2} = 0 \Rightarrow b = 2 + \frac{2}{\sqrt{5}}$ ,  $c = 2 + 2\sqrt{5}$

$$\text{Total width} = (1 + \sqrt{2}) + 2 \left(1 + \frac{1}{\sqrt{2}}\right) + 5 \left(2 + \frac{2}{\sqrt{5}}\right) + (2 + 2\sqrt{5}) = 15 + 2\sqrt{2} + 4\sqrt{5} \approx 26.77X$$

 - (2) [FET Sizing, 10 points] Size the transistors in the following pFET network to satisfy the time constant. **Try to minimize** the total width of the transistors.




$$\text{Total width} = \left(50 + \frac{8}{3}\right)X \approx 52.67X.$$

(If you minimize the path “g-b”, first,  $g=h=b=4X$ . Then,  $c=d=e=f=12X$ . In this case, the total width =  $2X + 3 \cdot 4X + 4 \cdot 12X = 62X$ .)


- (3) [FET Sizing, 10 points] We are going to design the following logic:

$$F = (a + b) \cdot (c + d)$$

We can design this logic as follows:

 


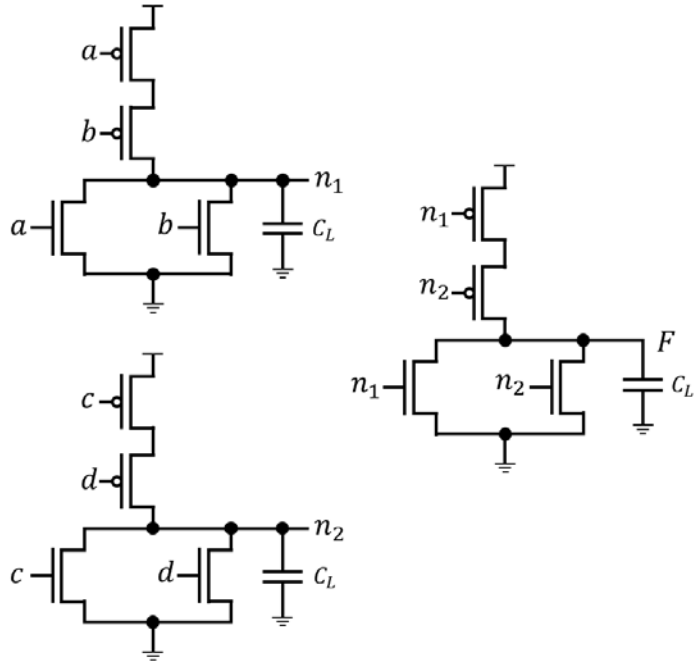The schematic shown above can be modeled as follows to compute the delay from the inputs to the output:



To simplify the problem, we assume that the delay from an input to the output is computed by  $\tau_1 + \tau_2$  where  $\tau_1$  and  $\tau_2$  are the time constants for charging or discharging the first and the second NOR gates, respectively. The target time constant is still  $R_n C_L$ . Size all the transistors in the three NOR gates to satisfy the target time constant. **Minimize** the total width of the transistors.

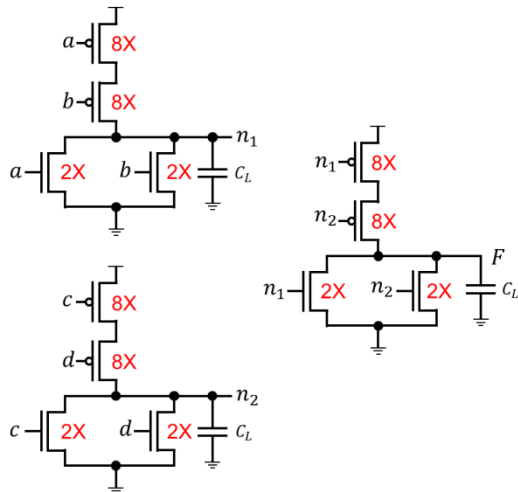1) Assuming  $\tau_1 = \tau_2 = \frac{R_n C_L}{2}$ , we get the following solution:



In this case, the total width is 60X.

2) However, we intuitively know that the first-stage NOR gates are the bottleneck for the area minimization. Suppose the first-stage NOR gates are  $aX$  NOR gates and the second-stage NOR gate is a  $bX$  NOR gate. Then, the delay of the first-stage NOR gate is  $\frac{R_n C_L}{a}$  and that of the second-stage NOR gate is  $\frac{R_n C_L}{b}$ . Satisfying the total delay leads to  $\frac{R_n C_L}{a} + \frac{R_n C_L}{b} = R_n C_L$ , so  $\frac{1}{a} + \frac{1}{b} = 1$ . The total area is  $(2a + b) \cdot (\text{area of a } 1X \text{ NOR gate})$ . Minimize  $2a + b$  when  $b = \frac{a}{a-1}$ .  $f(a) = 2a + \frac{a}{a-1}$ .  $f'(a) = 2 + \frac{(a-1)-a}{(a-1)^2} = 2 - \frac{1}{(a-1)^2} = 0 \Rightarrow a = 1 + \frac{1}{\sqrt{2}}$ ,  $b = 1 + \sqrt{2}$ . Thus, the first-stage NOR gates should be  $(1 + \frac{1}{\sqrt{2}})X$  and the second-stage NOR gate should be  $(1 + \sqrt{2})X$ .

In this case, the total width =  $10 \cdot \{(1 + \frac{1}{\sqrt{2}}) \cdot 2 + (1 + \sqrt{2})\} = 30 + 20\sqrt{2} \approx 58X$ .

3) In addition, we can consider different charging/discharging delays. Suppose the sizes of the nFETs and pFETs in the first-stage NORs are  $aX$  and  $bX$ , respectively, and those in the second-stage NOR are  $cX$  and  $dX$ , respectively. If the outputs of the first-stage NORs are 0 (the nFETs are turned on), the output of the second-stage NOR is 1 (the pFETs are turned on). Then,  $\tau_1 = \frac{R_n C_L}{a}$  and  $\tau_2 = \frac{4R_n C_L}{d}$ , so we obtain  $\frac{1}{a} + \frac{4}{d} \leq 1$ . Similarly, if the output of only one of the first-stage NORs is 1 (the pFETs are turned on), the output of the second-stage NOR is 0 (one of its nFETs is turned on). Then,  $\tau_1 = \frac{4R_n C_L}{b}$  and  $\tau_2 = \frac{R_n C_L}{c}$ , so we obtain  $\frac{4}{b} + \frac{1}{c} \leq 1$ . The total width =  $4a + 4b + 2c + 2d$ . Since the two terms are independent of each other, we minimize  $4a + 2d$  and  $4b + 2c$  separately. For  $4a + 2d$ , we obtain  $a = (1 + \sqrt{2})X$  and  $d = (4 + 2\sqrt{2})X$ . For  $4b + 2c$ , we obtain  $b = (4 + \sqrt{2})X$  and  $c = (1 + 2\sqrt{2})X$ .

The total width =  $(30 + 16\sqrt{2})X \approx 52.63X$ .

4) Furthermore, we might not need to size the two first-stage NOR gates equally. If you derive timing constraint inequalities for that, however, equal sizing of them gives us the best solution.