

Homework Assignment 8 (Due Apr. 19th at the beginning of the class)

- (1) [Interconnect Optimization, 30 points] The following net is given and we are supposed to insert buffers into the net to minimize the delay from the driver to the sink.



- Output resistance of the driver: R_o
- Input capacitance of the sink: C_s
- Output resistance of a buffer: R_o
- Input capacitance of a buffer: C_o
- Length of the net: L (um)
- Wire unit resistance: r (Ω/um)
- Wire unit capacitance: c (fF/um)

Find the # buffers and their locations.

Suppose we insert $n - 1$ buffers and length of each segment from the left is s_k .

Then, $\sum_{k=1}^n s_k = L$.

The delay of each segment except the rightmost one is $\tau_k = R_o \cdot (c \cdot s_k + C_o) + r \cdot s_k \cdot C_o + \frac{1}{2} r c s_k^2$. The delay of the rightmost segment is $\tau_n = R_o \cdot$

$(c \cdot s_n + C_s) + r \cdot s_n \cdot C_s + \frac{1}{2} r c s_n^2$. The total delay is $\tau = \sum_{k=1}^{n-1} \tau_k + \tau_n = R_o \cdot$

$c \cdot L + (n - 1) R_o C_o + R_o C_s + r C_o (s_1 + \dots + s_{n-1}) + r \cdot s_n \cdot C_s + \frac{1}{2} r c (s_1^2 + \dots + s_n^2)$.

Solve $\frac{\partial \tau}{\partial s_1} = 0, \frac{\partial \tau}{\partial s_2} = 0, \dots, \frac{\partial \tau}{\partial s_n} = 0$.

$\frac{\partial \tau}{\partial s_k} = r C_o - r C_s + \frac{1}{2} r c (2 s_k - 2 s_n) = 0$ for $(k = 1, 2, \dots, n - 1)$.

$s_k = s_n - \frac{C_o - C_s}{c}$. From $\sum_{k=1}^n s_k = L$, we get

$s_n = \frac{L}{n} + \frac{n-1}{n} \cdot \frac{C_o - C_s}{c}$.

Thus, $s_1 = s_2 = \dots = s_{n-1} = \frac{L-(C_o-C_S)/c}{n}$.

The total delay is $\tau = R_o \cdot c \cdot L + (n-1)R_oC_o + R_oC_S + rC_o \cdot \frac{n-1}{n}(L-b) + r \cdot C_S \cdot \left(\frac{L}{n} + \frac{n-1}{n} \cdot b\right) + \frac{1}{2}rc \left(\frac{L^2-b^2}{n} + b^2\right)$ where $b = \frac{C_o-C_S}{c}$.

Differentiating the above equation w.r.t. n , we get $\frac{d\tau}{dn} = R_oC_o + rC_o \cdot (L-b) \cdot$

$$\frac{1}{n^2} + rC_S \left(-\frac{L}{n^2} + \frac{b}{n^2}\right) - \frac{1}{2}rc \frac{L^2-b^2}{n^2} = R_oC_o + \frac{rC_o(L-b)+rC_S(b-L)-0.5rc(L^2-b^2)}{n^2} = 0.$$

$$\begin{aligned} \therefore n &= \sqrt{\frac{r((C_S - C_o) \cdot (L - b) + 0.5c(L^2 - b^2))}{R_oC_o}} \\ &= \sqrt{\frac{r \cdot (L - b) \cdot ((C_S - C_o) + 0.5c(L + b))}{R_oC_o}} \end{aligned}$$