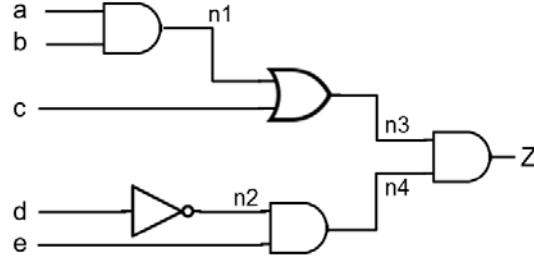


Homework Assignment 10

(Due Apr. 28th at the beginning of the class)

1. [Testing, 30 points] Find all input vectors that can detect the following stuck-fault errors.



$$Z = (a \cdot b + c) \cdot (\bar{d} \cdot e)$$

- 1) a s-a-0: $Z_f = c \cdot (\bar{d} \cdot e) \Rightarrow Z \oplus Z_f = \{(a \cdot b + c) \cdot (\bar{d} \cdot e)\} \oplus \{c \cdot (\bar{d} \cdot e)\} = 1 \Rightarrow (a \ b \ c \ d \ e) = (1 \ 1 \ 0 \ 0 \ 1)$
- 2) a s-a-1: $Z_f = (b + c) \cdot (\bar{d} \cdot e) \Rightarrow Z \oplus Z_f = \{(a \cdot b + c) \cdot (\bar{d} \cdot e)\} \oplus \{(b + c) \cdot (\bar{d} \cdot e)\} = 1 \Rightarrow (a \ b \ c \ d \ e) = (0 \ 1 \ 0 \ 0 \ 1)$
- 3) b s-a-0: $(a \ b \ c \ d \ e) = (1 \ 1 \ 0 \ 0 \ 1)$
- 4) b s-a-1: $(a \ b \ c \ d \ e) = (1 \ 0 \ 0 \ 0 \ 1)$
- 5) c s-a-0: $Z_f = (a \cdot b) \cdot (\bar{d} \cdot e) \Rightarrow Z \oplus Z_f = \{(a \cdot b + c) \cdot (\bar{d} \cdot e)\} \oplus \{(a \cdot b) \cdot (\bar{d} \cdot e)\} = 1 \Rightarrow (a \ b \ c \ d \ e) = (0 \ 0 \ 1 \ 0 \ 1), (0 \ 1 \ 1 \ 0 \ 1), (1 \ 0 \ 1 \ 0 \ 1)$
- 6) c s-a-1: $Z_f = (\bar{d} \cdot e) \Rightarrow Z \oplus Z_f = \{(a \cdot b + c) \cdot (\bar{d} \cdot e)\} \oplus \{(\bar{d} \cdot e)\} = 1 \Rightarrow (a \ b \ c \ d \ e) = (0 \ 0 \ 0 \ 0 \ 1), (0 \ 1 \ 0 \ 0 \ 1), (1 \ 0 \ 0 \ 0 \ 1)$
- 7) d s-a-0: $Z_f = (a \cdot b + c) \cdot (e) \Rightarrow Z \oplus Z_f = \{(a \cdot b + c) \cdot (\bar{d} \cdot e)\} \oplus \{(a \cdot b + c) \cdot (e)\} = 1 \Rightarrow (a \ b \ c \ d \ e) = (1 \ 1 \ 0 \ 1 \ 1), (1 \ 1 \ 1 \ 1 \ 1), (0 \ 0 \ 1 \ 1 \ 1), (0 \ 1 \ 1 \ 1 \ 1), (1 \ 0 \ 1 \ 1 \ 1)$
- 8) d s-a-1: $Z_f = 0 \Rightarrow Z \oplus Z_f = \{(a \cdot b + c) \cdot (\bar{d} \cdot e)\} \oplus \{0\} = 1 \Rightarrow (a \ b \ c \ d \ e) = (1 \ 1 \ 0 \ 0 \ 1), (1 \ 1 \ 1 \ 0 \ 1), (0 \ 0 \ 1 \ 0 \ 1), (0 \ 1 \ 1 \ 0 \ 1), (1 \ 0 \ 1 \ 0 \ 1)$
- 9) n1 s-a-0: $Z_f = c \cdot (\bar{d} \cdot e) \Rightarrow (a \ b \ c \ d \ e) = (1 \ 1 \ 0 \ 0 \ 1)$
- 10) n1 s-a-1: $Z_f = (\bar{d} \cdot e) \Rightarrow (a \ b \ c \ d \ e) = (0 \ 0 \ 0 \ 0 \ 1), (0 \ 1 \ 0 \ 0 \ 1), (1 \ 0 \ 0 \ 0 \ 1)$
- 11) n2 s-a-0:
 $Z_f = 0 \Rightarrow (a \ b \ c \ d \ e) = (1 \ 1 \ 0 \ 0 \ 1), (1 \ 1 \ 1 \ 0 \ 1), (0 \ 0 \ 1 \ 0 \ 1), (0 \ 1 \ 1 \ 0 \ 1), (1 \ 0 \ 1 \ 0 \ 1)$
- 12) n2 s-a-1:
 $Z_f = (a \cdot b + c) \cdot (e) \Rightarrow (a \ b \ c \ d \ e) = (1 \ 1 \ 0 \ 1 \ 1), (1 \ 1 \ 1 \ 1 \ 1), (0 \ 0 \ 1 \ 1 \ 1), (0 \ 1 \ 1 \ 1 \ 1), (1 \ 0 \ 1 \ 1 \ 1)$
- 13) n3 s-a-0:
 $Z_f = 0 \Rightarrow (a \ b \ c \ d \ e) = (1 \ 1 \ 0 \ 0 \ 1), (1 \ 1 \ 1 \ 0 \ 1), (0 \ 0 \ 1 \ 0 \ 1), (0 \ 1 \ 1 \ 0 \ 1), (1 \ 0 \ 1 \ 0 \ 1)$
- 14) n3 s-a-1: $Z_f = (\bar{d} \cdot e) \Rightarrow (a \ b \ c \ d \ e) = (0 \ 0 \ 0 \ 0 \ 1), (0 \ 1 \ 0 \ 0 \ 1), (1 \ 0 \ 0 \ 0 \ 1)$

15) n4 s-a-0:

$$Z_f = 0 \Rightarrow (a \ b \ c \ d \ e) = (1 \ 1 \ 0 \ 0 \ 1), (1 \ 1 \ 1 \ 0 \ 1), (0 \ 0 \ 1 \ 0 \ 1), (0 \ 1 \ 1 \ 0 \ 1), (1 \ 0 \ 1 \ 0 \ 1)$$