

Homework Assignment 6

(Due Mar. 30th at the beginning of the class)

1. [Wire Resistance and Capacitance, 20 points]

- [Submit] Compute the resistance of the following wire:

$$\circ R = (2.0 \cdot 10^{-8} \Omega \cdot m) \cdot \frac{100\mu m}{0.28\mu m \cdot 0.14\mu m} = \frac{0.02 \cdot 100}{0.28 \cdot 0.14} \Omega = 51.02 \Omega$$

$$\circ \rho = 2.0 \cdot 10^{-8} \Omega \cdot m$$

$$\circ \epsilon_{OX} = 2.0 \cdot 10^{-11} F/m$$

$$\circ \text{width: } 0.14\mu m$$

$$\circ \text{spacing between the wire and the ground plane: } 0.28\mu m$$

$$\circ \text{length: } 100\mu m$$

$$\circ \text{thickness: } 0.28\mu m$$

$$\circ \text{spacing between two laterally-adjacent wires: } 0.14\mu m$$

- [Submit] Compute the area capacitance of the above wire:

$$\circ C_{Area} = (2.0 \cdot 10^{-11} F/m) \cdot \frac{0.14\mu m \cdot 100\mu m}{0.28\mu m} = 1fF$$


- [Submit] Compute the lateral capacitance of the above wire.

$$\circ C_{Lateral} = (2.0 \cdot 10^{-11} F/m) \cdot \frac{0.28\mu m \cdot 100\mu m}{0.14\mu m} = 4fF$$

- [Submit] Compute the fringe capacitance of the above wire.

$$\circ C_{Fringe} = (2.0 \cdot 10^{-11} F/m) \cdot \ln\left(1 + \frac{0.28\mu m}{0.28\mu m}\right) * 100\mu m = 1.38fF$$

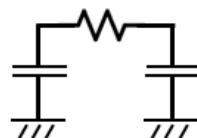- [Submit] The above wire is driven by a buffer whose output resistance is 1kΩ. The other end of the wire is connected to a gate whose input capacitance is 5fF. Compute Elmore delay at the load. $C_{wire} = 2 * C_{area} + 2 * C_{lateral} + 4 * C_{fringe}$. Use the PI model to model the above wire.




$$C_{wire} = 2fF + 8fF + 5.52fF = 15.52fF.$$


$$\begin{aligned} \tau &= R_{out}(C_{wire} + C_L) + R_{wire} \left(\frac{C_{wire}}{2} + C_L \right) = 1k(20.52f) + 51.02(12.76f) \\ &= 21.17ps. \end{aligned}$$

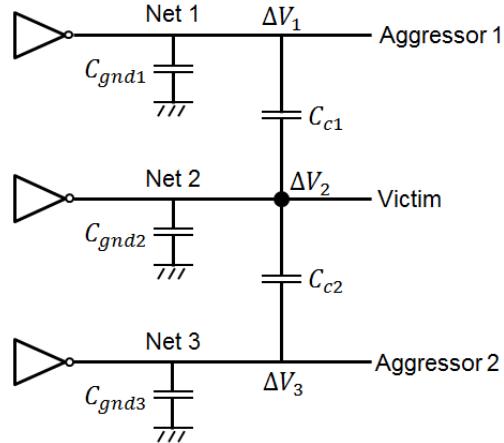2. [Coupling, 10 points]

- In real designs, a victim net is usually surrounded by multiple aggressors. The following models a victim net surrounded by two aggressors.



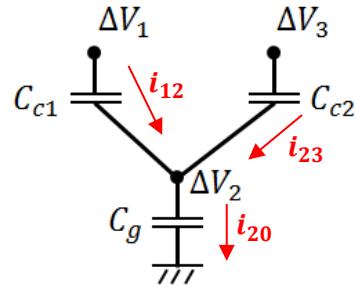- To compute ΔV_2 , we can use the following model:




- [Submit] Represent ΔV_2 as a function of ΔV_1 , ΔV_3 , C_{c1} , C_{c2} , and C_g .


$$\begin{aligned}
 & i_{12} + i_{23} = i_{20} \\
 & i_{12} = C_{c1} \frac{\Delta V_1 - \Delta V_2}{\Delta t}, i_{23} = C_{c2} \frac{\Delta V_3 - \Delta V_2}{\Delta t}, i_{20} = C_g \frac{\Delta V_2}{\Delta t} \\
 & C_{c1} \frac{\Delta V_1 - \Delta V_2}{\Delta t} + C_{c2} \frac{\Delta V_3 - \Delta V_2}{\Delta t} = C_g \frac{\Delta V_2}{\Delta t} \\
 & \Delta V_1 \cdot C_{c1} + \Delta V_3 \cdot C_{c2} = \Delta V_2 (C_{c1} + C_{c2} + C_g) \\
 & \therefore \Delta V_2 = \frac{\Delta V_1 \cdot C_{c1} + \Delta V_3 \cdot C_{c2}}{C_{c1} + C_{c2} + C_g}
 \end{aligned}$$

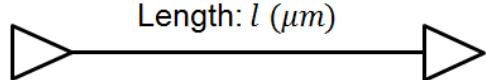3. [Elmore Delay, 10 points]

- We want to compute Elmore delay for the following net:



- This net is modeled as follows:

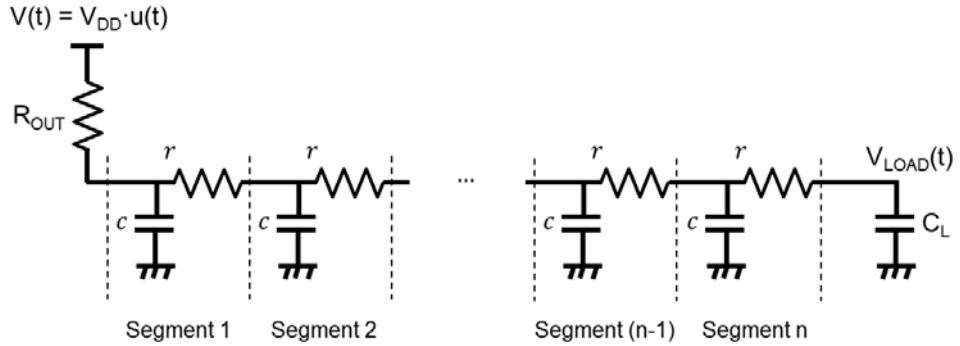

- R_w : Total wire resistance
- C_w : Total wire capacitance
- $r = \frac{R_w}{n}, c = \frac{C_w}{n}$
- [Submit] Compute Elmore Delay at the load when n goes to infinity. Represent the delay as a function of R_{OUT} , C_L , R_w , and C_w .

$$\begin{aligned}
 \tau_n &= R_{OUT}(C_w + C_L) + R_w C_L + r \cdot (n-1) \cdot c + r \cdot (n-2) \cdot c + \cdots + r \cdot c \\
 &= R_{OUT}(C_w + C_L) + R_w C_L + rc \frac{n(n-1)}{2} \\
 &= R_{OUT}(C_w + C_L) + R_w C_L + R_w C_w \frac{n(n-1)}{2n^2} \\
 \tau &= \lim_{n \rightarrow \infty} \tau_n = R_{OUT}(C_w + C_L) + R_w C_L + \frac{R_w C_w}{2}
 \end{aligned}$$