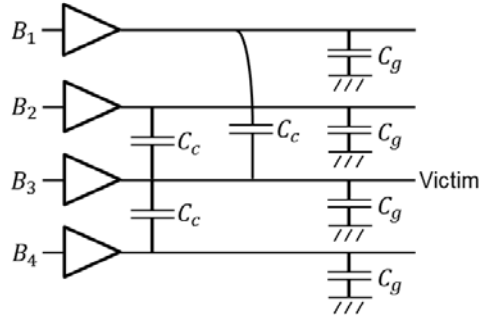


Homework Assignment 7

(Due Apr. 6th at the beginning of the class)

1. [Wire Coupling, **10 points**] Calculate effective capacitance for the victim net and transition patterns in the following figure.



Transition patterns (B ₁ B ₂ B ₃ B ₄)	Effective cap. of the victim net
0000 → 0010	$C_g + 3C_c$
1101 → 0010	$C_g + 6C_c$
0101 → 1010	$C_g + 4C_c$
0011 → 1100	$C_g + 4C_c$
0100 → 1111	$C_g + C_c$
1010 → 0101	$C_g + 4C_c$

2. [Coupling Minimization, **20 points**] Encode 25 using the FPF-CAC Encoding algorithm in the lecture note ($m=7$). Show all the details, i.e., v , f_k , d_k , r_k , etc. at each step.

$$(f_8, f_7, f_6, f_5, f_4, f_3, f_2, f_1) = (21, 13, 8, 5, 3, 2, 1, 1)$$

1. MSB: $v = 25 \geq f_{7+1} = f_8 = 21$

$$d_m = d_7 = 1$$

$$r_m = r_7 = v - f_7 = 25 - 13 = 12$$

2. $k = 6$

$$r_{k+1} = r_7 = 12 < f_{k+1} = f_7 = 13$$

$$r_{k+1} = r_7 = 12 \geq f_6 = 8$$

$$d_k = d_6 = d_{k+1} = d_7 = 1$$

$$r_k = r_6 = r_7 - f_6 * d_6 = 12 - 8 * 1 = 4$$

3. $k = 5$

$$r_{k+1} = r_6 = 4 < f_{k+1} = f_6 = 8$$

$$r_{k+1} = r_6 = 4 < f_5 = 5$$

$$d_k = d_5 = 0$$

$$r_k = r_5 = r_6 - f_5 * d_5 = 4 - 0 = 4$$

4. $k = 4$

$$r_{k+1} = r_5 = 4 < f_{k+1} = f_5 = 5$$

$$\begin{aligned}
r_{k+1} &= r_5 = 4 \geq f_4 = 3 \\
d_k &= d_4 = d_{k+1} = d_5 = 0 \\
r_k &= r_4 = r_5 - f_4 \cdot d_4 = 4 - 0 = 4 \\
5. \quad k &= 3 \\
r_{k+1} &= r_4 = 4 \geq f_{k+1} = f_4 = 3 \\
d_k &= d_3 = 1 \\
r_k &= r_3 = r_4 - f_3 \cdot d_3 = 4 - 2 \cdot 1 = 2 \\
6. \quad k &= 2 \\
r_{k+1} &= r_3 = 2 \geq f_{k+1} = f_3 = 2 \\
d_k &= d_2 = 1 \\
r_k &= r_2 = r_3 - f_2 \cdot d_2 = 2 - 1 \cdot 1 = 1 \\
7. \quad \text{LSB: } d_1 &= r_2 = 1 \\
\text{Answer: } &\mathbf{1100111}
\end{aligned}$$

3. [Buffer Insertion, **30 points**] In the second buffer insertion problem in the lecture note (pp. 34 – 37), we did not take the buffer delay into account. However, the buffer delay is not negligible in reality. Suppose the Elmore delay of a buffer is d . Find N , the number of buffers to insert.

$$\tau_{all} = R_{DR}(C_{wire} + N \cdot C_{in}) + R_{wire} \cdot C_{in} + d \cdot N + \frac{R_{wire} \cdot C_{wire}}{2L^2} (s_1^2 + s_2^2 + \dots + s_N^2)$$

$$\frac{\partial \tau_{all}}{\partial s_k} = 2 \cdot s_k - 2s_N = 0 \Rightarrow s_1 = s_2 = \dots = s_N$$

$$\tau_{all} = R_{DR}(C_{wire} + N \cdot C_{in}) + R_{wire} \cdot C_{in} + d \cdot N + \frac{R_{wire} \cdot C_{wire}}{2N}$$

$$\frac{\partial \tau_{all}}{\partial N} = R_{DR} \cdot C_{in} + d - \frac{R_{wire} \cdot C_{wire}}{2N^2} = 0$$

$$N = \sqrt{\frac{R_{wire} \cdot C_{wire}}{2(R_{DR} \cdot C_{in} + d)}}$$