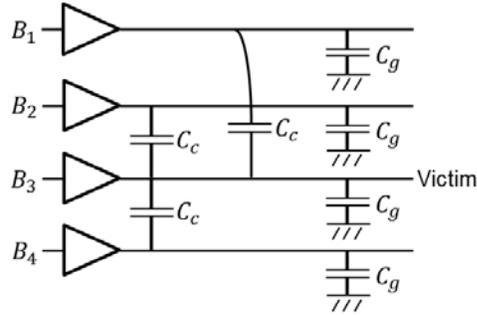


Homework Assignment 7

(Due Apr. 6th at the beginning of the class)

1. [Wire Coupling, **10 points**] Calculate effective capacitance for the victim net and transition patterns in the following figure.



Transition patterns ($B_1B_2B_3B_4$)	Effective cap. of the victim net
0000 \rightarrow 0010	
1101 \rightarrow 0010	
0101 \rightarrow 1010	
0011 \rightarrow 1100	
0100 \rightarrow 1111	
1010 \rightarrow 0101	

2. [Coupling Minimization, **20 points**] Encode 25 using the FPF-CAC Encoding algorithm in the lecture note ($m=7$). Show all the details, i.e., v , f_k , d_k , r_k , etc. at each step.
3. [Buffer Insertion, **30 points**] In the second buffer insertion problem in the lecture note (pp. 34 – 37), we did not take the buffer delay into account. However, the buffer delay is not negligible in reality. Suppose the Elmore delay of a buffer is d . Find N , the number of buffers to insert.
- [Hint] Add d to τ_k in slide 35. Then, derive τ_{all} . Differentiate τ_{all} with respect to s_k and find a relationship among $s_1, s_2, \dots,$ and s_N . Then, rewrite τ_{all} as a function of $R_{DR}, N, C_{in}, C_w, R_w,$ and d . Differentiate τ_{all} with respect to N and set it to 0 to find N .