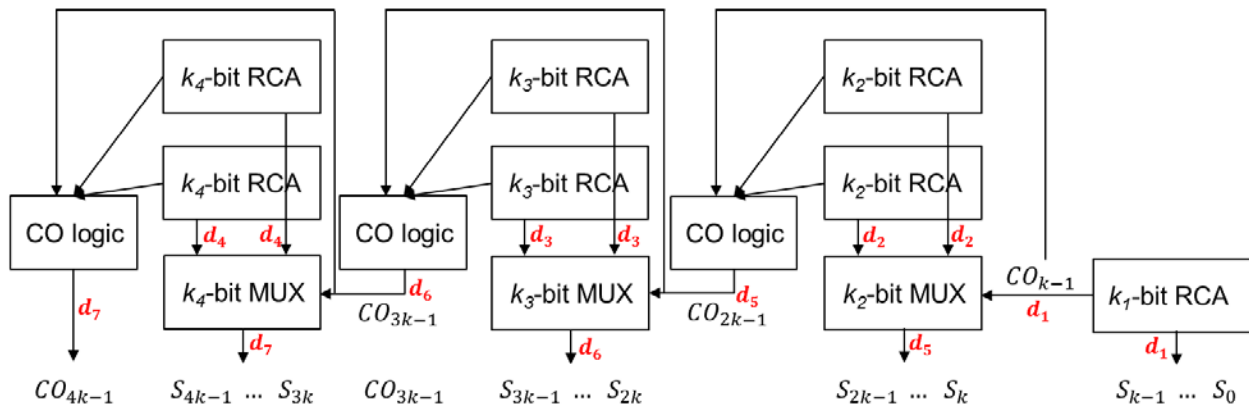


## Homework Assignment 9

(Due May 3<sup>rd</sup>, 12pm)

1. [Carry Select Adder, **40 points**] In the lecture note, we used k-bit adders to design an N-bit carry select adder. However, we can use variable-length adders instead of fixed-length adders. The following shows the specification of logic blocks we are going to use:

- N: 64
- Delay of a full adder:  $\Delta_{FA} = 100ps$
- Delay of a k-bit ripple carry adder (RCA):  $k \cdot \Delta_{FA}$
- Delay of a k-bit MUX (when  $k \geq 10$ ) and a CO logic:  $\varepsilon = 150ps$
- Architecture: We split N into four groups as follows:



Since N is 64, the above architecture should satisfy the following equation:

$$k_1 + k_2 + k_3 + k_4 = 64$$

We also assume that  $k_i \geq 10$  ( $i = 1 \sim 4$ ).

1) Represent delay of the 64-bit adder shown above as a function of  $k_1, k_2, k_3, k_4$ , and the MAX(a,b) function where “MAX(a, b) = a if (a>b) or b (if b>a)”.

- Delay of the  $k_1$ -bit RCA:  $d_1 = k_1 \cdot \Delta_{FA} = 100k_1$
- Delay of the  $k_2$ -bit RCA:  $d_2 = k_2 \cdot \Delta_{FA} = 100k_2$
- Delay of the  $k_3$ -bit RCA:  $d_3 = k_3 \cdot \Delta_{FA} = 100k_3$
- Delay of the  $k_4$ -bit RCA:  $d_4 = k_4 \cdot \Delta_{FA} = 100k_4$
- Arrival time (AT) at the output of the  $k_2$ -bit MUX and the first Carry-Out logic:  $d_5 = \text{MAX}(d_1, d_2) + \varepsilon = 150 + \text{MAX}(100k_1, 100k_2)$
- AT at the output of the  $k_3$ -bit MUX and the second Carry-Out logic:  $d_6 = \text{MAX}(d_3, d_5) + \varepsilon = 150 + \text{MAX}\{100k_3, 150 + \text{MAX}(100k_1, 100k_2)\}$
- AT at the output of the  $k_4$ -bit MUX and the third Carry-Out logic:  $d_7 = \text{MAX}(d_4, d_6) + \varepsilon = \boxed{150 + \text{MAX}[100k_4, 150 + \text{MAX}\{100k_3, 150 + \text{MAX}(100k_1, 100k_2)\}]}$

2) Compute the total delay when  $k_1 = k_2 = k_3 = k_4$ .

- $k_1 = k_2 = k_3 = k_4 = 16$ .
- $d_7 = 150 + \text{MAX}[1600, 150 + \text{MAX}\{1600, 150 + \text{MAX}(1600, 1600)\}]$   
 $= 150 + \text{MAX}[1600, 150 + \text{MAX}\{1600, 150 + 1600\}]$   
 $= 150 + \text{MAX}[1600, 150 + 1750]$   
 $= 150 + 1900 = \boxed{2050ps}$

3) Compute  $k_1, k_2, k_3$ , and  $k_4$  minimizing the delay and show the minimum delay. (Hint: (1) Use your intuition and some math. (2) If you want, you can program it to find  $k_1, k_2, k_3, k_4$ . In this case, you should show your program in your report).

1) We will first show that  $k_1 = k_2$  will give us an optimal delay. Suppose  $\text{MAX}(100k_1, 100k_2)$  affects the final delay. Then,  $k_1 = k_2$  will minimize  $\text{MAX}(100k_1, 100k_2)$ , which will minimize the final delay.

$$k_1 = k_2 \text{ leads to } d_7 = 150 + \text{MAX}[100k_4, 150 + \text{MAX}\{100k_3, 150 + 100k_1\}].$$

By the same reason,  $100k_3 = 150 + 100k_1$  will give us an optimal delay. From this, we get  $k_3 = k_1 + 1.5$ . However,  $k_3$  should be an integer. If  $k_3 \leq k_1 + 1$ , we get  $d_7 = 150 + \text{MAX}[100k_4, 150 + 150 + 100k_1]$ . However, reducing  $k_3$  will increase  $k_4$ , so let's set  $k_3$  to  $k_1 + 1$ .

$d_7 = 150 + \text{MAX}[100k_4, 300 + 100k_1]$ . Setting  $100k_4 = 300 + 100k_1$  will minimize  $d_7 \rightarrow k_4 = 3 + k_1$

From  $k_1 + k_2 + k_3 + k_4 = 64$ , we get  $k_1 + k_1 + (k_1 + 1) + (k_1 + 3) = 64 \rightarrow \boxed{k_1 = 15. k_2 = 15. k_3 = 16. k_4 = 18.}$

Delay =  $150 + \text{MAX}[1800, 150 + \text{MAX}\{1600, 150 + \text{MAX}(1500, 1500)\}] = \boxed{1950ps.}$

2) We can also use a computer program to simulate this. The following C/C++ code simulates it.

```
#include <stdio.h>

int max (int a, int b) {
    if ( a > b )
        return a;
    return b;
}
```

```

int main () {
    int min_delay = 100000000; // min. delay achieved

    for ( int k4 = 10 ; k4 <= 34 ; k4++ ) {
        for ( int k3 = 10 ; k3 <= (44-k4) ; k3++ ) {
            for ( int k2 = 10 ; k2 <= (54-k4-k3) ; k2++ ) {
                int k1 = 64 - (k4 + k3 + k2);
                int delay = 150+max(100*k4, 150+max(100*k3, 150+max(100*k1,
100*k2)));

                if ( delay <= min_delay ) {
                    printf (“(k4, k3, k2, k1, d) = (%d, %d, %d, %d, %d)\n”, k4, k3, k2,
k1, delay);
                    min_delay = delay;
                }
            }
        }
    }
    return 0;
}

```

You can also download the following file:

<http://eecs.wsu.edu/~ee434/Homework/add.cpp>

and compile it as follows (in the ee434-466 server):

```
g++ add.cpp
```

which will generate a.out in your directory. Then, run it to see its usage:

```
> ./a.out
```

The following shows the usage:

```
./a {delta_FA} {delta_MUX}
```

Run the program for the above problem as follows:

```
./a.out 100 150
```

which gives the following result (format: k4 k3 k2 k1 total delay in ps):

```
delta_FA: 100 (ps) delta_MUX: 150 (ps)
18 16 15 15 1950
```

You can also try some different combinations as follows:

```
./a.out 100 200
```


which gives the following result:

```
17 17 15 15 2100
18 16 15 15 2100
```

18 17 14 15 2100  
 18 17 15 14 2100  
 19 15 15 15 2100  
 19 16 14 15 2100  
 19 16 15 14 2100  
 19 17 13 15 2100  
 19 17 14 14 2100  
 19 17 15 13 2100

2. [Prefix Adder, **40 points**] Complete the following prefix adders by inserting merging blocks and drawing arrows (try to minimize the number of merging blocks inserted).

1)

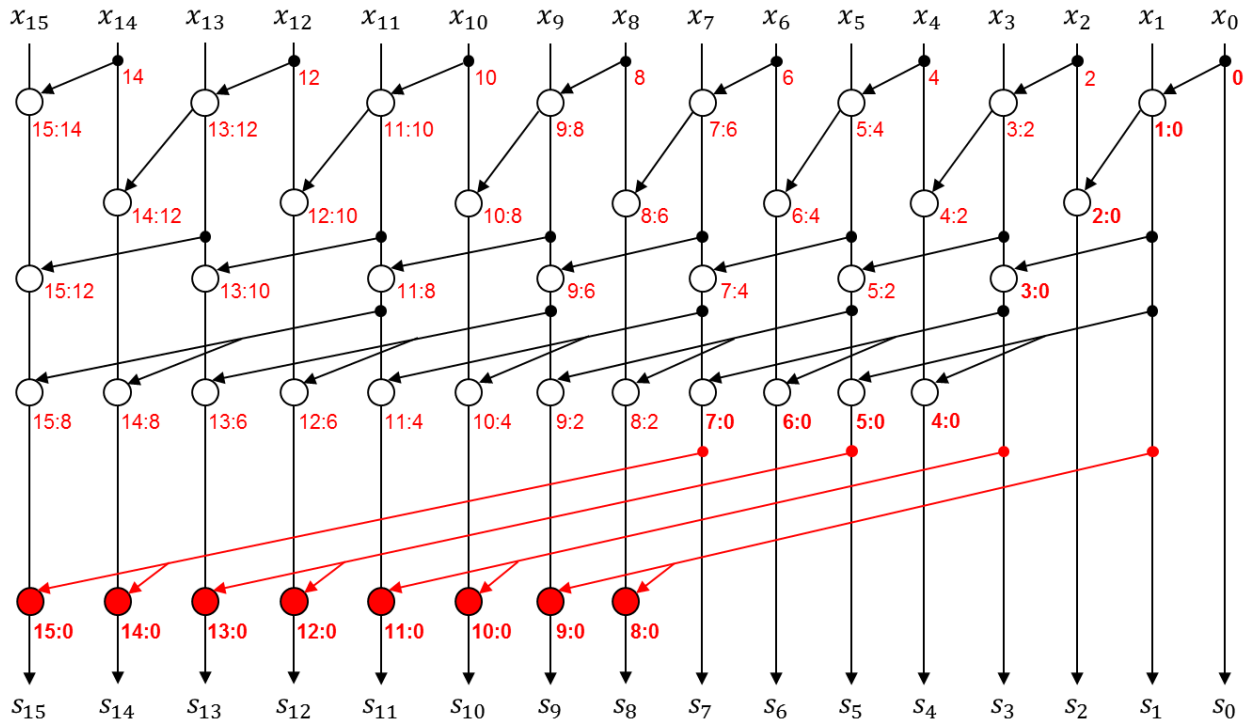

2)

