

Homework Assignment 4

(Due Mar. 4th at the beginning of the class)

0. Preparation for homework 4

- Download the following file into your working directory.
 - `wget http://www.eecs.wsu.edu/~ee434/Homework/hw04.tar.gz`
- Unzip it.
 - `tar xvzf hw04.tar.gz`
- Source `synopsys.sh`
 - `source synopsys.sh`

1. [Pseudo-nMOS, 20 points]

- Design a pseudo-nMOS inverter for the following design spec:
 - Simulate the inverter with the following load cap and input signal
 - Load cap: 10fF
 - The fall & rise transition time of the input signal: 10ps
 - Spec
 - Rise time < 100ps
 - Fall time < 100ps
 - $V_{OL} < 100\text{mV}$
 - $V_{OH} > 900\text{mV}$
 - $NM_L > 150\text{mV}$
 - $NM_H > 300\text{mV}$
- [Submit]
 - The size of the NMOS and PMOS transistors
 - Rise time, fall time
 - V_{IH} , V_{IL} , V_{OH} , V_{OL} , NM_L , NM_H
 - Average power for falling and rising transitions

(1) Let's first satisfy the fall and rise time constraints.


- $W_n=45\text{nm}$, $W_p=70\text{nm}$: $t_f=288\text{ps}$, $t_r=167\text{ps}$.
- $W_n=135\text{nm}$, $W_p=140\text{nm}$: $t_f=103\text{ps}$, $t_r=91.1\text{ps}$.
- $W_n=210\text{nm}$, $W_p=140\text{nm}$: $t_f=53.1\text{ps}$, $t_r=96.5\text{ps}$ (t_r is too close to 100ps, so let's upsize W_p).
- $W_n=210\text{nm}$, $W_p=210\text{nm}$: $t_f=64.4\text{ps}$, $t_r=59.4\text{ps}$.

(2) DC characteristics

- $W_n=210\text{nm}$ $W_p=210\text{nm}$: $V_{OL}>100\text{mV}$ (We should upsize the NMOS TR).
- $W_n=840\text{nm}$ $W_p=210\text{nm}$: $V_{OL}=120\text{mV}$
- $W_n=1260\text{nm}$ $W_p=210\text{nm}$: $V_{OL}=97\text{mV}$, $V_{IH}=575\text{mV}$, $V_{IL}=300\text{mV}$,
 $V_{OH}=940\text{mV} \Rightarrow NM_L=203\text{mV}$, $NM_H=365\text{mV}$, $p_{fall}=218\text{uW}$, $p_{rise}=66.5\text{uW}$

 
2. [Dynamic CMOS, 20 points]

- We design a three-input NAND gate using the dynamic CMOS design style.
- Open myNAND3_pex.cdl and see the netlist of the NAND gate. I drew a layout for the NAND gate and extracted parasitic RC. myNAND3_pex.cdl includes all the parasitic RC.
- Open myNAND3_simul.sp and see the netlist. It is used to simulate the NAND gate.
- The followings show the layout and schematic of the NAND gate.



- Add four signal waveforms (CK, A, B, C) to simulate charge sharing.
 - Load cap: 10fF
 - CK: $V_{DD} \rightarrow 0 \rightarrow V_{DD}$
 - When CK is V_{DD} (before it goes down to 0), set A, B, and C to V_{DD} so that it can fully discharge the output capacitor and all the parasitic capacitors.
 - Then, set A, B, and C to 0 before CK goes to 0.
 - Then, CK goes to 0 and the gate will charge the output capacitor.
 - Then, CK goes to V_{DD} .
 - Then, set C to V_{DD} so that charge sharing can happen between the output capacitor and the parasitic capacitor between MnC and MnB.
 - Perform the same simulation, but set both B and C to V_{DD} so that charge sharing can happen among the output capacitor, the parasitic capacitors between MnC and MnB and between MnB and MnA.
- [Submit]
 - Vout when only C is set to V_{DD} for $C_{out} = 10\text{fF}, 9\text{fF}, \dots, 1\text{fF}$.


Waveform

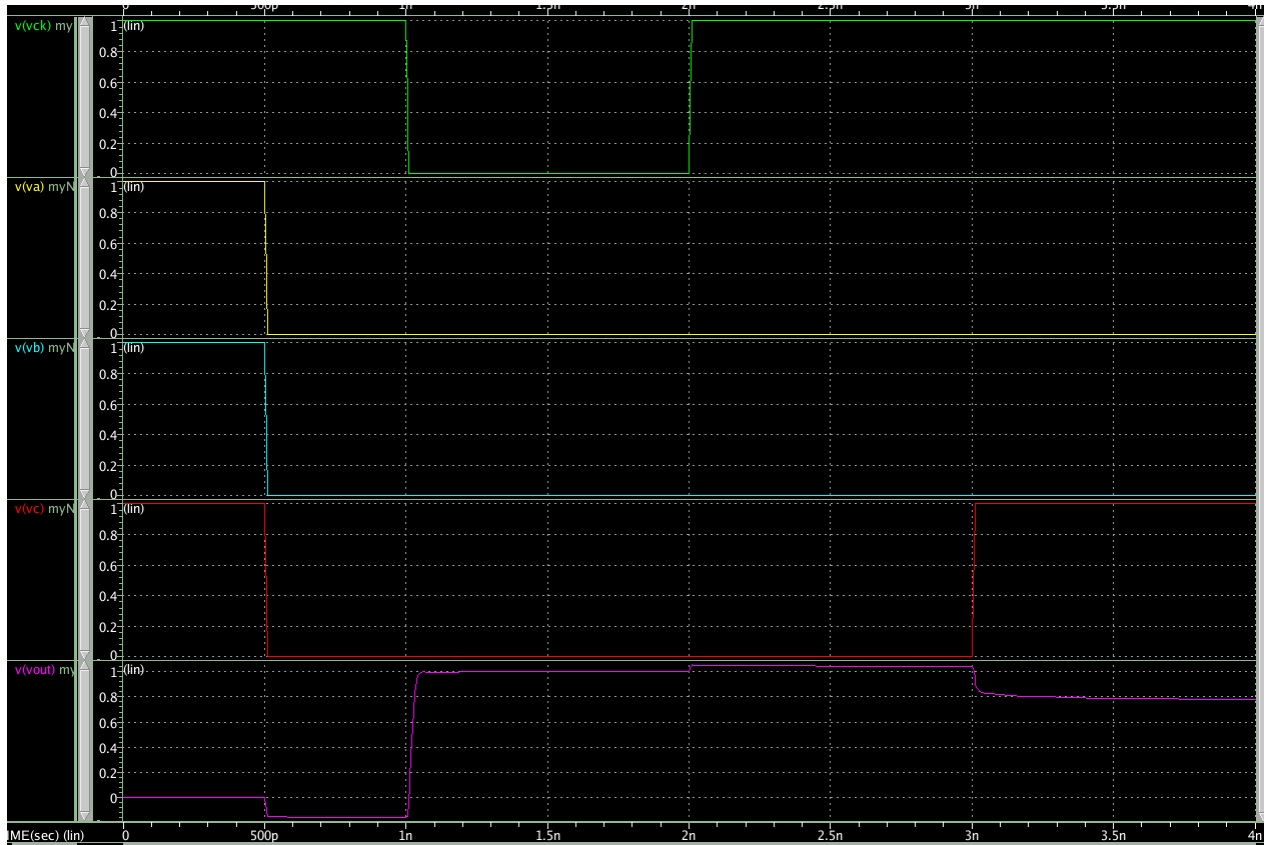

$C_{out} = 1fF \sim 10fF: V_{out} = 0.8V, 0.874V, 0.909V, 0.929V, 0.941V, 0.950V, \dots, 0.969V$

- **[Submit]**
 - V_{out} when both C and B are set to V_{DD} for $C_{out} = 10fF, 9fF, \dots, 1fF$.

Waveform

 


$C_{out} = 1\text{fF} \sim 10\text{fF}$: $V_{out} = 0.633\text{V}, 0.734\text{V}, \dots, 0.933\text{V}$

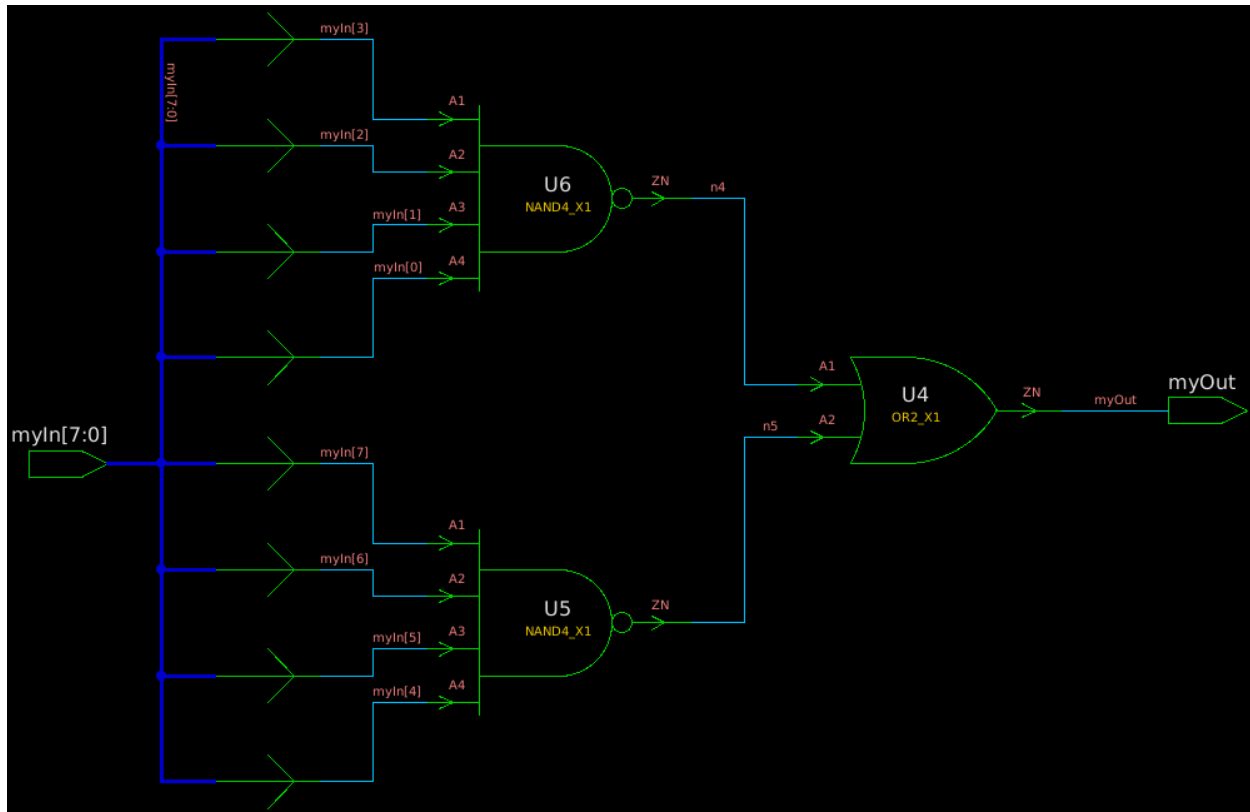3. [Synthesis, 20 points]

- In this problem, we will synthesize a netlist for a few gates.
- Make sure you have the following files in your working directory.
 - NangateOpenCellLibrary_typical_ecsm.db
 - nand8.v
- Source synopsys.sh.
- Run Design Compiler (DC).
 - design_vision -no_gui
- In DC, run the following commands.
 - set link_library {NangateOpenCellLibrary_typical_ecsm.db}
 - set target_library {NangateOpenCellLibrary_typical_ecsm.db}
 - read_file -format verilog {nand8.v}
 - compile -exact_map
 - write -format verilog -output nand8_mapped.v
 - exit
- The two “set” statements set up target libraries.
- “read_file” reads HDL source codes.
- “compile” compiles (synthesizes) the source codes.

- “write” writes the synthesized code into the file specified after “-output”.
- Open “nand8.v” and see the function of the module.
- Open “nand8_mapped.v” and see the function of the module. Are they equal?
- [Submit] Draw a schematic for the netlist of “nand8_mapped.v”.



- Implement a 20-input nand gate by modifying “nand8.v” and synthesize it.
- [Submit] Draw a schematic for the netlist of the synthesized 20-input nand gate.

Code:


```

module myNAND20 (myIn, myOut);
    input [19:0] myIn;
    output [19:0] myOut;

    assign myOut = !(myIn[0] && myIn[1] && myIn[2] && myIn[3] && myIn[4] && myIn[5]
    && myIn[6] && myIn[7] && myIn[8] && myIn[9] && myIn[10] && myIn[11] && myIn[12]
    && myIn[13] && myIn[14] && myIn[15] && myIn[16] && myIn[17] && myIn[18] &&
    myIn[19]);

endmodule

```

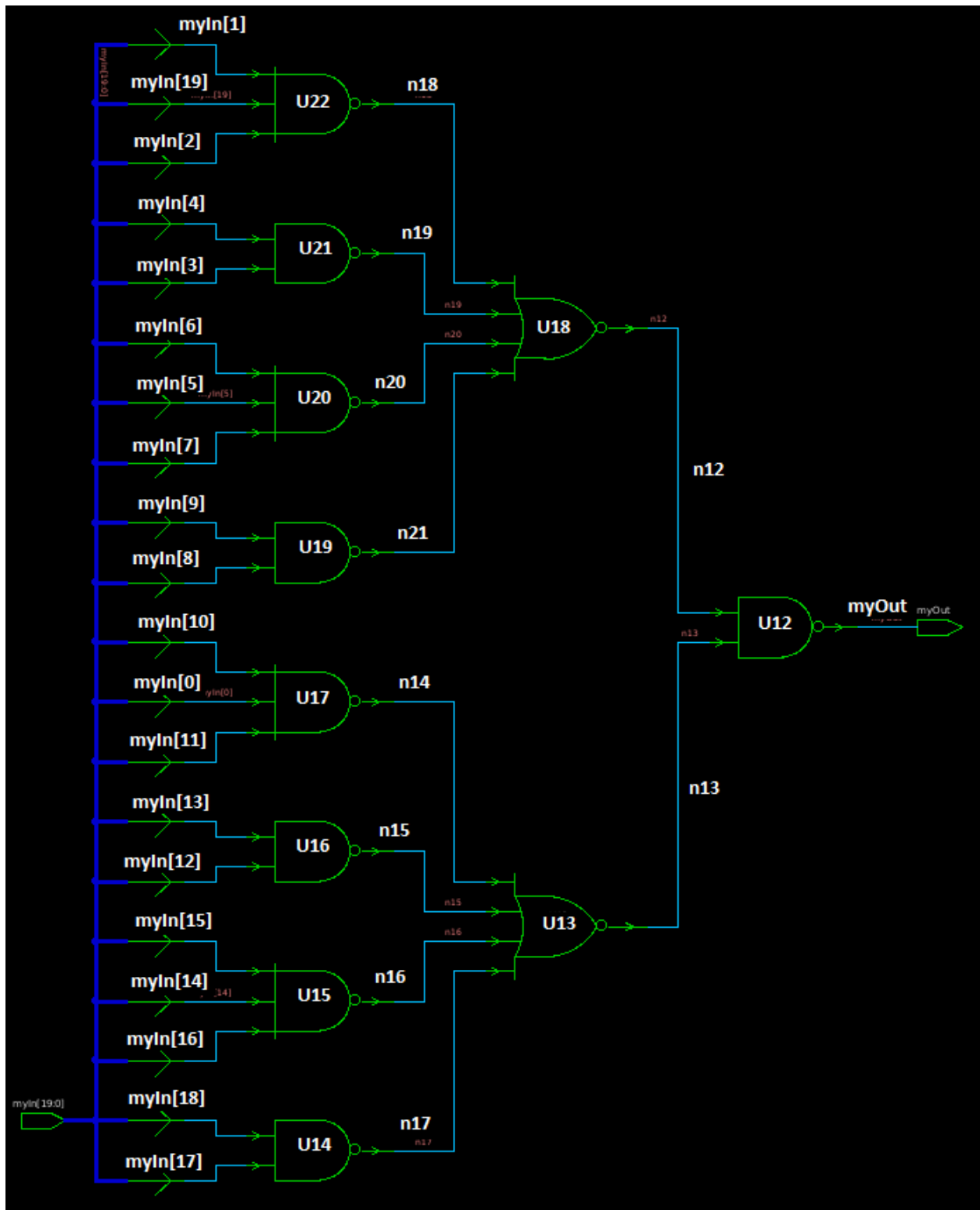

- Implement a full adder and synthesize it.
 - Primary inputs: A, B, CI
 - Primary outputs: S, CO

- Use ^, &&, and || for XOR, logical AND, and logical OR operations in Verilog.
- Use parentheses to prioritize the operations.
- Use two assignments, one for S and the other for CO.
- **[Submit]** Draw a schematic for the netlist of the synthesized full adder.

Code

```

module myFA1 (A, B, Cin, S, CO);
    input A, B, Cin;
    output S, CO;
    assign S = A ^ B ^ Cin;
    assign CO = (A && B) || (B && Cin) || (Cin && A);
endmodule

```

