

Electronic Analysis of CMOS Logic Gates

Dae Hyun Kim

EECS
Washington State University

References


- John P. Uyemura, “Introduction to VLSI Circuits and Systems,” 2002.
 - Chapter 7

Goal


- Understand how to perform electronic analysis of CMOS logic gates.
 - DC characteristics
 - Noise margin
 - Switching characteristics
 - Power

Analysis

 - DC Analysis
 - V_{in} vs. V_{out} = Voltage Transfer Characteristic (VTC)




 - Transient (switching) analysis
 - $V_{in}(t)$ vs. $V_{out}(t)$



CMOS Inverter – DC Characteristics

 - Logic swing
 - When $V_{in} = 0$
 - $V_{out} = V_{DD}$
 - Output high voltage $V_{OH} = V_{DD}$
 - When $V_{in} = V_{DD}$
 - $V_{out} = 0$
 - Output low voltage $V_{OL} = 0$
 - Logic swing
 - $V_L = V_{OH} - V_{OL} = V_{DD}$



CMOS Inverter – DC Characteristics

- Region A ($0 \leq V_{in} \leq V_{Tn}$)


- Mn

- $V_{GSn} = V_{in} - 0 = V_{in}$
 - $V_{GSn} < V_{Tn}$: **Cut-off**

- Mp

- $V_{SGp} = V_{DD} - V_{in}$
 - $V_{SDp} = V_{DD} - V_{out}$
 - $(V_{SGp} - |V_{Tp}|) - V_{SDp} = V_{out} - V_{in} - |V_{Tp}| > 0$
 - $V_{SGp} - |V_{Tp}| > V_{SDp}$: **Linear**

- $V_{out} \approx V_{DD}$

 

CMOS Inverter – DC Characteristics



- Region B ($V_{Tn} \leq V_{in} < \frac{V_{DD}}{2}$)

– Mn

- $V_{GSn} - V_{Tn} = V_{in} - V_{Tn} > 0$
- $V_{DSn} = V_{out}$
- $(V_{GSn} - V_{Tn}) - V_{DSn} = V_{in} - V_{Tn} - V_{out} < 0$
- $V_{GSn} - V_{Tn} < V_{DSn}$: **Saturation**

– Mp

- $V_{SGp} = V_{DD} - V_{in}$
- $V_{SDp} = V_{DD} - V_{out}$
- $(V_{SGp} - |V_{Tp}|) - V_{SDp} = V_{out} - V_{in} - |V_{Tp}| > 0$
- $V_{SGp} - |V_{Tp}| > V_{SDp}$: **Linear**

  

$$- V_{out} = (V_{in} - |V_{Tp}|) + \sqrt{(V_{in} - |V_{Tp}|)^2 - 2 \left(V_{in} - \frac{V_{DD}}{2} - |V_{Tp}| \right) V_{DD} - \frac{\beta_n}{\beta_p} (V_{in} - V_{Tn})^2}$$

CMOS Inverter – DC Characteristics

- Region C ($V_{in} \approx \frac{V_{DD}}{2}$)

- Mn

- $(V_{GSn} - V_{Tn}) - V_{DSn} = V_{in} - V_{Tn} - V_{out} < 0$
- $V_{GSn} - V_{Tn} < V_{DSn}$: **Saturation**

- Mp



- $(V_{SGp} - |V_{Tp}|) - V_{SDp} = V_{out} - V_{in} - |V_{Tp}| < 0$
- $V_{SGp} - |V_{Tp}| < V_{SDp}$: **Saturation**

- $I_{DSn} = \frac{\beta_n}{2} (V_M - V_{Tn})^2$

- $I_{SDp} = \frac{\beta_p}{2} (V_{DD} - V_M - |V_{Tp}|)^2$

- Solve $I_{DSn} = I_{SDp}$.

- $$V_M = \frac{V_{DD} - |V_{Tp}| + V_{Tn} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}}$$

  

CMOS Inverter – DC Characteristics

- Region D ($\frac{V_{DD}}{2} < V_{in} \leq V_{DD} - |V_{Tp}|$)


– Mn

- $V_{GSn} - V_{Tn} = V_{in} - V_{Tn} > 0$
- $V_{DSn} = V_{out}$
- $(V_{GSn} - V_{Tn}) - V_{DSn} = V_{in} - V_{Tn} - V_{out} > 0$
- $V_{GSn} - V_{Tn} > V_{DSn}$: **Linear**

– Mp


- $V_{SGp} = V_{DD} - V_{in}$
- $V_{SDp} = V_{DD} - V_{out}$
- $(V_{SGp} - |V_{Tp}|) - V_{SDp} = V_{out} - V_{in} - |V_{Tp}| < 0$
- $V_{SGp} - |V_{Tp}| < V_{SDp}$: **Saturation**

–
$$V_{out} = (V_{in} - V_{Tn}) - \sqrt{(V_{in} - V_{Tn})^2 - \frac{\beta_p}{\beta_n} (V_{in} - V_{DD} - |V_{Tp}|)^2}$$

 


CMOS Inverter – DC Characteristics

- Region E ($V_{DD} - |V_{Tp}| \leq V_{in} \leq V_{DD}$)
 - Mn
 - $V_{GSn} - V_{Tn} = V_{in} - V_{Tn} > 0$
 - $V_{DSn} = V_{out}$
 - $(V_{GSn} - V_{Tn}) - V_{DSn} = V_{in} - V_{Tn} - V_{out} > 0$
 - $V_{GSn} - V_{Tn} > V_{DSn}$: **Linear**
 - Mp
 - $V_{SGp} = V_{DD} - V_{in}$
 - $V_{SGp} - |V_{Tp}| < 0$: **Cut-off**
 - $V_{out} \approx 0$

 



CMOS Inverter – DC Characteristics

 - Voltage noise margin
 - $VNM_H = V_{OH} - V_{IH}$
 - $VNM_L = V_{IL} - V_{OL}$
- V_{IH} : Min. high input voltage
- V_{IL} : Max. low input voltage
- V_{OH} : Min. high output voltage
- V_{OL} : Max. low output voltage



CMOS Inverter – Switching Characteristics

  - t_r : rise time
- t_f : fall time
- C_{out} : total output capacitance
 - $C_{out} = C_{FET} + C_L$
 - C_{FET} : FET capacitance
 - $C_{FET} = C_{Dn} + C_{Dp}$
 - » $C_{Dn} = C_{GSn} + C_{DBn}$
 - » $C_{Dp} = C_{GSp} + C_{DBp}$
 - C_L : load capacitance



CMOS Inverter – Switching Characteristics

- Fall time
 - From $V_{out} = 0.9V_{DD}$ to $V_{out} = 0.1V_{DD}$

- Fall time calculation
 - Discharging (Natural response)

- $i = -C_{out} \frac{dV_{out}}{dt} = \frac{V_{out}}{R_n}$

- $R_n = \frac{1}{\beta_n(V_{DD} - V_{Tn})}$

- $V_{out}(t) = V_{DD} e^{-\frac{t}{\tau_n}}$

- $\tau_n = R_n C_{out}$ (time constant)


- $t = \tau_n \ln \left(\frac{V_{DD}}{V_{out}} \right)$

- $t_f = t(V_{out} = 0.1V_{DD}) - t(V_{out} = 0.9V_{DD}) = \tau_n \left(\ln 10 - \ln \frac{10}{9} \right) = \tau_n \ln 9$

- $t_f \approx 2.2\tau_n$


- $t_{HL} = t_f$

- t_{HL} : high-to-low time

 


CMOS Inverter – Switching Characteristics

- Rise time
 - From $V_{out} = 0.1V_{DD}$ to $V_{out} = 0.9V_{DD}$
- Rise time calculation
 - Charging (Step response)
 - $i = C_{out} \frac{dV_{out}}{dt} = \frac{V_{DD} - V_{out}}{R_p}$
 - $R_p = \frac{1}{\beta_p(V_{DD} - |V_{Tp}|)}$
 - $V_{out}(t) = V_{DD} \left(1 - e^{-\frac{t}{\tau_p}}\right)$
 - $\tau_p = R_p C_{out}$ (time constant)
 - $t = \tau_p \ln\left(\frac{V_{DD}}{V_{DD} - V_{out}}\right)$
 - $t_r = t(V_{out} = 0.9V_{DD}) - t(V_{out} = 0.1V_{DD}) = \tau_p \left(\ln 10 - \ln \frac{10}{9}\right) = \tau_p \ln 9$
 - $t_r \approx 2.2\tau_p$
 - $t_{LH} = t_r$
 - t_{LH} : low-to-high time

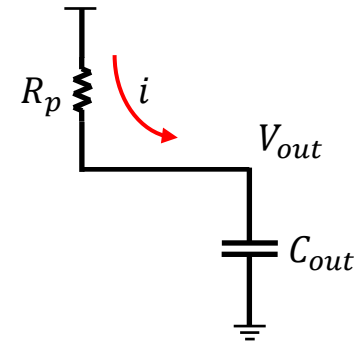


CMOS Inverter – Switching Characteristics

 - Transient simulation of a CMOS inverter



CMOS Inverter – Switching Characteristics

- Maximum signal frequency
 - The largest frequency
 - $f_{max} = \frac{1}{t_{HL}+t_{LH}} = \frac{1}{t_f+t_r} = \frac{1}{2.2(\tau_n+\tau_p)}$
 - Example
 - $R_n = R_p = 500\Omega$
 - $C_{out} = 10fF$
 - $f_{max} = \frac{1}{2.2(5ps+5ps)} \approx 45GHz$
- Propagation delay
 - Delay time from input to output
 - $t_p = \frac{t_{pf}+t_{pr}}{2}$
 - t_{pf} : output fall time ($V_{DD} \rightarrow \frac{V_{DD}}{2}$)
 - $t_{pf} = \tau_n \ln 2$
 - t_{pr} : output rise time ($0 \rightarrow \frac{V_{DD}}{2}$)
 - $t_{pr} = \tau_p \ln 2$


 


CMOS Inverter – General Analysis

- Output capacitance
 - $C_{out} = C_{FET} + C_L$
- Rise time
 - $t_r = \tau_p \ln 9 \approx 2.2R_p(C_{FET} + C_L) = t_{r0} + 2.2R_pC_L$
 - $R_p = \frac{1}{\beta_p(V_{DD} - |V_{Tp}|)}$
- Fall time
 - $t_f = \tau_n \ln 9 \approx 2.2R_n(C_{FET} + C_L) = t_{f0} + 2.2R_nC_L$
 - $R_n = \frac{1}{\beta_n(V_{DD} - V_{Tp})}$
- Speed vs. area
 - $\beta \uparrow \Rightarrow R \downarrow \Rightarrow t \downarrow$
 - Area goes up, but the logic is faster.


CMOS Inverter – Power Dissipation

- Power dissipation calculation
 - $P = V_{DD}I_{DD}$
 - $P = P_{DC} + P_{dyn}$
 - P_{DC} : DC power
 - Region A, E: $I_{DD} = 0$
 - Actually, there is leakage current I_{DDQ} .
 - » I_{DDQ} : quiescent leakage current
 - $P_{DC} = V_{DD}I_{DDQ}$
 - P_{dyn} : Dynamic power
 - Charging/Discharging
 - $Q_e = C_{out}V_{DD}$
 - $P = V_{DD}I_{DD} = V_{DD} \left(\frac{Q_e}{T} \right) = fC_{out}V_{DD}^2$
- $P = V_{DD}I_{DDQ} + fC_{out}V_{DD}^2$

  


NAND2 – DC Characteristics

- $V_{Tn,B}$ goes up.

 


	V_A	V_B
(i)	$0 \rightarrow V_{DD}$	$0 \rightarrow V_{DD}$
(ii)	V_{DD}	$0 \rightarrow V_{DD}$
(iii)	$0 \rightarrow V_{DD}$	V_{DD}

 


NAND2 – DC Characteristics

- V_M ($V_{in} = V_{out} = V_M$)
 - nFET network: $\frac{\beta_n}{2}$
 - pFET network: $2\beta_p$
 - Mn (V_A): $(V_{GSn} - V_{Tn}) - V_{DSn} = (V_M - V_{Tn}) - (< V_M) < 0$: **Saturation**
 - Mn (V_B): $(V_{GSn} - V_{Tn}) - V_{DSn} = (V_M - V_S - V_{Tn}) - (V_M - V_S) < 0$: **Saturation**
 - Mp: $(V_{SGp} - |V_{Tp}|) - V_{SDp} = (V_{DD} - V_M - |V_{Tp}|) - (V_{DD} - V_M) < 0$: **Saturation**
 - $I_{DSn} = \frac{(\beta_n)}{2} (V_M - V_{Tn})^2$
 - $I_{SDp} = \frac{(2\beta_p)}{2} (V_{DD} - V_M - |V_{Tp}|)^2$
 - Solve $I_{DSn} = I_{SDp}$.
 - $$V_M = \frac{V_{DD} - |V_{Tp}| + \frac{1}{2}V_{Tn} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \frac{1}{2}\sqrt{\frac{\beta_n}{\beta_p}}}$$
- For NANDk
 - $$V_M = \frac{V_{DD} - |V_{Tp}| + \frac{1}{k}V_{Tn} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \frac{1}{k}\sqrt{\frac{\beta_n}{\beta_p}}}$$

 


NOR2 – DC Characteristics

- $|V_{Tp,B}|$ goes up.

 


	V_A	V_B
(i)	$0 \rightarrow V_{DD}$	$0 \rightarrow V_{DD}$
(ii)	0	$0 \rightarrow V_{DD}$
(iii)	$0 \rightarrow V_{DD}$	0

 


NOR2 – DC Characteristics

- V_M ($V_{in} = V_{out} = V_M$)
 - nFET network: $2\beta_n$
 - pFET network: $\frac{\beta_p}{2}$
 - Mn: $(V_{GSn} - V_{Tn}) - V_{DSn} = (V_M - V_{Tn}) - V_M < 0$: **Saturation**
 - Mp (V_A): $(V_{SGp} - |V_{Tp}|) - V_{SDp} = (V_{DD} - V_M - |V_{Tp}|) - (V_{DD} - V_M) < 0$: **Saturation**
 - Mp (V_B): $(V_{SGp} - |V_{Tp}|) - V_{SDp} = (V_S - V_M - |V_{Tp}|) - (V_S - V_M) < 0$: **Saturation**
 - $I_{DSn} = \frac{2\beta_n}{2} (V_M - V_{Tn})^2$
 - $I_{SDp} = \frac{(\frac{\beta_p}{2})}{2} (V_{DD} - V_M - |V_{Tp}|)^2$
 - Solve $I_{DSn} = I_{SDp}$.
 - $$V_M = \frac{V_{DD} - |V_{Tp}| + 2V_{Tn} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + 2\sqrt{\frac{\beta_n}{\beta_p}}}$$
- For NORk
 - $$V_M = \frac{V_{DD} - |V_{Tp}| + kV_{Tn} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + k\sqrt{\frac{\beta_n}{\beta_p}}}$$

 

Elmore Delay

 
- How to estimate delay in general RC networks.
 - How to
 - Start at the target sink node.
 - Traverse the RC network toward the source.
 - Whenever there is a resistor, multiply its resistance and its downstream capacitance and add it to the total delay.
 - For two-pin nets



$$\tau = R_n(C_n + C_L) + R_{n-1}(C_{n-1} + C_n + C_L) + R_{n-2}(C_{n-2} + C_{n-1} + C_n + C_L) + \dots + R_3(C_3 + \dots + C_n + C_L) + R_2(C_2 + \dots + C_n + C_L) + R_1(C_1 + \dots + C_n + C_L) + R_{out}(C_1 + \dots + C_n + C_L)$$

Elmore Delay

 
- How to estimate delay in general RC networks.
 - For multi-pin nets



$$\begin{aligned} \tau(V_{out1}) = & R_n(C_n + C_{L1}) + R_{n-1}(C_{n-1} + C_n + C_{L1}) + \\ & R_{n-2}(C_{n-2} + C_{n-1} + C_n + C_{L1} + C_a + C_b + C_{L2}) + \\ & \dots + R_3(C_3 + \dots + C_n + C_{L1} + C_a + C_b + C_{L2}) + \\ & R_2(C_2 + \dots + C_n + C_{L1} + C_a + C_b + C_{L2}) + R_1(C_1 + \dots + C_n + C_{L1} + C_a + C_b + C_{L2}) + \\ & R_{out}(C_1 + \dots + C_n + C_{L1} + C_a + C_b + C_{L2}) \end{aligned}$$

NAND2 – Switching Characteristics

- t_r : rise time
- t_f : fall time
- C_{out} : total output capacitance
 - $C_{out} = C_{FET} + C_L$
 - C_{FET} : FET capacitance
 - $C_{FET} = C_{Dn} + 2C_{Dp}$
 - » $C_{Dn} = C_{GSn} + C_{DBn}$
 - » $C_{Dp} = C_{GSp} + C_{DBp}$
 - C_L : load capacitance
 - C_x : parasitic capacitance

 

NAND2 – Switching Characteristics

- Rise time


- If $AB: 11 \rightarrow 00$ (best case)

- $V_{out}(t) = V_{DD} \left(1 - e^{-\frac{t}{\tau_p}}\right)$
 - $\tau_p = \frac{R_p}{2} C_{out}$
 - $t_r \approx 2.2\tau_p$

- If $AB: 11 \rightarrow 10$ or $AB: 11 \rightarrow 01$ (worst case)

- $V_{out}(t) = V_{DD} \left(1 - e^{-\frac{t}{\tau_p}}\right)$
 - $\tau_p = R_p C_{out}$
 - $t_r \approx 2.2\tau_p$

- $t_r = 2.2R_p(C_{FET} + C_L)$

 

NAND2 – Switching Characteristics

- Fall time

- If $AB: 00 \rightarrow 11$ or $AB: 10 \rightarrow 11$ (best case)

- $V_{out}(t) = V_{DD} e^{-\frac{t}{\tau_n}}$

- $\tau_n = 2R_n C_{out}$

- $t_f \approx 2.2\tau_n$


- If $AB: 01 \rightarrow 11$ (worst case)

- $V_{out}(t) = V_{DD} e^{-\frac{t}{\tau_n}}$

- $\tau_n = 2R_n C_{out} + R_n C_x$


- $t_f \approx 2.2\tau_n$

- $t_f = 2.2[2R_n(C_{FET} + C_L)] + 2.2R_n C_x$

 

NOR2 – Switching Characteristics

- t_r : rise time
- t_f : fall time
- C_{out} : total output capacitance
 - $C_{out} = C_{FET} + C_L$
 - C_{FET} : FET capacitance
 - $C_{FET} = 2C_{Dn} + C_{Dp}$
 - » $C_{Dn} = C_{GSn} + C_{DBn}$
 - » $C_{Dp} = C_{GSp} + C_{DBp}$
 - C_L : load capacitance
 - C_x : parasitic capacitance

 

NOR2 – Switching Characteristics

- Fall time

- If $AB: 00 \rightarrow 11$ (best case)

- $V_{out}(t) = V_{DD} e^{-\frac{t}{\tau_n}}$

- $\tau_n = \frac{R_n}{2} C_{out}$

- $t_f \approx 2.2\tau_n$


- If $AB: 00 \rightarrow 10$ or $AB: 00 \rightarrow 01$ (worst case)

- $V_{out}(t) = V_{DD} e^{-\frac{t}{\tau_n}}$

- $\tau_n = R_n C_{out}$

- $t_f \approx 2.2\tau_n$

- $t_f = 2.2R_n C_{out}$

 

NOR2 – Switching Characteristics

- Rise time


- If $AB: 01 \rightarrow 00$ (best case)

- $V_{out}(t) = V_{DD} \left(1 - e^{-\frac{t}{\tau_p}}\right)$
 - $\tau_p = 2R_p C_{out}$
 - $t_r \approx 2.2\tau_p$

- If $AB: 10 \rightarrow 00$ or $AB: 11 \rightarrow 00$ (worst case)

- $V_{out}(t) = V_{DD} \left(1 - e^{-\frac{t}{\tau_p}}\right)$
 - $\tau_p = 2R_p C_{out} + R_p C_y$
 - $t_r \approx 2.2\tau_p$

 - $t_r = 2.2[2R_p(C_{FET} + C_L)] + 2.2R_p C_y$



Power Dissipation

- Dynamic power

- $P_{dyn} = \alpha f C V_{DD}^2$

- α : switching activity
 - f : clock frequency
 - C : capacitance

- More accurate formula


- $P_{dyn} = f V_{DD}^2 \sum_{i=1}^n \alpha_i C_i$

Transmission Gates and Pass Transistors

- Transmission gates

- Approximation

 - $R_{TG} = \max(R_n, R_p)$
 - $C_{in} = C_{nFET,source} + C_{pFET,drain}$



- Pass transistors

- Rise time

- $t_r = 18R_n C_{out}$

- Fall time

- $t_f = 2.94R_n C_{out}$

