

Lecture 23

Design for Testability (DFT):

Full-Scan

(Lecture 19alt in the Alternative Sequence)

- Definition
- Ad-hoc methods
- *Scan design*
 - Design rules
 - Scan register
 - Scan flip-flops
 - Scan test sequences
 - Overheads
 - Scan design system
- Summary

Definition

- *Design for testability* (DFT) refers to those design techniques that make test generation and test application cost-effective.
- DFT methods for digital circuits:
 - Ad-hoc methods
 - Structured methods:
 - *Scan*
 - *Partial Scan*
 - *Built-in self-test* (BIST)
 - *Boundary scan*
- DFT method for mixed-signal circuits:
 - Analog test bus

Ad-Hoc DFT Methods

- Good design practices learnt through experience are used as guidelines:
 - Avoid asynchronous (unclocked) feedback.
 - Make flip-flops initializable.
 - Avoid redundant gates. Avoid large fanin gates.
 - Provide test control for difficult-to-control signals.
 - Avoid gated clocks.
 - Consider ATE requirements (tristates, etc.)
- Design reviews conducted by experts or design auditing tools.
- Disadvantages of ad-hoc DFT methods:
 - Experts and tools not always available.
 - Test generation is often manual with no guarantee of high fault coverage.
 - Design iterations may be necessary.

Scan Design


- Circuit is designed using pre-specified design rules.
- Test structure (hardware) is added to the verified design:
 - Add a *test control* (TC) primary input.
 - Replace flip-flops by *scan flip-flops* (SFF) and connect to form one or more shift registers in the test mode.
 - Make input/output of each scan shift register controllable/observable from PI/PO.
- Use combinational ATPG to obtain tests for all testable faults in the combinational logic.
- Add shift register tests and convert ATPG tests into scan sequences for use in manufacturing test.

Scan Design Rules



- Use only clocked D-type of flip-flops for all state variables.
- At least one PI pin must be available for test; more pins, if available, can be used.
- All clocks must be controlled from PIs.
- Clocks must not feed data inputs of flip-flops.

Correcting a Rule Violation

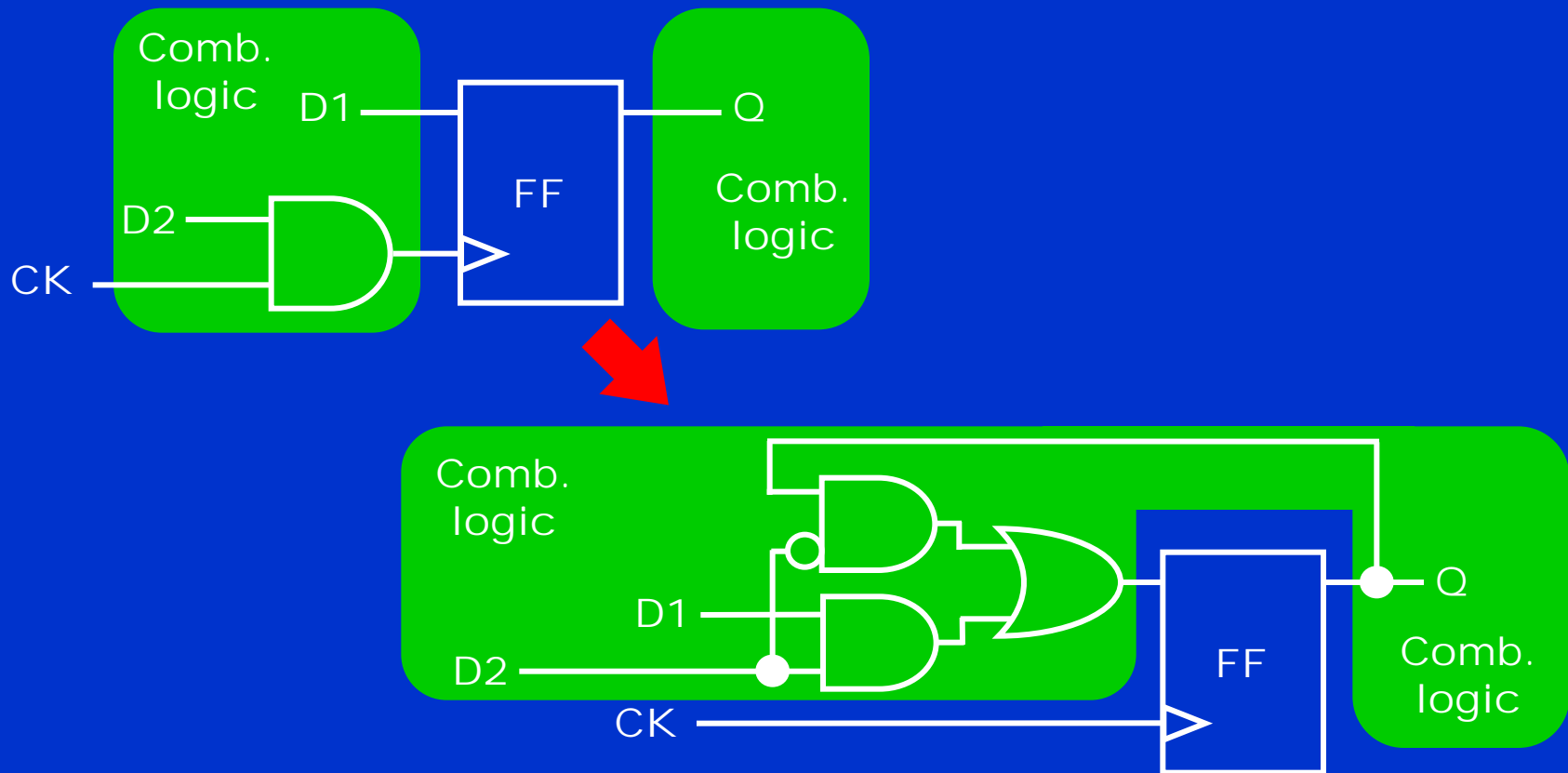
- All clocks must be controlled from PIs.




Scan Flip-Flop (SFF)

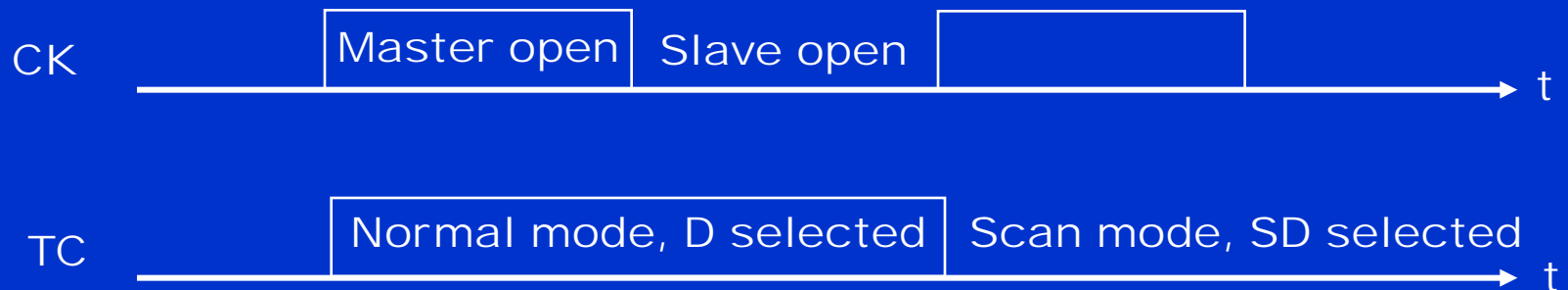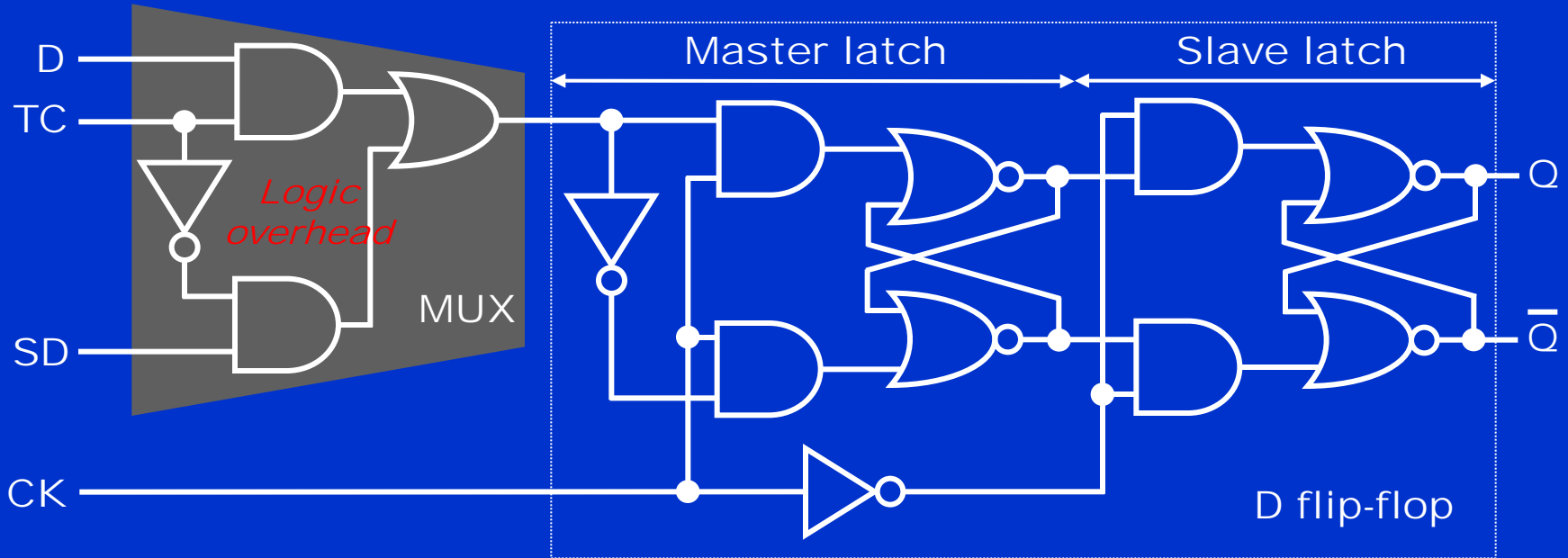

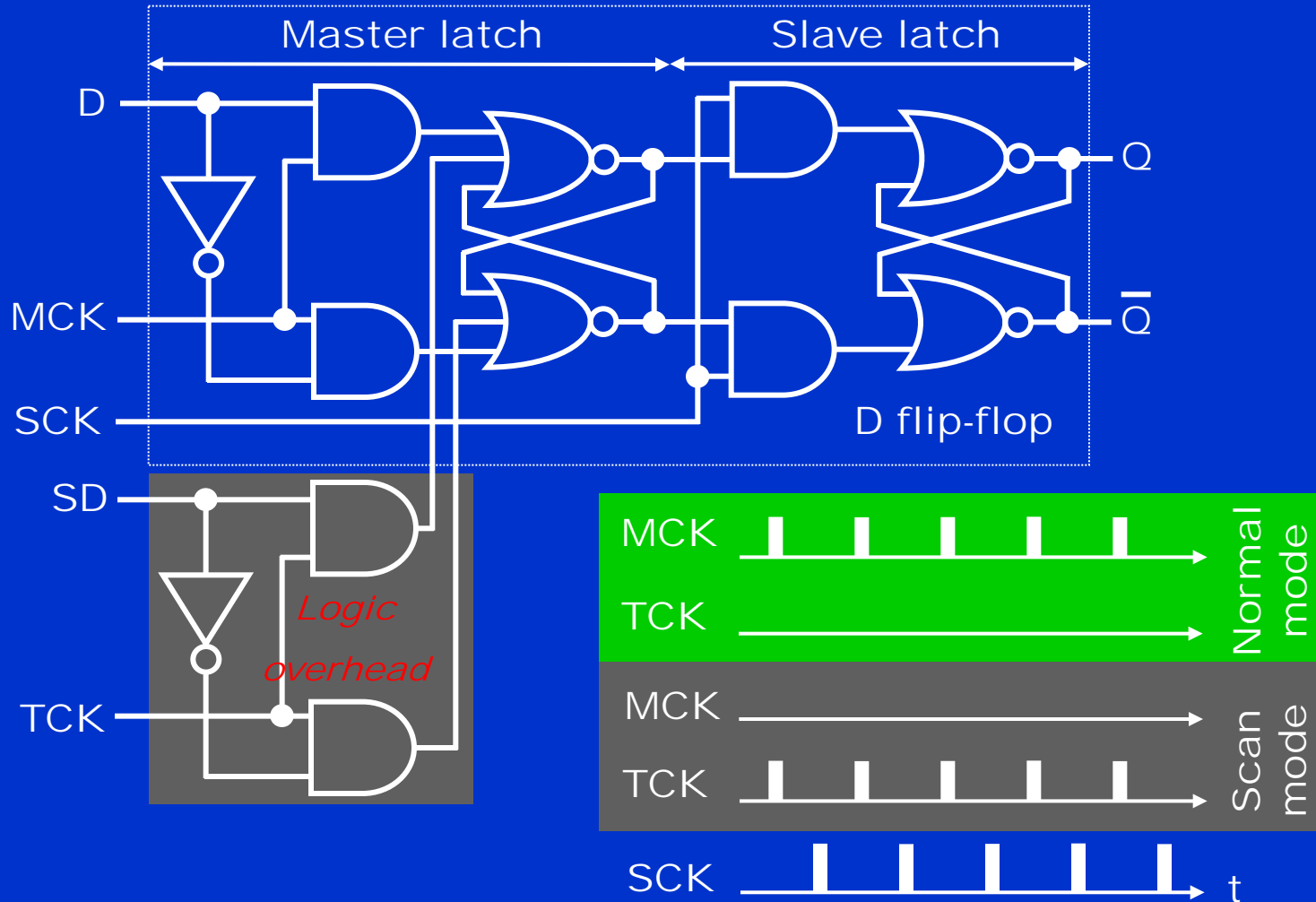Level-Sensitive Scan-Design Flip-Flop (LSSD-SFF)




Adding Scan Structure

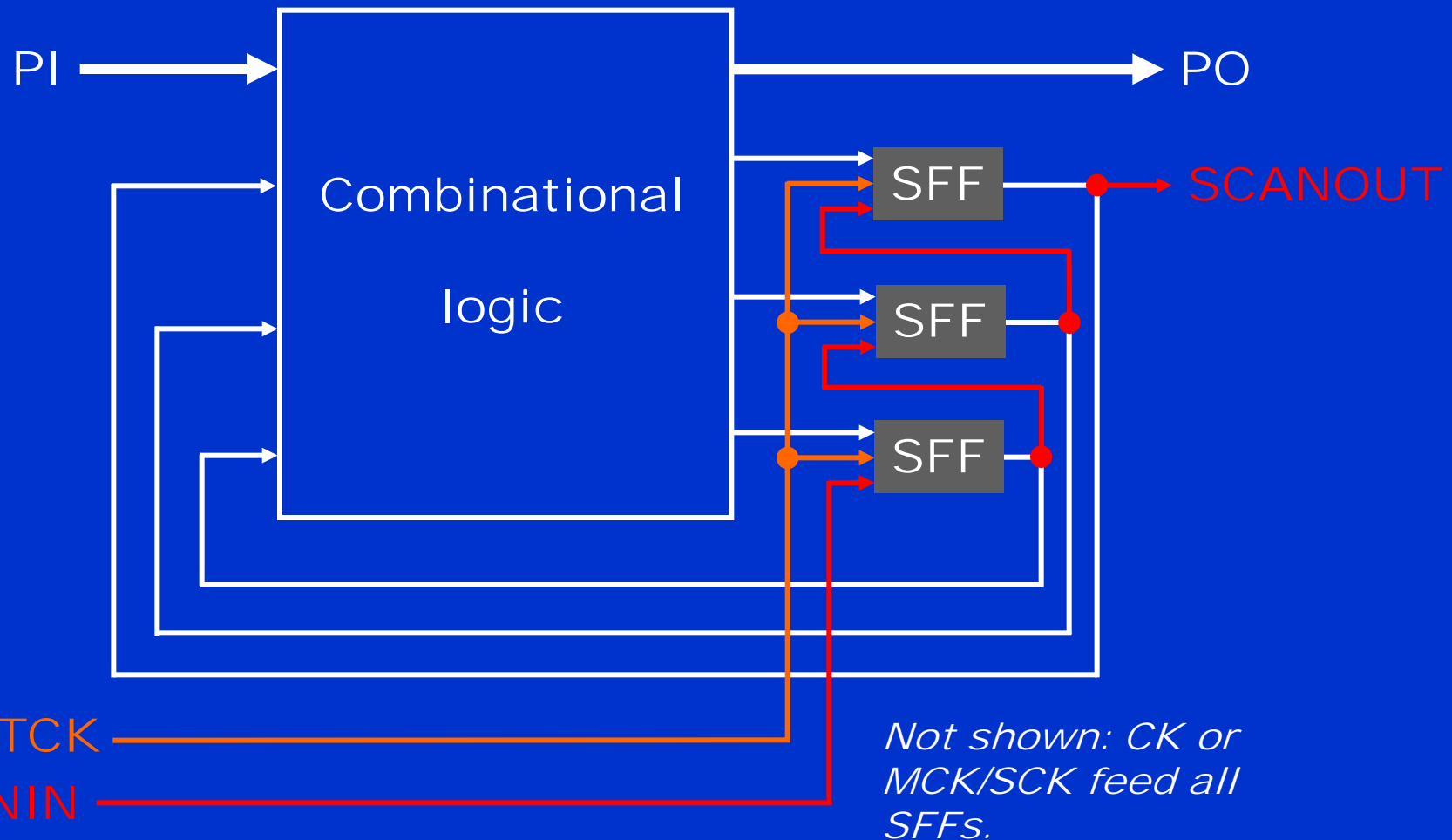


An Example

Combinational Circuit

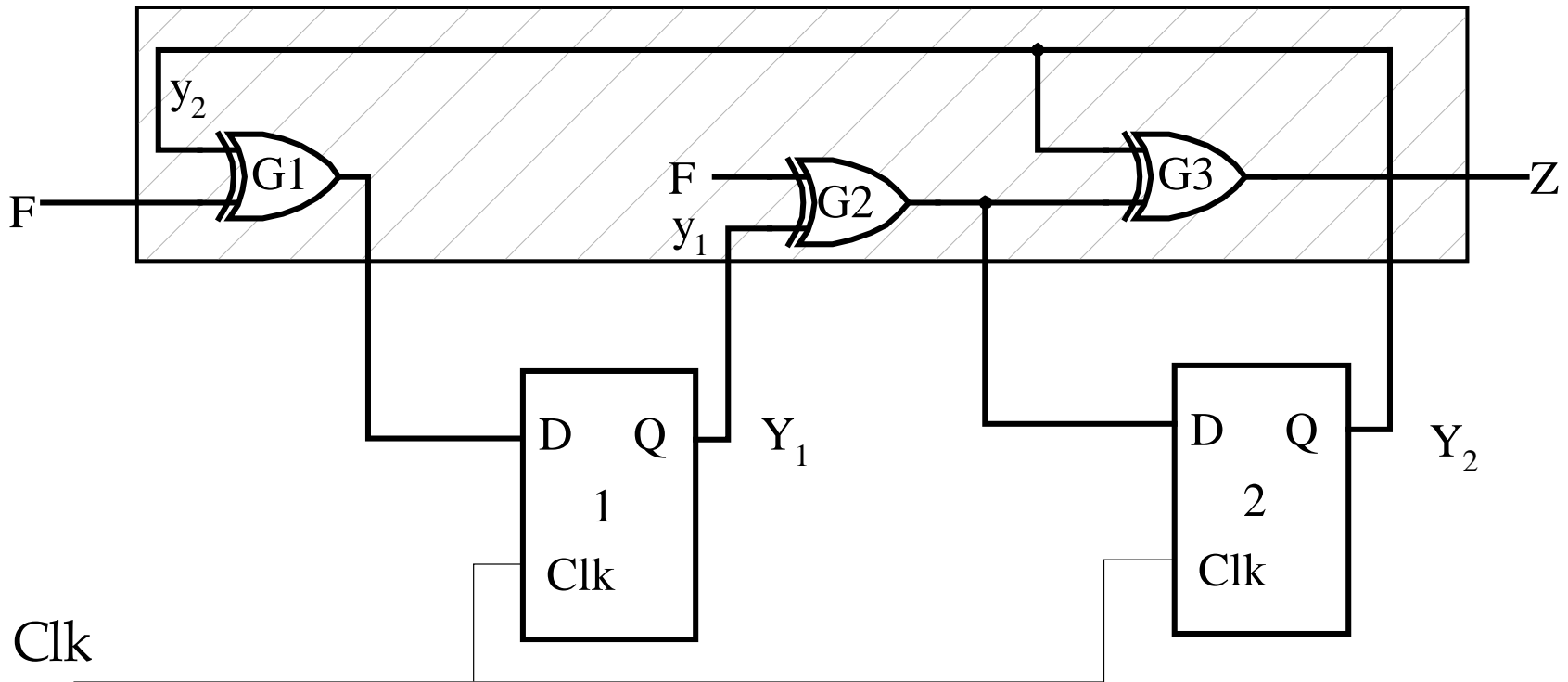


Inserting the Muxes


Combinational Circuit

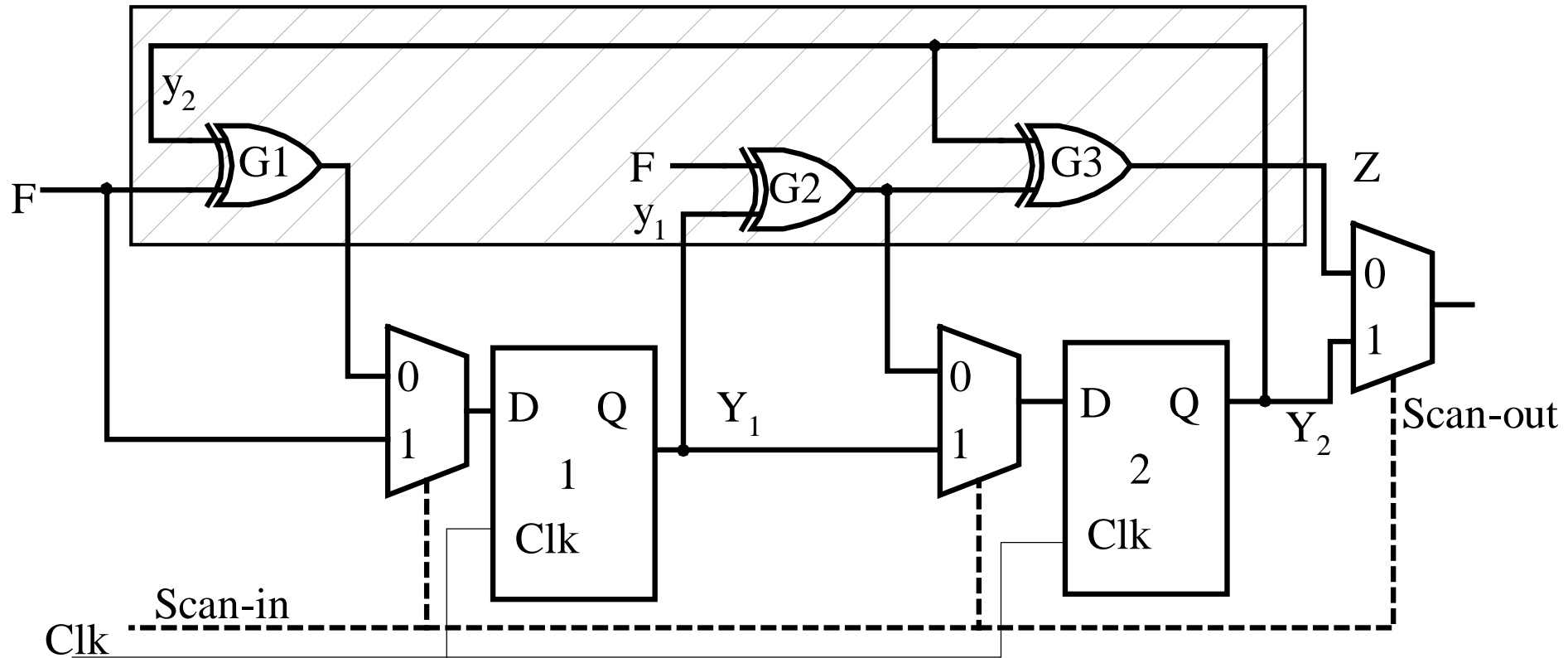

Comb. Test Vectors

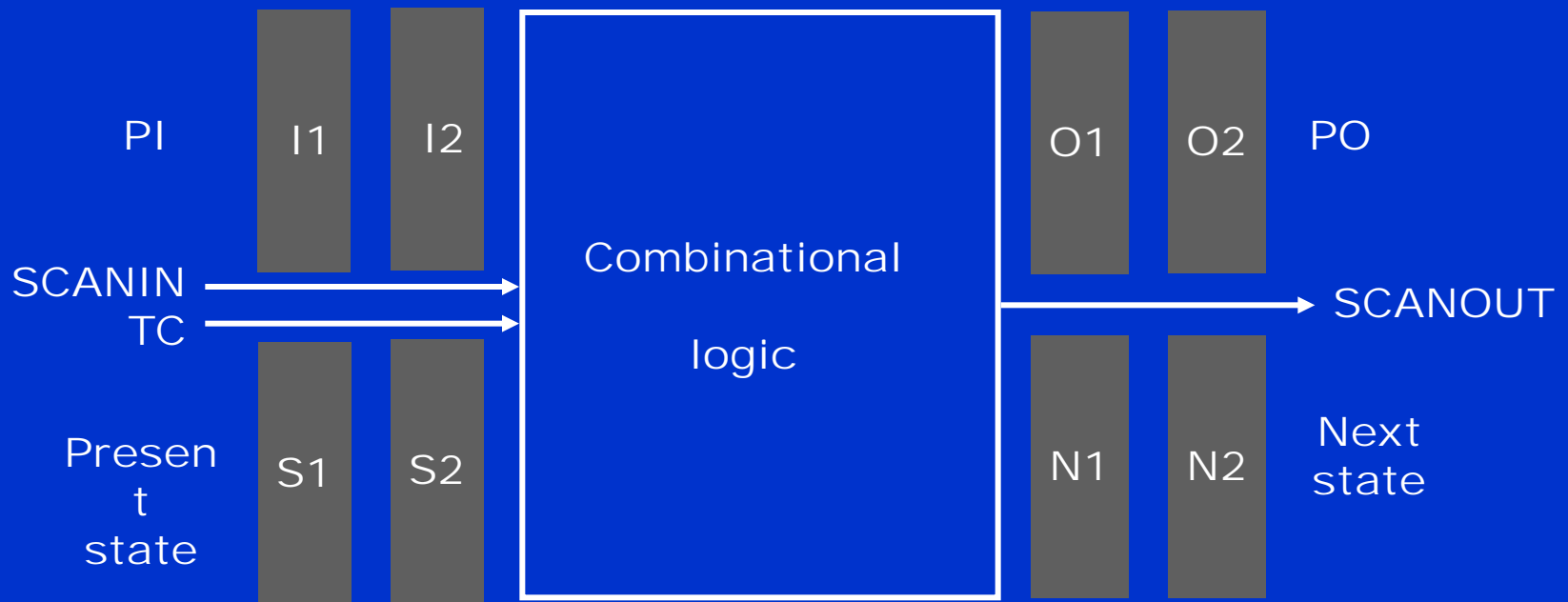

Comb. Test Vectors

 

Sequence length = $(n_{\text{comb}} + 1) n_{\text{sff}} + n_{\text{comb}}$ clock periods

n_{comb} = number of combinational vectors


n_{sff} = number of scan flip-flops

Testing Scan Register

- Scan register must be tested prior to application of scan test sequences.
- A shift sequence 00110011 . . . of length $n_{\text{sff}}+4$ in scan mode (TC=0) produces 00, 01, 11 and 10 transitions in all flip-flops and observes the result at SCANOUT output.
- Total scan test length: $(n_{\text{comb}} + 2) n_{\text{sff}} + n_{\text{comb}} + 4$ *clock periods*.
- Example: 2,000 scan flip-flops, 500 comb. vectors, total scan test length $\sim 10^6$ clocks.
- Multiple scan registers reduce test length.

Multiple Scan Registers

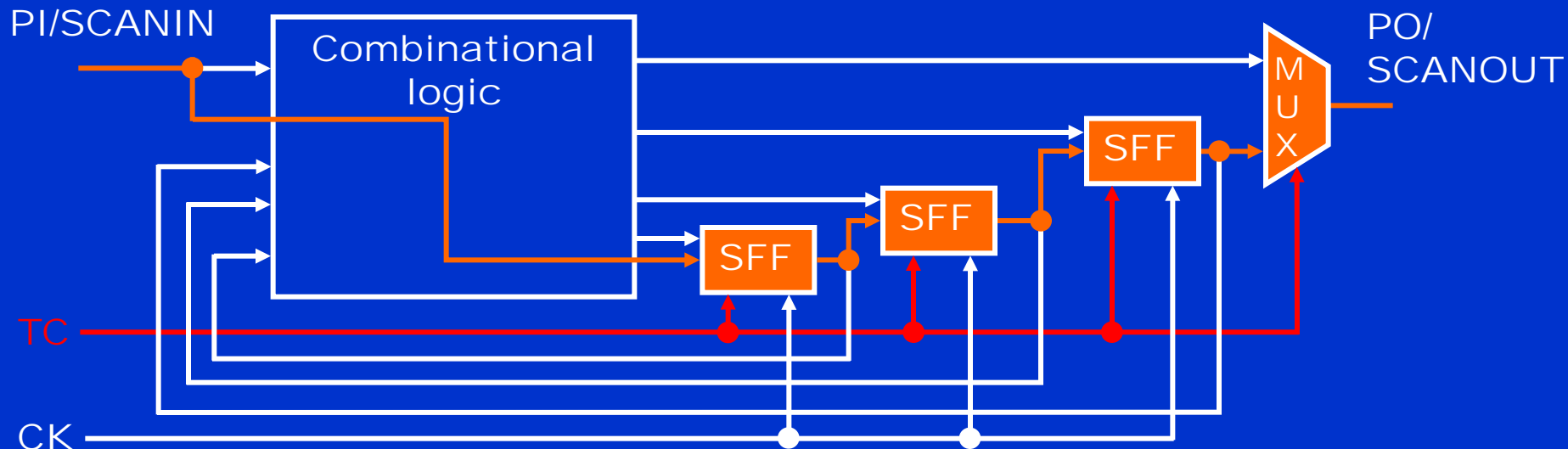- Scan flip-flops can be distributed among any number of shift registers, each having a separate *scanin* and *scanout* pin.
- Test sequence length is determined by the longest scan shift register.
- Just one *test control* (TC) pin is essential.




Scan Overheads


- IO pins: One pin necessary.
- Area overhead:
 - *Gate overhead* = $[4 n_{\text{sff}} / (n_{\text{g}} + 10 n_{\text{sff}})] \times 100\%$,
where n_{g} = *comb. gates*; n_{ff} = *flip-flops*;
Example – $n_{\text{g}} = 100\text{k gates}$, $n_{\text{sff}} = 2\text{k flip-flops}$, overhead = 6.7%.
 - More accurate estimate must consider scan wiring and layout area.
- Performance overhead:
 - Multiplexer delay added in combinational path; approx. two gate-delays.
 - Flip-flop output loading due to one additional fanout; approx. 5-6%.

Hierarchical Scan

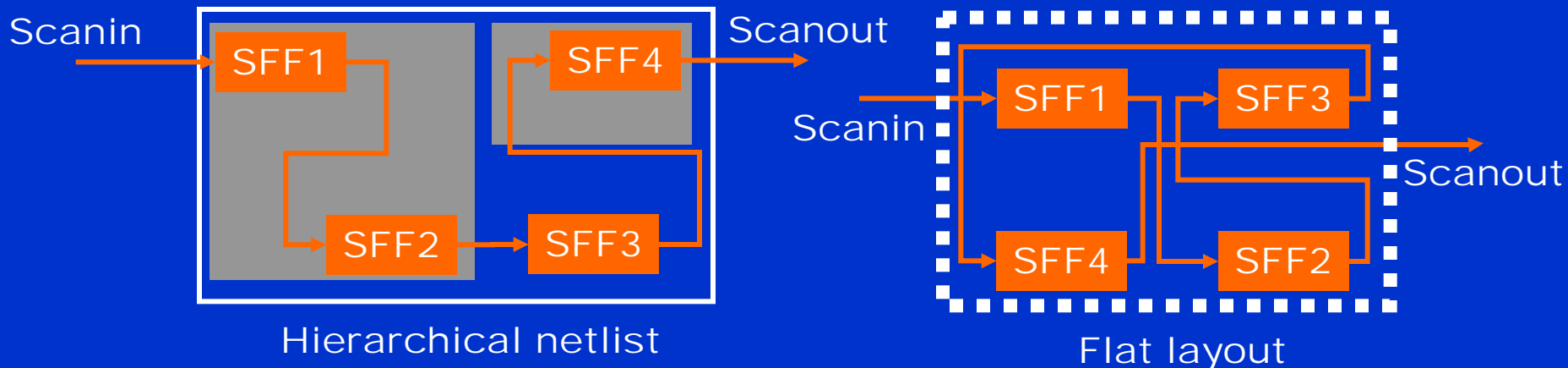- Scan flip-flops are chained within subnetworks before chaining subnetworks.
- Advantages:
 - Automatic scan insertion in netlist
 - Circuit hierarchy preserved – helps in debugging and design changes
- Disadvantage: Non-optimum chip layout.



Optimum Scan Layout

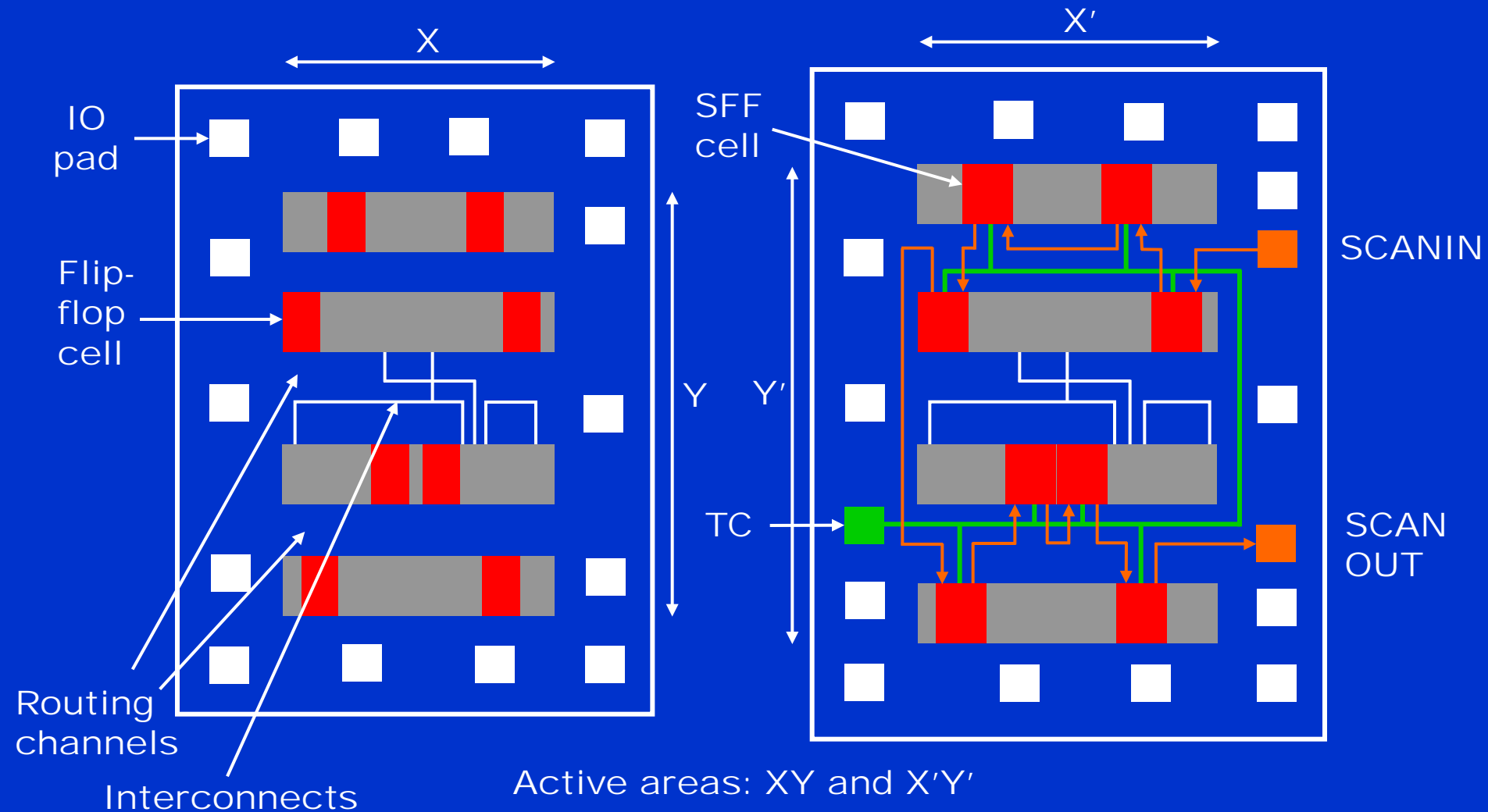

Scan Area Overhead

Linear dimensions of active area:

$$X = (C + S) / r$$

$$X' = (C + S + \alpha S) / r$$

$$Y' = Y + ry = Y + Y(1 - \beta) / T$$

Area overhead

$$= \frac{X'Y' - XY}{XY} \times 100\%$$

$$= \left[(1 + \alpha s) \left(1 + \frac{1 - \beta}{T} \right) - 1 \right] \times 100\%$$

$$= \left(\alpha s + \frac{1 - \beta}{T} \right) \times 100\%$$

y = track dimension, wire width+separation

C = total comb. cell width

S = total non-scan FF cell width

s = fractional FF cell area
= S/(C+S)

α = SFF cell width fractional increase

r = number of cell rows or routing channels

β = routing fraction in active area

T = cell height in track dimension y

Example: Scan Layout


- 2,000-gate CMOS chip
- Fractional area under flip-flop cells, $s = 0.478$
- Scan flip-flop (SFF) cell width increase, $\alpha = 0.25$
- Routing area fraction, $\beta = 0.471$
- Cell height in routing tracks, $T = 10$
- Calculated overhead = 17.24%
- Actual measured data:

Scan implementation	Area overhead	Normalized clock rate
None	0.0	1.00
Hierarchical	16.93%	0.87
Optimum layout	11.90%	0.91

ATPG Example: S5378

	Original	Full-scan
Number of combinational gates	2,781	2,781
Number of non-scan flip-flops (10 gates each)	179	0
Number of scan flip-flops (14 gates each)	0	179
Gate overhead	0.0%	15.66%
Number of faults	4,603	4,603
PI/PO for ATPG	35/49	214/228
Fault coverage	70.0%	99.1%
Fault efficiency	70.9%	100.0%
CPU time on SUN Ultra II, 200MHz processor	5,533 s	5 s
Number of ATPG vectors	414	585
Scan sequence length	414	105,662

Automated Scan Design

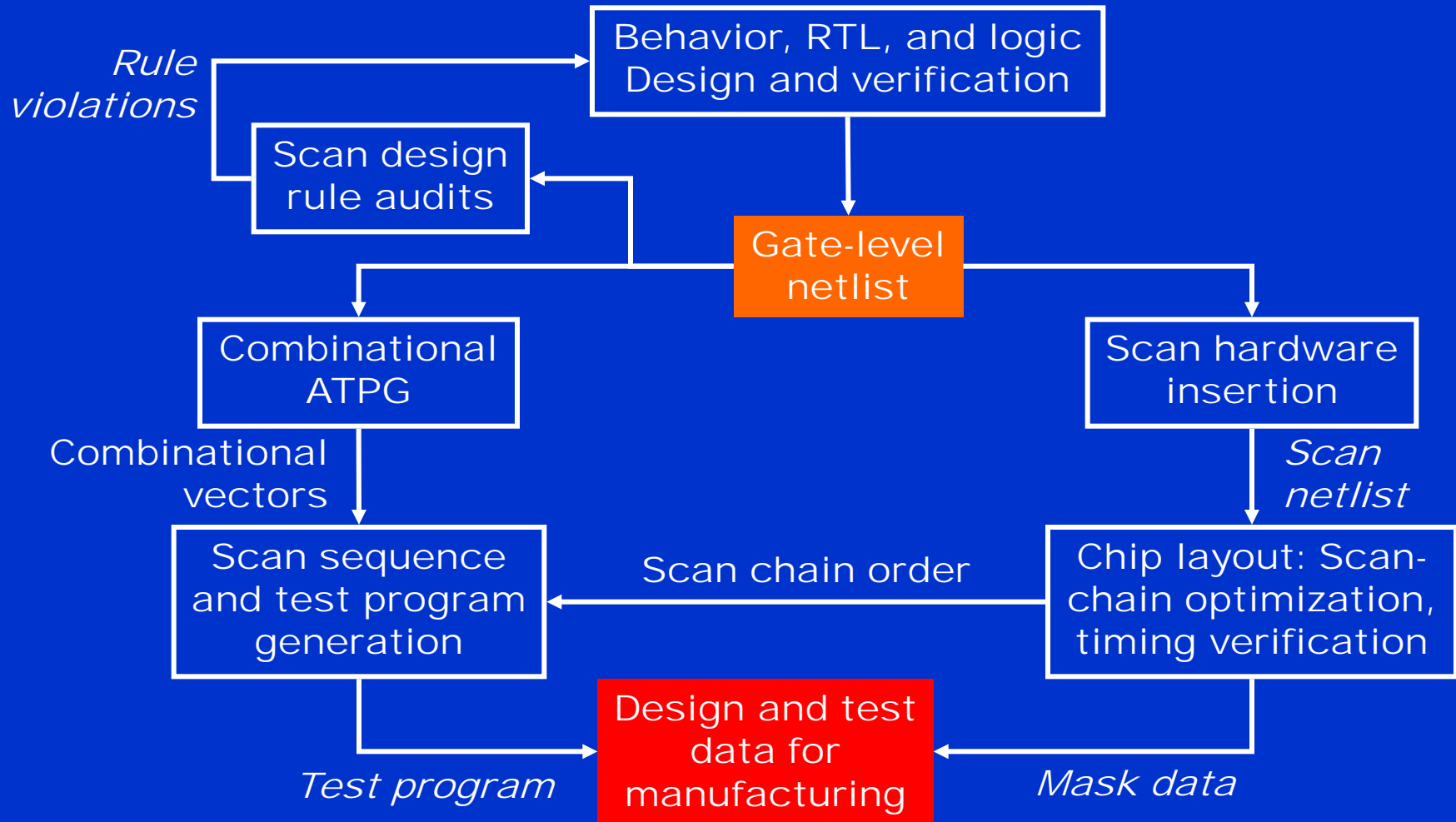

Timing and Power

- Small delays in scan path and clock skew can cause race condition.
- Large delays in scan path require slower scan clock.
- Dynamic multiplexers: Skew between TC and TC signals can cause momentary shorting of D and SD inputs.
- Random signal activity in combinational circuit during scan can cause excessive power dissipation.

Summary

- Scan is the most popular DFT technique:
 - Rule-based design
 - Automated DFT hardware insertion
 - Combinational ATPG
- Advantages:
 - Design automation
 - High fault coverage; helpful in diagnosis
 - Hierarchical – scan-testable modules are easily combined into large scan-testable systems
 - Moderate area (~10%) and speed (~5%) overheads
- Disadvantages:
 - Large test data volume and long test time
 - Basically a slow speed (DC) test