
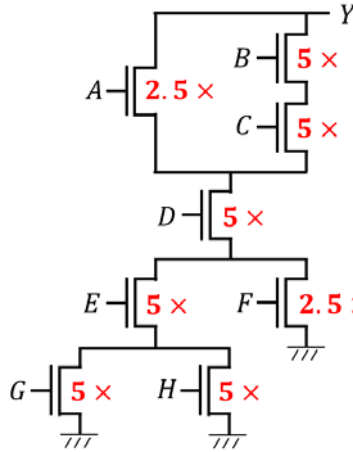


## Homework Assignment 5 (Due 4:10pm, Feb. 25)

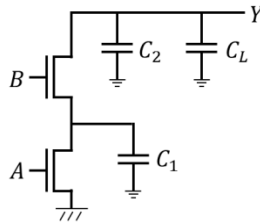(1) [Transistor Sizing, 20 points] The following shows a schematic of the NFET network of a static CMOS gate. Size the transistors so that the fall delay is less than or equal to  $R_n C_L$  where  $R_n$  is the resistance of a 1X NFET and  $C_L$  is the load capacitance. Try to minimize the total width. Find the total width.



(2) [Transistor Sizing, 40 points] The following shows a schematic of the NFET network of a static CMOS two-input NAND gate.  $C_L$  is a load capacitance. If we upsize the transistors, the drain and source capacitances increase. For more accurate transistor sizing, therefore, the figure shows two more capacitors,  $C_1$  and  $C_2$ . Find optimal sizes of transistor A and B minimizing the total area for timing constraint  $\tau_T = (d + 2)R_n c_0$ . See below for more details.



- Size of TR A:  $s_1$  (variable. You should find the optimal value of this variable.)
- Size of TR B:  $s_2$  (variable. You should find the optimal value of this variable.)
- $R_n$ : The resistance of a  $1 \times$  NFET (constant)
- $c_0$ : A unit capacitance (constant)

- $C_1 = c_0 \cdot (s_1 + s_2)$
- $C_2 = c_0 \cdot s_2$
- $C_L = c_0 \cdot k$  (constant,  $k$  is also a constant)
- Timing constraint: Delay =  $\tau_T = (d + 2)R_n c_0$  (constant,  $d$  is also a constant)
- The delay of the pull-down logic:  $\tau = R_2 \cdot (C_2 + C_L) + R_1 \cdot (C_1 + C_2 + C_L)$
- Total area:  $s_1 + s_2$

You can follow the instructions below:

- 1) You should satisfy the target timing constraint, which gives you an equation. Get the equation from the constraint, i.e., get an equation  $f(s_1, s_2, R_n, c_0, k, d) = 0$  from  $\tau = \tau_T$ . The equation will look like this:  $s_1 = \frac{\square \cdot s_2^2 + \square \cdot s_2}{\square \cdot s_2 - \square}$

$$\tau = \tau_T$$

$$\frac{R_n}{s_2} \cdot (c_0 \cdot s_2 + c_0 \cdot k) + \frac{R_n}{s_1} \cdot (c_0 \cdot s_1 + 2c_0 \cdot s_2 + c_0 \cdot k) = (d + 2)R_n c_0$$

$$\frac{k}{s_1} + \frac{k}{s_2} + \frac{2s_2}{s_1} = d$$

$$k \cdot s_1 + k \cdot s_2 + 2s_2^2 = ds_1 s_2$$

$$s_1 = \frac{2s_2^2 + k \cdot s_2}{ds_2 - k}$$

- 2) The total area is  $A = s_1 + s_2$ . Substitute  $s_1$  into  $A$  so that  $A$  is expressed as a single-variable function. Differentiate  $A$  w.r.t.  $s_2$  and set it to zero. It will give you two roots,  $s_2 = 0$  and  $s_2 = X$ . Find  $X$ . It will look like this:  $s_2 = \frac{\square \cdot k}{d}$ .

$$A = \frac{2s_2^2 + k \cdot s_2}{ds_2 - k} + s_2$$

$$\frac{dA}{ds_2} = 1 + \frac{(4s_2 + k)(ds_2 - k) - (2s_2^2 + k \cdot s_2)d}{(ds_2 - k)^2} = 0$$

$$s_2 = 0, \frac{2k}{d}$$

$$\therefore s_2 = \frac{2k}{d}$$

- 3) Find  $s_1$ . It will look like  $s_1 = \frac{\square \cdot k \cdot (d + \square)}{d^2}$ .

$$s_1 = \frac{2k(d+4)}{d^2}$$