
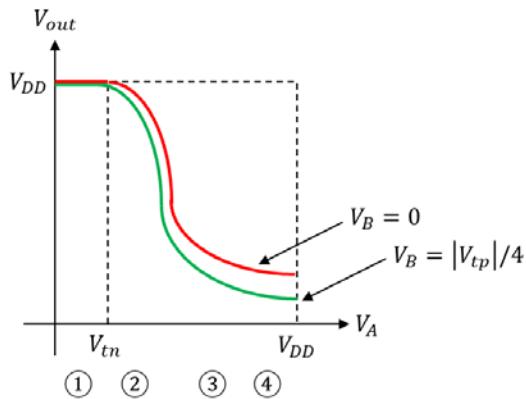


Homework Assignment 6

(Due 4:10pm, Mar. 8)

- (1) [DC Analysis, 40 points]** Draw two DC curves (V_A vs. V_L) for the following circuit for $V_B = 0$ (V) and $V_B = \frac{|V_{tp}|}{4}$ (V).

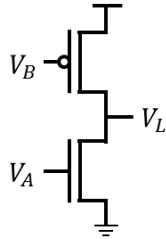

- | | |
|--|---|
| <p>① NFET: $V_{GS,n} = V_A < V_{tn}$: OFF
 PFET: $V_{SG,p} = V_{DD} - V_B > V_{tp}$: ON
 $V_L = V_{DD}$
 $V_{SD,p} = V_{DD} - V_{DD} \approx 0 < V_{SG,p} - V_{tp}$: Linear</p> | <p>③ NFET: $V_{GS,n} = V_A > V_{tn}$: ON, Saturation
 PFET: $V_{SG,p} = V_{DD} - V_B > V_{tp}$: ON
 $V_L \approx V_{DD}/2$
 $V_{SD,p} = V_{DD} - \frac{V_{DD}}{2} > V_{SG,p} - V_{tp}$: Saturation</p> |
| <p>② NFET: $V_{GS,n} = V_A > V_{tn}$: ON
 $V_{DS,n} \approx V_{DD} - 0 > V_{GS,n} - V_{tn}$: Saturation
 PFET: $V_{SG,p} = V_{DD} - V_B > V_{tp}$: ON
 $V_L \approx V_{DD}$
 $V_{SD,p} = V_{DD} - V_{DD} \approx 0 < V_{SG,p} - V_{tp}$: Linear</p> | <p>④ NFET: $V_{GS,n} = V_A > V_{tn}$: ON, Linear
 PFET: $V_{SG,p} = V_{DD} - V_B > V_{tp}$: ON
 $V_L \approx 0$
 $V_{SD,p} = V_{DD} - \frac{V_{DD}}{2} > V_{SG,p} - V_{tp}$: Saturation</p> |