

Homework Assignment 6
(Due 4:10pm, Mar. 8)

(1) [DC Analysis, 40 points] Draw two DC curves (V_A vs. V_L) for the following circuit for $V_B = 0$ (V) and $V_B = \frac{|V_{tp}|}{4}$ (V).

