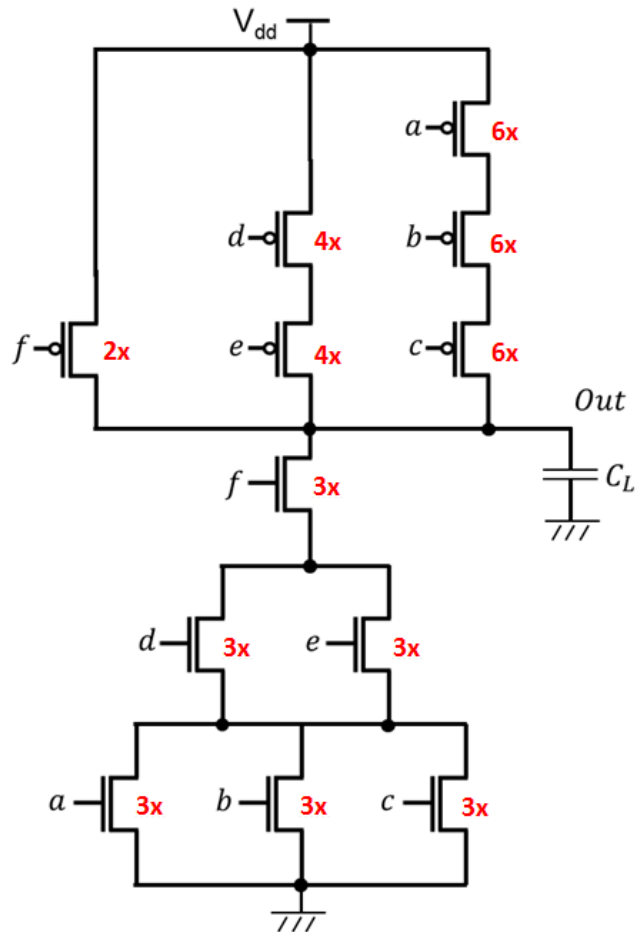


Homework Assignment 8
(Due 4:10pm, Feb. 12, email to daehyun@eecs.wsu.edu)


(1) [Design, 10 points] Solve Problem #4 of the EE434 2015 Spring Midterm Exam

1.



(2) [Design, 10 points] Solve Problem #4 of the EE434 2016 Spring Midterm Exam

1.

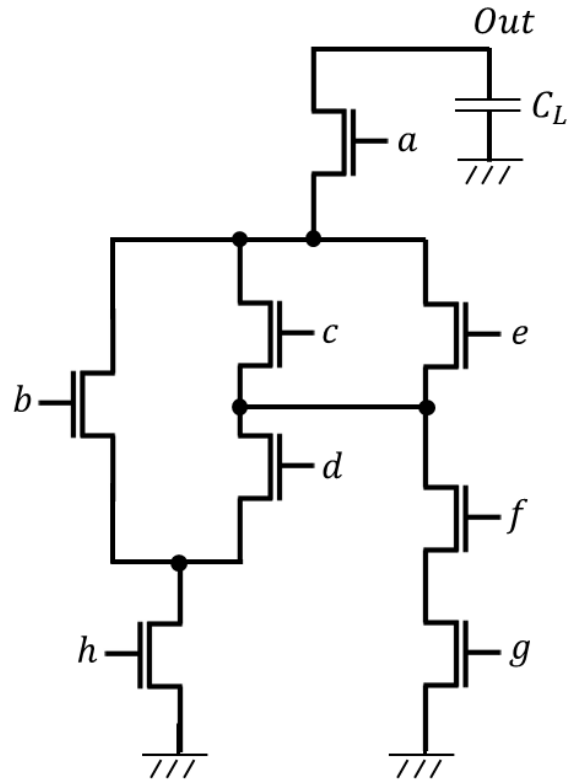


The worst-case path: (a-e-f-g) or (a-e-d-h) or (a-c-f-g) or (a-c-d-h), so we upsize all these transistors by 4X. Path (a-b-h) needs to be R_n , so b can be 2X.

a, c, d, e, f, g, h: 4X
b: 2X

(3) [Design, 10 points] Solve Problem #3 of the EE434 2017 Spring Midterm Exam

1.

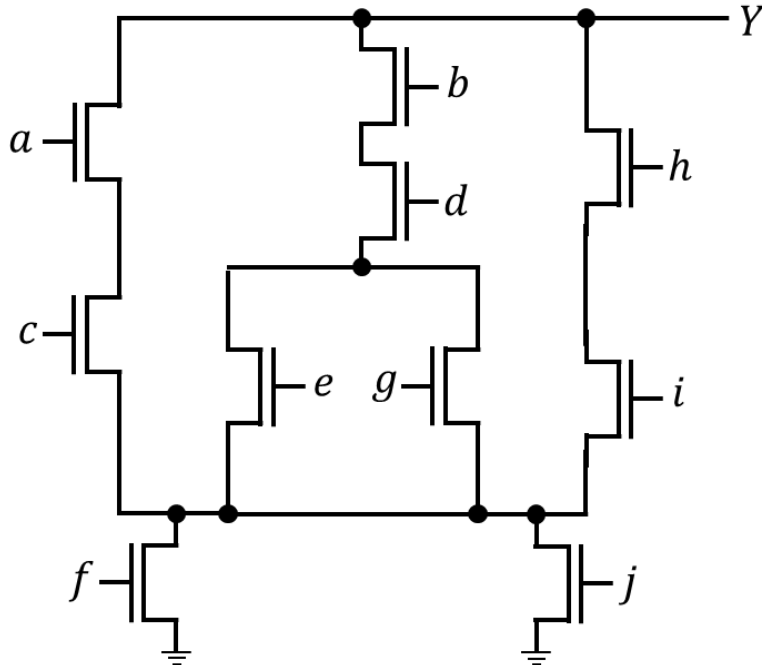

The longest path is b-d-e-f. Each of them is upsized to $4X$. Then, we get $a=c=h=i=8/3$.

- a: $8/3X$
- b: $4X$
- c: $8/3X$
- d: $4X$
- e: $4X$
- f: $4X$
- g: $4X$
- h: $8/3X$
- i: $8/3X$
- j: $4X$

Total width: $(34+2/3)X$

(If we upsize a-c-f first, $a=c=h=i=f=j=3X$. Then, $b=d=e=g=4.5X$. Total width = $36X$, which is worse than the above one.)

(4) [Design, 20 points] Solve Problem #5 of the EE434 2015 Spring Midterm Exam

1.

$$\text{Constraint: } \left(\frac{R_n}{a} + \frac{R_n}{b}\right) C_L = R_n C_L \Rightarrow \frac{1}{a} + \frac{1}{b} = 1$$

$$W = ak + b = ak + \frac{a}{a-1}$$

$$1) W' = k + \frac{(a-1)-a}{(a-1)^2} = k - \frac{1}{(a-1)^2} = 0 \Rightarrow \boxed{a = 1 + \frac{1}{\sqrt{k}} \Rightarrow b = 1 + \sqrt{k}}$$

2) $ak + b = c \Rightarrow$ Two functions, $b = -ak + c$ and $b = \frac{a}{a-1}$, should meet at a single point (confirm this by drawing their graphs).

$$\begin{aligned} &\Rightarrow -ak + c = \frac{a}{a-1} \text{ should have a single root. } \Rightarrow ka^2 - (k+c-1)a + \\ &c = 0 \text{ has a single root. } \Rightarrow (k+c-1)^2 - 4kc = 0 \Rightarrow (k-c-1)^2 = 0 \\ &\Rightarrow c = k+1 \pm 2\sqrt{k} \Rightarrow \\ &a = 1 \pm \frac{1}{\sqrt{k}} \Rightarrow a > 1, \text{ so } \boxed{a = 1 + \frac{1}{\sqrt{k}} \Rightarrow b = 1 + \sqrt{k}} \end{aligned}$$