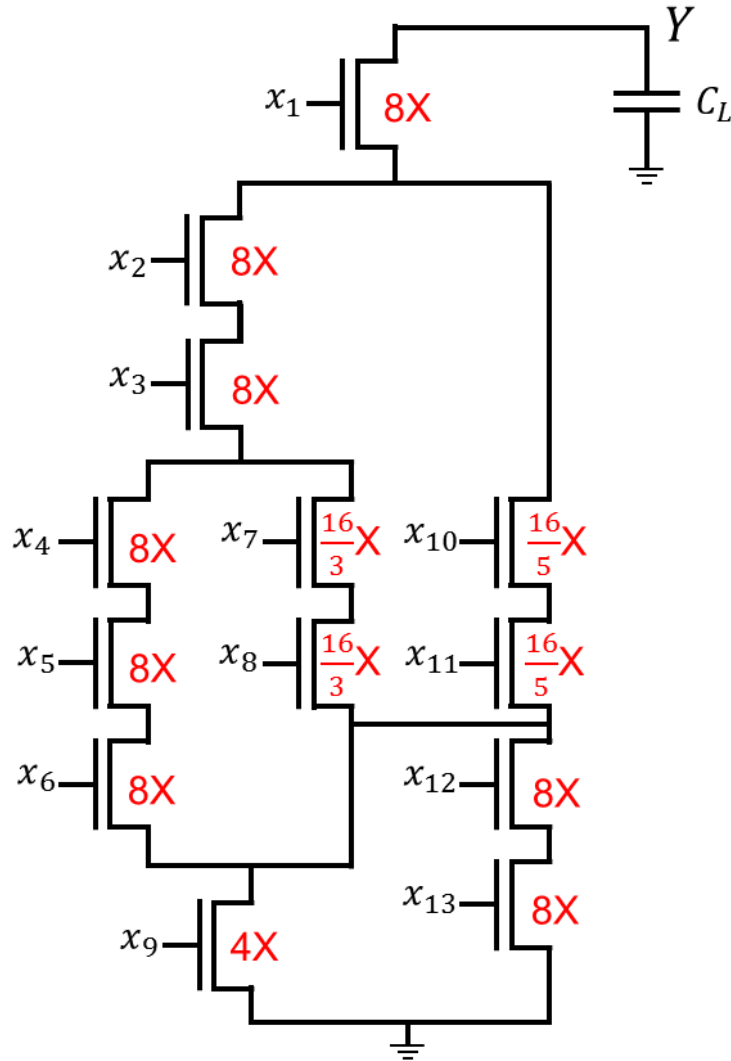


**Homework Assignment 9**  
**(Due 4:10pm, Feb. 14, email to [daehyun@eecs.wsu.edu](mailto:daehyun@eecs.wsu.edu))**

- (1) [TR Sizing, 20 points] The following shows a schematic of the NFET network of a static CMOS gate. Size the transistors so that the fall delay is less than or equal to  $R_n C_L$  where  $R_n$  is the resistance of a 1X NFET. Try to minimize the total width. Find the total width.



$W=85.07X$

- (2) [PDE, 10 points]  $x, y, z$  are variables and  $a, b, c$  are constants. Find the partial derivatives of  $F(x, y, z) = ax^4 + bx^2y^3z + cx^3y^2z^2 + x^2y^4$  with respect to  $x, y$ , and  $z$ .

$$\frac{\partial F}{\partial x} = 4ax^3 + 2bxy^3z + 3cx^2y^2z^2 + 2xy^4$$

$$\frac{\partial F}{\partial y} = 3bx^2y^2z + 2cx^3yz^2 + 4x^2y^3$$

$$\frac{\partial F}{\partial z} = bx^2y^3 + 2cx^3y^2z$$


- (3) [PDE, 10 points]  $x, y, z$  are variables. Find the partial derivatives of  $G(x, y, z) = \sin(y^2 + z^2) \cdot \cos(xyz)$  with respect to  $x, y$ , and  $z$ .

$$\frac{\partial G}{\partial x} = -\sin(y^2 + z^2) \sin(xyz) yz$$

$$\frac{\partial G}{\partial y} = 2ycos(y^2 + z^2) \cos(xyz) - \sin(y^2 + z^2) \sin(xyz) xz$$

$$\frac{\partial G}{\partial z} = 2zcos(y^2 + z^2) \cos(xyz) - \sin(y^2 + z^2) \sin(xyz) xy$$

 - (4) [Design, 20 points] The following (in the next page) shows an NFET network of
- $$Y = \overline{y \cdot (x_{1,1} \cdot x_{1,2} \cdot \dots \cdot x_{1,p_1} + x_{2,1} \cdot x_{2,2} \cdot \dots \cdot x_{2,p_2} + \dots + x_{k,1} \cdot x_{k,2} \cdot \dots \cdot x_{k,p_k})} = \overline{y \cdot \sum_{i=1}^k \prod_{j=1}^{p_k} x_{i,j}}$$
- (Notice that  $k, p_1, \dots, p_k$  are constants). Size the transistors so that the fall delay is less than or equal to  $R_n C_L$  where  $R_n$  is the resistance of a 1X NFET. Minimize the total width. Find the total width.



The width of  $x_{i,j}$ :  $w_i$

The width of  $y$ :  $Y$

Timing constraint for each path:  $\frac{1}{Y} + \sum_{j=1}^{p_i} \frac{1}{w_{i,j}} = \frac{1}{Y} + \frac{p_i}{w_i} = 1$  (for  $i = 1, \dots, k$ )


From the constraint:  $w_i = \frac{p_i \cdot Y}{Y-1}$

Total width  $W = Y + \sum p_i w_i = Y + \frac{Y}{Y-1} \cdot \sum p_i^2 = Y + \frac{sY}{Y-1}$  where  $s = \sum p_i^2$

$\frac{dW}{dY} = 1 + s \frac{(Y-1)-Y}{(Y-1)^2} = 1 - \frac{s}{(Y-1)^2} = 0$ , so  $Y = 1 + \sqrt{s}$

$$\begin{aligned} \therefore Y &= 1 + \sqrt{p_1^2 + p_2^2 + \dots + p_k^2} \\ w_i &= p_i \cdot \left( 1 + \frac{1}{\sqrt{p_1^2 + p_2^2 + \dots + p_k^2}} \right) \\ W &= \left( 1 + \sqrt{p_1^2 + p_2^2 + \dots + p_k^2} \right)^2 \end{aligned}$$

 - (5) [Design, 20 points] The following (in the next page) shows an NFET network of  $Y$  in Problem 4. Size the transistors so that the fall delay is less than or equal to  $R_n C_L$  where  $R_n$  is the resistance of a 1X NFET. Minimize the total width. Find the total width.



The width of the transistors in the  $i$ -th column:  $w_i$

Timing constraint for the  $i$ -th column:  $\frac{p_i+1}{w_i} = 1$

Thus,  $w_i = p_i + 1$

Total width:  $\sum (p_i + 1) \cdot w_i = \sum (p_i + 1)^2$

- (6) [Math, 10 points] Compare the total widths you found in Problem 4 and Problem 5. Which implementation is better (occupy smaller area)?

The design in Problem 4 is better.

$$\begin{aligned}
 W_{\text{problem5}} - W_{\text{problem4}} &= \sum (p_i + 1)^2 - \left(1 + \sqrt{p_1^2 + p_2^2 + \dots + p_k^2}\right)^2 \\
 &= \left\{ \sum p_i^2 + 2 \sum p_i + k \right\} - \left\{ \sum p_i^2 + 2\sqrt{p_1^2 + p_2^2 + \dots + p_k^2} + 1 \right\} \\
 &= 2 \left( \sum p_i - \sqrt{p_1^2 + p_2^2 + \dots + p_k^2} \right) + (k - 1)
 \end{aligned}$$

The first term is positive because  $(\sum p_i)^2 - (\sqrt{p_1^2 + p_2^2 + \dots + p_k^2})^2 = 2 \sum_{i,j,i \neq j} p_i p_j > 0$ . The second term is also positive or zero because  $k \geq 1$ .

Thus,  $W_{\text{problem5}} - W_{\text{problem4}} > 0$ .