
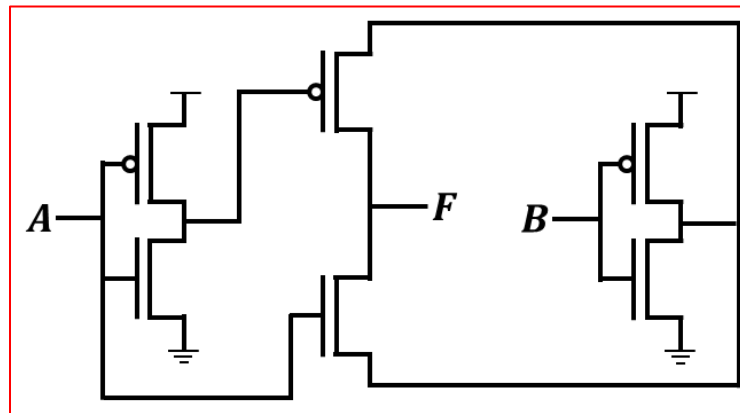


## Homework Assignment 10

(Due 4:10pm, Mar. 5, email to [daehyun@eecs.wsu.edu](mailto:daehyun@eecs.wsu.edu))

 - (1) [Layout, 20 points] Convert the following layout into a transistor-level schematic. Input: A, B. Output: F.



(2) [Layout, 20 points] Convert the following layout into a transistor-level schematic. Input: A, B, C. Output: F.

