 


Lab 2 (Due 23:59, Mar. 29th)

Size the NFETs in the following dynamic-CMOS circuit.



- Download <http://eecs.wsu.edu/~ee434/Labs/lab2.zip> and unzip it. There is lab2.sp. Use the netlist. You can change the widths of the NFETs in the netlist.
- Do not touch anything else except the widths of the NFETs.
- The width of a 1X transistor is 50nm.
- The width of each NFET should be an integer multiple of 50nm. For example, you can use 100nm (2X), 250nm (5X), etc., but you cannot use 67nm, 271nm, etc.
- Objective: Minimize the total width of the NFETs.
- Constraint: For each path, the fall delay should be less than or equal to 60ps.
- Use HSpice to simulate it.
- What to submit
 - Final netlist.

Grading criteria

- If all the paths satisfy the timing constraint:
 - Total area (A) $\leq 10,500\text{nm}$: 100 points
 - $10,500\text{nm} < A \leq 10,550\text{nm}$: 95 points

- $10,550\text{nm} < A \leq 10,600\text{nm}$: 90 points
- etc.
- If some of the paths do not satisfy the timing constraint:
 - $A \leq 10,500\text{nm}$: 100 points $- 2 * \sum(\text{Delay} - 60\text{ps})$ (Sum is for all the violating paths)
 - $10,500\text{nm} < A \leq 10,550\text{nm}$: 95 points $- 2 * \sum(\text{Delay} - 60\text{ps})$
 - etc.