


Homework Assignment 1 (Due Feb. 4th at the beginning of the class)

- (1) [Static CMOS Circuit, **5 points**] Draw a transistor-level schematic for the following function. Use six NMOS and six PMOS transistors.

$$F = \overline{A \cdot B + A \cdot C + B \cdot D}$$

- (2) [Static CMOS Circuit, **5 points**] Draw a transistor-level schematic for the above function. Use the smallest number of transistors.

 
- (3) [Static CMOS Circuit, **5 points**] An NMOS logic array for a function is shown below. Construct the PMOS circuit to complete the function.



- (4) [Static CMOS Circuit, **5 points**] Draw a transistor-level schematic for the following function.

$$F = A$$

 
- (5) [Logic Conversion, **5 points**] The two-input AND and OR gates use six transistors, but the two-input NAND and NOR gates use four transistors, so NAND and NOR gates are preferred to AND and OR gates in the design of CMOS circuits. Convert the following logic ($F = A + B + C$) into a new logic using only INV, two-input NAND, and two-input NOR gates. Use the smallest number of transistors.



- (6) [Static CMOS Circuit, **5 points**] Draw a transistor-level schematic for a two-input MUX ($F = \bar{S} \cdot A + S \cdot B$).

	S	
	0	1
F	A	B

 - (7) [CMOS gates, **5 points**] What is the intended function of the circuit shown in the figure below? What is the output swing?



- (8) [HSPICE simulation, **10 points**]

1. Create a work directory.

```
> mkdir ee434_hw01
```

```
> cd ee434_hw01
```

2. Download the following file into your directory.

```
> wget http://www.eecs.wsu.edu/~ee434/Homework/hw01.tar.gz
```

3. Unzip it.

```
> tar xvfz hw01.tar.gz
```


4. There are four files.

- 45nm_PTM_HP_v2.1.pm: 45nm transistor models for SPICE simulation.
- clr: run this to clear the files HSpice generates. (> ./clr)
- inv.sp: HSpice netlist for an inverter.
- synopsis.sh: a shell script to run HSpice.


5. Source the .sh file to enable running HSpice. (You have to run this whenever you connect to an EECS server).

```
> source synopsys.sh
```

 6. Open inv.sp and read the comments. You will be able to figure out the file format. The following visualizes the netlist.



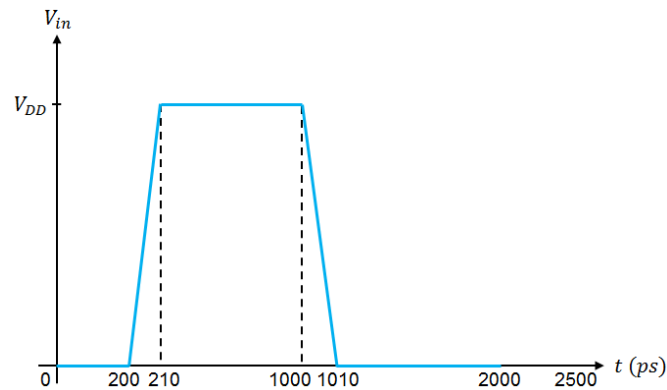7. The following visualizes the input signal ($V_{DD}=1$).



8. Run HSpice to simulate the given netlist.

```
> hspice inv.sp
```

9. You will see the following message.

```
>info:          ***** hspice job concluded
lic: Release hspice token(s)
real 0.36
user 0.06
sys 0.02
```

10. Scroll up and see the outputs. If you cannot see the whole output messages, you can re-direct the output to a file and open it.

```
> hspice inv.sp > output.txt
```

```
> vi output.txt
```

11. The leftmost column is the simulation time, the middle one is V_{in} , and the rightmost one is V_{out} .
12. See the two “measure” statements in inv.sp. The first and the second statements measure the 80%-20% fall time and 20%-80% rise time, respectively.
13. See the output and find “tfall” and “trise”. “tfall” is the fall time and “trise” is the rise time.

```

2.4990e-09      0.000e+00      1.000e-00
2.5000e-09      0.000e+00      1.000e-00
y
  tfall=  1.4672E-10  targ=  3.9465E-10  trig=  2.4793E-10
  trise=  1.4401E-10  targ=  1.1866E-09  trig=  1.0426E-09
          ***** job concluded
1***** HSPICE -- E-2010.12 32-BIT (Nov 20 2010) linux *****

```

14. In the above figure, the fall time is 146.7ps and the rise time is 144.0ps. They are balanced pretty well. See the width of the NMOS and PMOS transistors.
15. Change W_n (the width of the NMOS transistor) from 45nm to 90nm. Change W_p (the width of the PMOS transistor) from 70nm to 140nm. (so the inverter is 2x larger than the minimum-size inverter.) Re-run HSpice with these new widths and obtain rise and fall times.
16. **[Submit]** The rise time and the fall time.
17. Set W_n to 180nm and W_p to 280nm (INV_X4). Run HSpice and obtain new rise and fall times.
18. **[Submit]** The rise time and the fall time.
19. Set W_n to 90nm and W_p to 140nm. Set C_{out} to 20fF. Run HSpice and obtain new rise and fall times.
20. **[Submit]** The rise time and the fall time.
21. $W_n=90nm$. $W_p=140nm$. $C_{out}=20fF$. Change the rising and the falling transition times of the input signal from 10ps to 50ps, run HSpice, and obtain new rise and fall times.
22. **[Submit]** The rise time and the fall time.