 



EE 434
Homework Assignment 1
(Due Friday, 6th September 2013 at the beginning of the class)

- (1) Given the choice between NOR and NAND logic, which one would you prefer for implementation in static CMOS? Which one would you prefer in pseudo-NMOS? Explain. **(5 points)**
- (2) Implement a two-input MUX using static CMOS and Transmission gate logic. Which one needs more transistors? **(5 points)**
- (3) What is the intended function of the circuit shown in the figure below? What is the output swing? **(5 points)**



- (4) Design a pseudo-NMOS gate that implements the following function **(5 points)**
- $$F = \overline{A(B + C + D) + E \cdot F \cdot G}$$
- (5) A static CMOS NOR gate uses 4 transistors, while a pseudo-NMOS gate uses only 3. But as discussed in class, pseudo-NMOS has its own problems. Design a NOR gate using 3 transistors that does not have the problems of the pseudo-NMOS. You can assume that both the inputs and their complements are available. **(5 points)**

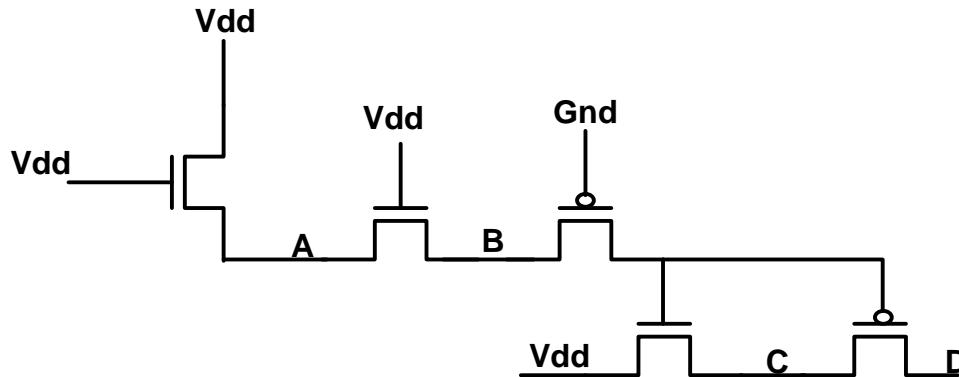- (6) Determine the voltage levels at the nodes A, B, C and D in the following circuit. **(4 points)**



- (7) Multiple-output Domino Logic: Implement the following three functions
 $(C + D)$
 $B(C + D)$
 $AB(C + D)$
 using a single domino logic. **(6 points)**

- (8) Size the transistors (in terms of W) in a three-input static CMOS NOR gate such that the circuit's rise and fall times are approximately equal. **(5 points)**