

Solution of HW 4

(1) Faulty functions for the circuit corresponding to the two faults are:

$$I(c \rightarrow s-a-0) = b(\overline{ab}) = b\overline{a}$$

$$I(f \rightarrow s-a-1) = (a+b)\overline{a} = b\overline{a}$$

(2) Faulty functions corresponding to the two faults are:


$$Z(c \rightarrow s-a-1) = \overline{ab}$$

$$Z(f \rightarrow s-a-1) = \overline{ab}$$

The two faulty functions are indistinguishable and hence the faults are equivalent.


(3) Fault Sites = #PIs + #Gates + #Fanout branches = 4 + 5 + 4 = 13

Equivalence collapsed set:

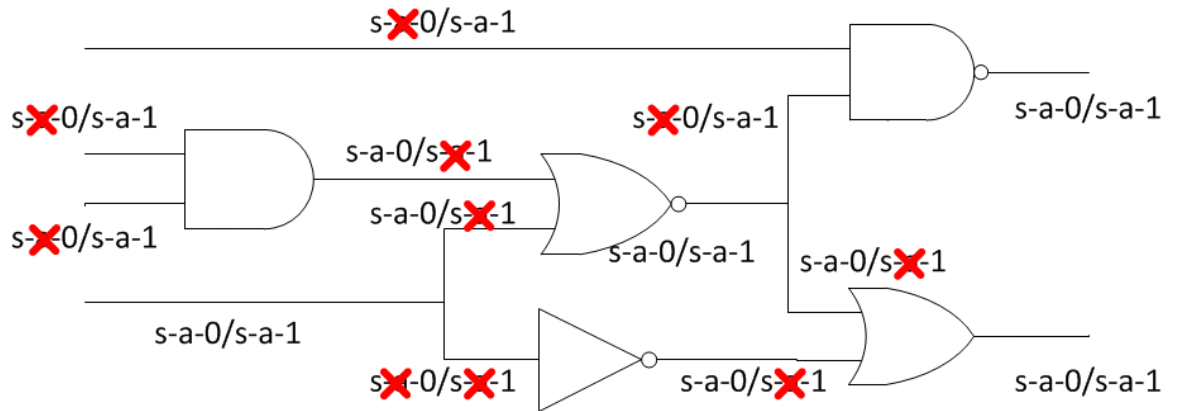

Collapse Ratio = 16/26 = 0.615

Dominance (& Equivalence) collapsed set:

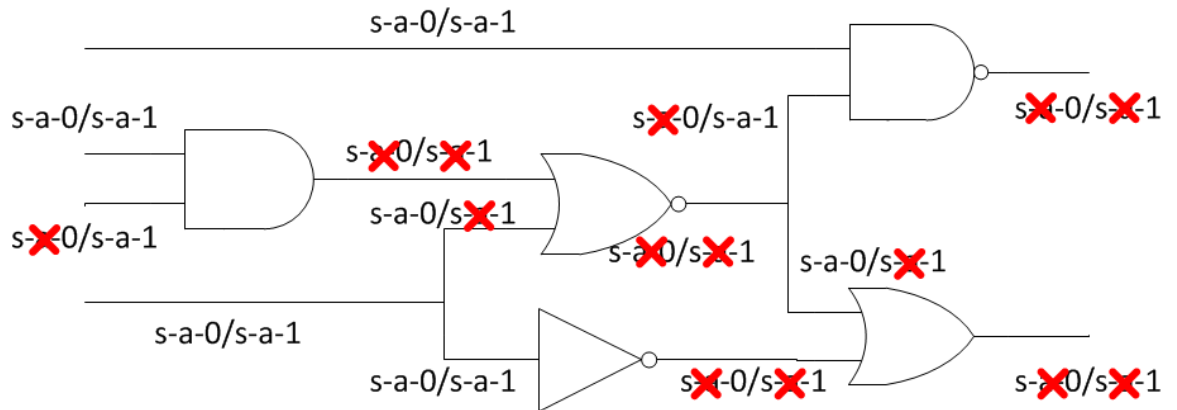

Collapse Ratio = 12/26 = 0.462