

**EE434**

**ASIC and Digital Systems**

**Midterm Exam 1**

**Feb. 27, 2019. (4:10pm – 5pm)**

**Instructor: Dae Hyun Kim ([daehyun@eecs.wsu.edu](mailto:daehyun@eecs.wsu.edu))**


**Name:**

**WSU ID:**

Problem	Points	
1	10	
2	10	
3	10	
4	20	
5	20	
6	10	
Total	80	
 
### Problem #1 (Static CMOS gates, 10 points)

The following shows the NFET network of a static CMOS gate. Express the output  $Y$  as a Boolean function of the inputs ( $A\sim J$ ). (You don't need to simplify the expression.)




## Problem #2 (Transmission Gates, 10 points)

Design (draw a schematic) the following Boolean function using transmission gates only.

$$Y = (A \oplus B) + \overline{(A \cdot B) \oplus C}$$

 
Available inputs:  $A, B, C, \bar{A}, \bar{B}, \bar{C}$ . You cannot use Power ( $V_{DD}$ ) and Ground ( $V_{SS}$ ). Use the following symbols for the transmission gates.



(# TGs  $\leq 6$ : 10 points.  $7 \leq$  # TGs  $\leq 8$ : 7 points.  $9 \leq$  # TGs  $\leq 10$ : 5 points. # TGs  $> 10$ : 0 points)
 
### Problem #3 (Transistor Sizing, 10 points)

Size the transistors in the following pull-down network.  $R_n$  is the resistance of a 1X NMOS transistor.  $C_L$  is the load capacitance. Ignore parasitic capacitances. Target delay:  $\tau_T \leq R_n \cdot C_L$ . Try to minimize the total area.



(Total width  $W \leq 31X$ : 10 points.  $31X < W \leq 32X$ : 8 points.  $32X < W \leq 34X$ : 5 points.  $34X < W$ : 3 points)

A:

B:

C:

D:

E:

F:

G:

H:


I:

Total:

### Problem #4 (Transistor Sizing, 20 points)

Solve either 4-(1) or 4-(2). You don't need to solve both.

 
(1) (20 points) Size the transistors in the following pull-down network.  $R_n$  is the resistance of a 1X NMOS transistor.  $C_L$  is the load capacitance. Ignore parasitic capacitances. Target delay:  $\tau_T \leq R_n \cdot C_L$ . Minimize the total area (i.e., size the transistors optimally).



(2) (12 points) Answer the following questions.

- (a) The optimal size of transistor A is greater than 4X (True / False).
- (b) The optimal size of transistor B is greater than 4X (T / F).
- (c) The optimal size of transistor B is equal to the optimal size of transistor D (T / F).
- (d) The optimal size of transistor E is greater than 2X (T / F).
- (e) The optimal size of transistor C is  $3 \times$  the optimal size of transistor E (T / F).
- (f) The sum of the optimal widths of all the transistors is greater than or equal to 18X (T / F).

**Problem #5 (Layout, 20 points)**

 


Signal input: A, D. Signal output: Y. Clock: CK

1) (10 points) Convert the layout into a transistor-level schematic.

2) (10 points) What is the function of the circuit?

**Problem #6 (Layout, 10 points)**

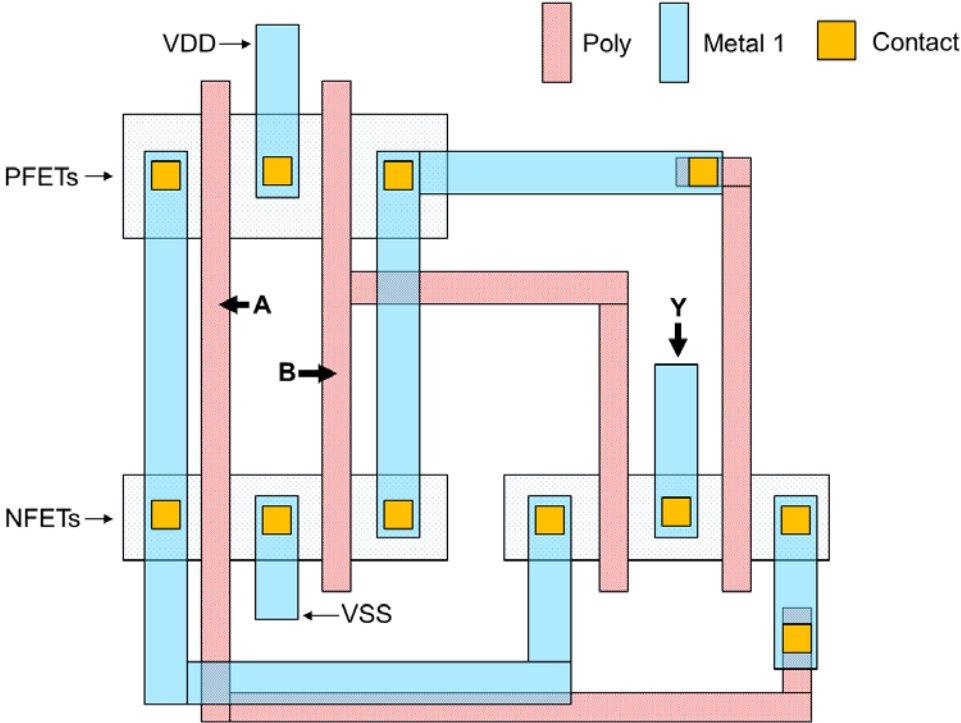

Input: A, B

Output: Y

What is the function of this circuit?