

# EE434

## ASIC and Digital Systems

### Midterm Exam 2

April 8, 2015. (5:10pm – 6pm)

Instructor: Dae Hyun Kim ([daehyun@eecs.wsu.edu](mailto:daehyun@eecs.wsu.edu))

**Name:**

**WSU ID:**



Problem	Points	
1	20	
2-1	13	
2-2	7	
3-1	10	
3-2	10	
4	20	
Total	80	

\* Allowed: Textbooks, cheat sheets, class notes, notebooks, calculators, watches

\* Not allowed: Electronic devices (smart phones, tablet PCs, laptops, etc.) except calculators and watches

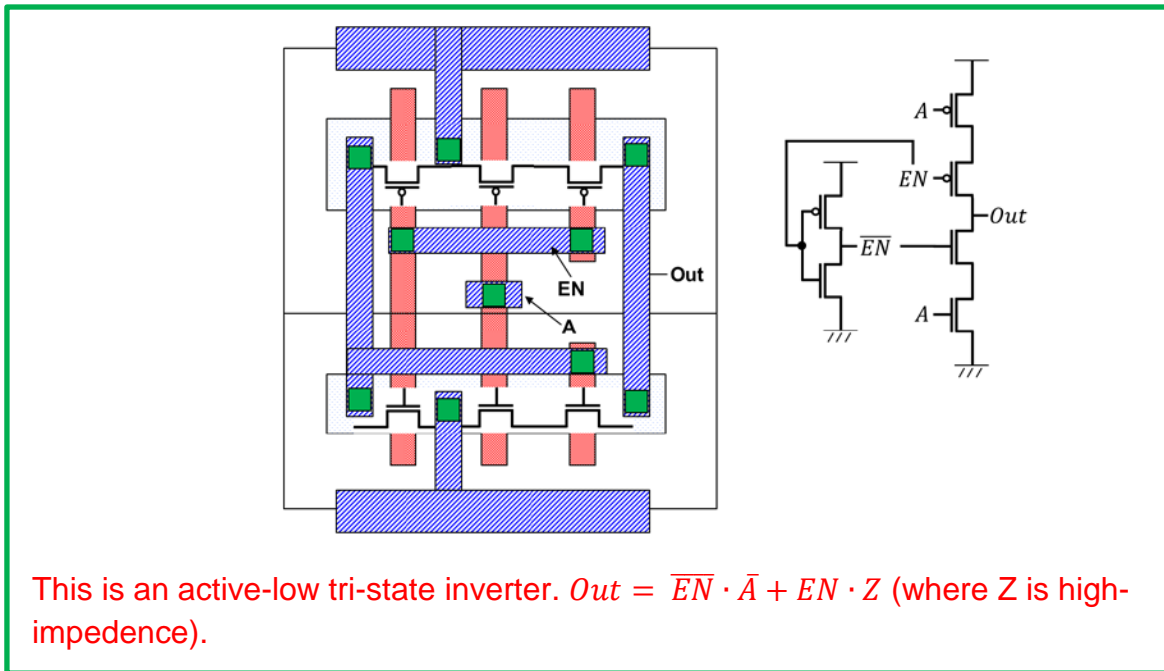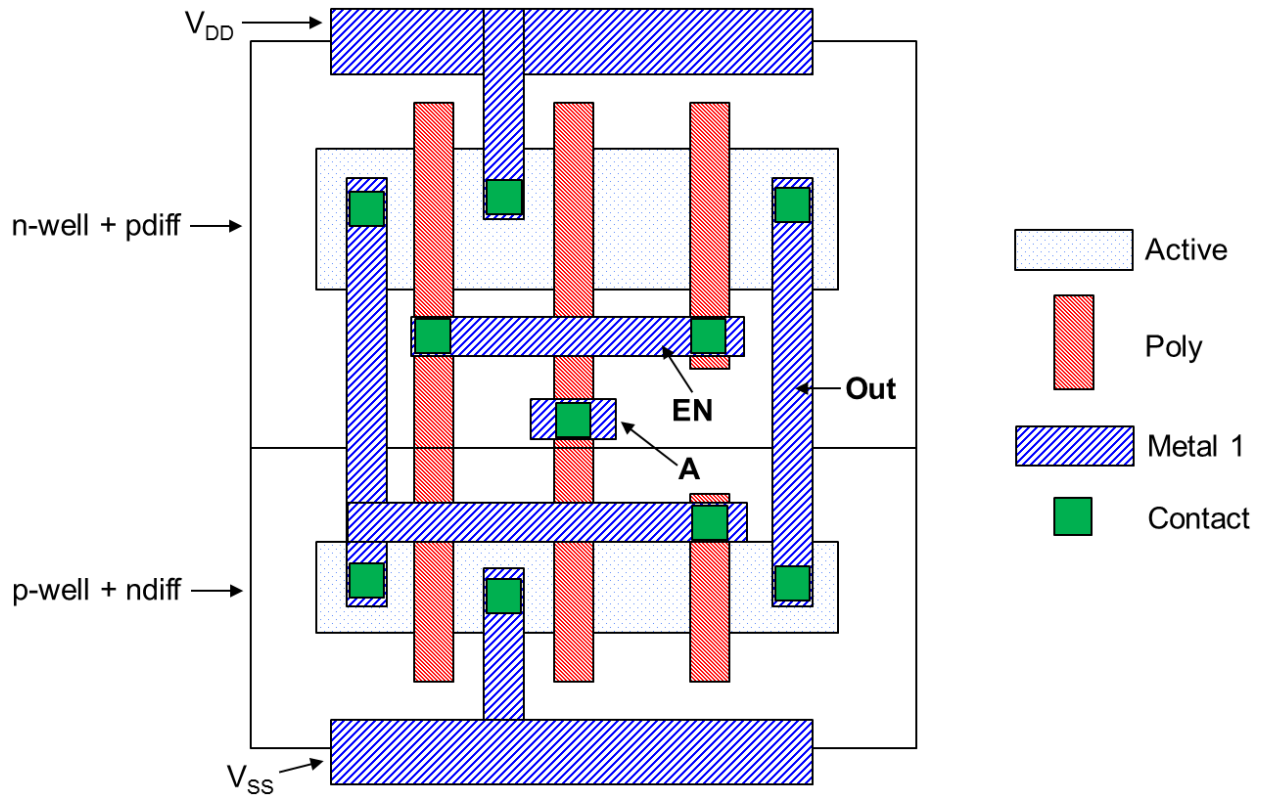
### Problem #1 (Layout, 20 points).

Represent *Out* as a Boolean function of *EN* and *A* or describe the function of the following layout in as much detail as possible (Primary inputs: *A*, *EN*. Primary output: *Out*).



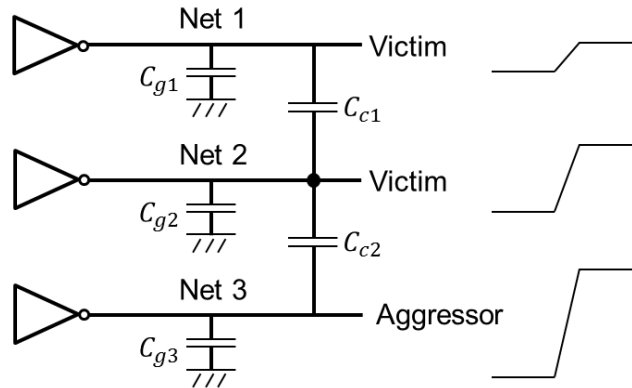
## Problem #2 (Coupling Analysis, 20 points).

Three nets are coupled through  $C_{c1}$  and  $C_{c2}$  as shown in the following figure:



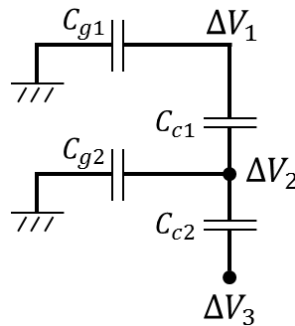Net 3 is the only aggressor and Net 2 and Net 1 are victims. Although Net 1 is not directly connected to Net 3, Net 1 is affected by the potential change of Net 2 when Net 3 switches. The above figure can be simplified as follows:



1 – 12 points) Derive  $\Delta V_2$  and  $\Delta V_1$  as a function of  $\Delta V_3$ ,  $C_{g1}$ ,  $C_{g2}$ ,  $C_{c1}$ , and  $C_{c2}$ .

$$i_{32} = C_{c2} \frac{d(V_3 - V_2)}{dt} = C_{g2} \frac{dV_2}{dt} + C_{c1} \frac{d(V_2 - V_1)}{dt}$$

$$i_{21} = C_{c1} \frac{d(V_2 - V_1)}{dt} = C_{g1} \frac{dV_1}{dt}$$

$$\text{From } i_{21}: C_{c1}(\Delta V_2 - \Delta V_1) = C_{g1}\Delta V_1 \rightarrow \Delta V_1 = \frac{C_{c1}}{C_{g1} + C_{c1}} \Delta V_2$$

$$\text{From } i_{32}: C_{c2}(\Delta V_3 - \Delta V_2) = C_{g2}\Delta V_2 + C_{c1}(\Delta V_2 - \Delta V_1)$$

$$\rightarrow C_{c2}\Delta V_3 = (C_{g2} + C_{c1} + C_{c2})\Delta V_2 - C_{c1}\Delta V_1 = \left( C_{g2} + C_{c1} + C_{c2} - \frac{C_{c1}^2}{C_{g1} + C_{c1}} \right) \Delta V_2$$

$$\rightarrow C_{c2}\Delta V_3 = \left( \frac{C_{g1}C_{g2} + C_{g2}C_{c1} + C_{g1}C_{c1} + C_{g1}C_{c2} + C_{c1}C_{c2}}{C_{g1} + C_{c1}} \right) \Delta V_2$$

$$\therefore \Delta V_2 = C_{c2} \left( \frac{C_{g1} + C_{c1}}{C_{g1}C_{g2} + C_{g2}C_{c1} + C_{g1}C_{c1} + C_{g1}C_{c2} + C_{c1}C_{c2}} \right) \Delta V_3$$

$$\Delta V_1 = \left( \frac{C_{c1}C_{c2}}{C_{g1}C_{g2} + C_{g2}C_{c1} + C_{g1}C_{c1} + C_{g1}C_{c2} + C_{c1}C_{c2}} \right) \Delta V_3$$

2 – 8 points) True/False questions (Hint: Use your intuition or the formulas you derived in the above problem).

a) If  $C_{g1}$  increases,  $\Delta V_1$  increases (true/false).

$$\Delta V_1 = \left( \frac{C_{c1}C_{c2}}{(C_{g2} + C_{c1} + C_{c2})C_{g1} + C_{g2}C_{c1} + C_{c1}C_{c2}} \right) \Delta V_3 \rightarrow \Delta V_1 \text{ decreases.}$$

b) If  $C_{g1}$  increases,  $\Delta V_2$  increases (true/false).

$$\Delta V_2 = \frac{C_{c2}}{\left( C_{g2} + C_{c1} + C_{c2} - \frac{C_{c1}^2}{C_{g1} + C_{c1}} \right)} \Delta V_3 \rightarrow \Delta V_2 \text{ decreases.}$$

c) If  $C_{g2}$  increases,  $\Delta V_1$  increases (true/false).

$$\Delta V_1 = \left( \frac{C_{c1}C_{c2}}{(C_{g1} + C_{c1})C_{g2} + C_{g1}C_{c1} + C_{g1}C_{c2} + C_{c1}C_{c2}} \right) \Delta V_3 \rightarrow \Delta V_1 \text{ decreases.}$$

d) If  $C_{g2}$  increases,  $\Delta V_2$  increases (true/false).

$$\Delta V_2 = C_{c2} \left( \frac{C_{g1} + C_{c1}}{(C_{g1} + C_{c1})C_{g2} + C_{g1}C_{c1} + C_{g1}C_{c2} + C_{c1}C_{c2}} \right) \Delta V_3 \rightarrow \Delta V_2 \text{ decreases.}$$

e) If  $C_{c1}$  increases,  $\Delta V_1$  increases (true/false).

$$\Delta V_1 = \left( \frac{C_{c2}}{K_1 + \frac{K_2}{C_{c1}}} \right) \Delta V_3 \rightarrow \Delta V_1 \text{ increases.}$$


f) If  $C_{c2}$  increases,  $\Delta V_1$  increases (true/false).

$$\Delta V_1 = \left( \frac{C_{c1}}{K_1 + \frac{K_2}{C_{c2}}} \right) \Delta V_3 \rightarrow \Delta V_1 \text{ increases.}$$

g) If  $C_{c2}$  increases,  $\Delta V_2$  increases (true/false).

$$\Delta V_2 = \frac{1}{\left( 1 + \frac{K}{C_{c2}} \right)} \Delta V_3 \rightarrow \Delta V_2 \text{ increases.}$$

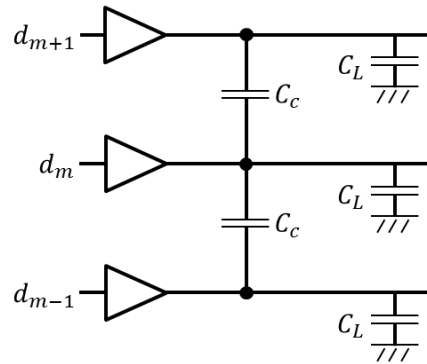
**Problem #3 (Coupling Minimization, 20 points).**



1 – 10 points) Compute effective capacitance for the net in the middle ( $d_m$ ) for the following transition patterns:

Transition patterns ( $d_{m+1} d_m d_{m-1}$ )	Effective cap of $d_m$
010 → 000	$C_L + 2C_c$
010 → 001	$C_L + 3C_c$
010 → 100	$C_L + 3C_c$
010 → 101	$C_L + 4C_c$

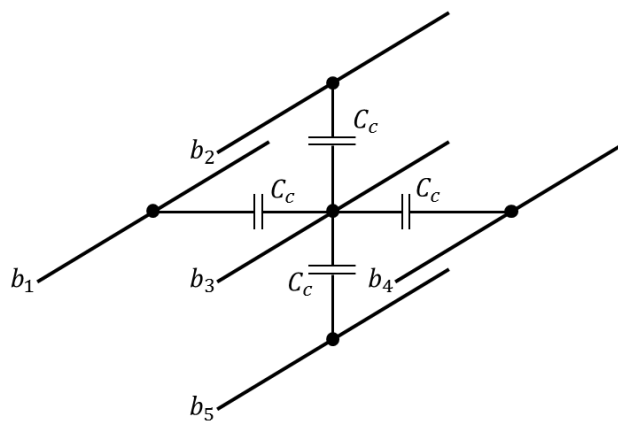2 – 10 points) A bus consisting of five bits ( $b_1 b_2 b_3 b_4 b_5$ ) is routed in three metal layers. Due to some unknown reasons, four of them ( $b_1 b_2 b_4 b_5$ ) are routed in parallel with  $b_3$ . The following shows the coupling capacitance among the five nets.




Due to the coupling between  $b_3$  and  $b_k$ , the worst-case effective coupling capacitance that  $b_3$  experiences will be  $8 \cdot C_c$ . List all transition patterns that make  $b_3$  experience  $8 \cdot C_c$  and  $7 \cdot C_c$ .

$8C_c$ : 00100 ↔ 11011

$7C_c$ : 00100 ↔ 11010 / 00100 ↔ 11001 / 00100 ↔ 10011 / 00100 ↔ 01011

11011 ↔ 00101 / 11011 ↔ 00110 / 11011 ↔ 01100 / 11011 ↔ 10100
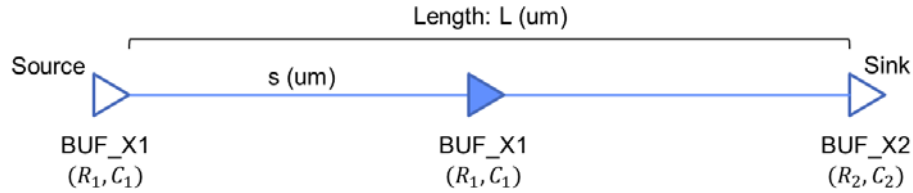
### Problem #4 (Buffer Insertion, 20 points).



A source (type: BUF\_X1) drives a sink (type: BUF\_X2) through a net and you are supposed to insert a buffer (type: BUF\_X1) between them as shown in the above figure. Find an optimal location of the buffer minimizing the total delay, i.e., represent “s” as a function of the following parameters.

- Output resistance of BUF\_X1:  $R_1$
- Input capacitance of BUF\_X1:  $C_1$
- Input capacitance of BUF\_X2:  $C_2$
- Total length of the net:  $L$  (um)
- Total wire resistance:  $R_w$
- Total wire capacitance:  $C_w$
- ( $C_w + C_2 > C_1$ )

$$\begin{aligned}
 \text{Delay} = \tau &= \left( R_1 \left( C_w \cdot \frac{s}{L} + C_1 \right) + R_w \cdot \frac{s}{L} \cdot C_1 + \frac{1}{2} \left( R_w \frac{s}{L} \right) \left( C_w \frac{s}{L} \right) \right) \\
 &+ \left( R_1 \left( C_w \cdot \frac{L-s}{L} + C_2 \right) + R_w \cdot \frac{L-s}{L} \cdot C_2 + \frac{1}{2} \left( R_w \frac{L-s}{L} \right) \left( C_w \frac{L-s}{L} \right) \right) \\
 &= R_1 C_w + R_1 C_1 + R_1 C_2 + R_w \left( \frac{s}{L} \cdot C_1 + \frac{L-s}{L} \cdot C_2 \right) + \frac{1}{2L^2} R_w C_w (s^2 + s^2 - 2Ls + L^2) \\
 \frac{d\tau}{ds} &= \frac{R_w C_1}{L} - \frac{R_w C_2}{L} + \frac{R_w C_w}{2L^2} (4s - 2L) = 0 \\
 s \left( \frac{2R_w C_w}{L^2} \right) &= \frac{R_w C_w}{L} + \frac{R_w (C_2 - C_1)}{L}
 \end{aligned}$$

$$\therefore s = \frac{L(C_w + C_2 - C_1)}{2C_w}$$