

# EE434

## ASIC and Digital Systems

### Midterm Exam 2

April 8, 2015. (5:10pm – 6pm)

Instructor: Dae Hyun Kim ([daehyun@eecs.wsu.edu](mailto:daehyun@eecs.wsu.edu))

**Name:**

**WSU ID:**


Problem	Points	
1	20	
2-1	13	
2-2	7	
3-1	10	
3-2	10	
4	20	
Total	80	

\* Allowed: Textbooks, cheat sheets, class notes, notebooks, calculators, watches

\* Not allowed: Electronic devices (smart phones, tablet PCs, laptops, etc.) except calculators and watches

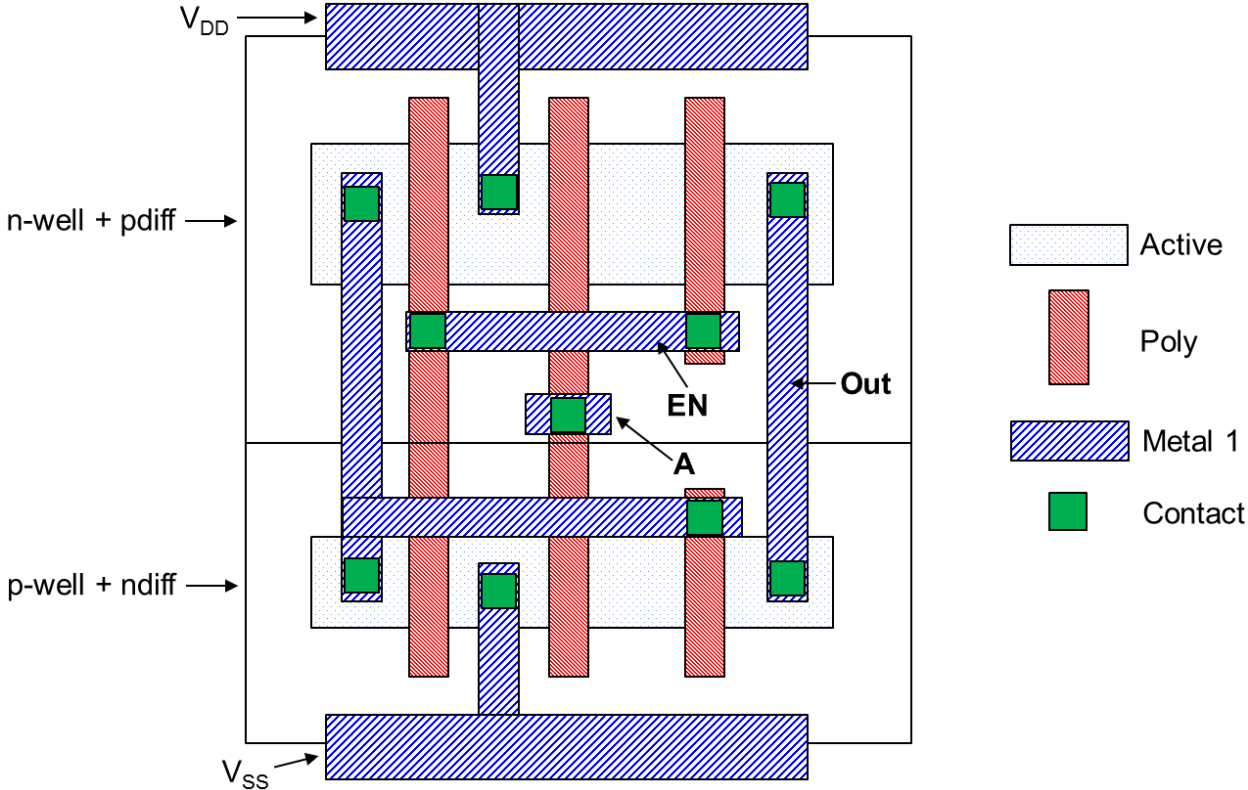
**Problem #1 (Layout, 20 points).**

Represent *Out* as a Boolean function of *EN* and *A* or describe the function of the following layout in as much detail as possible (Primary inputs: *A*, *EN*. Primary output: *Out*).



 
## Problem #2 (Coupling Analysis, 20 points).

Three nets are coupled through  $C_{c1}$  and  $C_{c2}$  as shown in the following figure:



 Net 3 is the only aggressor and Net 2 and Net 1 are victims. Although Net 1 is not directly connected to Net 3, Net 1 is affected by the potential change of Net 2 when Net 3 switches. The above figure can be simplified as follows:




1 – 13 points) Derive  $\Delta V_2$  and  $\Delta V_1$  as a function of  $\Delta V_3$ ,  $C_{g1}$ ,  $C_{g2}$ ,  $C_{c1}$ , and  $C_{c2}$ .

2 – 7 points) True/False questions (Hint: Use your intuition or the formulas you derived in the above problem).

- If  $C_{g1}$  increases,  $\Delta V_1$  increases (true/false).
- If  $C_{g1}$  increases,  $\Delta V_2$  increases (true/false).
- If  $C_{g2}$  increases,  $\Delta V_1$  increases (true/false).
- If  $C_{g2}$  increases,  $\Delta V_2$  increases (true/false).
- If  $C_{c1}$  increases,  $\Delta V_1$  increases (true/false).
- If  $C_{c2}$  increases,  $\Delta V_1$  increases (true/false).
- If  $C_{c2}$  increases,  $\Delta V_2$  increases (true/false).

 
**Problem #3 (Coupling Minimization, 20 points).**



1 – 10 points) Compute effective capacitance for the net in the middle ( $d_m$ ) for the following transition patterns:


Transition patterns ( $d_{m+1} d_m d_{m-1}$ )	Effective cap of $d_m$
010 → 000	
010 → 001	
010 → 100	
010 → 101	

 2 – 10 points) A bus consisting of five bits ( $b_1 b_2 b_3 b_4 b_5$ ) is routed in three metal layers. Due to some unknown reasons, four of them ( $b_1 b_2 b_4 b_5$ ) are routed in parallel with  $b_3$ . The following shows the coupling capacitance among the five nets.



Due to the coupling between  $b_3$  and  $b_k$ , the worst-case effective coupling capacitance that  $b_3$  experiences will be  $8 \cdot C_c$ . List all transition patterns that make  $b_3$  experience  $8 \cdot C_c$  and  $7 \cdot C_c$ .
 
### Problem #4 (Buffer Insertion, 20 points).



A source (type: BUF\_X1) drives a sink (type: BUF\_X2) through a net and you are supposed to insert a buffer (type: BUF\_X1) between them as shown in the above figure. Find an optimal location of the buffer minimizing the total delay, i.e., represent “s” as a function of the following parameters.

- Output resistance of BUF\_X1:  $R_1$
- Input capacitance of BUF\_X1:  $C_1$
- Input capacitance of BUF\_X2:  $C_2$
- Total length of the net:  $L$  (um)
- Total wire resistance:  $R_w$
- Total wire capacitance:  $C_w$
- $(C_w + C_2 > C_1)$