

# EE434

## ASIC and Digital Systems

### Midterm Exam 1

February 25, 2015. (5:10pm – 6pm)

Instructor: Dae Hyun Kim ([daehyun@eecs.wsu.edu](mailto:daehyun@eecs.wsu.edu))

**Name:**

**WSU ID:**


Problem	Points	
1	10	
2	10	
3	10	
4	10	
5	10	
6	10	
7	10	
8	10	
Total	80	

\* Allowed: Textbooks, cheat sheets, class notes, notebooks, calculators, watches

\* Not allowed: Electronic devices (smart phones, tablet PCs, laptops, etc.) except calculators and watches
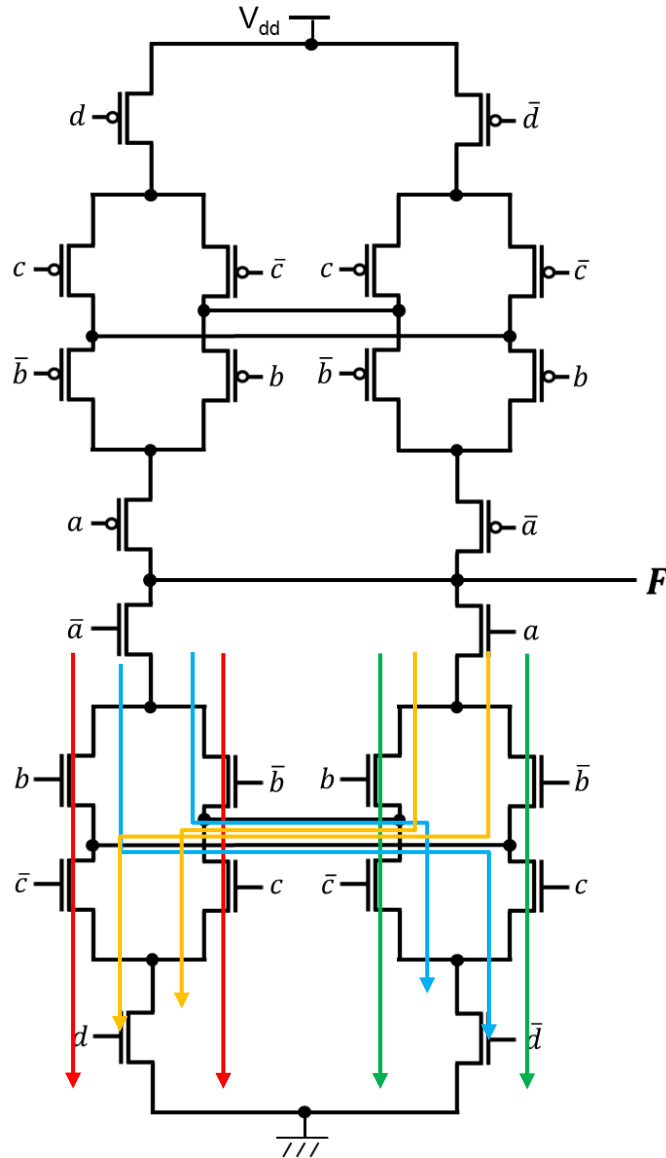
### Problem #1 (Static CMOS gates, 10 points).

Represent  $F$  as a function of  $a, b, c,$  and  $d$ .




$$\begin{aligned}
 \bar{F} &= \bar{a}d(b\bar{c} + \bar{b}c) + a\bar{d}(b\bar{c} + \bar{b}c) + \bar{a}\bar{d}(bc + \bar{b}\bar{c}) + ad(bc + \bar{b}\bar{c}) \\
 &= (\bar{a}d + a\bar{d})(b\bar{c} + \bar{b}c) + (\bar{a}\bar{d} + ad)(bc + \bar{b}\bar{c}) \\
 &= (a \oplus d)(b \oplus c) + \overline{(a \oplus d)(b \oplus c)} \\
 &= \overline{(a \oplus d) \oplus (b \oplus c)}
 \end{aligned}$$

$$\therefore F = a \oplus b \oplus c \oplus d$$


 
### Problem #3 (CMOS Logic, 10 points).

What is the functionality of the following circuit? Describe the functionality in as much detail as possible.



$$CK=1 \rightarrow X1=\bar{D} \rightarrow Q=\overline{X1}=D$$

If  $D=0 \rightarrow X1=1 \rightarrow Q=0 \rightarrow X1=1$  (no conflict)

If  $D=1 \rightarrow X1=0 \rightarrow Q=1$

$CK=0 \rightarrow$  The PDN of the right half is off.

If  $D=0 \rightarrow X1=1 \rightarrow mp1$  is off  $\rightarrow Q$  is floating (hold)


If  $D=1, Q=0 \rightarrow X1=1 \rightarrow mp1$  is off  $\rightarrow Q$  is floating (hold)

If  $D=1, Q=1 \rightarrow X1$  is floating (hold)  $\rightarrow Q$  is floating (hold)

so, this is a **tri-state D-latch**.

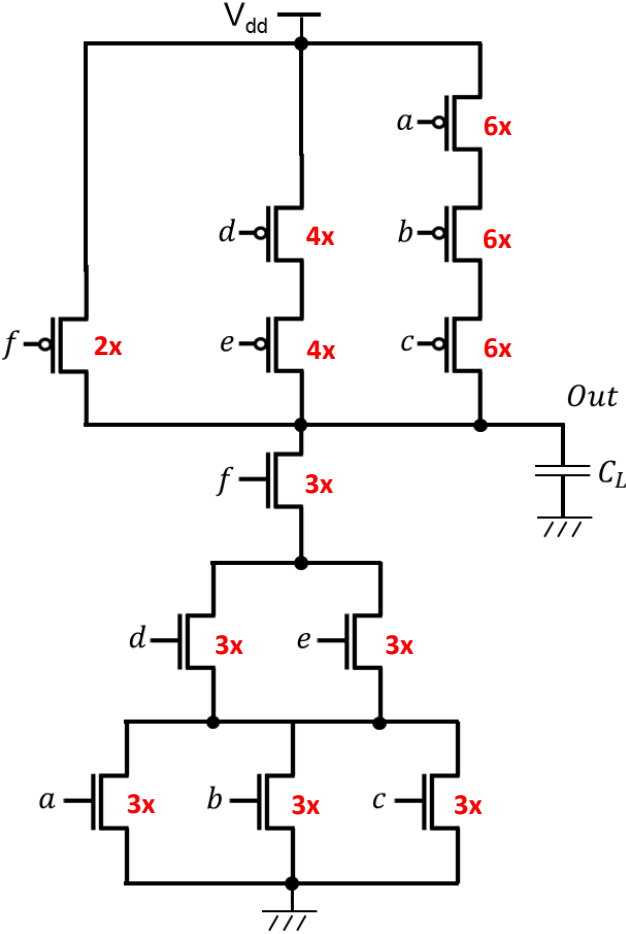
**Problem #4 (Transistor Sizing, 10 points).**

Size the transistors in the following gate.  $R_n$  is the resistance of a 1X NMOS transistor.  $\mu_n = 2 \cdot \mu_p$ . Ignore all the parasitic capacitances. Target time constant:  $\tau_{target} = R_n \cdot C_L$ . Try to minimize the total area.


 
## Problem #5 (Transistor Sizing, 10 points).

We want to design a  $k$ -input NOR gate. However, the static CMOS gate design methodology is not suitable for the design of the  $k$ -input NOR gate due to area overhead in the pull-up network and the body-bias effect. Therefore, we are going to design it using the dynamic CMOS design methodology. The following shows a schematic of the  $k$ -input NOR gate.



$R_n$  is the resistance of a 1X NMOS transistor.  $\mu_n = 2 \cdot \mu_p$ . Ignore all the parasitic capacitances. Target time constant:  $\tau_{target} = R_n \cdot C_L$ . All the transistors for  $x_1 \sim x_k$  are upsized to  $aX$  and the transistor for  $CK$  is upsized to  $bX$  ( $a$  and  $b$  are **real** numbers). We minimize the total width,  $Width = a \cdot k + b$ . Find  $a$  and  $b$  (i.e., derive  $a$  (and  $b$ ) as a function of  $k$ ) minimizing the total width.

$$\text{Constraint: } \left( \frac{R_n}{a} + \frac{R_n}{b} \right) C_L = R_n C_L \Rightarrow \frac{1}{a} + \frac{1}{b} = 1$$

$$W = ak + b = ak + \frac{a}{a-1}$$

$$1) W' = k + \frac{(a-1)-a}{(a-1)^2} = k - \frac{1}{(a-1)^2} = 0 \Rightarrow \boxed{a = 1 + \frac{1}{\sqrt{k}} \Rightarrow b = 1 + \sqrt{k}}$$


2)  $ak + b = c \Rightarrow$  Two functions,  $b = -ak + c$  and  $b = \frac{a}{a-1}$ , should meet at a single point (confirm this by drawing their graphs).

$\Rightarrow -ak + c = \frac{a}{a-1}$  should have a single root.  $\Rightarrow ka^2 - (k + c - 1)a + c = 0$  has a single root.  $\Rightarrow (k + c - 1)^2 - 4kc = 0 \Rightarrow (k - c - 1)^2 = 0 \Rightarrow c = k + 1 \pm 2\sqrt{k} \Rightarrow$

$$a = 1 \pm \frac{1}{\sqrt{k}} \Rightarrow a > 1, \text{ so } \boxed{a = 1 + \frac{1}{\sqrt{k}} \Rightarrow b = 1 + \sqrt{k}}$$

## Problem #6 (Elmore Delay, 10 points).

 6-1. Compute Elmore delay at LOAD1 and LOAD2, i.e., represent the delay at LOAD1 (and LOAD2) as a function of  $R_1 \sim R_4$ ,  $C_1$ ,  $C_2$ ,  $C_{LOAD1}$ , and  $C_{LOAD2}$ .



At LOAD1:  $R_1(C_1 + C_2 + C_{LOAD1} + C_{LOAD2}) + R_2(C_2 + C_{LOAD1}) + R_3C_{LOAD1}$

At LOAD2:  $R_1(C_1 + C_2 + C_{LOAD1} + C_{LOAD2}) + R_4C_{LOAD2}$


6-2. Compute Elmore delay at LOAD1 for  $R_1 = R_2 = R_3 = 1k\Omega$ ,  $C_1 = C_2 = C_{LOAD1} = 10fF$ ,  $R_4 = 0.1k\Omega$ , and  $C_{LOAD2} = 1pF$ . Then, compute Elmore delay at LOAD1 for  $R_1 = R_2 = R_3 = 1k\Omega$ ,  $C_1 = C_2 = C_{LOAD1} = 10fF$ ,  $R_4 = 10M\Omega$ , and  $C_{LOAD2} = 1pF$ . This result is called “resistive shielding”. Discuss a limitation of the Elmore delay model in terms of the resistive shielding effect.

At LOAD1:  $1k(10f+10f+10f+1p) + 1k(10f+10f) + 1k(10f) = (1k*1030f) + (1k*20f) + (1k*10f)$   
 $= 1030ps + 20ps + 10ps = 1060ps$

The Elmore delay at LOAD1 is not affected by  $R_4$ . If  $R_4$  is sufficiently small, the Elmore delay at LOAD1 should include  $C_{LOAD2}$ . However, if  $R_4$  is sufficiently large, we can assume that the Load2 branch does not exist, so the Elmore delay at LOAD1 should not include  $C_{LOAD2}$ . The Elmore delay model does not distinguish these two cases.
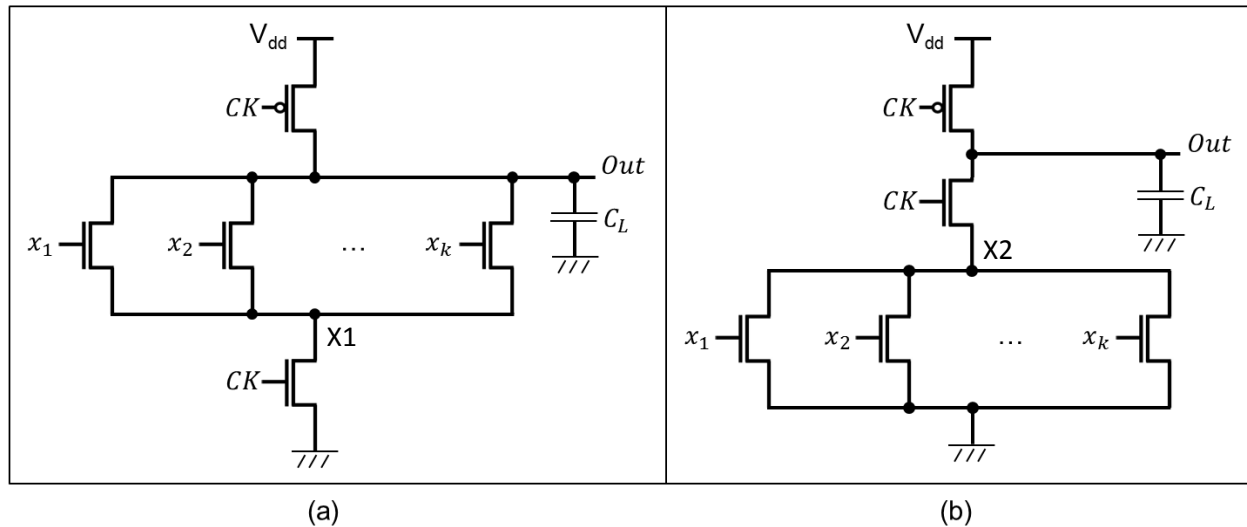
### Problem #7 (Dynamic CMOS, 10 points).

Compare the following implementations for a dynamic-CMOS  $k$ -input NOR gate. Are there any problems in (a)? in (b)?




(a) does not have any charge sharing problem. When  $CK=0$ , the PMOS transistor charges the output capacitor and X1 (if any  $x_i$  is 1).

(b) suffers from charge sharing. When  $CK=0$ , the PMOS transistor charges the output capacitor only. When  $CK=1$  and  $x_1=\dots=x_k=0$ , charge sharing happens between the output capacitor and the parasitic capacitor at X2.


 
## Problem #8 (DC Characteristics, 10 points).

The following circuit is called “pseudo-PMOS”. Sketch a DC characteristic curve of the pseudo-PMOS inverter and properly split the curve into regions. In each region, show the status (cut-off, linear, saturation) of each transistor ( $m_n$  and  $m_p$ ).



- 1)  $m_n$ :  $V_{gs} - V_t = V_{DD} - V_{tn} > 0$  (always),  $V_{ds} = V_{out}$ 
  - i)  $V_{gs} - V_t < V_{ds} \Rightarrow V_{DD} - V_{tn} < V_{out} \Rightarrow$  saturation
  - ii)  $V_{DD} - V_{tn} > V_{out} \Rightarrow$  linear
- 2)  $m_p$ :  $|V_{gs}| - |V_t| = V_{DD} - V_{in} - |V_{tp}|$ ,  $|V_{ds}| = V_{DD} - V_{out}$ 
  - i)  $|V_{gs}| - |V_t| < 0 \Rightarrow V_{in} > V_{DD} - |V_{tp}| \Rightarrow$  cut-off
  - ii)  $V_{gs} - V_t < V_{ds} \Rightarrow V_{out} < V_{in} + |V_{tp}| \Rightarrow$  saturation
  - iii)  $V_{gs} - V_t > V_{ds} \Rightarrow V_{out} > V_{in} + |V_{tp}| \Rightarrow$  linear

\*) Depending on the size of the NMOS and PMOS transistors, the highest output voltage might be less than  $V_{DD} - V_{tn}$ . In this case, the NMOS transistor is in the linear mode even when  $V_{in}$  is close to 0.