

EE434

ASIC and Digital Systems

Midterm Exam 1

Mar. 4, 2020. (2:10pm – 3pm)

Instructor: Dae Hyun Kim (daehyun@eecs.wsu.edu)

Name:

WSU ID:

Problem	Points	
1	10	
2	10	
3	10	
4	10	
5	10	
6	10	
7	10	
8	10	
Total	80	


Problem #1 (Static CMOS gates, 10 points)

Design the following logic using the static CMOS design methodology. Try to minimize the # transistors. Available input: A, B, C, D .


$$Y = \overline{A + \overline{B} \cdot \overline{C} \cdot \overline{D}}$$

If we design it directly, we will need eight TRs + six TRs (for three inverters) = 14 TRs.

 However, if we design $Y = \overline{A + \overline{B} \cdot \overline{C} \cdot \overline{D}} = \overline{\overline{A} \cdot (B + C + D)}$, we will need eight TRs + four TRs (two for the inverter for \overline{A} and two for the outer (last-level) inverter).



 Left: $8 + 2 + 2 + 2 = 14$ TRs (7 points)




Right: $8 + 2 + 2 = 12$ TRs (10 points)

Problem #2 (Static CMOS gates, 10 points)

Design the following logic using the static CMOS design methodology. Try to minimize the # transistors. Available input: A, B, C, D .

$$Y = A \cdot B \cdot (\bar{C} + \bar{D})$$

 
$$Y = \overline{\bar{A} + \bar{B} + C \cdot D}$$



8 + 4 = 12 TRs (10 points)

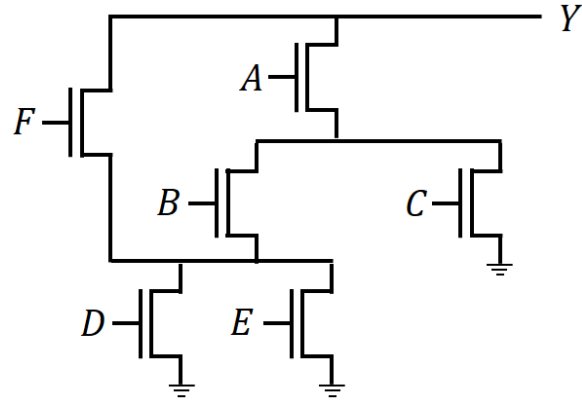Problem #3 (Static CMOS gates, 10 points)


The following shows the NFET network of a static CMOS gate. Express the output Y as a Boolean function of the inputs ($A \sim F$). (You don't need to simplify the expression.)



$$Y = \overline{F(D + E + BC) + A(C + B(D + E))}$$

 Problem #4 (Static CMOS gates, 10 points)

The following shows the PFET network of a static CMOS gate. Express the output Y as a Boolean function of the inputs ($A \sim E$). (You don't need to simplify the expression.)




$$Y = (\bar{A} \cdot (\bar{B} + \bar{C}) + \bar{D}) \cdot \bar{E} = \overline{(A + BC) \cdot D + E}$$

Problem #5 (Transmission Gates, 10 points)


Design (draw a schematic) the following Boolean function using transmission gates only.

$$Y = A \oplus (B \cdot (C \oplus D))$$

 Available inputs: $A, B, C, D, 0, 1$. Use the following symbols for the transmission gates.



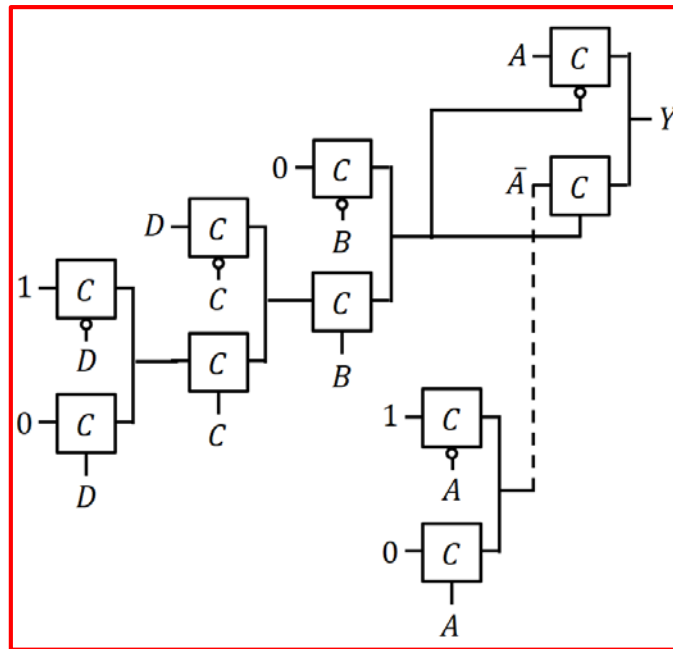(# TGs ≤ 12: 10 points. 13 ≤ # TGs ≤ 15: 7 points. 16 ≤ # TGs ≤ 18: 5 points. # TGs > 18: 3 points)



Problem #6 (Sequential Logic, 10 points)

The following truth table shows the function of a sequential logic. CK is the clock signal. A, B, D, E, and F are data or control (e.g., reset) signals. What does the gate do??
Explain the function in detail.


A	B	D	E	F	CK		Q ⁺
0	X	0	E	X	↓		E
0	X	1	X	F	↓		F
1	B	X	X	X	↓		B
X	X	X	X	X	↑		Q
X	X	X	X	X	0 or 1		Q

It is a negative-edge-triggered D-FF with the following features:

- A and D are used as input signal selectors as follows:
 - A=0, D=0: E is the data input.
 - A=0, D=1: F is the data input.
 - A=1: B is the data input.

 Problem #7 (Analysis, 10 points)


What do the following circuits do? (You can ignore the numbers in the schematics.) For each schematic, you can draw a truth table or express the output as a function of the inputs.



(a)

$$O = A \cdot \bar{B} + \bar{A} \cdot B = A \oplus B$$

(JSSC'97)

 


(b)

$$F = A \cdot \bar{C} + \bar{A} \cdot (B \cdot \bar{D} + \bar{B} \cdot \bar{E})$$

(JSSC'96)

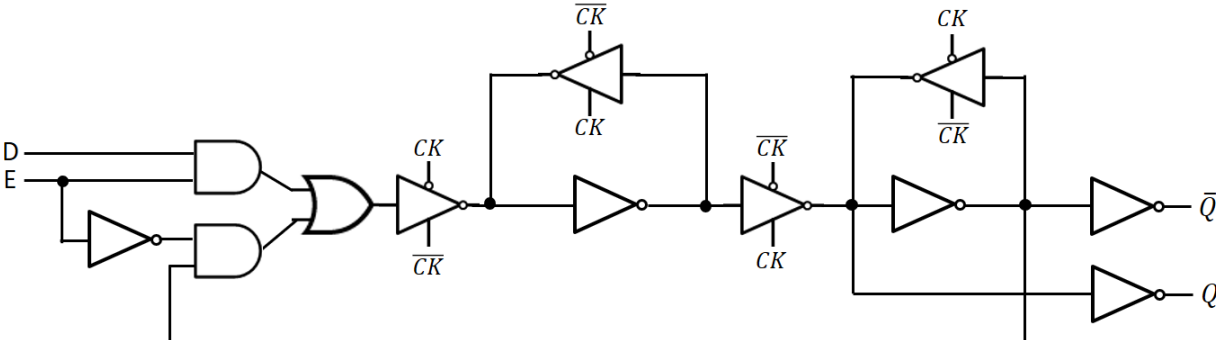Problem #8 (Sequential Logic, 10 points)

Explain the function of the following logic. CK: Clock. D, E: Data and/or control input.



If E=0, Q=hold regardless of the clock signal.

If E=1, it is a normal positive-edge-triggered D-F/F (in this case, D is the data input).