

EE466
VLSI System Design

Midterm Exam

Oct. 25, 2018. (4:15pm – 5:30pm)

Instructor: Dae Hyun Kim (daehyun@eecs.wsu.edu)

Name:

WSU ID:

Problem	Points	
1	10	
2	10	
3	5	
4	10	
5	5	
6	10	
7	10	
8	10	
Total	70	

* Allowed: Textbooks, cheat sheets, class notes, notebooks, calculators, watches

* Not allowed: Electronic devices (smart phones, tablet PCs, laptops, etc.) except calculators and watches


Problem #1 (Static CMOS Gates, 10 points).

Draw a transistor-level schematic for the following Boolean function (Available input: $A, B, C, D, \bar{A}, \bar{B}, \bar{C}, \bar{D}$). Use the static CMOS gate design. Minimize the # TRs.

TRs ≤ 22 : 10 points. $23 \leq$ # TRs ≤ 24 : 8 points. $25 \leq$ # TRs ≤ 26 : 6 points. $27 \leq$ # TRs: 4 points.

$$F = A + (B \oplus (\bar{C} \oplus \bar{D}))$$

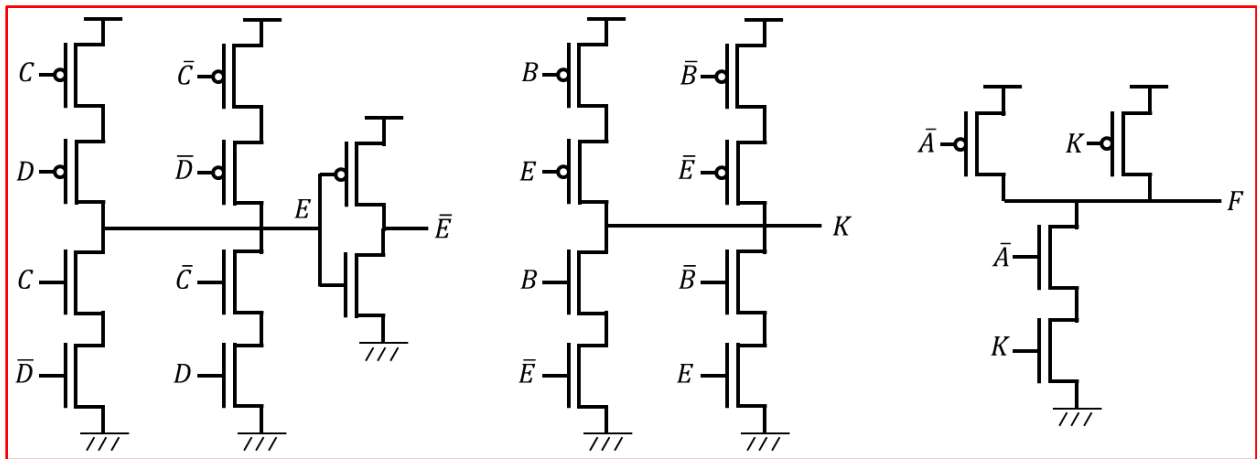
$$F = A + \overline{(B \oplus (\bar{C} \oplus \bar{D}))} = \bar{A} \cdot B \oplus (\bar{C} \oplus \bar{D})$$



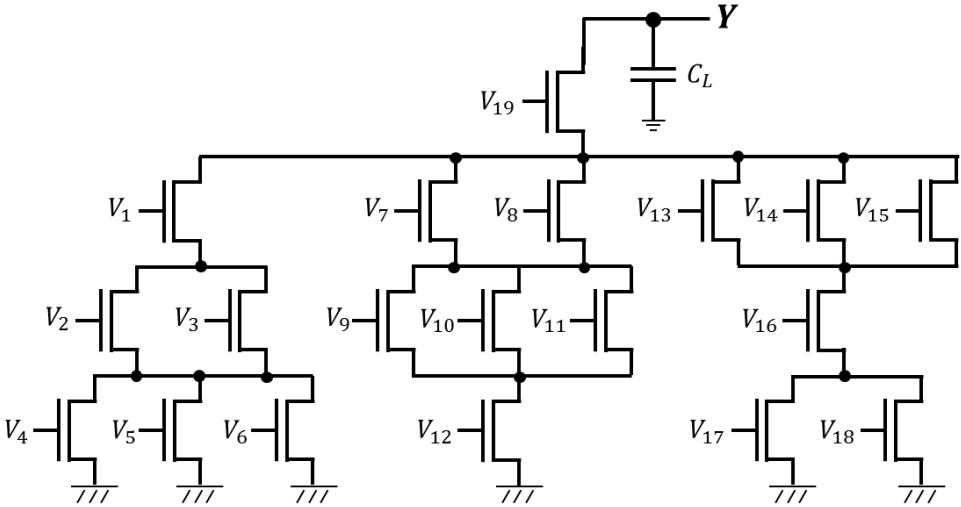Problem #2 (Transistor Sizing, 10 points).


Size the transistors in the following pull-down network of a static CMOS gate. R_n is the resistance of a 1X NMOS transistor. C_L is the load cap. Ignore parasitic capacitances. Target timing constraint: $\tau = R_n \cdot C_L$. Try to minimize the total area.

Area $\leq 80X$: 10 points. $80X < \text{Area} \leq 82X$: 8 points. $82X < \text{Area} \leq 84X$: 6 points. $84X < \text{Area}$: 4 points.



The worst case is that only one path is activated (e.g., V_{19}, V_1, V_2, V_4). Thus, each of them is upsized to 4X. Thus, all of them are upsized to 4X. Total area: 76X.

 
Problem #3 (Switching Analysis, 5 points).



All the transistors in the figure shown above have the same width W . Ignore parasitic RC. All the inputs are 0V at time 0. At time t , some of the input voltages switch from 0 to V_{DD} . Which one of the following has the smallest falling delay?


- 1) V_{19}, V_1, V_2, V_5 switch from 0 to VDD. $R = \frac{4}{w}$
- 2) $V_{19}, V_1, V_2, V_3, V_5$ switch from 0 to VDD. $R = \frac{1}{w} + \frac{1}{2w} + \frac{1}{w} + \frac{1}{w} = \frac{7}{2w} = \frac{3.5}{w}$
- 3) $V_{19}, V_7, V_8, V_{10}, V_{12}$ switch from 0 to VDD. $R = \frac{3.5}{w}$
- 4) $V_{19}, V_7, V_9, V_{12}, V_{13}, V_{14}, V_{15}, V_{16}$ switch from 0 to VDD. $R = \frac{4}{w}$
- 5) $V_{19}, V_1, V_2, V_6, V_7, V_9, V_{12}, V_{13}, V_{16}, V_{18}$ switch from 0 to VDD. $R = \frac{3}{3w} + \frac{1}{w} = \frac{2}{w}$
- 6) $V_{19}, V_1, V_2, V_4, V_7, V_8, V_9, V_{10}, V_{11}, V_{13}, V_{14}, V_{15}, V_{16}$ switch from 0 to VDD. $R = \frac{4}{w}$

Problem #4 (DC Analysis, 10 points).

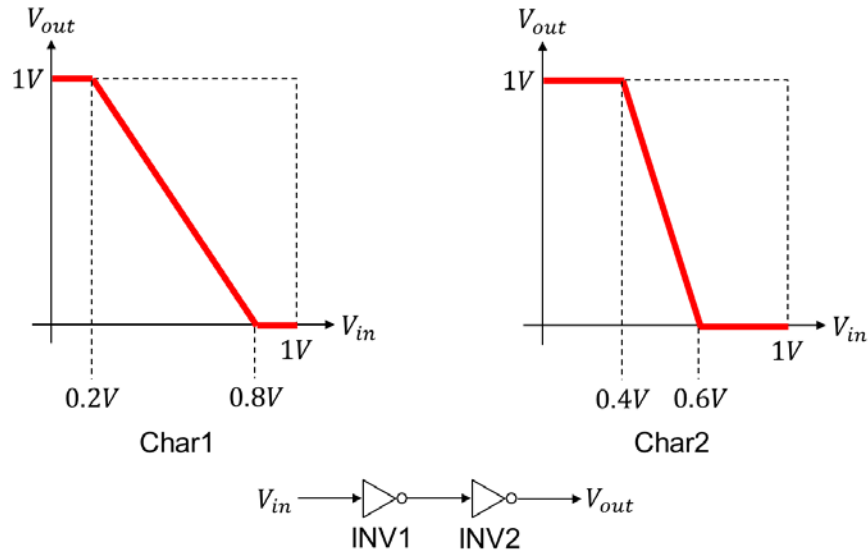


The gate-level schematic shows a buffer composed of two inverters.

 1) Draw a DC characteristic curve (Char1 is for INV1 and Char2 is for INV2). You should show not only the curve, but also some important numbers in the curve.




 2) Draw a DC characteristic curve (Char1 is for INV2 and Char2 is for INV1). You should show not only the curve, but also some important numbers in the curve.




 Problem #5 (Sequential Logic, 5 points).

The following shows a schematic of a positive-edge-triggered D-FF.




 What does the following circuit do? Can you explain any differences between the two circuits?



The second one is also a positive-edge-triggered D-FF. The Clock-to-Q delay of the second one is shorter than that of the first one.

 
Problem #6 (Sequential Logic, 10 points).



Describe the function of the circuit shown above.

It is a positive-edge-triggered D-FF.

 Problem #7 (Sequential Logic, 10 points).



Describe the function of the circuit shown above.

It is a positive-edge-triggered D-FF.

Problem #8 (Static CMOS Gates, 10 points).

Draw a dual PFET network of the following NFET network between nodes X and Y. Use eight PFETs only.

