
Arithmetic Circuits

High-Speed Adders

Dae Hyun Kim


EECS

Washington State University

Full Adder


- Input: A, B, CI (Carry-in)
- Output: S, CO (Carry-out)
 - $S = A \oplus B \oplus CI$
 - $CO = A \cdot B + B \cdot CI + CI \cdot A = A \cdot B + CI \cdot (A + B)$

A	B	CI	S	CO
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


Two-Operand n -bit Adder

 - Input: $A[n - 1: 0]$, $B[n - 1: 0]$, CI
- Output: $S[n - 1: 0]$, CO
- For two's complement subtraction, there could be a control signal s .
 - $s = 0$: addition ($A + B$)
 - In this case, we compute $A + B$, so $CI = 0$.
 - $s = 1$: subtraction ($A - B$)
 - In this case, we compute $A + \bar{B} + 1$, so B is inverted and $CI = 1$.




n -bit Ripple Carry Adder (delay: $O(n)$)

 - C_k : Carry
- Delay computation
 - FA delay: d
 - n -bit RCA delay: $n \cdot d$
 - $O(n)$
 - Example
 - $n: 64, d: 50ps$ (45nm) \rightarrow delay = 3.2ns (Clock: 312.5MHz)
- Bottleneck: Carry propagation
- Solution: Parallelization




$2k$ -bit Carry Select Adder

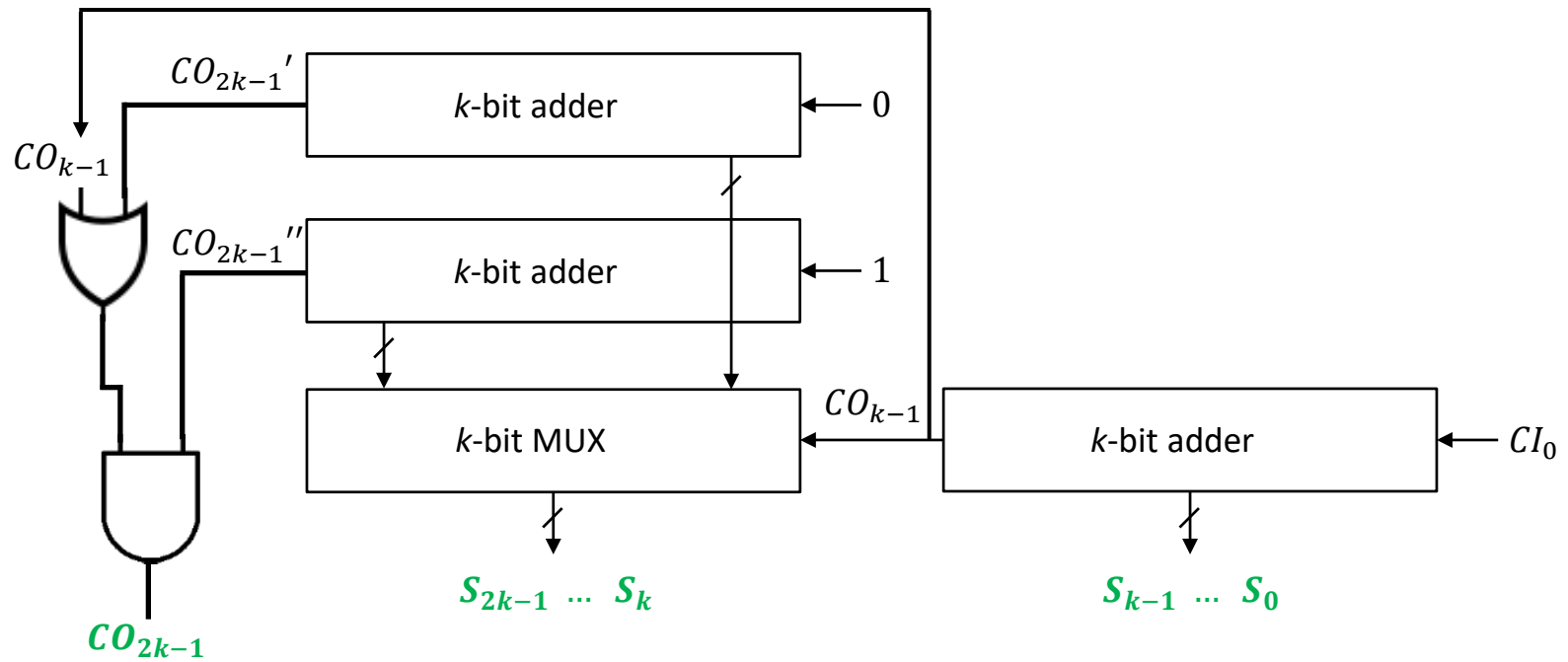

2k-bit Carry Select Adder


○ Example

$i:$	7	6	5	4		3	2	1	0	$CI_0 = 0$
$A_i:$	1	0	1	1		0	1	1	0	
$B_i:$	0	0	1	0		1	1	0	1	

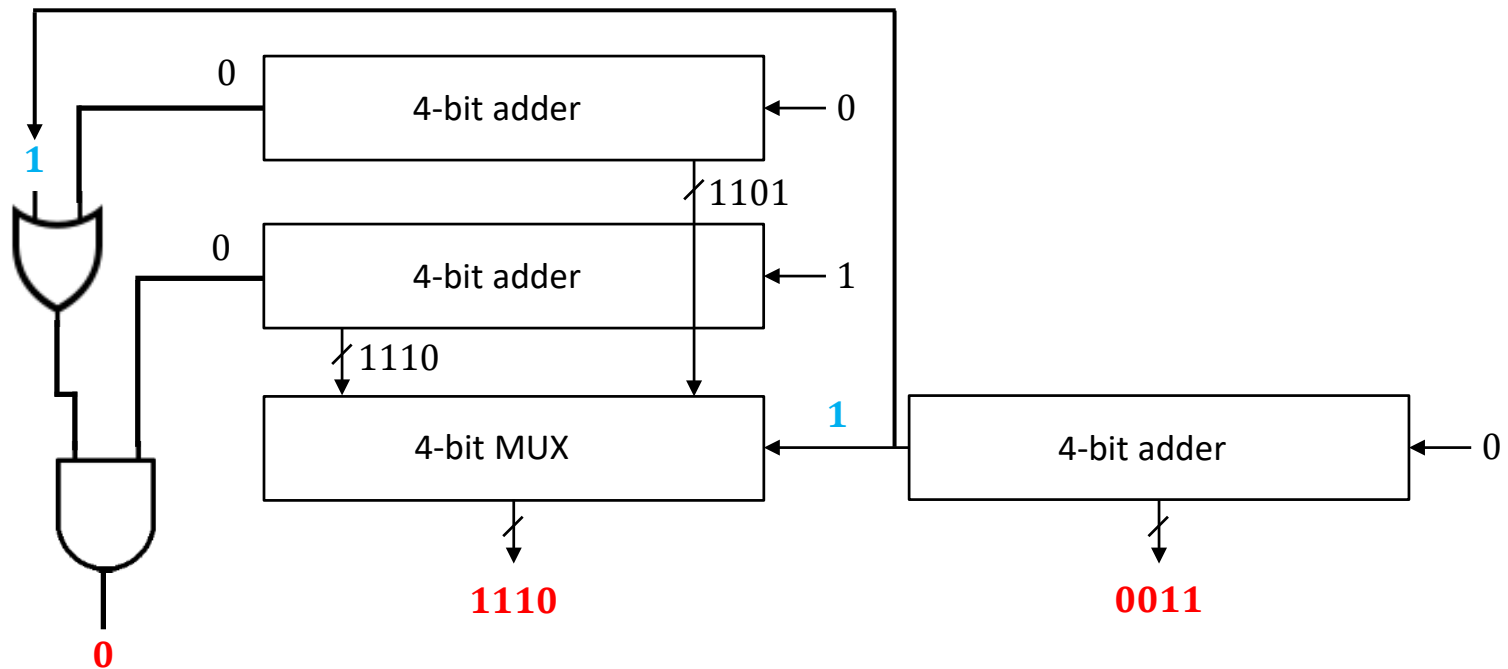

$2k$ -bit Carry Select Adder

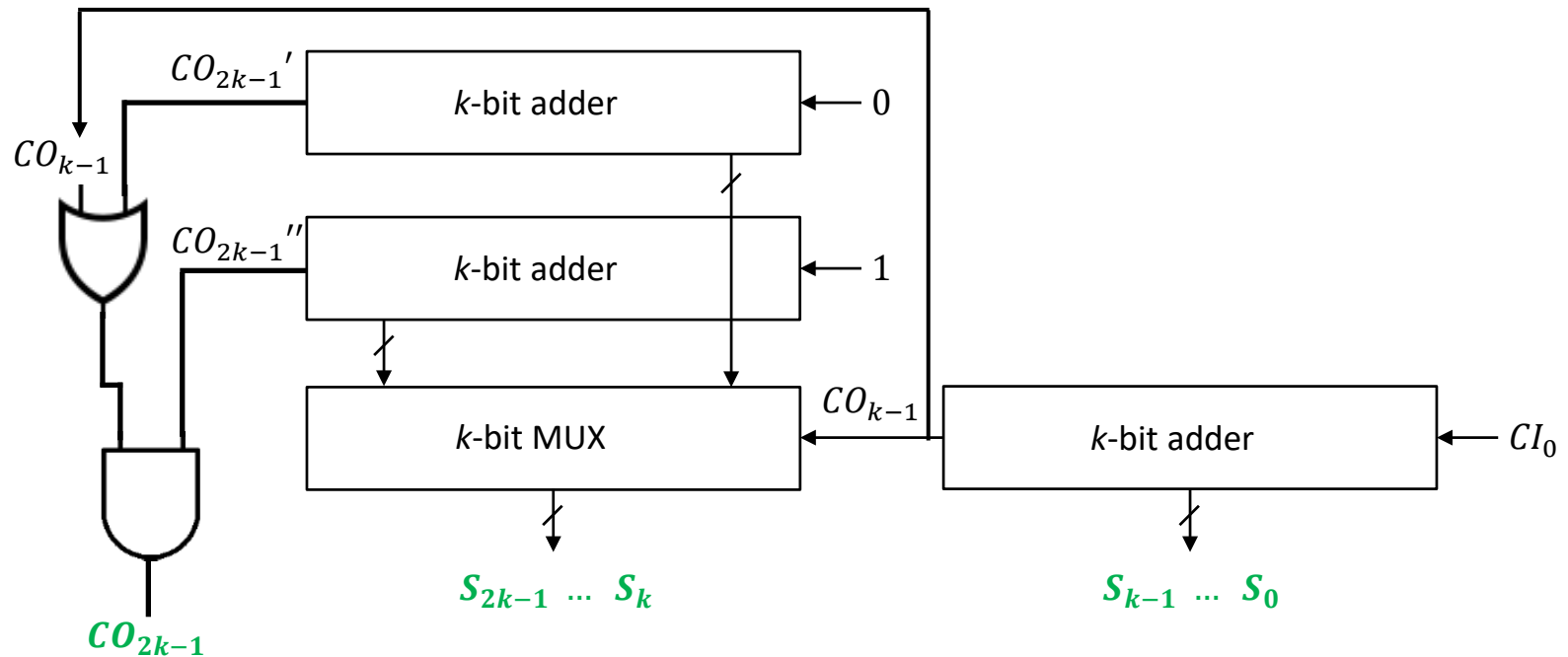- Delay analysis
 - Delay of a k -bit adder + delay of (a MUX or two gates)




Carry Select Adder

○ Parallelization

▪ Example: $4k$ -bit carry select adder

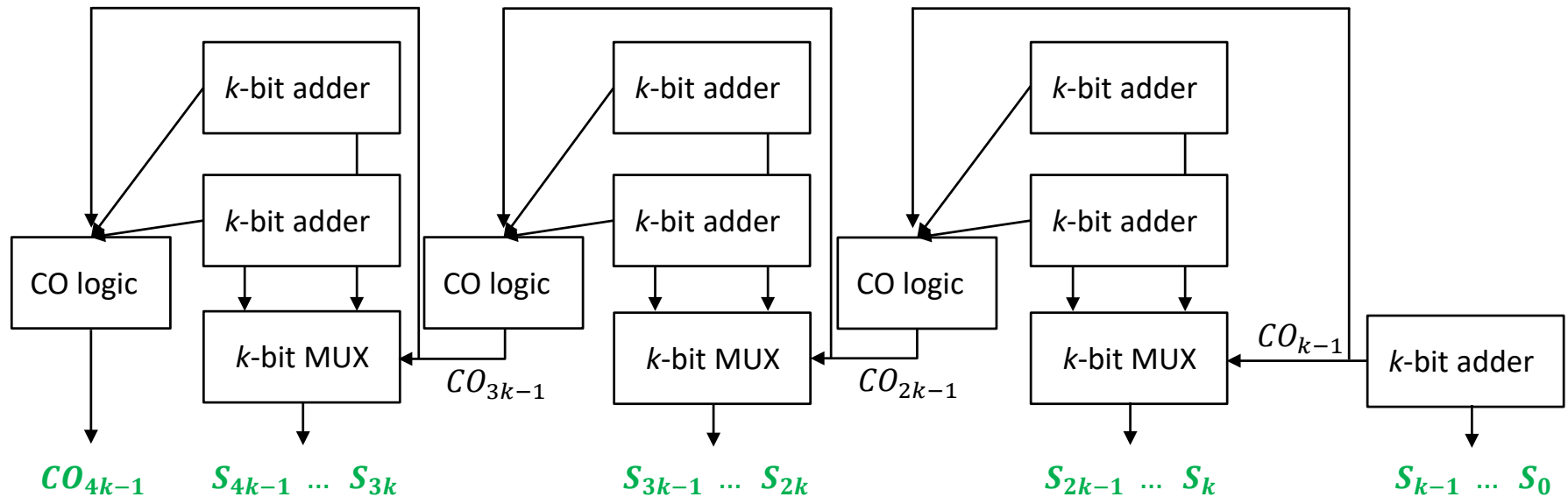- Delay: Delay of a k -bit adder + $2 \cdot$ (CO logic delay) + (CO logic delay or a MUX delay)



n -bit Carry Select Adder (delay: $O(\sqrt{n})$)

- Optimization
 - Find the optimal # stages minimizing the total delay.
- Assumption
 - Delay of a full-adder (FA): d
 - The k -bit adder is a ripple-carry adder.
 - Delay: $k \cdot d$
 - Delay of a carry-out logic or a MUX: e
- # stages: $\frac{n}{k}$ (find k minimizing the delay)
- Delay: $\tau = k \cdot d + e \cdot \left(\frac{n}{k} - 1\right)$
 - $\frac{d\tau}{dk} = d - \frac{e \cdot n}{k^2} = 0$
 - $k = \sqrt{\frac{e \cdot n}{d}}$ (so the optimal # stages is $\frac{n}{k} = \sqrt{\frac{d \cdot n}{e}}$)
 - Delay: $\tau = 2\sqrt{d \cdot e \cdot n} - e \rightarrow O(\sqrt{n})$

n -bit Carry Select Adder (delay: $O(\sqrt{n})$)

- Example

- $n: 64, d: 50ps, e: 50ps$

- $k = \sqrt{\frac{50 \cdot 64}{50}} = 8$ (8-bit ripple-carry adder)

- Delay: $\tau = 2\sqrt{50 \cdot 50 \cdot 64} - 50 = 750ps$ (4.3X improvement)

- Delay of a 64-bit RCA: $64 \cdot 50 = 3,200ps$

Carry Signals

- $C_k = (A_{k-1} \cdot B_{k-1}) + (A_{k-1} \oplus B_{k-1}) \cdot C_{k-1}$
- $C_1 = (A_0 \cdot B_0) + (A_0 \oplus B_0) \cdot C_0$
- $C_2 = (A_1 \cdot B_1) + (A_1 \oplus B_1) \cdot C_1 = [(A_1 \cdot B_1) + (A_1 \oplus B_1) \cdot (A_0 \cdot B_0)] + [(A_1 \oplus B_1) \cdot (A_0 \oplus B_0) \cdot C_0]$
- $C_3 = (A_2 \cdot B_2) + (A_2 \oplus B_2) \cdot C_2 =$
 $[(A_2 \cdot B_2) + (A_2 \oplus B_2) \cdot (A_1 \cdot B_1) + (A_2 \oplus B_2) \cdot (A_1 \oplus B_1) \cdot (A_0 \cdot B_0)] +$
 $[(A_2 \oplus B_2) \cdot (A_1 \oplus B_1) \cdot (A_0 \oplus B_0) \cdot C_0]$
- $C_4 = (A_3 \cdot B_3) + (A_3 \oplus B_3) \cdot C_3 =$
 $[(A_3 \cdot B_3) + (A_3 \oplus B_3) \cdot (A_2 \cdot B_2) + (A_3 \oplus B_3) \cdot (A_2 \oplus B_2) \cdot (A_1 \cdot B_1) + (A_3 \oplus B_3) \cdot (A_2 \oplus B_2) \cdot (A_1 \oplus B_1) \cdot (A_0 \cdot B_0)] +$
 $[(A_3 \oplus B_3) \cdot (A_2 \oplus B_2) \cdot (A_1 \oplus B_1) \cdot (A_0 \oplus B_0) \cdot C_0]$
- Black: generated only by A_k and B_k .
- Green: generated by A_k , B_k , and C_0 .
- Generation: $g_i = A_i \cdot B_i$
- Propagation: $p_i = A_i \oplus B_i$

- $C_1 = g_0 + p_0 \cdot C_0$
- $C_2 = g_1 + p_1 \cdot g_0 + p_1 \cdot p_0 \cdot C_0$
- $C_3 = g_2 + p_2 \cdot g_1 + p_2 \cdot p_1 \cdot g_0 + p_2 \cdot p_1 \cdot p_0 \cdot C_0$
- $C_4 = g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0 + p_3 \cdot p_2 \cdot p_1 \cdot p_0 \cdot C_0$

Carry Skip Adder


- Carry (C_4)

- $C_4 = g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0 + p_3 \cdot p_2 \cdot p_1 \cdot p_0 \cdot C_0$

Group carry generation

Group carry propagation

- Split the input into a few groups.

 

- Group carry generation

- $g_{3:0} = g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0$

- Group carry propagation


- $p_{3:0} = p_3 \cdot p_2 \cdot p_1 \cdot p_0$

- Carry generation

- $C_4 = g_{3:0} + p_{3:0} \cdot C_0$

Carry Skip Adder

 - 4-bit blocks
 - Generates $g_{k:k-3}$ and $p_{k:k-3}$ all in parallel.
 - Propagate C_0 to the last stage quickly.




- If $g_{k:k-3}$ is 1, $p_{k:k-3}$ is 0, so $g_{k:k-3}$ is passed to the next stage (generated).
- If $g_{k:k-3}$ is 0 and $p_{k:k-3}$ is 1, C_k is passed to the next stage (propagated).
- If $g_{k:k-3}$ is 0 and $p_{k:k-3}$ is 0, 0 is passed to the next stage (killed).

Carry Skip Adder

○ Example

 - $A = 1101\ 1011\ 0111\ 1010$
- $B = 0101\ 0101\ 1101\ 0101$
- $C_0 = 1$



n -bit Carry Skip Adder (delay: $O(\sqrt{n})$)

- Optimization
 - Find the optimal # stages minimizing the total delay.
- Assumption
 - Delay of a full-adder (FA): d
 - The k -bit adder is a ripple-carry adder.
 - Delay: $k \cdot d$
 - Delay of a gate or a MUX: e
- # stages: $\frac{n}{k}$ (find k minimizing the delay)
- Delay
 - g_i, p_i : e
 - $p_{i:i-3}$: $2e$
 - $g_{i:i-3}$: $3e$ (two-stage logic, AND-OR)
 - Delay: $\tau = 3e + \left(\frac{n}{k} - 1\right) \cdot e + k \cdot d$
 - $\frac{d\tau}{dk} = d - \frac{e \cdot n}{k^2} = 0$
 - $k = \sqrt{\frac{e \cdot n}{d}}$ (so the optimal # stages is $\frac{n}{k} = \sqrt{\frac{d \cdot n}{e}}$)
 - Delay: $\tau = 2\sqrt{d \cdot e \cdot n} + 2e \rightarrow O(\sqrt{n})$
 - Example: 900ps for $n = 64, d = e = 50ps$

***n*-bit Conditional Sum Adder (Delay: $O(\log_2 n)$)**

- Main idea
 - Generate two sets of outputs for a given group of operand bits.
 - Set 1: assuming the incoming carry is zero.
 - Set 2: assuming the incoming carry is one.
 - Once the incoming carry is known, select the correct set of outputs.
-

Conditional Sum Adder

- Generate two sets of outputs

	$i:$	7	6	5	4	3	2	1	0
	$A_i:$	1	0	1	1	0	1	1	0
	$B_i:$	0	0	1	0	1	1	0	1
Step 1	$S_i^0:$	1	0	0	1	1	0	1	1
	$CO_i^0:$	0	0	1	0	0	1	0	0
	$S_i^1:$	0	1	1	0	0	1	0	
	$CO_i^1:$	1	0	1	1	1	1	1	

$$CI_0 = 0$$

Conditional Sum Adder

- Merge two bits

	$i:$	7	6	5	4	3	2	1	0
	$A_i:$	1	0	1	1	0	1	1	0
	$B_i:$	0	0	1	0	1	1	0	1
Step 1	$S_i^0:$	1	0	0	1	1	0	1	1
	$CO_i^0:$	0	0	1	0	0	1	0	0
Step 2	$S_i^0:$	1	0	0	1	0	0	1	1
	$CO_i^0:$	0	0	1	1	1	1	0	0
Step 1	$S_i^1:$	0	1	1	0	0	1	0	
	$CO_i^1:$	1	0	1	1	1	1	1	
Step 2	$S_i^1:$	1	1	1	0	0	1		
	$CO_i^1:$	0		1		1			

$$CI_0 = 0$$

Conditional Sum Adder

- Merge four bits

	$i:$	7	6	5	4	3	2	1	0
	$A_i:$	1	0	1	1	0	1	1	0
	$B_i:$	0	0	1	0	1	1	0	1
Step 1	$S_i^0:$	1	0	0	1	1	0	1	1
	$CO_i^0:$	0	0	1	0	0	1	0	0
Step 1	$S_i^1:$	0	1	1	0	0	1	0	
	$CO_i^1:$	1	0	1	1	1	1	1	
Step 2	$S_i^0:$	1	0	0	1	0	0	1	1
	$CO_i^0:$	0		1		1		0	
Step 2	$S_i^1:$	1	1	1	0	0	1		
	$CO_i^1:$	0		1		1			
Step 3	$S_i^0:$	1	1	0	1	0	0	1	1
	$CO_i^0:$	0		1		1			
Step 3	$S_i^1:$	1	1	1	0				
	$CO_i^1:$	0		1					

$$CI_0 = 0$$

Conditional Sum Adder

- Merge eight bits (final)

	$i:$	7	6	5	4	3	2	1	0
	$A_i:$	1	0	1	1	0	1	1	0
	$B_i:$	0	0	1	0	1	1	0	1
Step 1	$S_i^0:$	1	0	0	1	1	0	1	1
	$CO_i^0:$	0	0	1	0	0	1	0	0
Step 2	$S_i^1:$	0	1	1	0	0	1	0	
	$CO_i^1:$	1	0	1	1	1	1	1	
Step 3	$S_i^0:$	1	0	0	1	0	0	1	1
	$CO_i^0:$	0		1		1		0	
Step 3	$S_i^1:$	1	1	1	0				
	$CO_i^1:$	0		1		1			
Result		1	1	1	0	0	0	1	1

$$CI_0 = 0$$

①

Conditional Sum Adder

○ Exercise

	$i:$	7	6	5	4	3	2	1	0
	$A_i:$	1	0	1	1	0	1	1	0
	$B_i:$	0	0	1	0	1	1	0	1
Step 1	$S_i^0:$								
	$CO_i^0:$								
Step 2	$S_i^1:$								
	$CO_i^1:$								
Step 3	$S_i^0:$								
	$CO_i^0:$								
Step 3	$S_i^1:$								
	$CO_i^1:$								
Result									

$$CI_0 = 1$$

Conditional Sum Adder

- Delay analysis

	$i:$	7	6	5	4	3	2	1	0
	$A_i:$	1	0	1	1	0	1	1	0
	$B_i:$	0	0	1	0	1	1	0	1
Step 1	$S_i^0:$	1	0	0	1	1	0	1	1
	$CO_i^0:$	0	0	1	0	0	1	0	0
	$S_i^1:$	0	1	1	0	0	1	0	
	$CO_i^1:$	1	0	1	1	1	1	1	
Step 2	$S_i^0:$	1	0	0	1	0	0	1	1
	$CO_i^0:$	0		1		1			
	$S_i^1:$	1	1	1	0	0	1		
	$CO_i^1:$	0		1		1			
Step 3	$S_i^0:$	1	1	0	1	0	0	1	1
	$CO_i^0:$	0				1			
	$S_i^1:$	1	1	1	0				
	$CO_i^1:$	0							

$$\tau = \Delta_{FA}$$

$$\tau = \Delta_{FA} + \Delta_{MUX}$$

$$\tau = \Delta_{FA} + 2\Delta_{MUX}$$

n -bit Conditional Sum Adder

- Delay analysis
 - Delay of a 1-bit adder: d
 - Delay of a MUX: m
 - Delay: $\tau = d + (\log_2 n - 1) \cdot m \Rightarrow O(\log_2 n)$
 - $d = 50ps, m = 50ps, n = 64$
 - $\tau = 300ps$

	RCA	Carry Select	Carry Skip	Conditional Sum
Delay	$O(n)$	$O(\sqrt{n})$	$O(\sqrt{n})$	$O(\log_2 n)$
64-bit	3,200ps	750ps	900ps	300ps

Prefix Adder

- Generation: $g_i = A_i \cdot B_i$
 - $g_i = 1$ only when $(A_i, B_i) = (1,1)$
- Propagation: $p_i = A_i \oplus B_i$ (conceptually $A_i \oplus B_i$, practically $A_i + B_i$)
 - $p_i = 1$ only when $(A_i, B_i) = (1,0)$ or $(0,1)$
- $C_1 = g_0 + p_0 \cdot C_0$
- $C_2 = g_1 + p_1 \cdot g_0 + p_1 \cdot p_0 \cdot C_0 = g_1 + p_1 \cdot C_1$
- $C_3 = g_2 + p_2 \cdot g_1 + p_2 \cdot p_1 \cdot g_0 + p_2 \cdot p_1 \cdot p_0 \cdot C_0 = g_2 + p_2 \cdot C_2$
- $C_4 = g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0 + p_3 \cdot p_2 \cdot p_1 \cdot p_0 \cdot C_0 = g_3 + p_3 \cdot C_3$
- In general
 - $C_{i+1} = g_i + p_i \cdot C_i$
 - $S_i = A_i \oplus B_i \oplus C_i = p_i \oplus C_i$
- Question: How can we quickly generate all the carry signals?

Prefix Adder

$$\circ C_1 = \underbrace{g_0}_{g_{0:0}} + \underbrace{p_0}_{p_{0:0}} \cdot C_0$$

$$\circ C_2 = g_1 + p_1 \cdot C_1 = \underbrace{g_1 + p_1 \cdot g_0}_{g_{1:0}} + \underbrace{p_1 \cdot p_0}_{p_{1:0}} \cdot C_0 = g_{1:0} + p_{1:0} \cdot C_0$$

$$\circ C_3 = g_2 + p_2 \cdot C_2 = \underbrace{g_2 + p_2 \cdot g_1 + p_2 \cdot p_1 \cdot g_0}_{g_{2:0}} + \underbrace{p_2 \cdot p_1 \cdot p_0}_{p_{2:0}} \cdot C_0 = g_{2:0} + p_{2:0} \cdot C_0$$

$$\circ C_4 = g_3 + p_3 \cdot C_3 = \underbrace{g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0}_{g_{3:0}} + \underbrace{p_3 \cdot p_2 \cdot p_1 \cdot p_0}_{p_{3:0}} \cdot C_0 = g_{3:0} + p_{3:0} \cdot C_0$$

○ In general

- $C_{i+1} = g_i + p_i \cdot C_i = g_{i:0} + p_{i:0} \cdot C_0$
- Thus, the question is how to generate $g_{i:0}$ and $p_{i:0}$ quickly and not with an excessive use of gates.

Prefix Adder

○ Observation

- $p_{i:0} = p_i \cdot p_{i-1} \cdot \dots \cdot p_1 \cdot p_0 = (p_i \cdot \dots \cdot p_{i-k}) \cdot (p_{i-k-1} \cdot \dots \cdot p_0) = p_{i:i-k} \cdot p_{i-k-1:0}$

- $g_{i:0} = \overbrace{g_i + (p_i \cdot g_{i-1}) + (p_i \cdot p_{i-1} \cdot g_{i-2}) + \dots + (p_i \cdot p_{i-1} \cdot \dots \cdot p_{i-k+1} \cdot g_{i-k})}^{g_{i:i-k}} + \underbrace{(p_i \cdot \dots \cdot p_{i-k} \cdot g_{i-k-1}) + (p_i \cdot \dots \cdot p_{i-k-1} \cdot g_{i-k-2}) + \dots + (p_i \cdot \dots \cdot p_0 \cdot g_0)}_{(p_i \cdot p_{i-1} \cdot \dots \cdot p_{i-k}) \cdot (g_{i-k-1} + p_{i-k-1} \cdot g_{i-k-2} + \dots + p_{i-k-1} \cdot \dots \cdot p_0 \cdot g_0)} = p_{i:i-k} \cdot g_{i-k-1:0}$

- Thus, we can break down $p_{i:0}$ and $g_{i:0}$ into two components.

- $p_{i:0} = p_{i:i-k} \cdot p_{i-k-1:0}$
- $g_{i:0} = g_{i:i-k} + p_{i:i-k} \cdot g_{i-k-1:0}$

- In general

- $p_{i:m} = p_{i:i-k} \cdot p_{i-k-1:m}$
- $g_{i:m} = g_{i:i-k} + p_{i:i-k} \cdot g_{i-k-1:m}$

Prefix Adder


- How to obtain $p_{i:m}$ and $g_{i:m}$ systematically

- $p_{i:m} = p_{i:i-k} \cdot p_{i-k-1:m}$
- $g_{i:m} = g_{i:i-k} + p_{i:i-k} \cdot g_{i-k-1:m}$

- In other words, we need

- $p_{i:i-k}$
- $g_{i:i-k}$
- $p_{i-k-1:m}$
- $g_{i-k-1:m}$


- Symbol

 

$$(g_{i:m}, p_{i:m}) = (g_{i:i-k} + p_{i:i-k} \cdot g_{i-k-1:m}, p_{i:i-k} \cdot p_{i-k-1:m})$$

Prefix Adder

○ Example

 


$$g_i = A_i \cdot B_i$$

$$p_i = A_i + B_i$$

Carry network


Prefix Adder

 - Kogge-Stone adder (min. logic depth, min. fanout, large area, high routing complexity)




Prefix Adder

 - Brent-Kung adder (max. logic depth, min. area)




Prefix Adder

 - Ladner-Fischer adder (min. logic depth, large fanout)



Prefix Adder

 - Han-Carlson adder (Brent-Kung + Kogge-Stone)



Prefix Adder

○ Delay analysis

- Generation of p_i and g_i : d
 - Merging logic \bigcirc : $2d$
 - Sum: $2d$
 - Delay: $d + k \cdot (2d) + 2d + 2d$
 - d : Generation of p_i and g_i
 - $k \cdot (2d)$: Generation of $p_{i:0}$ and $g_{i:0}$ (k : logic depth)
 - $2d$: Calculation of C_i
 - $2d$: Calculation of S_i
 - Example (16-bit adder)
 - Ripple carry: $d + 15d + 2d + 2d = 20d$
 - Kogge-Stone: $d + 4d + 2d + 2d = 9d$ (k is $\log_2 n$)
 - Brent-Kung: $d + 6d + 2d + 2d = 11d$
 - Ladner-Fischer: $d + 4d + 2d + 2d = 9d$
 - Han-Carlson: $d + 5d + 2d + 2d = 10d$
-

Carry-Lookahead Adder


- To calculate C_{i+1}
 - Use $g_{i:0}$ and $p_{i:0}$: Prefix adder
 - Use some C_k : Carry-lookahead adder
- Observation
 - $C_1 = g_0 + p_0 \cdot C_0$
 - $C_2 = g_1 + p_1 \cdot g_0 + p_1 \cdot p_0 \cdot C_0$
 - $C_3 = g_2 + p_2 \cdot g_1 + p_2 \cdot p_1 \cdot g_0 + p_2 \cdot p_1 \cdot p_0 \cdot C_0$
 - $C_4 = g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0 + p_3 \cdot p_2 \cdot p_1 \cdot p_0 \cdot C_0$

 - $C_5 = g_4 + p_4 \cdot C_4$
 - $C_6 = g_5 + p_5 \cdot g_4 + p_5 \cdot p_4 \cdot C_4$
 - $C_7 = g_6 + p_6 \cdot g_5 + p_6 \cdot p_5 \cdot g_4 + p_6 \cdot p_5 \cdot p_4 \cdot C_4$
 - $C_8 = g_7 + p_7 \cdot g_6 + p_7 \cdot p_6 \cdot g_5 + p_7 \cdot p_6 \cdot p_5 \cdot g_4 + p_7 \cdot p_6 \cdot p_5 \cdot p_4 \cdot C_4$

 - ...


Carry-Lookahead Adder

- A 4-bit carry lookahead logic

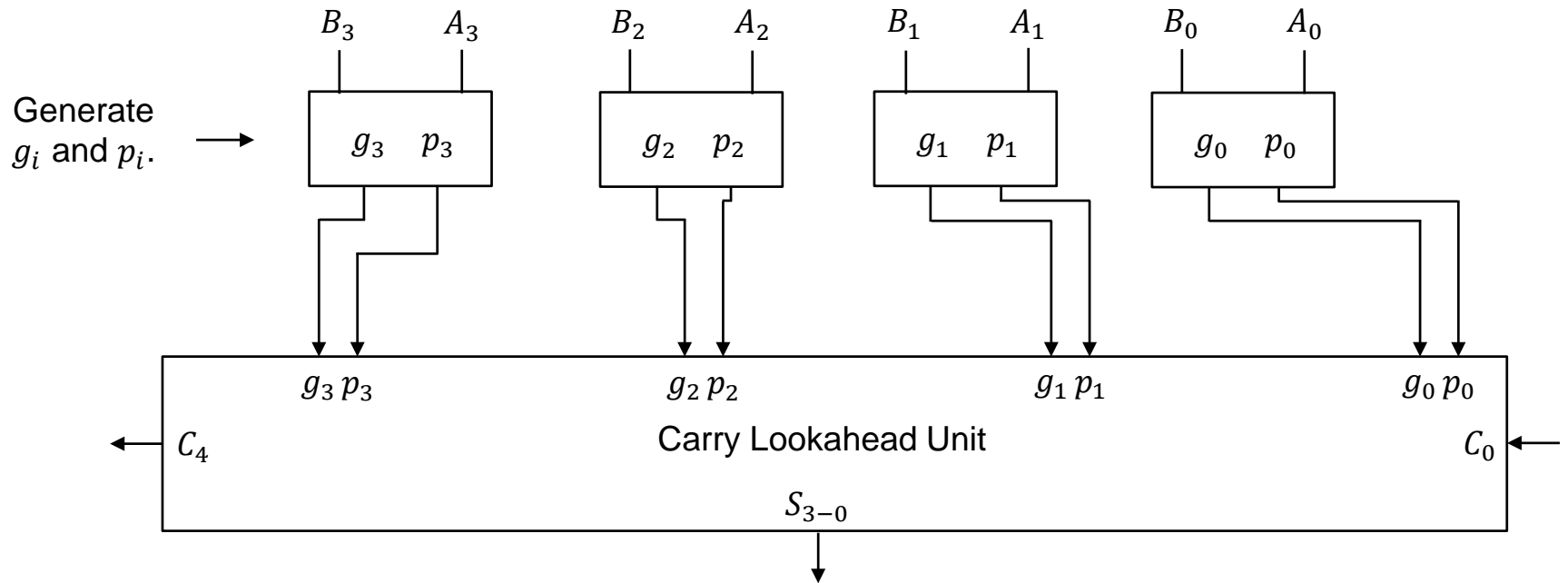

Carry-Lookahead Adder

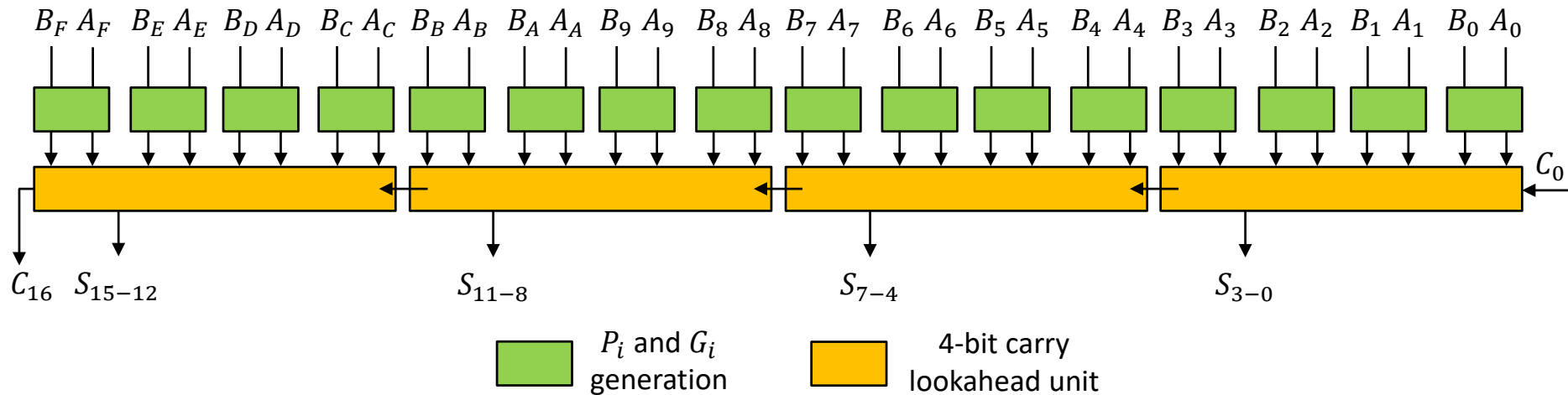- A **one-level** 16-bit carry lookahead adder




- How to compute C_i

- $C_4 = g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0 + p_3 \cdot p_2 \cdot p_1 \cdot p_0 \cdot C_0$
- $C_5 = g_4 + p_4 \cdot C_4$
- $C_8 = g_7 + p_7 \cdot g_6 + p_7 \cdot p_6 \cdot g_5 + p_7 \cdot p_6 \cdot p_5 \cdot g_4 + p_7 \cdot p_6 \cdot p_5 \cdot p_4 \cdot C_4$
- $C_9 = g_8 + p_8 \cdot C_8$
- $C_{16} = g_{15} + p_{15} \cdot g_{14} + p_{15} \cdot p_{14} \cdot g_{13} + p_{15} \cdot p_{14} \cdot p_{13} \cdot g_{12} + p_{15} \cdot p_{14} \cdot p_{13} \cdot p_{12} \cdot C_{12}$

Carry-Lookahead Adder

○ Two-level carry lookahead adder

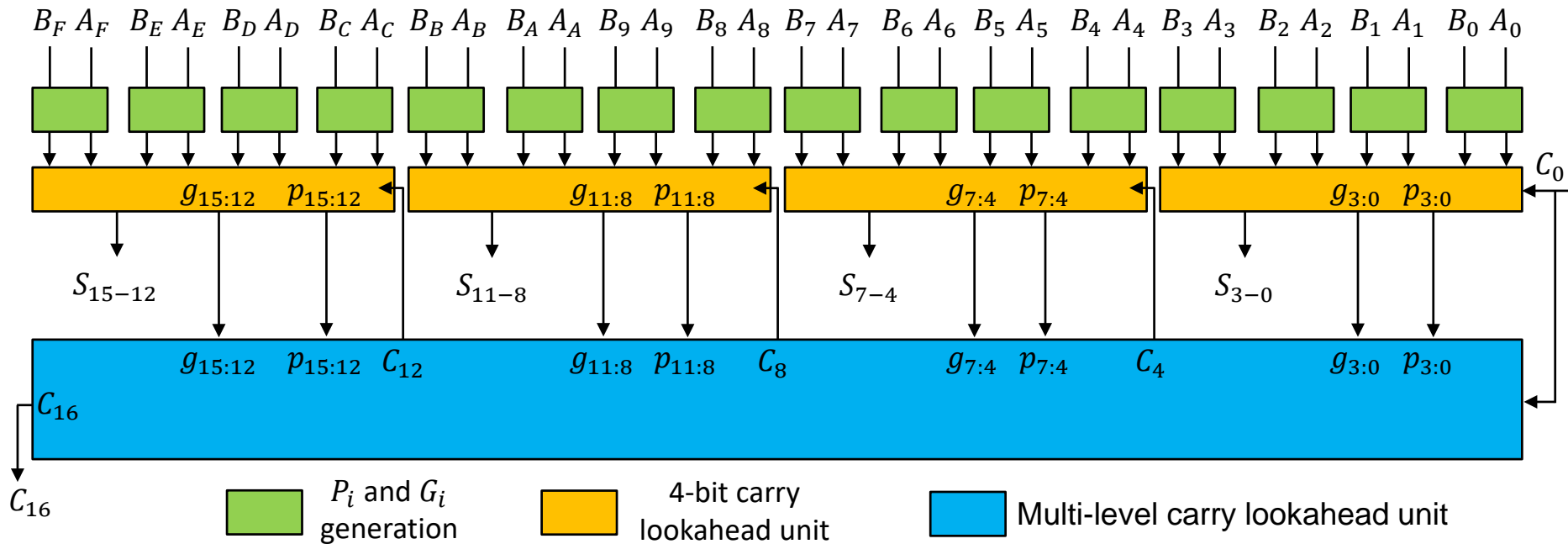



○ How to generate C_i

- $C_4 = g_{3:0} + p_{3:0} \cdot C_0$
- $C_8 = g_{7:4} + p_{7:4} \cdot g_{3:0} + p_{7:4} \cdot p_{3:0} \cdot C_0$

Carry-Lookahead Adder

○ How to generate C_i in 2-level CLA


- $C_1 = g_0 + p_0 \cdot C_0$
 - $C_2 = g_1 + p_1 \cdot g_0 + p_1 \cdot p_0 \cdot C_0$
 - $C_3 = g_2 + p_2 \cdot g_1 + p_2 \cdot p_1 \cdot g_0 + p_2 \cdot p_1 \cdot p_0 \cdot C_0$
 - $C_4 = g_{3:0} + p_{3:0} \cdot C_0$  In the 2-level carry lookahead unit
- } In the 1-level carry lookahead unit

- $C_5 = g_4 + p_4 \cdot C_4$
 - $C_6 = g_5 + p_5 \cdot g_4 + p_5 \cdot p_4 \cdot C_4$
 - $C_7 = g_6 + p_6 \cdot g_5 + p_6 \cdot p_5 \cdot g_4 + p_6 \cdot p_5 \cdot p_4 \cdot C_4$
 - $C_8 = g_{7:4} + p_{7:4} \cdot g_{3:0} + p_{7:4} \cdot p_{3:0} \cdot C_0$  In the 2-level carry lookahead unit
- } In the 1-level carry lookahead unit

- $C_9 = g_8 + p_8 \cdot C_8$
- $C_{10} = g_9 + p_9 \cdot g_8 + p_9 \cdot p_8 \cdot C_8$
- $C_{11} = g_{10} + p_{10} \cdot g_9 + p_{10} \cdot p_9 \cdot g_8 + p_{10} \cdot p_9 \cdot p_8 \cdot C_8$
- $C_{12} = g_{11:8} + p_{11:8} \cdot g_{7:4} + p_{11:8} \cdot p_{7:4} \cdot g_{3:0} + p_{11:8} \cdot p_{7:4} \cdot p_{3:0} \cdot C_0$
- $C_{16} = g_{15:12} + p_{15:12} \cdot g_{11:8} + p_{15:12} \cdot p_{11:8} \cdot g_{7:4} + p_{15:12} \cdot p_{11:8} \cdot p_{7:4} \cdot g_{3:0} + p_{15:12} \cdot p_{11:8} \cdot p_{7:4} \cdot p_{3:0} \cdot C_0$
 - Notice that C_{16} should be generated by a 3-level carry lookahead unit.

Carry-Lookahead Adder

64-bit CLA

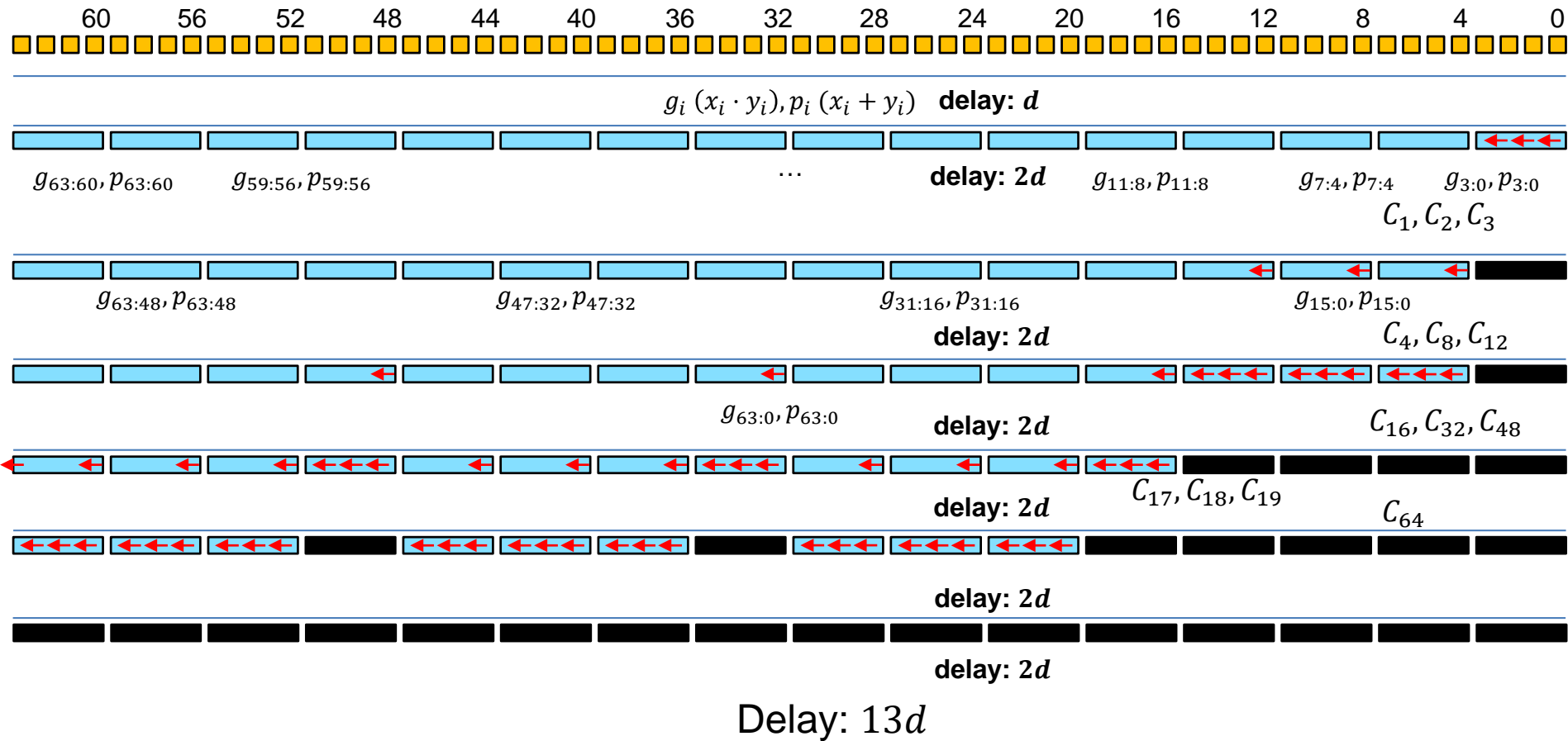

Carry-Lookahead Adder

- Example: How is S_{53} is calculated and what is the delay of the calculation?
 - Sum
 - $S_{53} = p_{53} \oplus C_{53}$ (C_{53} is the delay bottleneck)
 - Calculate the group that C_{53} belongs to.
 - $53 \bmod 4 = 1$
 - Represent C_{53} w.r.t. the incoming carry C_{52} in the group
 - $C_{53} = g_{52} + p_{52} \cdot C_{52}$ (level 1)
 - Calculate the logic that generates C_{52}
 - $52/16 = 3.\text{xxx}$
 - $C_{52} = g_{51:48} + p_{51:48} \cdot C_{48}$ (level 2)
 - Calculate the logic that generates C_{48}
 - $48/64 = 0.\text{xxx}$
 - $C_{48} = g_{47:32} + p_{47:32} \cdot g_{31:16} + p_{47:32} \cdot p_{31:16} \cdot g_{15:0} + p_{47:32} \cdot p_{31:16} \cdot p_{15:0} \cdot C_0$ (level 3)
 - Calculation of $g_{i:i-15}$ (or $p_{i:i-15}$)
 - $g_{15:0} = g_{15:12} + p_{15:12} \cdot g_{11:8} + p_{15:12} \cdot p_{11:8} \cdot g_{7:4} + p_{15:12} \cdot p_{11:8} \cdot p_{7:4} \cdot g_{3:0}$
 - Calculation of $g_{i:i-3}$
 - $g_{3:0} = g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0$
 - Calculation of g_i
 - $g_0 = A_0 \cdot B_0$
 - Delay calculation (backtrace)
 - $d + 2d + 2d + 2d + 2d + 2d + 2d = 13d$

Carry-Lookahead Adder

- Example: How is S_{64} is calculated and what is the delay of the calculation?
 - Sum
 - $S_{64} = p_{64} \oplus C_{64}$ (C_{64} is the delay bottleneck)
 - Calculate the group that C_{64} belongs to.
 - $64 \bmod 4 = 0$
 - $64 \bmod 16 = 0$
 - $64 \bmod 64 = 0$ (this means C_{64} is calculated in the level-3 carry lookahead unit)
 - Represent C_{64} w.r.t. the incoming carry C_0 in the group
 - $C_{64} = g_{63:0} + p_{63:0} \cdot C_0$ (level 3)
 - Calculation of $g_{i:i-63}$ (or $p_{i:i-63}$)
 - $g_{63:0} = g_{63:48} + p_{63:48} \cdot g_{47:32} + p_{63:48} \cdot p_{47:32} \cdot g_{31:0} + p_{63:48} \cdot p_{47:32} \cdot p_{31:16} \cdot g_{15:0}$
 - Calculation of $g_{i:i-15}$ (or $p_{i:i-15}$)
 - $g_{15:0} = g_{15:12} + p_{15:12} \cdot g_{11:8} + p_{15:12} \cdot p_{11:8} \cdot g_{7:4} + p_{15:12} \cdot p_{11:8} \cdot p_{7:4} \cdot g_{3:0}$
 - Calculation of $g_{i:i-3}$
 - $g_{3:0} = g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0$
 - Calculation of g_i
 - $g_0 = A_0 \cdot B_0$
 - Delay calculation (backtrace)
 - $d + 2d + 2d + 2d + 2d + 2d = 11d$