

---

# **Arithmetic Circuits**

**High-Speed Multipliers**

Dae Hyun Kim

EECS  
Washington State University

---

# Multiplication

---

- We will use the unsigned binary number system.
  - (Signed multiplication is similar to unsigned multiplication.)
- Example

$$\begin{array}{r} 10101111 \\ \times 11010111 \\ \hline 10101111 \\ 10101111 \\ 10101111 \\ 00000000 \\ 10101111 \\ 00000000 \\ 10101111 \\ \hline 100100101111001 \end{array}$$

# Theory

---

- Suppose we multiply two  $n$ -bit unsigned binary numbers,  $A$  and  $B$ .
- How many bits do we need to represent the result?
  - $A, B: [0, 2^n - 1]$
  - $M = A * B: [0, 2^{2n} - 2^{n+1} + 1]$ 
    - The max. value that can be represented by  $2n - 1$  bits:  $2^{2n-1} - 1$
    - $(2^{2n} - 2^{n+1} + 1) - (2^{2n-1} - 1) = 2^{2n-1} - 2^{n+1} + 2 > 0$
    - The max. value that can be represented by  $2n$  bits:  $2^{2n} - 1$
    - $(2^{2n} - 2^{n+1} + 1) - (2^{2n} - 1) = -2^{n+1} + 2 < 0$
  - Therefore, we need  $2n$  bits to represent  $A * B$ .

# What to Calculate to Obtain $A * B$

---

- Add the partial products.

$$\begin{array}{r} 10101111 \quad A \\ \times 11010111 \quad B \\ \hline 10101111 \\ 10101111 \\ 10101111 \\ 00000000 \\ 10101111 \\ 00000000 \\ 10101111 \\ \hline 10101111 \end{array}$$

Partial product ( $A * B_0$ )  
Partial product ( $A * B_1$ )  
  
Partial product ( $A * B_{n-1}$ )

---

- How many partial products do we add?

- $n$

# Sequential Addition


---

- Add  $A * B_0$  and  $A * B_1$ 
  - $PS_{1:0} = A * B_0 + A * B_1$
- Then, add  $PS_{1:0}$  and  $A * B_2$ 
  - $PS_{2:0} = PS_{1:0} + A * B_2$
- ...
- Add  $PS_{n-2:0}$  and  $A * B_{n-1}$ :  $PS_{n-1:0}$ 
  - How many adders do we need: 1
  - Delay:  $(n - 1) \cdot d_A$  where  $d_A$  is the delay of an  $(n + 1)$ -bit adder.
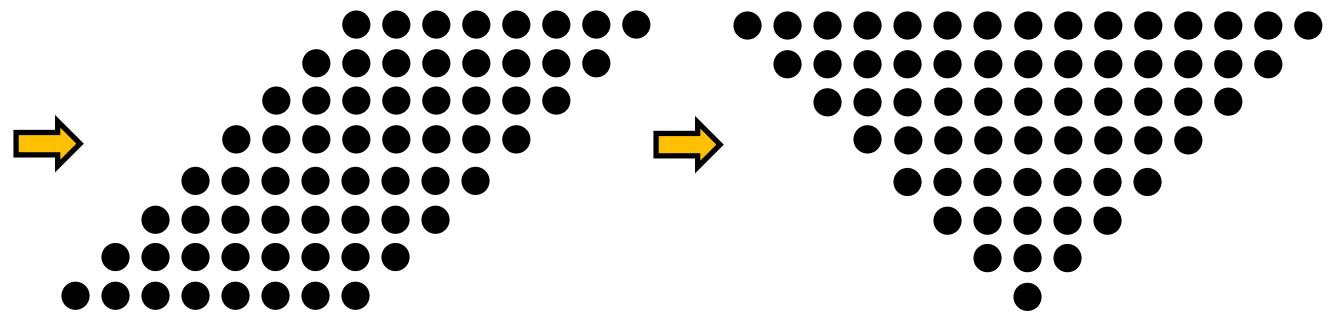
# Parallel Addition


- Add all the bits

$$\begin{array}{r} 10101111 \\ \times 11010111 \\ \hline 10101111 \\ 10101111 \\ 10101111 \\ 00000000 \\ 10101111 \\ 00000000 \\ 10101111 \\ 10101111 \\ \hline 1001001011111001 \end{array}$$



# Parallel Addition


- Use HAs and FAs

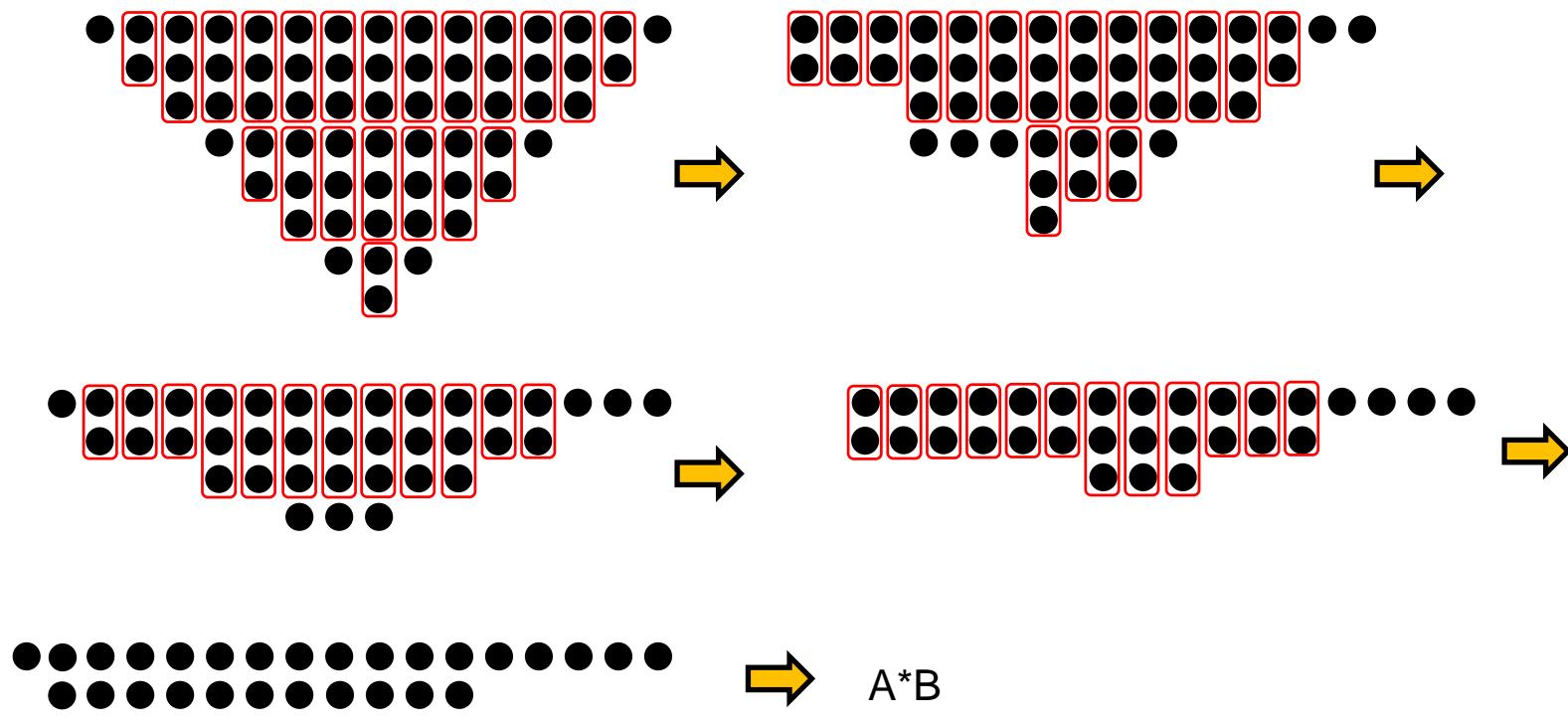

Carry-propagation adder (CPA)
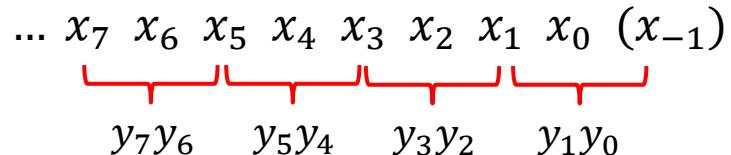
# Modified Booth Encoding

- How to reduce # partial products (for  $A^*X$ )



$x_i$	$x_{i-1}$	$x_{i-2}$	$y_i$	$y_{i-1}$	Operation	Comments
0	0	0	0	0	+0	string of zeros
0	1	0	0	1	+A	a single 1
1	0	0	$\bar{1}$	0	-2A	beginning of 1's
1	1	0	0	$\bar{1}$	-A	beginning of 1's
0	0	1	0	1	+A	end of 1's
0	1	1	1	0	+2A	end of 1's
1	0	1	0	$\bar{1}$	-A	a single 0
1	1	1	0	0	+0	string of 1's

# Modified Booth Encoding

- Example

$$\begin{array}{r} A \quad 01101101 \\ *X \quad 00101011(0) \\ \hline A \quad 01101101 \\ *Y \quad 0101'01'01' \\ \hline & -A \\ & -A \\ & +A \\ \hline & -01101101 \\ & -01101101 \\ & +01101101 \\ \hline \end{array}$$

$x_i$	$x_{i-1}$	$x_{i-2}$	$y_i$	$y_{i-1}$	Operation
0	0	0	0	0	+0
0	1	0	0	1	+A
1	0	0	1	0	-2A
1	1	0	0	1	-A
0	0	1	0	1	+A
0	1	1	1	0	+2A
1	0	1	0	1	-A
1	1	1	0	0	+0