



Logic Design with MOSFETs

Dae Hyun Kim

EECS

Washington State University

References


- John P. Uyemura, “Introduction to VLSI Circuits and Systems,” 2002.
 - Chapter 2
- Neil H. Weste and David M. Harris, “CMOS VLSI Design: A Circuits and Systems Perspective,” 2011.
 - Chapter 1

Goal


- Design logic gates using MOSFETs (NMOS and PMOS)

Signals and Wires

 
- Signals
 - $0 = V_{SS} = \text{Ground} = \text{GND} = \text{Low} = 0\text{V}$
 - $1 = V_{DD} = \text{Power} = \text{PWR} = \text{High} = 5\text{V}, 3.3\text{V}, 1.5\text{V}, 1.2\text{V}, 1.0\text{V}, \text{etc.}$



- Wires

 



No connection

 



Connection

Ideal Switches



- Switch

  

- Assert-high switch

  


- Assert-low switch

  

Series/Parallel Connections of Switches

- Series

 


AND operation

(y is defined only when $a = 1$ and $b = 1$)

(y is undefined if $a = 0$ or $b = 0$)

a	b	y
0	0	undefined
0	1	
1	0	x
1	1	

- Parallel

 

OR operation

(y is defined only when $a = 1$ or $b = 1$)


(y is undefined if $a = 0$ and $b = 0$)

a	b	y
0	0	undefined
0	1	x
1	0	
1	1	

Inverter Design with Switches



- Inverter
 - The output is defined both when $a = 0$ and when $a = 1$.

a	y
0	1
1	0

 

Inverter Design with Switches

- Two inverter designs

 
 


Why?



MOSFETs as Switches

- MOSFET: Metal-Oxide-Semiconductor Field-Effect Transistor
 - n-channel MOSFET = nFET = NMOS
 - p-channel MOSFET = pFET = PMOS
 - Complementary MOS: CMOS

- Symbols

  

$$(V_D \geq V_S)$$

  

$$(V_S \geq V_D)$$

MOSFETs as Switches

- Threshold voltage



- nFET: $V_{Tn} > 0$

- pFET: $V_{Tp} < 0$

- nFET

- OFF: $V_{GSn} \leq V_{Tn}$

- ON: $V_{GSn} > V_{Tn}$

 
 


Logic translation

- pFET

- OFF: $V_{SGp} \leq |V_{Tp}|$

- ON: $V_{SGp} > |V_{Tp}|$

  


Logic translation

MOSFETs as Switches

- Example (PTM High-Performance 45nm High-K Metal Gate)
 - V_{DD} : 1.0V
 - V_{T_n} : 0.46893V
 - V_{T_p} : -0.49158V
- Example (PTM High-Performance 32nm High-K Metal Gate)
 - V_{DD} : 0.9V
 - V_{T_n} : 0.49396V
 - V_{T_p} : -0.49155V
- Example (PTM High-Performance 22nm High-K Metal Gate)
 - V_{DD} : 0.8V
 - V_{T_n} : 0.50308V
 - V_{T_p} : -0.4606V

Pass Characteristics

- nFET

 


$V_{in} \uparrow$	$V_{GS} \downarrow$	$V_{out} \uparrow$
0	V_{DD}	0
0.1	$V_{DD} - 0.1$	0.1
...
$V_{DD} - V_{Tn}$	V_{Tn}	$V_{DD} - V_{Tn}$
V_{DD}	V_{Tn}	$V_{DD} - V_{Tn}$

Logic 0 transfer: **strong logic 0**

Logic 1 transfer: **weak logic 1**

- pFET

 



$V_{in} \downarrow$	$V_{SG} \downarrow$	$V_{out} \downarrow$
V_{DD}	V_{DD}	V_{DD}
$V_{DD} - \varepsilon$	$V_{DD} - \varepsilon$	$V_{DD} - \varepsilon$
...
$ V_{Tp} $	$ V_{Tp} $	$ V_{Tp} $
0	0	$ V_{Tp} $

Logic 1 transfer: **strong logic 1**

Logic 0 transfer: **weak logic 0**



Pass Characteristics

  - SPICE simulation (45nm technology)
 - nFET



Pass Characteristics

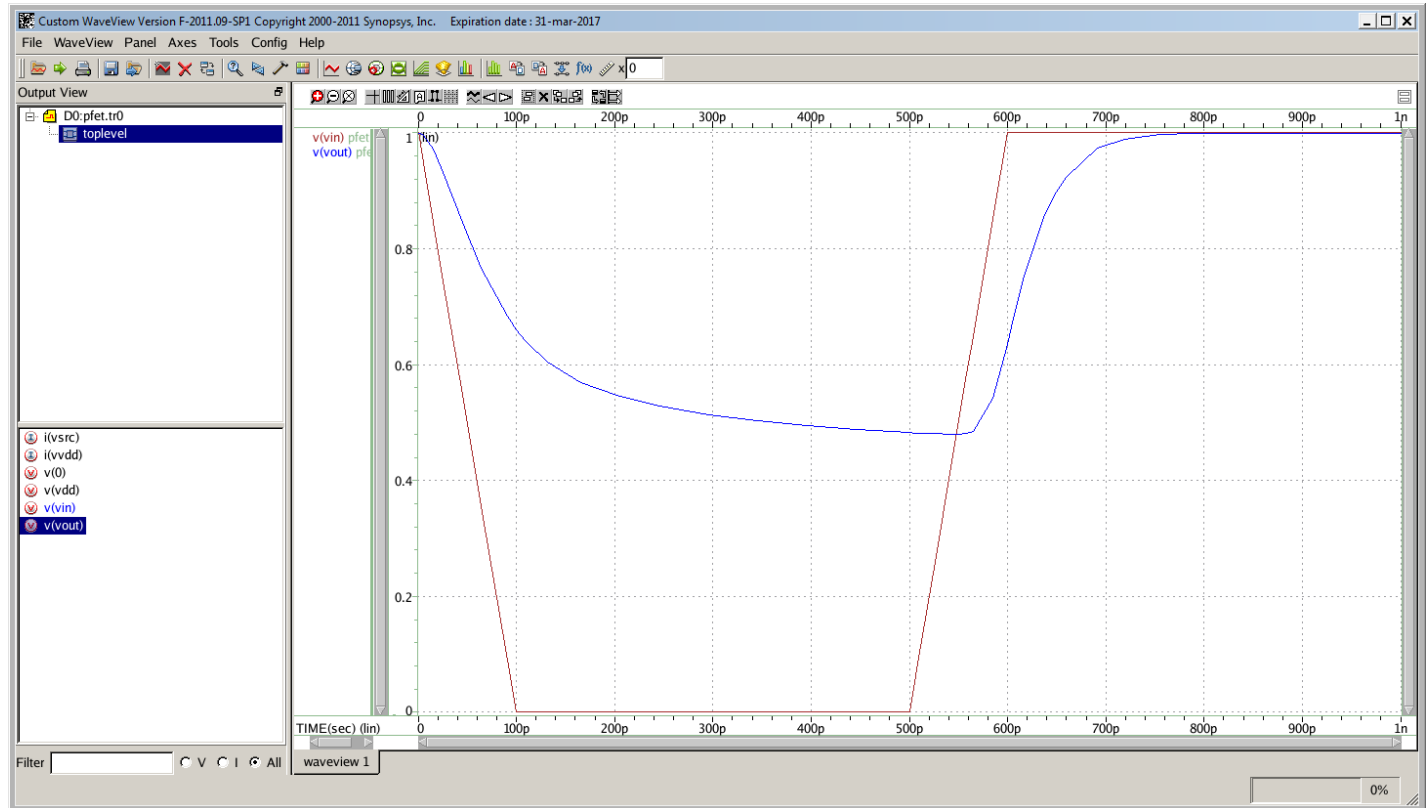 - SPICE simulation (45nm technology)
 - pFET




Pass Characteristics

- nFET
 - **Strong logic 0** transfer
 - Weak logic 1 transfer
- pFET
 - **Strong logic 1** transfer
 - Weak logic 0 transfer
- CMOS
 - Use pFETs to pass logic 1.
 - Use nFETs to pass logic 0.


Basic Logic Gates in CMOS

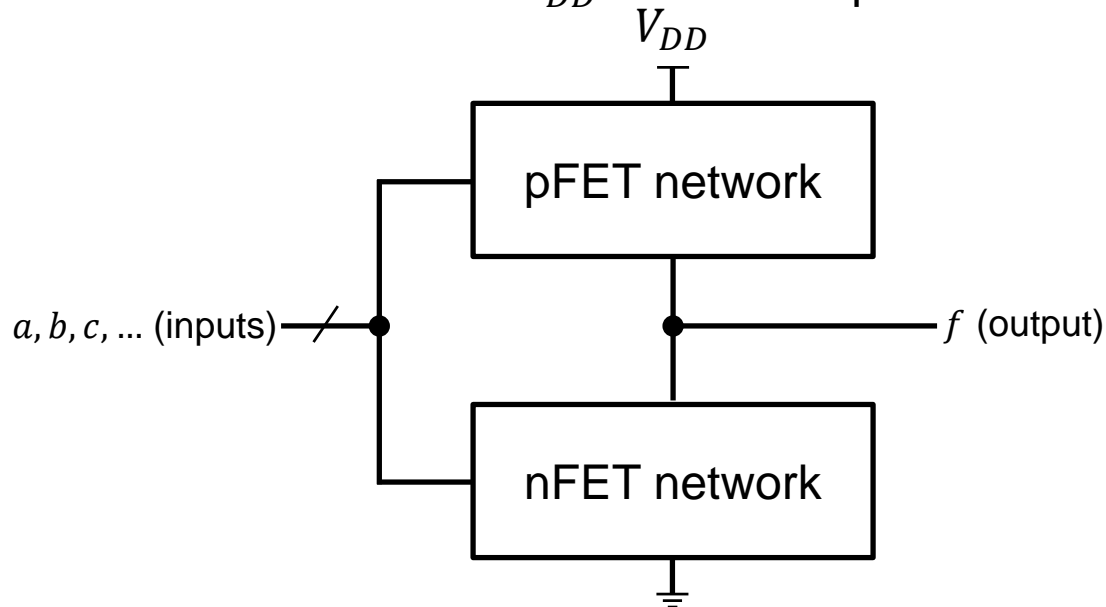- Principles
 - Construct the nFET network using only nFETs and the pFET network using only pFETs.
 - If the output is 1, the pFET network connects V_{DD} to the output and the nFET network disconnects V_{SS} and the output.
 - If the output is 0, the nFET network connects V_{SS} to the output and the pFET network disconnects V_{DD} and the output.




Basic Logic Gates in CMOS

- Inverter

 


TRs: 2
nFET: 1
pFET: 1

 

$$f = \bar{x} \cdot 1 + x \cdot 0 = \bar{x}$$


Basic Logic Gates in CMOS

- SPICE simulation



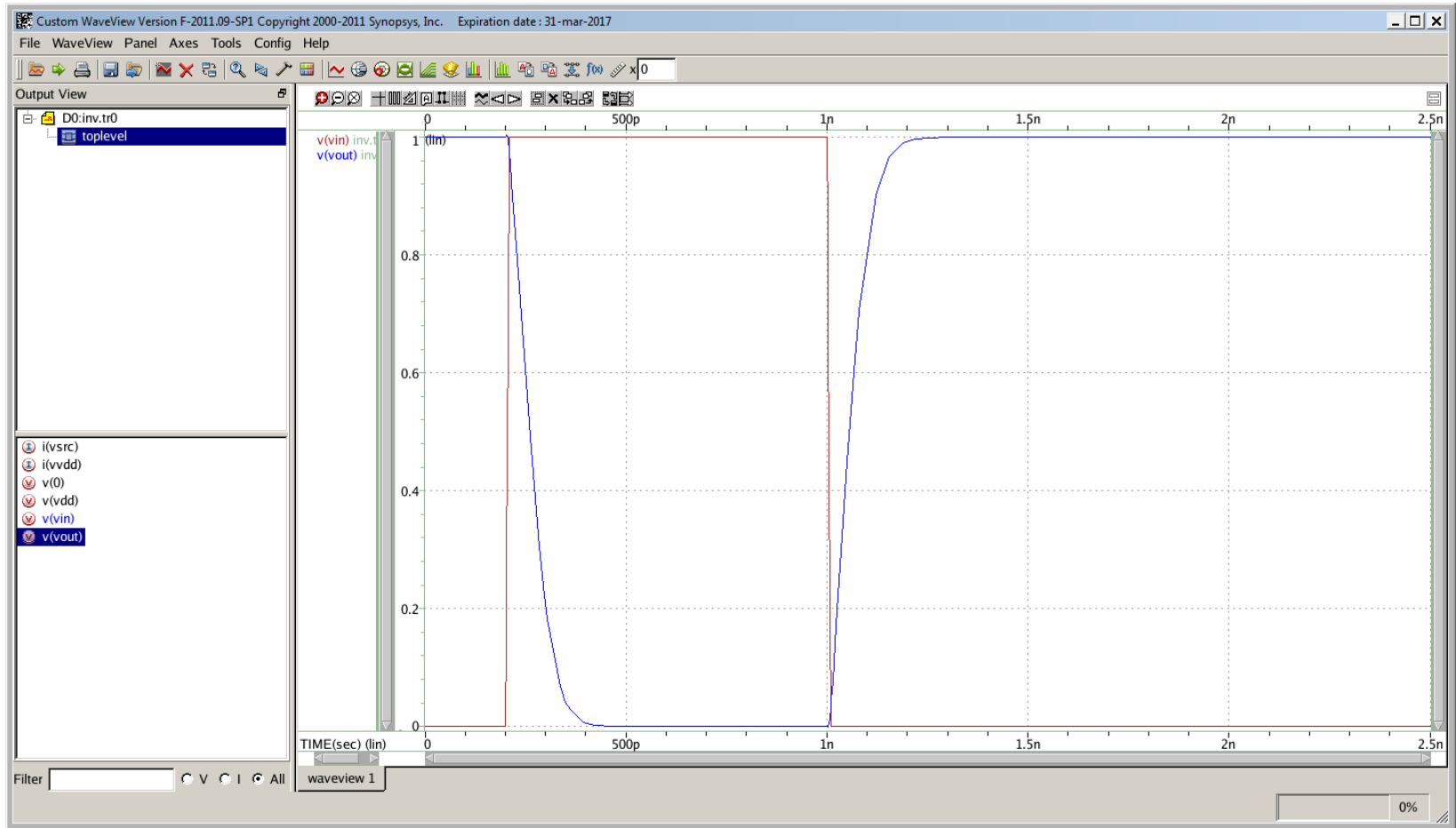


Basic Logic Gates in CMOS

- Two-input NAND (NAND2)

 


TRs: 4
nFETs: 2
pFETs: 2

   

$$f = \bar{a} \cdot \bar{b} \cdot 1 + \bar{a} \cdot b \cdot 1 + a \cdot \bar{b} \cdot 1 + a \cdot b \cdot 0 = \bar{a} + \bar{b} = \overline{a \cdot b}$$


Basic Logic Gates in CMOS

- SPICE simulation



 


Basic Logic Gates in CMOS

- Two-input NOR (NOR2)

 


TRs: 4
nFETs: 2
pFETs: 2

   

$$f = \bar{a} \cdot \bar{b} \cdot 1 + \bar{a} \cdot b \cdot 0 + a \cdot \bar{b} \cdot 0 + a \cdot b \cdot 0 = \bar{a} \cdot \bar{b} = \overline{a + b}$$

Basic Logic Gates in CMOS

- SPICE simulation

 


Complex Logic Gates in CMOS

- Example


$$f = \overline{a \cdot (b + c)}$$

- Using logic gates

 

TRs: 14
nFETs: 7
pFETs: 7

- Using logic gates

 

TRs: 10
nFETs: 5
pFETs: 5

- Using TRs

TRs: 6
nFETs: 3
pFETs: 3

Complex Logic Gates in CMOS


- How to design

- Inverter

$$f = \bar{x} = \boxed{\bar{x}} \cdot 1 + \boxed{x} \cdot 0$$

pFET network
(connects 1 and the output)

nFET network
(connects 0 and the output)

 


- NAND2

$$f = \overline{a \cdot b} = (\overline{a \cdot b}) \cdot 1 + (a \cdot b) \cdot 0 = \boxed{(\bar{a} + \bar{b})} \cdot 1 + \boxed{(a \cdot b)} \cdot 0$$

pFET network
(expressed by $\bar{a} + \bar{b}$)

nFET network
(expressed by $a \cdot b$)

 



Complex Logic Gates in CMOS

- How to design f
 - Express $f = A \cdot 1 + B \cdot 0 = F(\overline{x_1}, \dots, \overline{x_n}) \cdot 1 + \overline{F(x_1, \dots, x_n)} \cdot 0$
 - Design a pFET network using $A = F(\overline{x_1}, \dots, \overline{x_n})$.
 - pFETs are ON when the inputs are 0.
 - Design an nFET network using $B = \overline{F(x_1, \dots, x_n)}$.
 - nFETs are ON when the inputs are 1.

  - Example

$$f = \overline{a \cdot (b + c)}$$


$$- f = \overline{a \cdot (b + c)} \cdot 1 + a \cdot (b + c) \cdot 0 = \underbrace{(\overline{a} + \overline{b} \cdot \overline{c})}_{\text{pFET network}} \cdot 1 + \underbrace{a \cdot (b + c)}_{\text{nFET network}} \cdot 0$$



Complex Logic Gates in CMOS

- Example

$$f = \overline{a \cdot (b + c)}$$

 




TRs: 6
nFETs: 3
pFETs: 3

Complex Logic Gates in CMOS

- Structured logic design
 - Design a given Boolean equation using nFETs and pFETs.
- Assume that only non-inverted input signals are given.
 - a, b, c, \dots are given.
 - $\bar{a}, \bar{b}, \bar{c}, \dots$ are not given. If you need them, you should generate them.

Complex Logic Gates in CMOS

- Design methodology 1
 - When $f = \overline{S(x_1, \dots, x_n)}$ (S is a function of non-inverted variables)
 - $f = \bar{S} = \bar{S} \cdot 1 + S \cdot 0$
 - Design an nFET network for S using x_1, \dots, x_n .
 - Design a pFET network for \bar{S} using $\bar{x}_1, \dots, \bar{x}_n$.
 - Connect them to V_{DD}, V_{SS}, f .
 - Example: $f = \overline{a \cdot (b + c)}$
 - $f = \overline{a \cdot (b + c)} \cdot 1 + a \cdot (b + c) \cdot 0$
 - Design an nFET network for $a \cdot (b + c)$.
 - Design a pFET network for $\overline{a \cdot (b + c)} = \bar{a} + \bar{b} \cdot \bar{c}$.
 - Connect them.

   

Complex Logic Gates in CMOS

- Design methodology 2

- When $f = \overline{S(x_1, \dots, x_n)}$

- $f = \bar{S} = \bar{S} \cdot 1 + S \cdot 0$

- Design an nFET network for S .

- Design a pFET network with a dual logic of the nFET network.

- Dual of $f(x_1, \dots, x_n, 0, 1, AND, OR) = f(x_1, \dots, x_n, 1, 0, OR, AND)$

- Connect them.




- Example: $f = \overline{a \cdot (b + c)}$

- $f = \overline{a \cdot (b + c)} \cdot 1 + a \cdot (b + c) \cdot 0$

- Design an nFET network for $a \cdot (b + c)$.

- Dual of $a \cdot (b + c) = a + (b \cdot c) = a + b \cdot c$.

- Connect them.

   

Complex Logic Gates in CMOS

- Dual logic

- $f(x_1, \dots, x_n, 0, 1, AND, OR)^D = f(x_1, \dots, x_n, 1, 0, OR, AND)$

- Example

- $(A \cdot B)^D = A + B$

- $(A + B)^D = A \cdot B$

- $(1 \cdot A)^D = 0 + A = A$

- $(1 + A)^D = 0 \cdot A = 0$

- $(0 \cdot A)^D = 1 + A = 1$

- $(0 + A)^D = 1 \cdot A = A$

- Principles of the dual logic

- The nFET and the pFET networks work complementarily.

- If the nFET network is ON (i.e., connects V_{SS} to the output), the pFET network is OFF (i.e., disconnect the output from V_{DD}) and vice versa.

- If two networks are dual, they work complementarily.

- Prove!

Complex Logic Gates in CMOS

- Principles of the dual logic

- $f = \overline{S(x_1, \dots, x_n)} = f = \overline{S(x_1, \dots, x_n)} \cdot 1 + S(x_1, \dots, x_n) \cdot 0$


- $\overline{S(x_1, \dots, x_n)} = \overline{S(x_1, \dots, x_n, 0, 1, AND, OR)} = S(\overline{x_1}, \dots, \overline{x_n}, 1, 0, OR, AND) = S(\overline{x_1}, \dots, \overline{x_n})^D$ (De Morgan's law)

- A pFET is ON when its control variable (x_i) is 0.

- Thus, the pFET network is the dual of the nFET network.


Complex Logic Gates in CMOS

 - Design methodology 3
 - When $f = S(x_1, \dots, x_n)$ (S is a function of non-inverted variables)
 - $f = S = \bar{\bar{S}}$
 - Design \bar{S} and add an inverter at the output.
 - Example: $f = a \cdot (b + c)$
 - $f = a \cdot (b + c) = \overline{\overline{a \cdot (b + c)}}$
 - Design $\overline{a \cdot (b + c)}$.
 - Add an inverter at the output.




Complex Logic Gates in CMOS

 - Design methodology 4
 - When $f = \overline{S(\overline{x_1}, \dots, \overline{x_n})}$ (S is a function of inverted variables)
 - Generate inverted inputs ($\overline{x_1}, \dots, \overline{x_n}$) from the given inputs (x_1, \dots, x_n).
 - Design S using the inverted inputs.
 - Example: $f = \overline{\overline{a} \cdot (\overline{b} + \overline{c})}$
 - Inverters are not shown for brevity.



Complex Logic Gates in CMOS

- Design methodology 5
 - When $f = \overline{S(\overline{x_1}, \dots, \overline{x_n})}$
 - $f = \overline{S(\overline{x_1}, \dots, \overline{x_n})} = S(x_1, \dots, x_n)^D = \overline{\overline{S(x_1, \dots, x_n)^D}}$
 - Design $\overline{S(x_1, \dots, x_n)^D}$ using the given inputs.
 - Add an inverter at the output.
 - Example: $f = \overline{\overline{a} + (\overline{b} \cdot \overline{c})}$
 - $f = a \cdot (b + c) = \overline{\overline{a \cdot (b + c)}}$

 

Complex Logic Gates in CMOS

- Design methodology 6
 - When $f = S(\overline{x_1}, \dots, \overline{x_n})$
 - $f = S = \overline{\overline{S}}$
 - Generate inverted inputs $(\overline{x_1}, \dots, \overline{x_n})$ from the given inputs (x_1, \dots, x_n) .
 - Design \overline{S} using the inverted inputs and add an inverter at the output.
- Design methodology 7
 - When $f = S(\overline{x_1}, \dots, \overline{x_n})$
 - $f = \overline{\overline{S(\overline{x_1}, \dots, \overline{x_n})}} = \overline{S(x_1, \dots, x_n)^D}$
 - Design S^D using the given non-inverted inputs (x_1, \dots, x_n) .
- Design methodology 8
 - When $f = S(x_1, \overline{x_1}, \dots, \overline{x_n})$ or $\overline{\overline{S(x_1, \overline{x_1}, \dots, \overline{x_n})}}$
 - Convert the given function into an appropriate form to simplify the logic.
 - Design it.



Complex Logic Gates in CMOS

- Examples (assuming only non-inverted inputs are available)
 - $f = a \cdot b$ (AND2)
 - Design $f = \overline{a \cdot b}$ and add an inverter at the output. (# TRs: 6)
 - Design $f = \overline{\overline{a \cdot b}} = \overline{\overline{a} + \overline{b}}$ with two inverters to generate \overline{a} and \overline{b} . (# TRs: 8)
 - $f = \overline{\overline{a \cdot b + c \cdot d}}$
 - Add two inverters to generate \overline{a} and \overline{c} , then design f . (# TRs: 12)
 - $f = \overline{s} \cdot a + s \cdot b$ (2:1 MUX)



Complex Logic Gates in CMOS

- Bubble pushing (how to construct a pFET network)
 - $f = A \cdot 1 + B \cdot 0 = F(\overline{x_1}, \dots, \overline{x_n}) \cdot 1 + F(x_1, \dots, x_n)^D \cdot 0$



$$f = a \cdot b \cdot 0$$

  


$$f = (a + b) \cdot 0$$

  

$$f = \bar{a} \cdot \bar{b} \cdot 1$$

  


$$f = (\bar{a} + \bar{b}) \cdot 1$$

 

Complex Logic Gates in CMOS

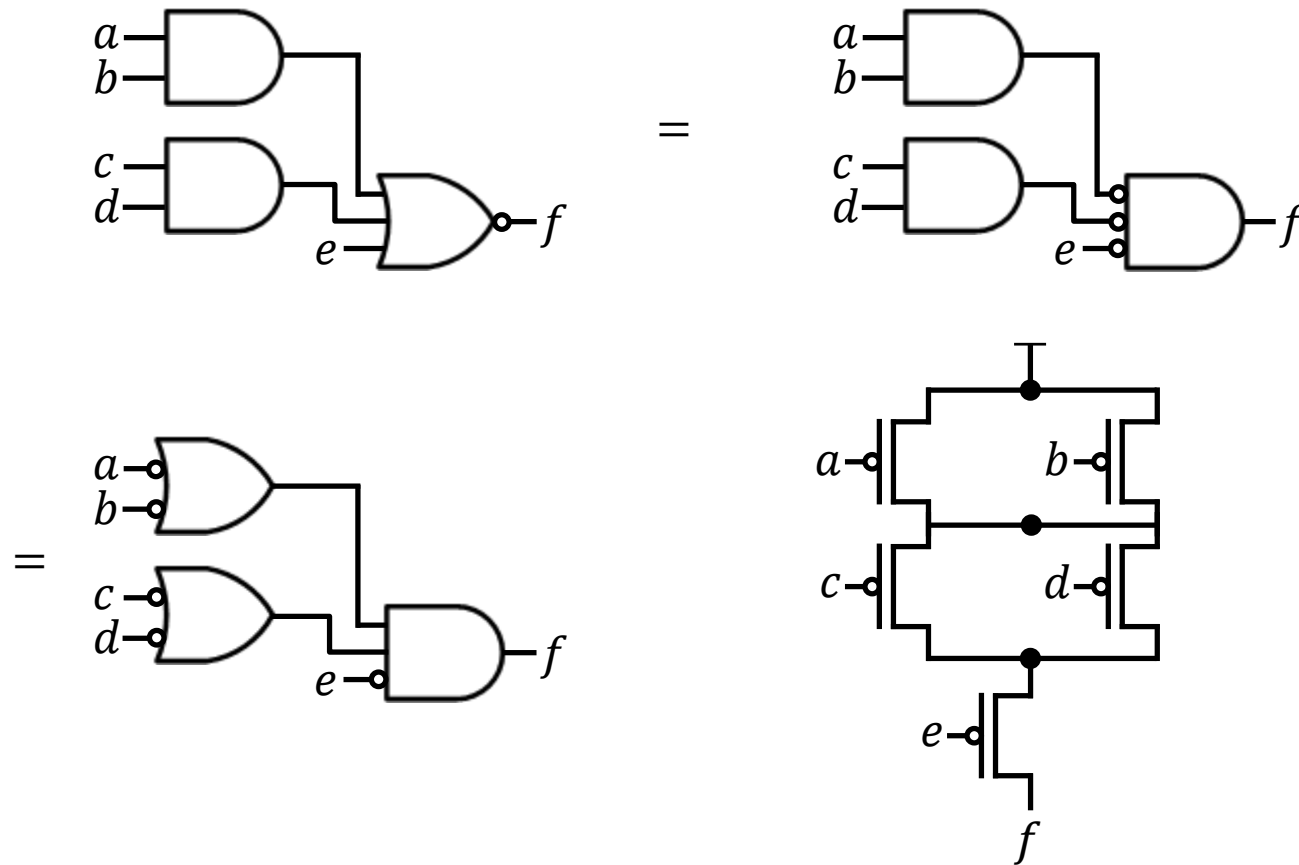- Bubble pushing (how to construct a pFET network)
 - Example





Complex Logic Gates in CMOS

- XOR

- $a \oplus b = a \cdot \bar{b} + \bar{a} \cdot b = \overline{a \cdot b + \bar{a} \cdot \bar{b}}$ (#TRs: 8+4(for the two inverters))

- XNOR

  - $\overline{a \oplus b} = a \cdot b + \bar{a} \cdot \bar{b} = \overline{a \cdot \bar{b} + \bar{a} \cdot b}$ (#TRs: 8+4(for the two inverters))




Complex Logic Gates in CMOS

- Structured logic analysis
 - Derive a Boolean equation for a given transistor-level schematic.
- Analysis methodology 1
 - Convert the nFET network into a Boolean equation (only when the pFET network is the dual of the nFET network.)
 - Notice that the nFET network passes logic 0.

 
- Example

- $f = \overline{a \cdot b + \bar{a} \cdot \bar{b}} = (\bar{a} + \bar{b}) \cdot (a + b) = a \cdot \bar{b} + \bar{a} \cdot b$



Complex Logic Gates in CMOS

 
- Analysis methodology 2
 - Identify all the paths from V_{SS} to the output (only when the pFET network is the dual of the nFET network.)
 - Merge them into a single Boolean equation.
 - Negate the output.
- Example
 - Path 1: $b \cdot a$
 - Path 2: $c \cdot a$
 - Merge: $b \cdot a + c \cdot a = a \cdot (b + c)$
 - Negate: $\overline{a \cdot (b + c)}$
 - $f = \overline{a \cdot (b + c)}$



Pass Transistors


- nFET

 - $g = 0$: OFF
- $g = 1$: ON
 - $a = 0$: $b = \text{strong } 0$
 - $a = 1$: $b = \text{weak } 1$




- pFET

 - $g = 1$: OFF
- $g = 0$: ON
 - $a = 0$: $b = \text{weak } 0$
 - $a = 1$: $b = \text{strong } 1$



Transmission Gate Circuits

- Transistor circuit

 

- Behaviors


- When $s = 0$: Both nFET and pFET are OFF.
- When $s = 1$: Both nFET and pFET are ON.
 - If $x = 0$, the nFET perfectly transmits it to y (nFET is good at transferring 0.)
 - If $x = 1$, the pFET perfectly transmits it to y (pFET is good at transferring 1.)

- Disadvantage


- Needs \bar{s} .
- Does not restore the input signals.

Transmission Gate Circuits


 

- Logic design using transmission gates
 - MUX: $f = \bar{s} \cdot x_0 + s \cdot x_1$



- XNOR

 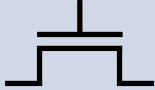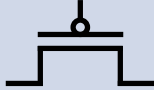


Pass Transistors vs. Transmission Gates

	Pass TR.		Transmission Gates
Symbols			
Signal strength	Strong 0 Weak 1	Weak 0 Strong 1	Strong 0 Strong 1
Area	A	rA ($r > 1$)	$(1 + r)A$
Control signal	g	g	g, \bar{g}

Buffer

- $Y = A$

 




- Buffers are used for
 - Signal restoration
 - Interconnect optimization

Tristate Inverter

- Truth table



EN	Y
0	Z
1	\bar{A}

- Symbol & Schematic

   


Tristate Buffer

- Symbol

  


- Gate-level schematic

 

Sequential Circuit – D Latch


- Positive-level-sensitive D latch

CLK	Q
0	hold
1	D

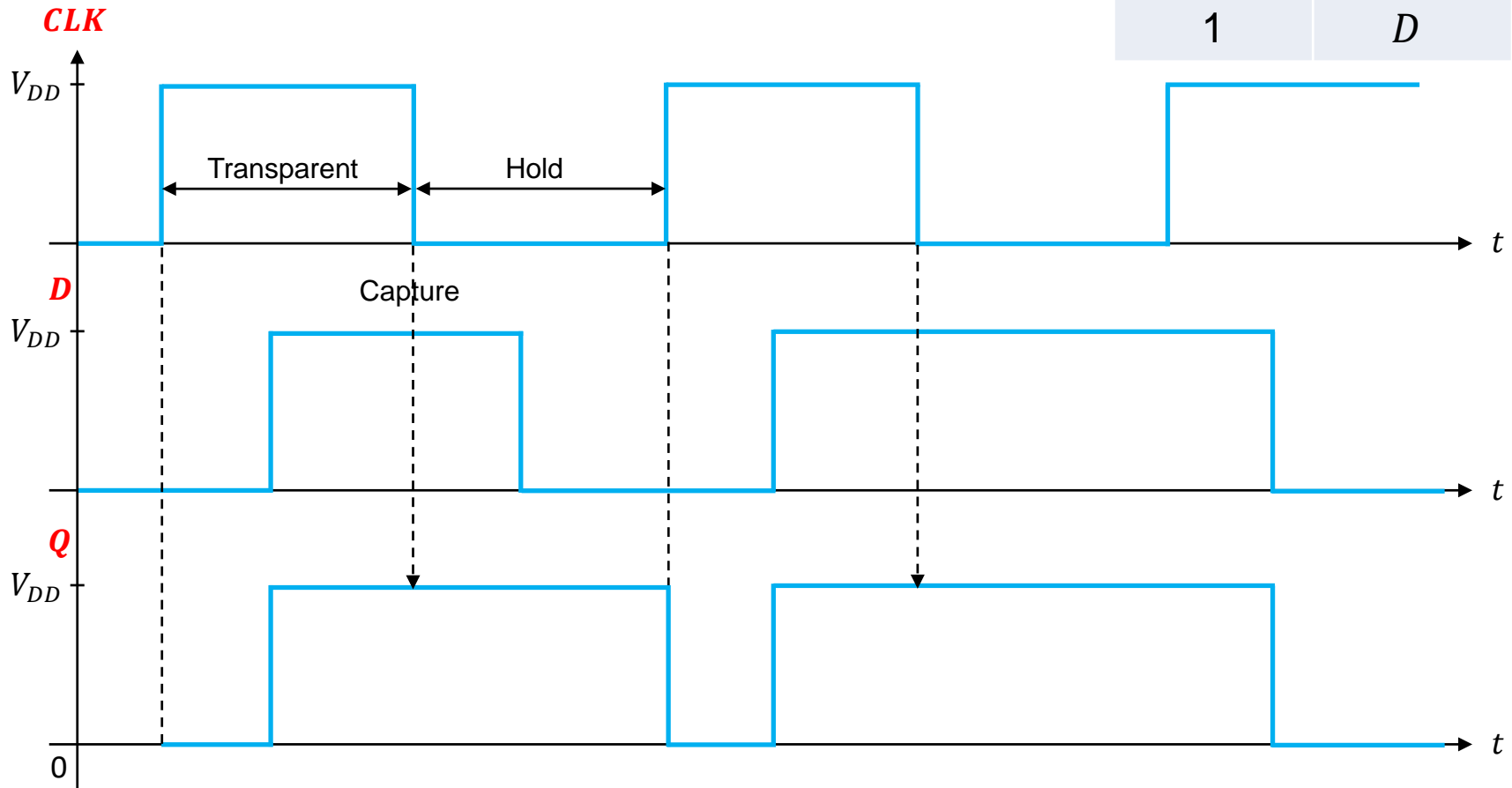

Sequential Circuit – D Latch


- Schematic

 

Sequential Circuit – D Flip-Flop

- Positive-edge-triggered D flip-flop

CLK	Q
0, 1	hold
↑	catch D

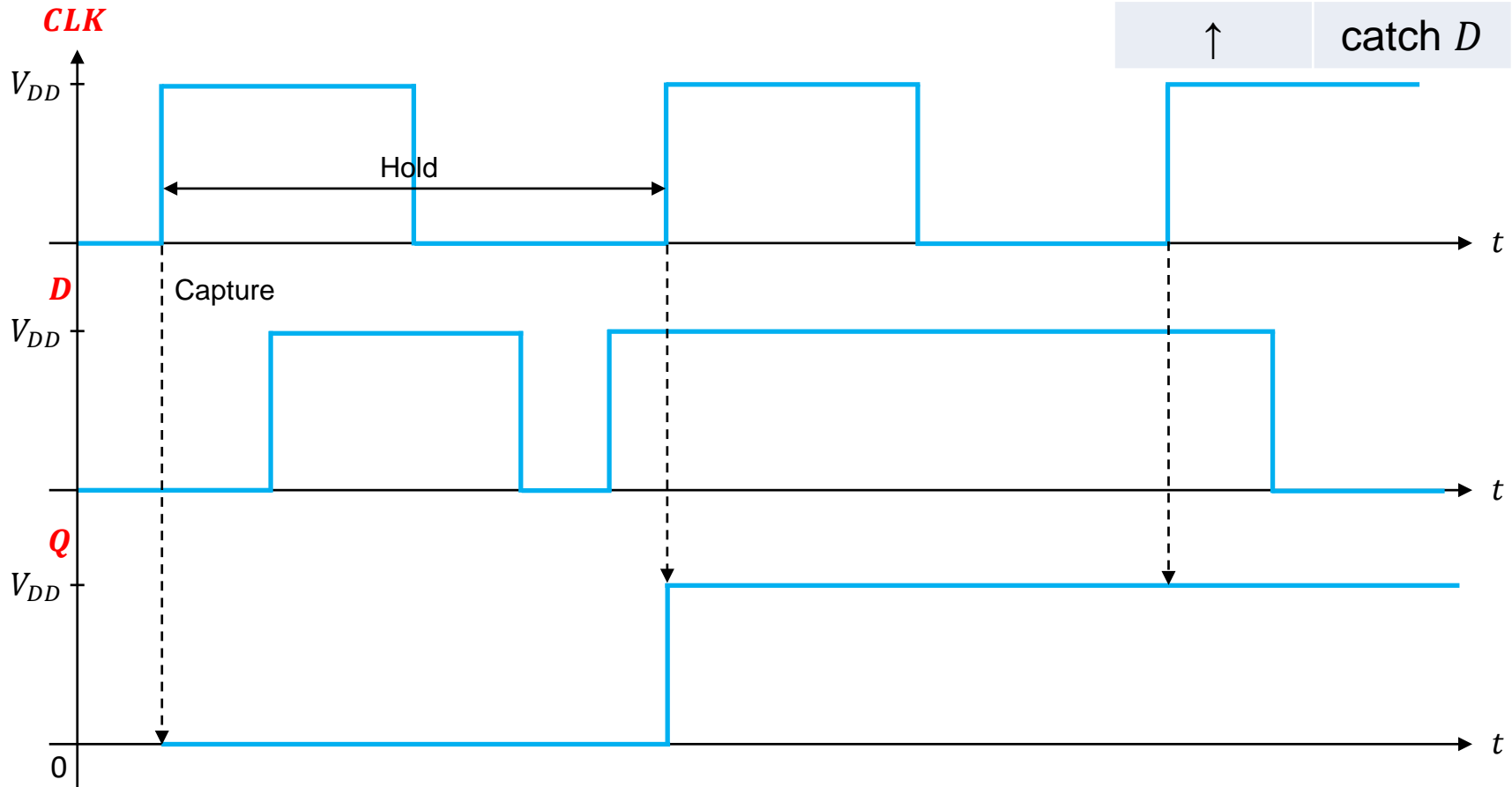

Sequential Circuit – D Flip-Flop

- Schematic

