

**EE434**

**ASIC and Digital Systems**

**Midterm Exam 2**

**Mar. 31, 2017. (4:10pm – 5pm)**

**Instructor: Dae Hyun Kim ([daehyun@eecs.wsu.edu](mailto:daehyun@eecs.wsu.edu))**

**Name:**

**WSU ID:**



Problem	Points	
1	10	
2	10	
3	10	
4	10	
5	10	
Total	50	

\* Allowed: Textbooks, cheat sheets, class notes, notebooks, calculators, watches

\* Not allowed: Electronic devices (smart phones, tablet PCs, laptops, etc.) except calculators and watches
 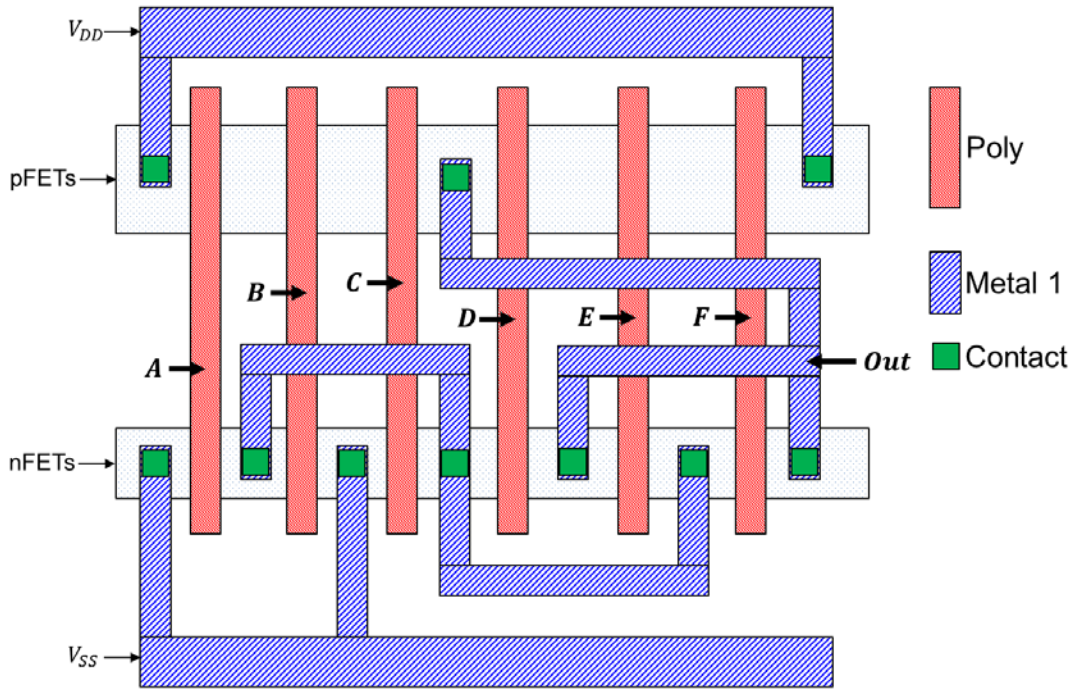
### Problem #1 (Layout, 10 points).

Represent *Out* as a Boolean function of *A, B, C, D, E, F*.




$$Y = \overline{(A + B + C) \cdot (D + E + F)}$$
 
## Problem #2 (DC Characteristics, 10 points).


An infinite chain of inverters is defined as follows:



All the inverters are identical, i.e., have the same characteristics. The above chain is modeled as a block diagram as follows:



 where  $Noise\ k$  is the  $k$ -th noise and  $Source$  is a signal generator and  $V_{Source} = V_{DD} \cdot u(t)$  (i.e., 0 if  $t < 0$  and  $V_{DD}$  if  $t \geq 0$ ).  $V_{DD} = 1V$ . The DC characteristic of an inverter is approximated using three segments as follows (If  $V_{in} \geq V_{DD}$ ,  $V_{out} = 0$ . If  $V_{in} \leq 0$ ,  $V_{out} = V_{DD}$ ):



$$\begin{aligned}
 1) \quad V_{out} &= \frac{V_{OH} - V_{DD}}{V_{IL}} \cdot V_{in} + V_{DD} \\
 2) \quad V_{out} &= \frac{V_{OL} - V_{OH}}{V_{IH} - V_{IL}} \cdot (V_{in} - V_{IH}) + V_{OL} \\
 3) \quad V_{out} &= -\frac{V_{OL}}{V_{DD} - V_{IH}} \cdot (V_{in} - V_{DD})
 \end{aligned}$$

Each noise source is an independent voltage signal and its range is as follows ( $V_N > 0$ ):

- $|V_{noise}| \leq V_N$

Compute the max. value of  $V_N$  that does not cause signal inversion for the following two cases (Note: Signal inversion occurs if a signal reaches 0.5V when it should be 0 or 1):

- Case 1)  $V_{OL} = 0V, V_{OH} = 1V, V_{IL} = 0.4V, V_{IH} = 0.6V$
- Case 2)  $V_{OL} = 0V, V_{OH} = 1V, V_{IL} = 0.4V, V_{IH} = 0.8V$


Case 1) In this case,  $y = -5x + 3$  in Region 2. The high noise margin is  $0.4V$ , so is the low noise margin. Suppose  $V_N$  is  $(0.4 + \delta)V$  where  $\delta > 0$ . Let's take a look at the worst cases.

- Input of inverter m:  $1V$
- Output of inverter m:  $0V$
- Input of inverter (m+1):  $(0.4 + \delta)V // a(n) = 0.4 + b(n)$
- Output of inverter (m+1):  $(1.0 - 5\delta)V // -5a(n) + 3 = 1 - 5b(n)$
- Input of inverter (m+2):  $(0.6 - 6\delta)V // -5a(n) + 2.6 - \delta = 0.6 - 5b(n) - \delta$
- Output of inverter (m+2):  $(30\delta)V // 25a(n) - 10 + 5\delta = 25b(n) + 5\delta$
- Input of inverter (m+3):  $(0.4 + 31\delta)V // a(n+1) = 25a(n) - 9.6 + 6\delta = 0.4 + 25b(n) + 6\delta \rightarrow b(n+1) = 25b(n) + 6\delta, a(n+1) = 0.4 + b(n+1)$
- ...

$a(n+1) = 0.4 + b(n+1)$  and  $b(n+1) = 25b(n) + 6\delta$ . Since  $b(n)$  goes to infinity as  $n$  increases, so signal inversion happens.

If  $V_N$  is  $0.4V$

 
- Input of inverter m:  $1V$
- Output of inverter m:  $0V$
- Input of inverter (m+1):  $0.4V$
- Output of inverter (m+1):  $1V$
- Input of inverter (m+2):  $0.6V$
- Output of inverter (m+2):  $0V$
- Input of inverter (m+3):  $0.4V$
- ...



Thus, if  $\delta > 0$ , signal inversion will eventually occur no matter how small  $\delta$  is. Thus, the maximum  $V_N$  is  $0.4V$  in this case.

Case 2) In this case,  $y = -2.5x + 2$  in Region 2. When the output is 0.4V, the input voltage is 0.64V. Suppose  $V_N$  is  $X(V)$  where  $X$  is between 0.2V and 0.4V. Let's take a look at the worst cases.

 - Input of inverter m: 1V
- Output of inverter m: 0V
- Input of inverter (m+1):  $X(V)$
- Output of inverter (m+1): 1V
- Input of inverter (m+2):  $(1 - X)V$
- Output of inverter (m+2):  $(-0.5 + 2.5X)V$
- Input of inverter (m+3):  $(-0.5 + 3.5X)V$



If  $(-0.5 + 3.5X)V$  is greater than 0.4V, the output voltage is less than 1V, then a positive feedback loop is formed, so we solve the following inequality:


$$(-0.5 + 3.5X)V \leq 0.4V$$

Thus,  $V_N \approx 0.257V$ .
 
### Problem #3 (Elmore Delay, 10 points).

The RC tree shown below has two delay constraints as follows:

- The delay from the driver to  $V_{L1}$  should be less than or equal to  $900ps$ .
- The delay from the driver to  $V_{L2}$  should be less than or equal to  $6823ps$ .




Currently, the delay at  $V_{L1}$  is  $1k * 11f + 1k * 12f + \dots + 1k * 29f + 1k * 59f + 1k * 60f + \dots + 1k * 79f = 1829ps$ , so is the delay at  $V_{L2}$ .

You are supposed to insert only one buffer in the RC tree to satisfy the delay constraints at both  $V_{L1}$  and  $V_{L2}$ . You can insert the buffer only into one of the designated nodes ( $n1 \sim n60$ ). The buffer has the following characteristics:

- Input capacitance:  $10fF$
- Internal delay:  $20ps$
- Output resistance:  $1k\Omega$

 When you insert a buffer into a node, the RC tree before and after the buffer are separated as follows (assuming the buffer is inserted into  $n2$  in the figure above):



In this case (inserting a buffer into n2), the delay at  $V_{L1}$  is  $[1k * 11f + 1k * 12f + \dots + 1k * 29f + 1k * 59f + 1k * 60f + \dots + 1k * 77f + 1k * 77f] + [20ps] + [1k * 11f + 1k * 12f] = (1749 + 20 + 23)ps = 1792ps$ , so is the delay at  $V_{L2}$ . As you see, the delay is reduced from  $1829ps$  to  $1792ps$ .

Insert a buffer into one of the nodes (n1 ~ n60) so that it satisfies the delay constraints at both  $V_{L1}$  and  $V_{L2}$ . Then, compute the Elmore delay at  $V_{L1}$ .

(Help: The sum of  $a, a + 1, a + 2, \dots, n$  is  $\frac{(n+a)(n-a+1)}{2}$ . For example,  $5 + 6 + \dots + 10 = \frac{(10+5)(10-5+1)}{2} = 45$ .)

If I insert a buffer into node n21, the delay at  $V_{L1}$  is

$$\begin{aligned} & (1k * 11f + 1k * 12f + \dots + 1k * 29f + 1k * 29f) + (20ps) \\ & + (1k * 40f + 1k * 41f + \dots + 1k * 60f) \\ & = (380ps + 29ps) + (20ps) + (1050ps) = 1479ps \end{aligned}$$

If I insert a buffer into node n41, the delay at  $V_{L1}$  is

$$\begin{aligned} & (1k * 11f + 1k * 12f + \dots + 1k * 29f) + (1k * 40f + 1k * 41f + \dots + 1k * 60f) \\ & = (380ps) + (1050ps) = 1430ps \end{aligned}$$

If I insert a buffer into node n20, the delay at  $V_{L1}$  is

$$\begin{aligned} & (1k * 11f + 1k * 12f + \dots + 1k * 29f) + (1k * 59f) + (1k * 59f) + (20ps) \\ & + (1k * 11f + 1k * 12f + \dots + 1k * 30f) \\ & = (380ps) + (59ps) + (59ps) + (20ps) + (410ps) = 928ps \end{aligned}$$

If I insert a buffer into node n19, the delay at  $V_{L1}$  is

$$\begin{aligned} & (1k * 11f + 1k * 12f + \dots + 1k * 29f) + (1k * 59f) + (1k * 60f) + (1k * 60f) + (20ps) \\ & + (1k * 11f + 1k * 12f + \dots + 1k * 29f) \\ & = (380ps) + (59ps) + (60ps) + (20ps) + (380ps) = \mathbf{899ps} \end{aligned}$$

Node: n19

Elmore delay at  $V_{L1}$ : 899ps

### Problem #4 (Pseudo-nMOS, 10 points).

Draw a pseudo-nMOS schematic for  $Y = \overline{A \cdot B \cdot C + (D + E) \cdot F}$  and properly size the nFETs to achieve the following output level for logic output 0:

- $V_{out} \leq 0.1V_{DD}$

Use the following parameters:

- Resistance of a  $1 \times$  nFET = Resistance of a  $2 \times$  pFET
- The size of the pFET:  $4 \times$
- Do not use the transistor-mode-based computation for sizing. You can just use the resistance values for sizing.
- Do not oversize the nFETs.


The resistance of the pFET is  $R_n/2$  where the resistance of a  $1X$  nFET is  $R_n$ . Suppose the resistance of an nFET path is  $R_k$ . Then,  $\frac{R_k}{(\frac{R_n}{2} + R_k)} \leq 0.1$ , so  $R_k \leq \frac{1}{18}R_n$ .

For  $A=B=C=1$ :

$$3 \cdot R = \frac{1}{18}R_n \Rightarrow R = \frac{1}{54}R_n \Rightarrow A = B = C = 54 \times$$

For  $F=1$  and  $(D \text{ or } E=1)$ :

 
$$2 \cdot R = \frac{1}{18}R_n \Rightarrow R = \frac{1}{36}R_n \Rightarrow D = E = F = 36 \times$$




 
## Problem #5 (Capacitive Coupling, 10 points).

The following figure models the coupling effect between two adjacent wires.



$V_1(t)$  is an aggressor and  $V_2(t)$  is a victim.  $V_2(t)$  is as follows:

$$V_2(t) = \frac{V_{DD}}{2} \left[ e^{-\frac{t}{\tau_1}} - e^{-\frac{t}{\tau_2}} \right] u(t)$$

where

- $\tau_1 = R(C + C_L + 2C_C)$
- $\tau_2 = R(C + C_L)$

In this case, the max. value of  $V_2(t)$  is found by differentiating  $V_2(t)$  with respect to  $t$ . The max. value occurs when  $t$  is

$$t_{max} = \frac{R(C + C_L)(C + C_L + 2C_C)}{2} \cdot \ln \frac{C + C_L + 2C_C}{C + C_L}$$

and the max. value of  $V_2(t)$  is

$$V_{2,max} = \frac{V_{DD}}{2} \cdot \left( 1 - \frac{\tau_2}{\tau_1} \right) \cdot \left( \frac{\tau_2}{\tau_1} \right)^{\frac{\tau_2}{2RC_C}}$$

Answer the following questions (Hint: Use the above formula or your intuition to solve this problem):

- If  $C_C$  increases,  $V_{2,max}$  increases. (True/False)
- If  $C$  increases,  $V_{2,max}$  increases. (True/False)
- If  $C_L$  increases,  $V_{2,max}$  increases. (True/False)
- If  $R$  increases,  $V_{2,max}$  increases. (True/False)
- The max. value of  $V_2(t)$  can be greater than  $V_{DD}/2$ . (True/False)

(Hint:  $\lim_{x \rightarrow \infty} \left(\frac{1}{x}\right)^{\frac{1}{x}} = 1$ .  $\lim_{x \rightarrow \infty} \left(\frac{x}{x+c}\right)^{\frac{x}{c}} = e$ .  $\left(\frac{x}{x+c}\right)^{\frac{x}{c}} > 1$ . (when  $c > 0$ ))

$$V_{2,max} = \frac{V_{DD}}{2} \cdot \left(1 - \frac{C + C_L}{C + C_L + 2C_C}\right) \cdot \left(\frac{C + C_L}{C + C_L + 2C_C}\right)^{\frac{C+C_L}{2C_C}}$$

$$\left(1 - \frac{C+C_L}{C+C_L+2C_C}\right) = a, \quad \frac{C+C_L}{C+C_L+2C_C} = b, \quad \text{and} \quad \frac{C+C_L}{2C_C} = d.$$

- If  $C_C$  increases,  $a$  approaches 1 and  $b$  and  $d$  approach 0, so  $b^d$  approaches 1. Thus,  $V_{2,max}$  increases (approaches  $\frac{V_{DD}}{2}$ ).
- If  $C$  increases,  $a$  approaches 0 and  $b^d$  approaches  $e$ , so  $V_{2,max}$  decreases (approaches 0).
- $C_L$  and  $C$  are interchangeable, so if  $C_L$  increases,  $V_{2,max}$  decreases (approaches 0).
- $V_{2,max}$  does not include  $R$ , so it does not increase even if  $R$  increases.
- $a$  is less than 1.  $b^d$  is less than 1. Thus,  $V_{2,max}$  is less than  $V_{DD}/2$ .