

EE434

ASIC and Digital Systems

Midterm Exam 1

Feb. 16, 2018. (4:10pm – 5pm)

Instructor: Dae Hyun Kim (daehyun@eecs.wsu.edu)

Name:

WSU ID:

Problem	Points	
1	10	
2	10	
3	10	
4	10	
5	10	
6	10	
Total	60	

* Allowed: Textbooks, cheat sheets, class notes, notebooks, calculators, watches


* Not allowed: Electronic devices (smart phones, tablet PCs, laptops, etc.) except calculators and watches

Problem #2 (Transmission Gates, 10 points)

Design (draw a schematic) the following Boolean function using transmission gates only.

$$Y = A \oplus B \oplus C$$

 Available inputs: $A, B, C, \bar{A}, \bar{B}, \bar{C}$. You cannot use Power (V_{DD}) and Ground (V_{SS}). Use the following symbols for the transmission gates.



Design constraint: The total # transmission gates should be less than or equal to 10.


(# TGs ≤ 10 : 10 points. $11 \leq$ # TGs ≤ 12 : 7 points. $13 \leq$ # TGs ≤ 14 : 5 points. # TGs > 14 : 0 points)

Problem #3 (Design, 10 points)

Design (draw a schematic) a two-bit comparator using transmission gates only. The following shows a truth table for the comparator:

A1	A0	B1	B0	Y1
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

 Available inputs: $A1, A0, B1, B0, \overline{A1}, \overline{A0}, \overline{B1}, \overline{B0}$. You cannot use Power (V_{DD}) and Ground (V_{SS}). Use the following symbols for the transmission gates.




Design constraint: The total # transmission gates should be less than or equal to 12.

(# TGs ≤ 12 : 10 points. $13 \leq$ # TGs ≤ 14 : 7 points. $15 \leq$ # TGs ≤ 16 : 5 points. # TGs > 16 : 0 points)

 Problem #4 (Transistor Sizing, 10 points)

Size the transistors in the following pull-down network. R_n is the resistance of a 1X NMOS transistor. Ignore parasitic capacitances. Target time constant: $\tau_{target} \leq R_n \cdot C_L$. Try to minimize the total area.




(Total width $W \leq 48X$: 10 points. $W \leq 50X$: 8 points. $W \leq 52X$: 5 points. $W > 52X$: 3 points)

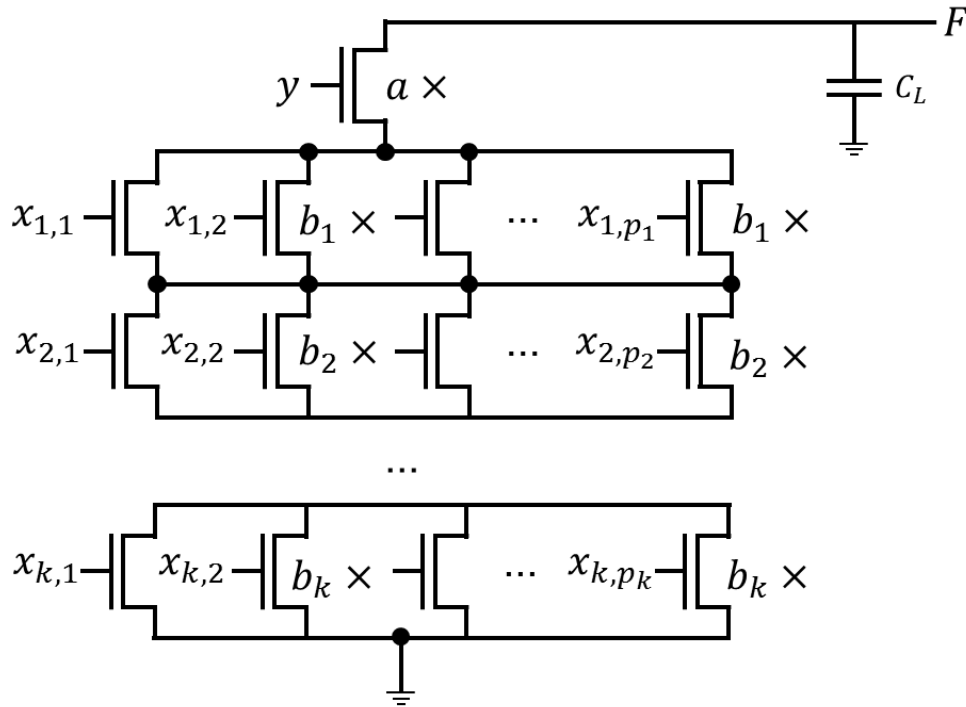Problem #5 (Transistor Sizing, 10 points)

The following shows an NFET network of

$$F = y \cdot (x_{1,1} + \dots + x_{1,p_1}) \cdot (x_{2,1} + \dots + x_{2,p_2}) \cdot \dots \cdot (x_{k,1} + \dots + x_{k,p_k})$$




Notice that k, p_1, \dots, p_k are constants. The fall delay should be less than or equal to $R_n C_L$ where R_n is the resistance of a $1 \times$ NFET. The NFET y is upsized to $a \times$ and each NFET connected to $x_{i,j}$ is upsized to $b_i \times$. We minimize the total width

$$W = a + b_1 \cdot p_1 + b_2 \cdot p_2 + \dots + b_k \cdot p_k.$$


Find a (the size of the NFET connected to input y) that minimizes the total width (i.e., represent a as a function of p_1, p_2, \dots, p_k).

 Problem #6 (Pass Transistor, 10 points)


The following schematic implements an XOR gate using pass transistors.



 The inverter at the output restores the signal so that the output swing can be $[0, V_{DD}]$. The following plots show the V_{DS} characteristic of the NFET when its gate voltage is V_{DD} and the V_{DS} characteristic of the PFET when its gate voltage is 0.



 The following plot shows the input-output characteristic of the inverter.



V_{tn} and $|V_{tp}|$ are the threshold voltages of the NFET and the PFET, respectively.
 A, B, \bar{A}, \bar{B} are either 0V (for 0) or V_{DD} (for 1). The swing of the final output $A \oplus B$ should be $[0, V_{DD}]$, i.e., 0V if $A \oplus B = 0$ and V_{DD} if $A \oplus B = 1$. Find all inequalities for the full output swing. (Hint: The inequalities might consist of V_{DD}, V_{tn} , and $|V_{tp}|$.)