

EE434

ASIC and Digital Systems

Midterm Exam 1

Feb. 27, 2019. (4:10pm – 5pm)

Instructor: Dae Hyun Kim (daehyun@eecs.wsu.edu)


Name:

WSU ID:

| Problem | Points | |
|---------|--------|--|
| 1 | 10 | |
| 2 | 10 | |
| 3 | 10 | |
| 4 | 20 | |
| 5 | 20 | |
| 6 | 10 | |
| Total | 80 | |

 Problem #1 (Static CMOS gates, 10 points)

The following shows the NFET network of a static CMOS gate. Express the output Y as a Boolean function of the inputs ($A \sim J$). (You don't need to simplify the expression.)




$$Y = \overline{AB(F + GH + IJ + DEJ) + CD(F + GH + IJ) + CE(J + IF + IGH)}$$

Problem #2 (Transmission Gates, 10 points)

Design (draw a schematic) the following Boolean function using transmission gates only.

$$Y = (A \oplus B) + \overline{(A \cdot B) \oplus C}$$

 Available inputs: $A, B, C, \bar{A}, \bar{B}, \bar{C}$. You cannot use Power (V_{DD}) and Ground (V_{SS}). Use the following symbols for the transmission gates.




(# TGs ≤ 6 : 10 points. $7 \leq$ # TGs ≤ 8 : 7 points. $9 \leq$ # TGs ≤ 10 : 5 points. # TGs > 10 : 0 points)

$$AB = 00: Y = \bar{C}$$

$$AB = 01: Y = 1$$


$$AB = 10: Y = 1$$

$$AB = 11: Y = C$$

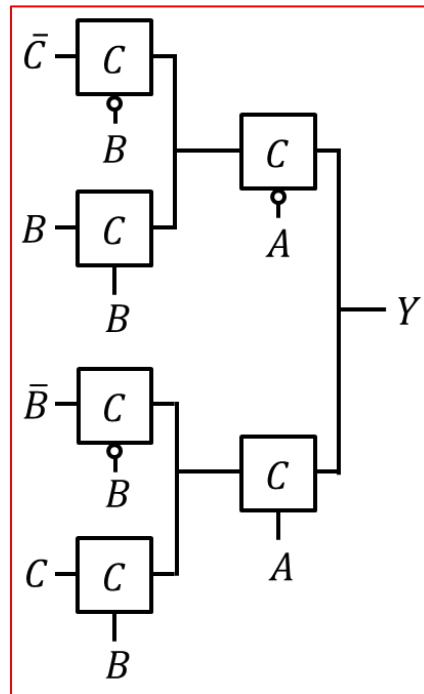

 Problem #3 (Transistor Sizing, 10 points)

Size the transistors in the following pull-down network. R_n is the resistance of a 1X NMOS transistor. C_L is the load capacitance. Ignore parasitic capacitances. Target delay: $\tau_T \leq R_n \cdot C_L$. Try to minimize the total area.



(Total width $W \leq 31X$: 10 points. $31X < W \leq 32X$: 8 points. $32X < W \leq 34X$: 5 points. $34X < W$: 3 points)

Longest paths: A-B-C-D, A-F-G-H, so they are upsized to 4X.

A: 4X

B: 4X

C: 4X

D: 4X

E: 2X

F: 4X

G: 4X

H: 4X

I: 4/3X


Total: 94/3X (31.33X)

Transistor A is a bottleneck, so if we upsize it to $5X$, B,C,D,F,G,H can be upsized to $15/4X$. In this case, E becomes $15/8X$ and I becomes $5/4X$. The total width in this case is $245/8X$, which is $30.625X$.

Problem #4 (Transistor Sizing, 20 points)

Solve either 4-(1) or 4-(2). You don't need to solve both.

 (1) (20 points) Size the transistors in the following pull-down network. R_n is the resistance of a 1X NMOS transistor. C_L is the load capacitance. Ignore parasitic capacitances. Target delay: $\tau_T \leq R_n \cdot C_L$. Minimize the total area (i.e., size the transistors optimally).



A: aX , B,C,D: bX , E: cX

$$\frac{1}{a} + \frac{3}{b} = 1, \frac{1}{a} + \frac{1}{c} = 1$$

$$b = \frac{3a}{a-1}, c = \frac{a}{a-1}$$

$$W = a + 3b + c = a + \frac{9a}{a-1} + \frac{a}{a-1} = a + 10 \frac{a}{a-1}$$


$$W' = 1 + \frac{10(a-1) - 10a}{(a-1)^2} = 0$$

$$a = 1 + \sqrt{10}, b = 3 + \frac{3}{\sqrt{10}}, c = 1 + \frac{1}{\sqrt{10}}, W = 11 + 2\sqrt{10}$$

(2) (12 points) Answer the following questions.


- (a) The optimal size of transistor A is greater than 4X True / False).
- (b) The optimal size of transistor B is greater than 4X (T / F).
- (c) The optimal size of transistor B is equal to the optimal size of transistor D T / F).
- (d) The optimal size of transistor E is greater than 2X (T / F).
- (e) The optimal size of transistor C is $3 \times$ the optimal size of transistor E T / F).
- (f) The sum of the optimal widths of all the transistors is greater than or equal to 18X (T / F).

Problem #5 (Layout, 20 points)

 

Signal input: A, D. Signal output: Y. Clock: CK

 
1) (10 points) Convert the layout into a transistor-level schematic.



2) (10 points) What is the function of the circuit?

This is a positive-edge-triggered D-F/F with an asynchronous active-low reset signal A.

Problem #6 (Layout, 10 points)

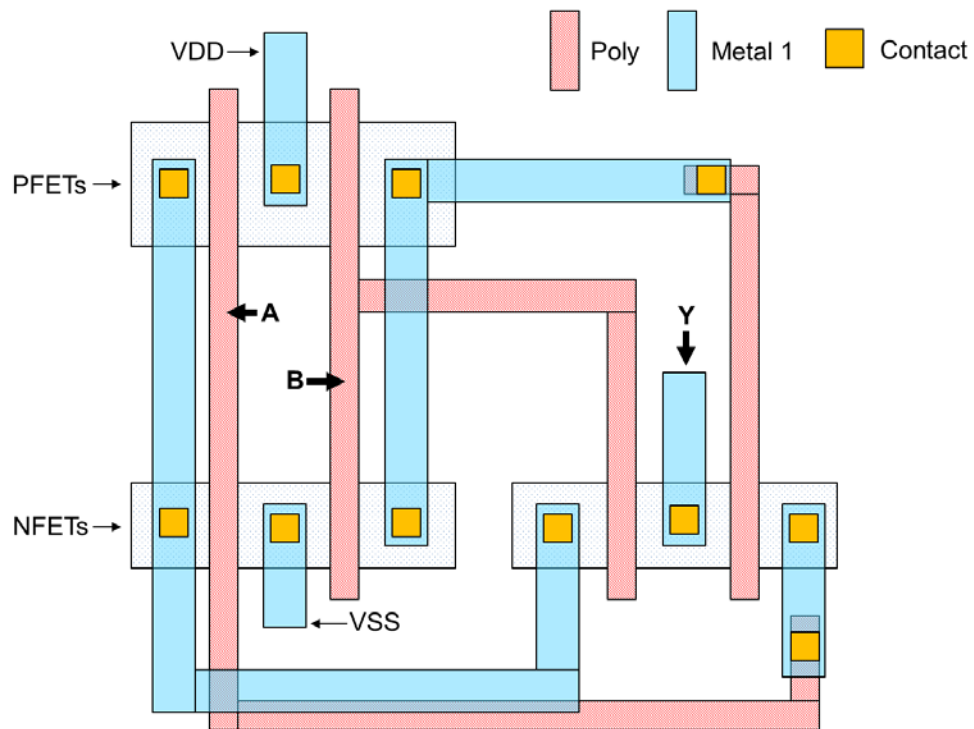

Input: A, B

Output: Y

What is the function of this circuit?

It is an XOR gate. $Y = A \oplus B$.