

EE466

VLSI System Design

Midterm Exam

Oct. 24, 2018. (4:15pm – 5:30pm)

Instructor: Dae Hyun Kim (daehyun@eecs.wsu.edu)

Name:

WSU ID:

Problem	Points	
1	10	
2	10	
3	10	
4	10	
5	10	
6	10	
7	10	
8	10	
Total	80	

* Allowed: Textbooks, cheat sheets, class notes, notebooks, calculators, watches

* Not allowed: Electronic devices (smart phones, tablet PCs, laptops, etc.) except calculators and watches


Problem #1 (Static CMOS Gates, 10 points).

Draw a transistor-level schematic for the NFET network of the following Boolean function (Available input: $A, B, C, D, \bar{A}, \bar{B}, \bar{C}, \bar{D}$). Use the static CMOS gate design. Minimize the # TRs.

TRs ≤ 12 : 10 points. $13 \leq$ # TRs ≤ 14 : 8 points. $15 \leq$ # TRs ≤ 16 : 5 points.

$$F = \overline{A \oplus (B \oplus (CD))}$$


$$\begin{aligned} \bar{F} &= A \oplus (B \oplus (CD)) = A \oplus (\bar{B} \oplus \bar{E}) = A(B \oplus E) + \bar{A} \cdot \bar{B} \oplus \bar{E} = A \cdot (B\bar{E} + \bar{B}E) + \bar{A} \cdot (BE + \bar{B}\bar{E}) \\ &= A \cdot (B(\bar{C} + \bar{D}) + \bar{B}CD) + \bar{A} \cdot (BCD + \bar{B}(\bar{C} + \bar{D})) \\ &= (AB + \bar{A}\bar{B})(\bar{C} + \bar{D}) + (A\bar{B} + \bar{A}B)CD \end{aligned}$$

 

 Problem #2 (Transistor Sizing, 10 points).

Size the transistors in the following pull-down network of a static CMOS gate. R_n is the resistance of a 1X NMOS transistor. C_L is the load cap. Ignore all the parasitic capacitances. Target timing constraint: $\tau = R_n \cdot C_L$. Try to minimize the total area.

Area $\leq 36X$: 10 points. $36X < \text{Area} \leq 38X$: 7 points. $38X < \text{Area}$: 4 points.



The longest path: x_1 - x_2 - x_3 - x_4 -(x_5 or x_7). All of them become 5X.

x_1 : 5X

x_2 : 5X

x_3 : 5X

x_4 : 5X



x_5 : 5X

x_6 : 2.5X

x_7 : 5X

x_8 : 5/3X

Problem #3 (DC Analysis, 10 points).

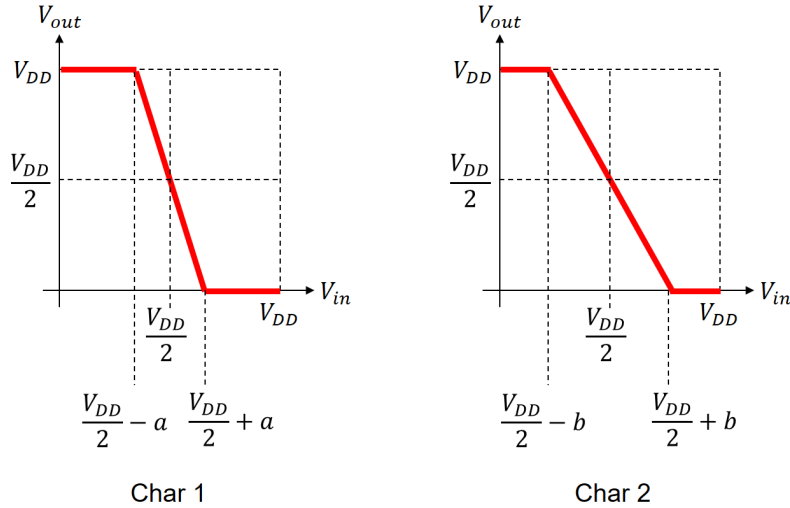 


The gate-level schematic shows a buffer composed of two inverters.

Buffer 1: Char 1 for INV1 and Char 2 for INV2


Buffer 2: Char 2 for INV1 and Char1 for INV2

Prove that the two buffers have the same DC characteristics.

 Both of them have the same DC curve as follows:




Problem #4 (Logic Analysis, 10 points).

 

Describe the function of the circuit shown above.

Dual-edge-triggered D-FF.

Problem #6 (Logic Analysis, 10 points).

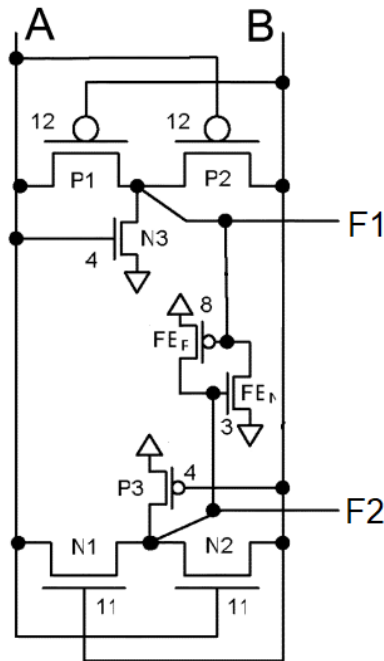

The above circuit has two inputs (A, B) and two outputs (F1 and F2).

(1) Express F1 as a Boolean function of A and B.

$$F1 = A \oplus B$$


(2) Express F2 as a Boolean function of A and B.

$$F2 = \overline{A \oplus B}$$

(3) Does it have any static power consumption problem? Explain why (or why not).

When $A=1, B=0$, N3 is ON, but P1 is ON and A is connected to F1, so there is static power consumption. Same for $A=0, B=1$.

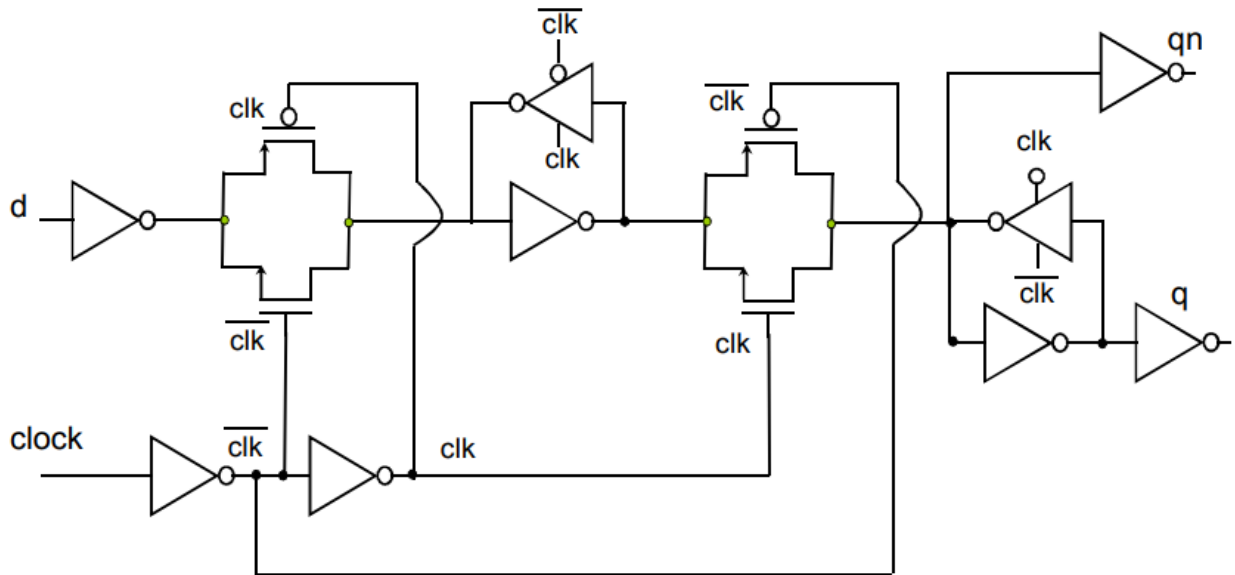Problem #7 (Sequential Logic, 10 points).



The circuit shown above is a positive-edge-triggered D FF. Notice that all the inverters and transmission gates have finite delays.

(1) Estimate the hold time of the FF for input $D=0$.

The first TG will be turned off after two inverter delays. If D switches from 1 to 0, the output of the inverter connected to D will be 1 after one inverter delay. Thus, as long as D holds 0 for one inverter delay (+ delta), it is safe.

(2) Estimate the hold time for input $D=1$.


For the same reason, the hold time is one inverter delay + delta for $D=1$.

(3) Estimate the signal delay (from a clock rising edge at the clock input to Q).

When CK goes high, the second TG is closed after two inverter delays. Then, Q changes after a TG delay + two inverter delays.

 Problem #8 (Power Consumption, 10 points).

The following figure shows an inverter with a parasitic cap and a load cap ($10C$). The parasitic cap is proportional to the sizes of the transistors connected to the cap. The PFET is upsized to bX and the NFET is upsized to aX . $\frac{\mu_n}{\mu_p} = 2$. The rising delay should be $\leq 20R_nC$ where R_n is the resistance of a $1X$ NFET. The falling delay should be $\leq 10R_nC$. Both a and b are integers.



Can you find a and b minimizing the power consumption and satisfying the given timing constraints? Notice that there are only a few combinations of (a, b) you need to calculate to answer this problem.

The rise delay is $t_r = \frac{R_p}{b} \cdot (a + b + 10)C$ and the fall delay is $t_f = \frac{R_n}{a} \cdot (a + b + 10)C$. The power consumption is $f(a + b + 10)CV_{DD}^2$, so minimizing the power is minimizing $a + b$.

$$t_r = \frac{2R_n}{b} \cdot (a + b + 10)C \leq 20R_nC, \text{ so } a + b + 10 \leq 10b, \text{ so } a + 10 \leq 9b.$$

$$t_f = \frac{R_n}{a} \cdot (a + b + 10)C \leq 10R_nC, \text{ so } a + b + 10 \leq 10a, \text{ so } b + 10 \leq 9a.$$

$$\frac{a+10}{9} \leq b \leq 9a - 10.$$

If $a=1$, b is negative.

If $a=2$, $1.XX \leq b \leq 8$, so b is 2 (to minimize $a+b$). In this case, $a+b=4$.

If $a=3$, $b=2$. If $a \geq 4$, $a+b \geq 5$.

Thus, $a = 2X, b = 2X$.