

**EE434**

**ASIC and Digital Systems**

**Final Exam**

**May 5, 2020. (8am – 10am)**


**Instructor: Dae Hyun Kim ([daehyun@eecs.wsu.edu](mailto:daehyun@eecs.wsu.edu))**

**Name:**

**WSU ID:**

Problem	Points	
1	30	
2	40	
3	30	
4	50	
5	20	
6	50	
7	40	
Total	260	

## Problem #1 (Interconnects, 30 points)

 

The figure shows a net composed of three wire segments. The length and unit wire R and C of section  $k$  ( $k = 1, 2, 3$ ) are  $l_k$ ,  $r_k$ , and  $c_k$ , respectively as shown in the figure. The output resistance of the driver is  $R_0$ , the input capacitance of the sink is  $C_2$ , and the output resistance, input capacitance, and the delay of a buffer is  $R_1$ ,  $C_1$ , and  $d_1$ , respectively. We are going to insert a buffer into the second section. The first and third sections are not bufferable.

(1) Find the optimal location for the buffer insertion (express the location as a function of the constants). (10 points)

Let's assume that the distance from the left side of the second section to the buffer is  $x$  (um) (so,  $0 \leq x \leq l_2$ ). Then, the delay of the left side of the buffer is

$$\tau_1 = R_0(c_1 l_1 + c_2 x + C_1) + r_1 l_1(c_2 x + C_1) + \frac{1}{2} r_1 c_1 l_1^2 + r_2 x C_1 + \frac{1}{2} r_2 c_2 x^2$$

The delay of the right side is

$$\tau_2 = R_1(c_2(l_2 - x) + c_3 l_3 + C_2) + r_2(l_2 - x)(c_3 l_3 + C_2) + \frac{1}{2} r_2 c_2 (l_2 - x)^2 + r_3 l_3 C_2 + \frac{1}{2} r_3 c_3 l_3^2$$

and the total delay is

$$\tau = \tau_1 + d_1 + \tau_2$$

$$\frac{d\tau}{dx} = R_0 c_2 + r_1 l_1 c_2 + r_2 C_1 + r_2 c_2 x - R_1 c_2 - r_2 (c_3 l_3 + C_2) - r_2 c_2 (l_2 - x) = 0$$

$$x(2r_2 c_2) = (R_1 - R_0)c_2 + (C_2 - C_1)r_2 - r_1 c_2 l_1 + r_2 c_3 l_3 + r_2 c_2 l_2$$

$$\therefore x = \frac{1}{2} \left\{ \frac{R_1 - R_0}{r_2} + \frac{C_2 - C_1}{c_2} - \frac{r_1}{r_2} l_1 + l_2 + \frac{c_3}{c_2} l_3 \right\}$$

(2) Answer the following questions. (Correct: +2 points. Wrong: -1 point. No answer: 0.)

(1) If  $R_0 = R_1$ ,  $C_1 = C_2$ ,  $r_1 = r_2 = r_3$ ,  $c_1 = c_2 = c_3$ , and  $l_1 = l_2 = l_3$ , then  $x = \frac{1}{2}l_2$ . (True / False)

(2) If  $R_0 < R_1$ ,  $C_1 = C_2$ ,  $r_1 = r_2 = r_3$ ,  $c_1 = c_2 = c_3$ , and  $l_1 = l_2 = l_3$ , then  $x < \frac{1}{2}l_2$ . (True / False)

(3) If  $R_0 = R_1$ ,  $C_1 < C_2$ ,  $r_1 = r_2 = r_3$ ,  $c_1 = c_2 = c_3$ , and  $l_1 = l_2 = l_3$ , then  $x < \frac{1}{2}l_2$ . (True / False)

(4) If  $R_0 = R_1$ ,  $C_1 = C_2$ ,  $r_1 < r_2 = r_3$ ,  $c_1 = c_2 = c_3$ , and  $l_1 = l_2 = l_3$ , then  $x < \frac{1}{2}l_2$ . (True / False)

(5) If  $R_0 = R_1$ ,  $C_1 = C_2$ ,  $r_1 = r_2 > r_3$ ,  $c_1 = c_2 = c_3$ , and  $l_1 = l_2 = l_3$ , then  $x < \frac{1}{2}l_2$ . (True / False)

(6) If  $R_0 = R_1$ ,  $C_1 = C_2$ ,  $r_1 = r_2 = r_3$ ,  $c_1 < c_2 = c_3$ , and  $l_1 = l_2 = l_3$ , then  $x < \frac{1}{2}l_2$ . (True / False)


(7) If  $R_0 = R_1$ ,  $C_1 = C_2$ ,  $r_1 = r_2 = r_3$ ,  $c_1 = c_2 > c_3$ , and  $l_1 = l_2 = l_3$ , then  $x < \frac{1}{2}l_2$ . (True / False)

(8) If  $R_0 = R_1$ ,  $C_1 = C_2$ ,  $r_1 = r_2 = r_3$ ,  $c_1 = c_2 = c_3$ , and  $l_1 < l_2 = l_3$ , then  $x < \frac{1}{2}l_2$ . (True / False)

(9) If  $R_0 = R_1$ ,  $C_1 = C_2$ ,  $r_1 = r_2 = r_3$ ,  $c_1 = c_2 = c_3$ , and  $l_1 = l_2 > l_3$ , then  $x < \frac{1}{2}l_2$ . (True / False)

(10) If  $r_3$  increases,  $x$  increases (i.e., the optimal buffer location is shifted to the right.) (True / False)

## Problem #2 (Interconnects, 40 points)

 

The figure shows a net composed of a long wire whose unit resistance and capacitance are  $r$  and  $c$ , respectively. We want to insert two buffers, Buffer 1 and Buffer 2 ( $0 \leq x$ ,  $0 \leq y$ ,  $x + y \leq L$ ). The output resistance ( $R_{\#}$ ), input capacitance ( $C_{\#}$ ), and internal delay ( $d_{\#}$ ) of each cell are shown above.

(a) Find the optimal locations for Buffer 1 and Buffer 2 (express  $x$  (and also  $y$ ) as a function of the constants). Hint: Express the total delay as a function of  $x$  and  $y$ . Then, different it w.r.t.  $x$  and set it to zero. Differentiate it w.r.t.  $y$  and set it to zero. Then, you get two equations for two variables,  $x$  and  $y$ . Solve it. (12 points)

$$\tau_1 = R_0(C_1 + cx) + rxC_1 + \frac{1}{2}rcx^2$$

$$\tau_2 = R_1\{C_2 + c(L - x - y)\} + r(L - x - y)C_2 + \frac{1}{2}rc(L - x - y)^2$$

$$\tau_3 = R_2(C_3 + cy) + ryC_3 + \frac{1}{2}rcy^2$$

Total delay  $\tau = \tau_1 + d_1 + \tau_2 + d_2 + \tau_3$

$$\frac{\partial \tau}{\partial x} = R_0c + rC_1 + rcx - R_1c - rC_2 - rc(L - x - y) = 0$$

$$\frac{\partial \tau}{\partial y} = R_2c + rC_3 + rcy - R_1c - rC_2 - rc(L - x - y) = 0$$

$$2rcx + rcy = rcL + (R_1 - R_0)c + (C_2 - C_1)r$$

$$rcx + 2rcy = rcL + (R_1 - R_2)c + (C_2 - C_3)r$$

$$\therefore x = \frac{1}{3} \left\{ L + \frac{R_1 + R_2 - 2R_0}{r} + \frac{C_2 + C_3 - 2C_1}{c} \right\}$$

$$y = \frac{1}{3} \left\{ L + \frac{R_0 + R_1 - 2R_2}{r} + \frac{C_1 + C_2 - 2C_3}{c} \right\}$$


(b) Answer the following questions. (Correct: +2 points. Wrong: -1 point. No answer: 0.)

Notice that if  $x$  increases, Buffer 1 is shifted to the right.

However, if  $y$  increases, Buffer 2 is shifted to the left.

- (1) If  $R_0 = R_1 = R_2$  and  $C_1 = C_2 = C_3$ , then  $x = \frac{1}{3}L$ . (**True** / False)
- (2) If  $R_0 = R_1 = R_2$  and  $C_1 = C_2 = C_3$ , then  $y = \frac{1}{3}L$ . (**True** / False)
- (3) If  $R_0$  increases,  $x$  increases. (True / **False**)
- (4) If  $R_0$  increases,  $y$  increases. (**True** / False)
- (5) If  $R_1$  increases,  $x$  increases. (**True** / False)
- (6) If  $R_1$  increases,  $y$  increases. (**True** / False)
- (7) If  $R_2$  increases,  $x$  increases. (**True** / False)
- (8) If  $R_2$  increases,  $y$  increases. (True / **False**)
- (9) If  $C_1$  increases,  $x$  increases. (True / **False**)
- (10) If  $C_1$  increases,  $y$  increases. (**True** / False)
- (11) If  $C_2$  increases,  $x$  increases. (**True** / False)
- (12) If  $C_2$  increases,  $y$  increases. (**True** / False)
- (13) If  $C_3$  increases,  $x$  increases. (**True** / False)
- (14) If  $C_3$  increases,  $y$  increases. (True / **False**)
 
### Problem #3 (Interconnects, 30 points)



The figure shows a long wire whose length, unit resistance and capacitance are  $L$ ,  $r$ , and  $c$ , respectively. We want to insert a buffer ( $0 \leq x \leq L$ ). The size of the buffer is  $s$  and its output resistance, input capacitance, and internal delay are as follows:

- Output resistance:  $\frac{R}{s}$  (where  $R$  is a constant)
- Input capacitance:  $sP$  (where  $P$  is a constant)
- Internal delay:  $sD$  (where  $D$  is a constant)

Notice that there are two variables,  $x$  and  $s$ .

(a) Express the total delay as a function of the variables and the constants. (7 points)

$$\tau = R_0(cx + sP) + rx(sP) + \frac{1}{2}rcx^2 + sD + \frac{R}{s}\{c(L - x) + C_2\} + r(L - x)C_2 + \frac{1}{2}rc(L - x)^2$$

(b) Assuming the location ( $x$ ) is given (i.e., you can treat it as a constant.), find the optimal size ( $s$ ) of the buffer, .i.e., express the optimal value of  $s$  as a function of the constants and  $x$ . (7 points)

$$\frac{\partial \tau}{\partial s} = R_0P + rxP + D - \frac{R\{c(L - x) + C_2\}}{s^2} = 0$$


$$s = \sqrt{\frac{R\{c(L - x) + C_2\}}{(R_0 + rx)P + D}}$$

(c) Answer the following questions. (Correct: +2 points. Wrong: -1 point. No answer: 0.)

- (1) If  $x$  increases,  $s$  increases. (True / **False**)
- (2) If  $R$  increases,  $s$  increases. (**True** / False)
- (3) If  $c$  increases,  $s$  increases. (**True** / False)
- (4) If  $C_2$  increases,  $s$  increases. (**True** / False)
- (5) If  $R_0$  increases,  $s$  increases. (True / **False**)
- (6) If  $r$  increases,  $s$  increases. (True / **False**)
- (7) If  $P$  increases,  $s$  increases. (True / **False**)

(8) If  $D$  increases,  $s$  increases. (True / **False**)

### Problem #4 (Coupling, 50 points)

 

The figure shows three parallel nets. The coupling capacitance between Net 1 and Net 2 is  $C_c$ . The coupling capacitance between Net 2 and Net 3 is  $2C_c$ . The following shows a three-bit binary encoding technique for four decimal numbers (0, 1, 2, 3).

Value	Encoding
0	000
1	010
2	101
3	111

(1) Calculate the total effective capacitance of Net 1 for all possible transitions (0→1, 0→2, 0→3, 1→0, 1→2, 1→3, 2→0, 2→1, 2→3, 3→0, 3→1, 3→2) for the encoding technique, i.e., calculate the sum of the effective capacitances of Net 1 for all possible transitions. (10 points)

0→1: 0, 0→2:  $C_g + C_c$ , 0→3:  $C_g$ , 1→0: 0, 1→2:  $C_g + 2C_c$ , 1→3:  $C_g + C_c$ , 2→0:  $C_g + C_c$ , 2→1:  $C_g + 2C_c$ , 2→3: 0, 3→0:  $C_g$ , 3→1:  $C_g + C_c$ , 3→2: 0. (Notice that a→b and b→a have the same effective capacitance.)

Total effective capacitance:  $8C_g + 8C_c$

(2) Repeat it for Net 2. (10 points)

0→1:  $C_g + 3C_c$ , 0→2: 0, 0→3:  $C_g$ , 1→2:  $C_g + 6C_c$ , 1→3: 0, 2→3:  $C_g + 3C_c$ .

Total effective capacitance:  $8C_g + 24C_c$

(3) Repeat it for Net 3. (10 points)

0→1: 0, 0→2:  $C_g + C_c$ , 0→3:  $C_g$ , 1→2:  $C_g + 4C_c$ , 1→3:  $C_g + 2C_c$ , 2→3: 0

Total effective capacitance:  $8C_g + 14C_c$

Thus, the total effective capacitance for all the nets for all the possible transitions is  
 $24C_g + 46C_c$



(4) Find a new three-bit encoding of the four values (0, 1, 2, 3) that minimizes the total effective capacitance of the three nets for all possible transitions (Assume  $C_g = C_c$ ). (20 points)

Value	Encoding
0	000
1	100
2	110
3	111

In this case,

$$0 \rightarrow 1: C_g + C_c (\text{Net 1}) + 0 (\text{Net 2}) + 0 (\text{Net 3}) = C_g + C_c$$

$$0 \rightarrow 2: C_g (\text{Net 1}) + C_g + 2C_c (\text{Net 2}) + 0 (\text{Net 3}) = 2C_g + 2C_c$$

$$0 \rightarrow 3: C_g (\text{Net 1}) + C_g (\text{Net 2}) + C_g (\text{Net 3}) = 3C_g$$

$$1 \rightarrow 2: 0 (\text{Net 1}) + C_g + 3C_c (\text{Net 2}) + 0 (\text{Net 3}) = C_g + 3C_c$$


$$1 \rightarrow 3: 0 (\text{Net 1}) + C_g + C_c (\text{Net 2}) + C_g (\text{Net 3}) = 2C_g + C_c$$

$$2 \rightarrow 3: 0 (\text{Net 1}) + 0 (\text{Net 2}) + C_g + 2C_c (\text{Net 3}) = C_g + 2C_c$$

$$\text{Total effective capacitance (for Net 1, 2, and 3): } 20C_g + 18C_c = 38C_g$$
 
## Problem #5 (Testing, 20 points)

The following shows  $H = (a + b) \oplus (c \cdot d) \oplus (\overline{e \oplus f})$ . Answer the following questions.



(1) Find all input vectors that can detect a s-a-0 fault at input  $a$ . (10 points)

$$H \oplus H_f = \{(a + b) \oplus (c \cdot d) \oplus (\overline{e \oplus f})\} \oplus \{(b) \oplus (c \cdot d) \oplus (\overline{e \oplus f})\} = 1$$

Thus,  $a$  should be 1. Then,

$$H(a = 1) \oplus H_f = \{1 \oplus (c \cdot d) \oplus (\overline{e \oplus f})\} \oplus \{(b) \oplus (c \cdot d) \oplus (\overline{e \oplus f})\} = 1$$

Thus,  $b$  should be 0. Then,

$$H(ab = 10) \oplus H_f = \{1 \oplus (c \cdot d) \oplus (\overline{e \oplus f})\} \oplus \{(c \cdot d) \oplus (\overline{e \oplus f})\} = 1$$

Now, it is always true regardless of  $c, d, e, f$ .

Answer:  $(abcdef) = (10XXXX)$  (where X is a don't care).

(2) Find all input vectors that can detect a s-a-1 fault at input  $e$ . (10 points)

$$H \oplus H_f = \{(a + b) \oplus (c \cdot d) \oplus (\overline{e \oplus f})\} \oplus \{(a + b) \oplus (c \cdot d) \oplus (\overline{1 \oplus f})\} = 1$$

$$H \oplus H_f = \{(a + b) \oplus (c \cdot d) \oplus (\overline{e \oplus f})\} \oplus \{(a + b) \oplus (c \cdot d) \oplus f\} = 1$$

Thus,  $e$  should be 0. Then,


$$H(e = 0) \oplus H_f = \{(a + b) \oplus (c \cdot d) \oplus (\overline{f})\} \oplus \{(a + b) \oplus (c \cdot d) \oplus f\} = 1$$

Now, this is always true for any  $(a, b, c, d, f)$ .

Answer:  $(abcdef) = (XXXX0X)$
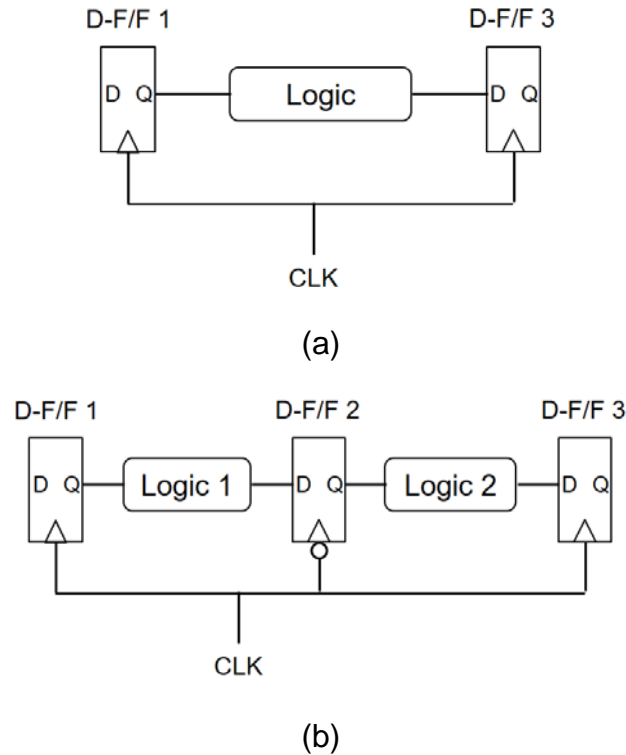
## Problem #6 (Static Timing Analysis, 50 points)

The following shows two pipelining methodologies. Figure (a) shows a logic in a single pipeline stage. Figure (b) shows a partitioned version in which two pipeline stages are cascaded and the flip-flop in the middle is negative-edge-triggered.



### Parameters

- $d_1, d_2, d_3$ : The delay from the clock source to Flip-Flop 1, 2, 3
- $c_1, c_2, c_3$ : Clock-to-Q delay ( $T_{CQ}$ ) of Flip-Flop 1, 2, 3
- $s_1, s_2, s_3$ : Setup time of Flip-Flop 1, 2, 3
- $T_A, T_B$ : Clock period for Figure (a) and (b)
- $N (\gg 1)$ : # instructions to execute
- $T_L$ : The logic delay in Figure (a). In Figure (b), the delay of each logic is  $\frac{T_L}{2}$ .
- Execution time of the system in Figure (a):  $(N + 1) \cdot T_A$
- Execution time of the system in Figure (b):  $(N + 3) \cdot T_B$

For the clock periods, we use the minimum clock periods that satisfy all the setup time constraints. Notice that the clock duty cycle is 50%.

(1) The system in Figure (a) has one setup time constraint. Show the inequality. (10 points)

$$d_1 + c_1 + T_L \leq d_3 + T_A - s_3$$

(2) The system in Figure (b) has two setup time constraints. Show the inequalities. (16 points)

$$d_1 + c_1 + \frac{T_L}{2} \leq d_2 + \frac{T_B}{2} - s_2$$

$$d_2 + \frac{T_B}{2} + c_2 + \frac{T_L}{2} \leq d_3 + T_B - s_3$$

(3) Now, you have execution times for Figure (a) and (b). Answer the following questions. (24 points)


For Figure (a),  $T_A = d_1 + c_1 + T_L - d_3 + s_3$

For Figure (b),  $T_B = d_1 - d_3 + c_1 + c_2 + T_L + s_2 + s_3$

- (a) For Figure (a): If  $d_1$  increases, the execution time increases (**True** / False).
- (b) For Figure (a): If  $c_1$  increases, the execution time increases (**True** / False).
- (c) For Figure (a): If  $T_L$  increases, the execution time increases (**True** / False).
- (d) For Figure (a): If  $d_3$  increases, the execution time increases (True / **False**).
- (e) For Figure (a): If  $s_3$  increases, the execution time increases (**True** / False).
- (f) For Figure (b): If  $d_1$  increases, the execution time increases (**True** / False).
- (g) For Figure (b): If  $c_1$  increases, the execution time increases (**True** / False).
- (h) For Figure (b): If  $T_L$  increases, the execution time increases (**True** / False).
- (i) For Figure (b): If  $d_3$  increases, the execution time increases (True / **False**).
- (j) For Figure (b): If  $s_2$  increases, the execution time increases (**True** / False).
- (k) For Figure (b): If  $s_3$  increases, the execution time increases (**True** / False).
- (l) For Figure (b): If  $c_2$  increases, the execution time increases (**True** / False).
 
## Problem #7 (Static Timing Analysis, 40 points)

The following shows two gates B and C, which are in the middle of a circuit.



“A gate has a (setup or hold) time violation” means that at least one of the paths going through the gate violates given (setup or hold) time constraints.

(1) Is it possible that gate B has a setup-time violation and gate C has a setup-time violation? Explain why.

Yes. The violation path goes through both B and C.

(2) Is it possible that gate B has a setup-time violation and gate C has a hold-time violation? Explain why.

Yes. gate B has a large delay, so it has a setup-time violation, but gate C has a small delay, so it has a hold-time violation (the hold-time violation path comes from the lower path of gate C).

(3) Is it possible that gate B has a hold-time violation and gate C has a setup-time violation? Explain why.

Yes. Both gate B and gate C have short delays, but a gate connected to the output of gate C could have a long delay.

(4) Is it possible that gate B has a hold-time violation and gate C has a hold-time violation? Explain why.

Yes. Both gate B and gate C have very small delays, so a path going through gate B and gate C could violate a hold-time constraint.