

EE434

ASIC and Digital Systems

Final Exam

May 2, 2023. (1:30pm – 3:30pm)

Instructor: Dae Hyun Kim

Name:

WSU ID:


Problem	Points	
1	100	
2	90	
3	100	
4	90	
Total	380	

* Allowed: Books, cheat sheets, class notes, notebooks, calculators, watches, laptops, smartphones, tablet PCs, etc.

* Not allowed: Chatting apps, iMessage, etc. (basically, don't talk to anyone)

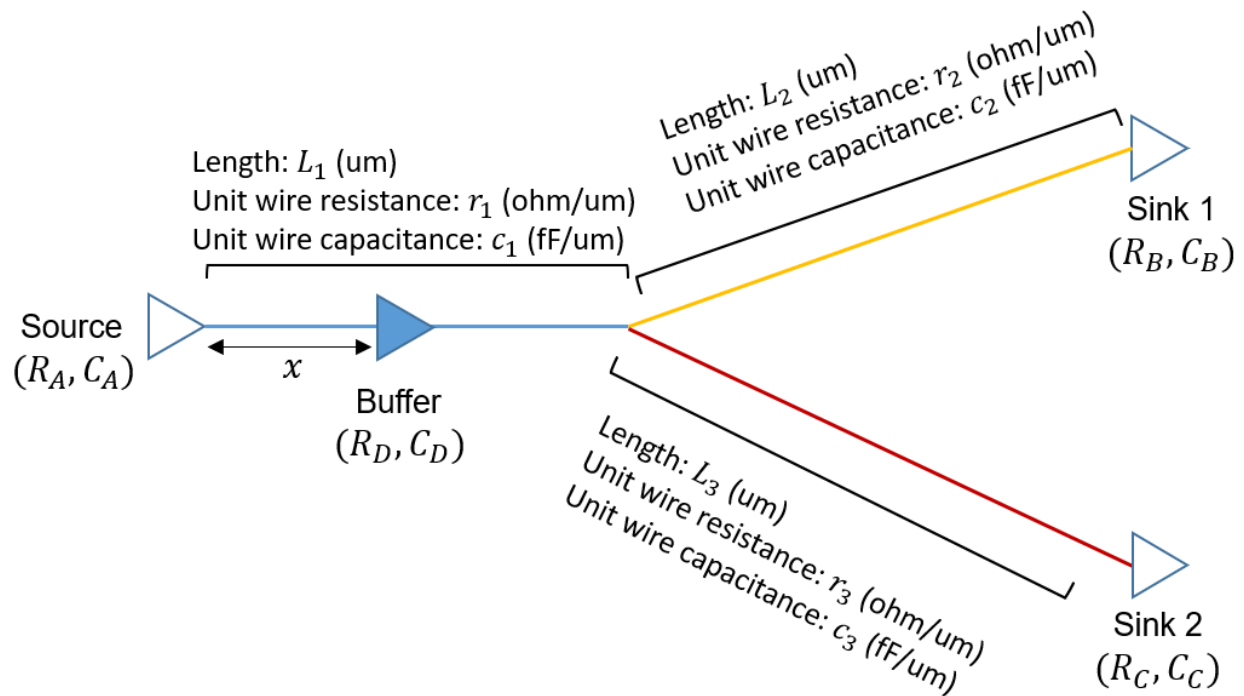Problem #1 (Interconnect Optimization, 100 points)

The following figure shows a net optimized by a buffer.



Notice that (R, C) is the (output resistance, input capacitance) of the corresponding cell. x is the optimal location of the buffer ($0 < x < L_1$). We ignore the internal delay of the buffer. Use the PI model for each wire segment for delay estimation. We want to minimize the delay from the source to Sink 1 in this problem.

(1) Express the delay from the source to Sink 1 before the buffer insertion. (10 points)

$$d_{1,before} =$$

(2) Express the delay from the source to Sink 1 after the buffer insertion. (10 points)

$$d_{1,after} =$$

(3) Assuming the buffer insertion reduces the delay from the source to Sink 1, find the optimal location x of the buffer. (10 points)

(4) Answer the following questions. Correct: +5 points. Wrong: -5 points. Min: 0 points.

- If L_1 increases, then x increases too. (True / False)
- If L_2 increases, then x increases too. (True / False)
- If L_3 increases, then x increases too. (True / False)
- If R_A increases, then x increases too. (True / False)
- If R_D increases, then x increases too. (True / False)
- If C_B increases, then x increases too. (True / False)
- If C_C increases, then x increases too. (True / False)
- If C_D increases, then x increases too. (True / False)


(5) Answer the following questions. Correct: +5 points. Wrong: -5 points. Min: 0 points.

Assume $R_D < R_A$. Assume C_D is negligible.

- If r_1 increases, then x increases too. (True / False)
- If r_2 increases, then x increases too. (True / False)
- If r_3 increases, then x increases too. (True / False)
- If c_1 increases, then x increases too. (True / False)
- If c_2 increases, then x increases too. (True / False)
- If c_3 increases, then x increases too. (True / False)

 Problem #2 (Interconnect Optimization, 90 points)

The following figure shows a net optimized by a buffer.



Notice that (R, C) is the (output resistance, input capacitance) of the corresponding cell. x is the optimal location of the buffer ($0 < x < L_2$). We ignore the internal delay of the buffer. Use the PI model for each wire segment for delay estimation. We want to minimize the delay from the source to Sink 1 in this problem.

(1) Express the delay from the source to Sink 1 after the buffer insertion. (10 points)

$$d_{1,after} =$$

(2) Assuming the buffer insertion reduces the delay from the source to Sink 1, find the optimal location x of the buffer. (10 points)

(3) Answer the following questions. Correct: +5 points. Wrong: -5 points. Min: 0 points.

- If L_1 increases, then x increases too. (True / False)
- If L_2 increases, then x increases too. (True / False)
- If R_A increases, then x increases too. (True / False)
- If R_D increases, then x increases too. (True / False)
- If C_B increases, then x increases too. (True / False)
- If C_D increases, then x increases too. (True / False)

(4) Answer the following questions. Correct: +10 points. Wrong: -10 points. Min: 0 points.

Notice that the optimal location x of the buffer found above (in Problem 2-2) is independent of L_3 and C_C (i.e., x does not have L_3 and C_C). In fact, however, the optimal location x is also dependent on L_3 and C_C . Answer the following questions NOT based on x you found above, BUT based on your intuition and knowledge considering the real-world factors.

- If L_3 increases, then x increases too. (True / False)
- If C_C increases, then x increases too. (True / False)


(5) Answer the following questions. Correct: +5 points. Wrong: -5 points. Min: 0 points.

Assume $R_D < R_A$. Assume C_D is negligible.

- If r_1 increases, then x increases too. (True / False)
- If r_2 increases, then x increases too. (True / False)
- If c_1 increases, then x increases too. (True / False)
- If c_2 increases, then x increases too. (True / False)

 Problem #3 (Interconnect Optimization, 100 points)

The following figure shows a net optimized by three buffers.



Notice that (R, C) is the (output resistance, input capacitance) of the corresponding cell. x, y, z are the optimal locations of Buffer 1, 2, 3, respectively ($0 < x < L_1, 0 < y < L_2, 0 < z < L_3$). We ignore the internal delays of the buffers. We want to minimize both the delay from the source to Sink 1 and the delay from the source to Sink 2 in this problem.

Do not use the mathematical models we studied in the class. Instead, use your intuition to answer the following questions.

(1) Answer the following questions. Correct: +5 points. Wrong: -5 points. Min: 0 points.

- If L_1 increases, then x increases too. (True / False)
- If L_1 increases, then y increases too. (True / False)
- If L_2 increases, then x increases too. (True / False)
- If L_2 increases, then y increases too. (True / False)
- If L_2 increases, then z increases too. (True / False)

(2) Answer the following questions. Correct: +5 points. Wrong: -5 points. Min: 0 points.


- If R_A increases, then x increases too. (True / False)
- If R_A increases, then y increases too. (True / False)
- If R_D increases, then x increases too. (True / False)
- If R_D increases, then y increases too. (True / False)

- If R_E increases, then x increases too. (True / False)
- If R_E increases, then y increases too. (True / False)
- If R_E increases, then z increases too. (True / False)

(3) Answer the following questions. Correct: +5 points. Wrong: -5 points. Min: 0 points.

- If C_D increases, then x increases too. (True / False)
- If C_D increases, then y increases too. (True / False)
- If C_E increases, then x increases too. (True / False)
- If C_E increases, then y increases too. (True / False)
- If C_E increases, then z increases too. (True / False)
- If C_B increases, then x increases too. (True / False)
- If C_B increases, then y increases too. (True / False)
- If C_B increases, then z increases too. (True / False)

Problem #4 (Coupling, 90 points)

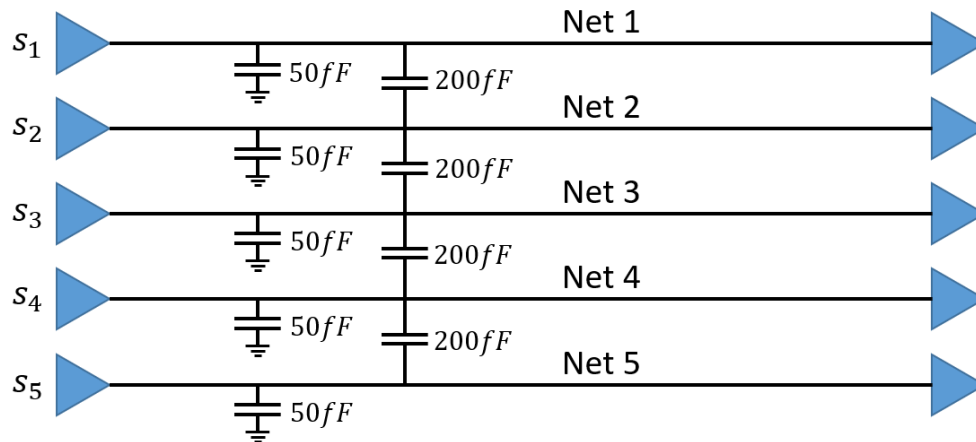

This figure shows a bus composed of five nets. The following shows the data we are going to transfer through the bus:

$$0(\text{initial}) \rightarrow 5 \rightarrow 11 \rightarrow 4$$

We compute the power consumption for a signal transition as follows:

$$P = C_{t,eff} V_{DD}^2$$

where $V_{DD} = 1V$ and $C_{t,eff}$ is the sum of the effective capacitances.

(1) Compute the power consumption of the data transfer using the conventional 5-bit binary codes for the data. (20 points)

(2) Compute the power consumption of the data transfer using the 5-bit forbidden pattern free crosstalk avoidance code. Ignore the power consumption of the encoder/decoder. (20 points)

(3) Let's estimate the efficiency of the forbidden pattern free crosstalk avoidance code (FPF-CAC). (50 points)

- The Fibonacci sequence is defined as follows:
 - $f_1 = 1$
 - $f_2 = 1$
 - $f_{k+2} = f_{k+1} + f_k$
- Complete the following. (10 points)
 - $f_3 =$
 - $f_4 =$
 - $f_5 =$
 - $f_6 =$
 - $f_7 =$
 - $f_8 =$
 - $f_9 =$
 - $f_{10} =$
 - $f_{11} =$
 - $f_{12} =$
 - $f_{13} =$
 - $f_{14} =$
- In page 33 of the interconnect lecture note, the # bits we need to represent a number in FPF-CAC is determined by the “MSB stage”. For a given data (number) v , we should find the max. f_{m+1} satisfying $v \geq f_{m+1}$. For example, if $v = 19$, $f_1 \leq \dots \leq f_7 \leq 19 < f_8$, so the max. f_{m+1} satisfying the above condition is f_7 . Thus, $m + 1 = 7$, so $m = 6$, so we need 6 bits to represent 19 in FPF-CAC.
- The max. data (number) that an m -bit FPF-CAC code can represent is as follows (Complete the following from $m = 7$ to 12) (20 points):
 - $m = 1: 1$
 - $m = 2: 2$
 - $m = 3: 4$
 - $m = 4: 7$
 - $m = 5: 12$
 - $m = 6: 20$
 - $m = 7:$
 - $m = 8:$
 - $m = 9:$
 - $m = 10:$
 - $m = 11:$
 - $m = 12:$
- Similarly, the max. data (number) that an m -bit conventional binary code (e.g., $20 = 10100_2$) can represent is as follows (Complete the following from $m = 7$ to 12) (10 points):
 - $m = 1: 1$
 - $m = 2: 3$

- $m = 3: 7$
- $m = 4: 15$
- $m = 5: 31$
- $m = 6: 63$
- $m = 7:$
- $m = 8:$
- $m = 9:$
- $m = 10:$
- $m = 11:$
- $m = 12:$
- Thus, the efficiency is estimated as follows (Complete the following from $m = 7$ to 12) (10 points):
 - $m = 1: 1/1 = 1.0$
 - $m = 2: 2/3 = 0.67$
 - $m = 3: 4/7 = 0.57$
 - $m = 4: 7/15 = 0.47$
 - $m = 5: 12/31 = 0.39$
 - $m = 6: 20/63 = 0.32$
 - $m = 7:$
 - $m = 8:$
 - $m = 9:$
 - $m = 10:$
 - $m = 11:$
 - $m = 12:$