

**EE434**

**ASIC and Digital Systems**

**Midterm Exam 2**

**Apr. 7, 2023. (2:10pm – 3pm)**

**Instructor: Dae Hyun Kim**

**Name:**

**WSU ID:**


Problem	Points	
1	10	
2	10	
3	10	
4	10	
5	20	
6	20	
7	10	
Total	90	

**Problem #1 (Static CMOS, 10 points)**

Design the following function (draw a transistor-level schematic) using the static CMOS logic design methodology. Available input:  $A, B, C, D, E$ . Try to minimize the # TRs.


$$Y = A \cdot B \cdot C + \bar{D} \cdot \bar{E}$$
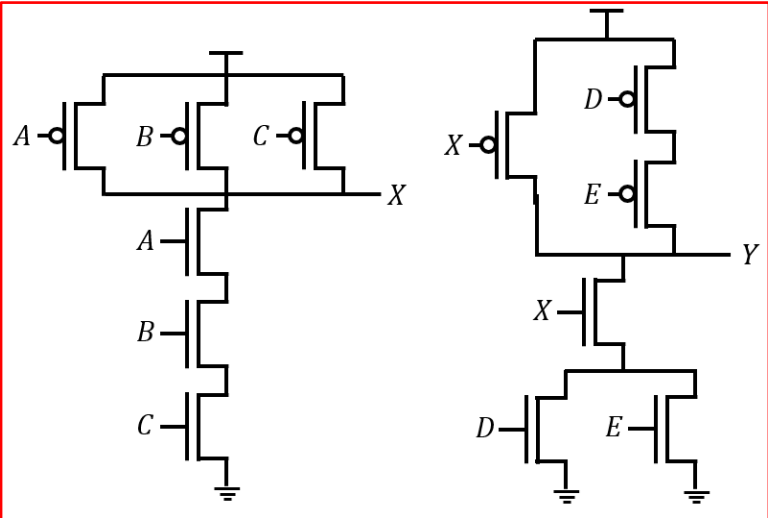
$$Y = \overline{A \cdot B \cdot C + \bar{D} \cdot \bar{E}} = \overline{A \cdot B \cdot C} \cdot (D + E)$$


 
## Problem #2 (Static CMOS, 10 points)

The following schematic shows the NFET network of a static CMOS logic gate.




Express the output  $Y$  as a function of the input signals.

$$Y = \overline{A(CH + (DF + E)G) + B(H + C(DF + E)G)}$$

 
### Problem #3 (Static CMOS, 10 points)

The following schematic shows the NFET network of a static CMOS logic gate.



Design a PFET network for the logic gate. Try to minimize # TRs.


$$Y = \overline{A(D + CE) + B(E + CD)}$$

 



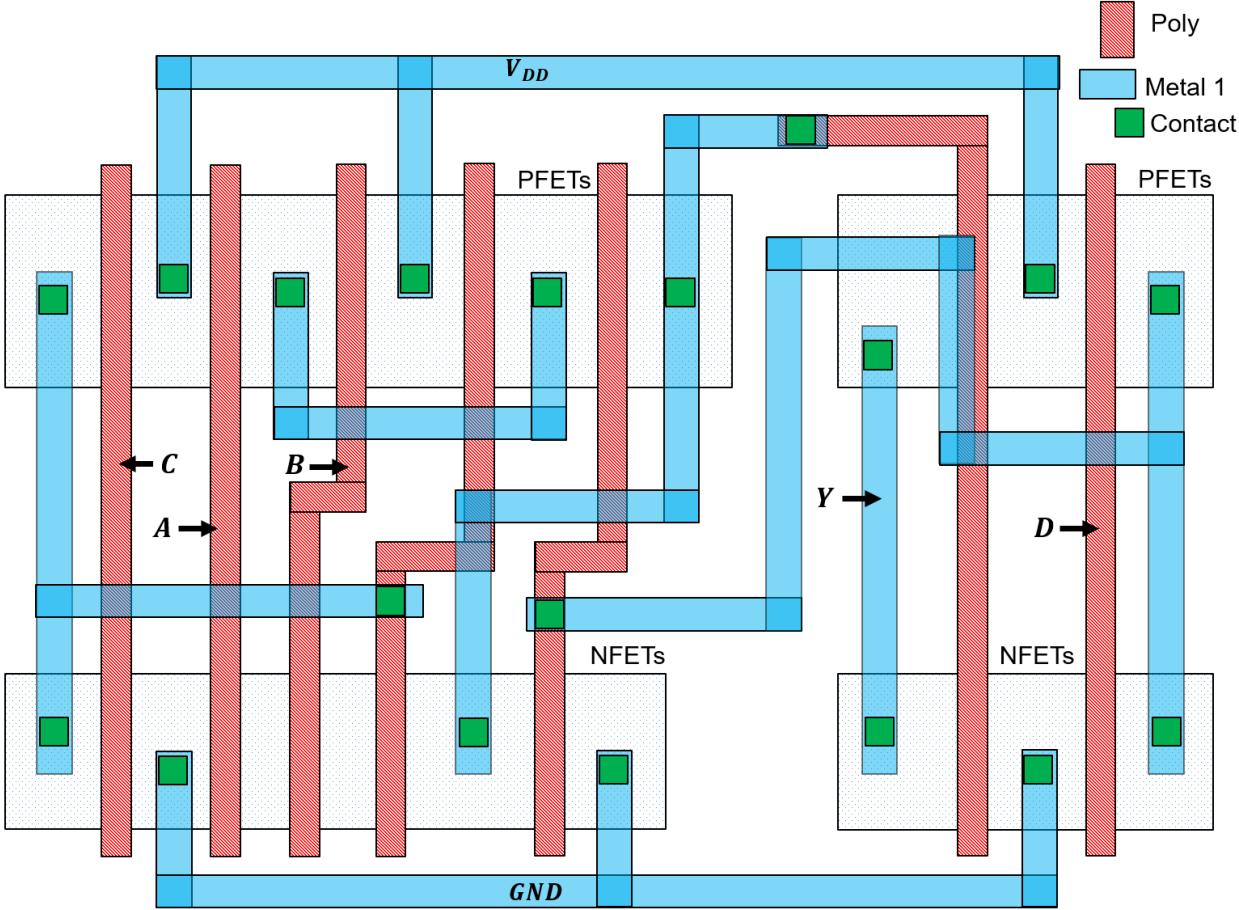**Problem #5 (Layout, 20 points)**


Express the output  $Y$  as a Boolean function of the input signals,  $A$ ,  $B$ ,  $C$ , and  $D$ .



$$Y = ABC\bar{C} + \bar{D}$$

 
### Problem #6 (DC Analysis, 20 points)

The following shows a design of  $Y = A \cdot B + C$ .



$W_X$  is the width of the transistor X. Assume that the transistors have some proper widths.

 - (1) Draw its DC characteristic curve for  $B = 1, C = 0$ , and  $A$  switches from 0 to 1. Just a rough sketch will be accepted. (10 points)




(2) Answer the following questions. Correct: +2 points, Wrong: -2 points, No answer: 0.  
Min: 0 points.

- If  $W_{N,A}$  goes up, then the DC curve is shifted upward always at  $V_A = \frac{V_{DD}}{2}$ . (True / False)
- If  $W_{N,C}$  goes up, then the DC curve is shifted upward always at  $V_A = \frac{V_{DD}}{2}$ . (True / False)
- If  $W_{P,A}$  goes up, then the DC curve is shifted downward always at  $V_A = \frac{V_{DD}}{2}$ . (True / False)
- If  $W_{P,C}$  goes up, then the DC curve is shifted downward always at  $V_A = \frac{V_{DD}}{2}$ . (True / False)
- If  $W_{N,Y}$  goes up, then the DC curve is shifted upward always at  $V_A = \frac{V_{DD}}{2}$ . (True / False)


 
### Problem #7 (Sequential Logic, 10 points)

What does the following circuit do? Describe its functionality in as much detail as possible. (D: data input. CK: clock. Q: data output)



Positive-edge-triggered D FF