

**EE434**

**ASIC and Digital Systems**

**Midterm Exam**

**Mar. 6, 2024. (2:10pm – 3pm)**

**Instructor: Dae Hyun Kim**

**Name:**

**WSU ID:**

Problem	Points	
1	10	
2	20	
3	10	
4	10	
5	10	
6	10	
7 (Bonus)	10	
Total	80	

## Problem #1 (15 points)

Answer the following questions for a digital system that has multiple pipeline stages.  
Correct: +2 points. Wrong: -2 points. No answer: 0 points. Minimum: 0 points.

(Notice: Suppose a problem says, "If A happens, then B happens. (True / False)". In this case, if B can happen in some cases and cannot happen in some other cases, the answer is False. In other words, the answer is True only if B always happens when A happens.

For example, "If  $x > 0$  and  $y > 10$ , then  $y > x$ ." This is false because  $y < x$  can also happen (e.g.,  $x=20$ ,  $y=15$ ).

On the other hand, "If  $x*y > 0$  and  $y > 0$ , then  $x > 0$ ." This is true because if  $y > 0$ , then dividing both sides of  $x*y > 0$  by  $y$  leads to  $x > 0$ .

(1) Assume  $WNS < 0$  and  $TNS < 0$ . If you reduce the delay of a net in the system, WNS goes up. (True / False)

(2) Assume  $WNS < 0$  and  $TNS < 0$ . If you reduce the delay of a net in the system, TNS goes up. (True / False)


(3) Assume  $WNS = 0$ . If the delay of a gate goes up, then WNS goes down. (True / False)

(4) Suppose all the paths in the pipeline stages have setup time violations. If the delay of a gate goes down, then WNS goes up. (True / False)

(5) Suppose all the paths in the pipeline stages have setup time violations. If the delay of a gate goes down, then TNS goes up. (True / False)
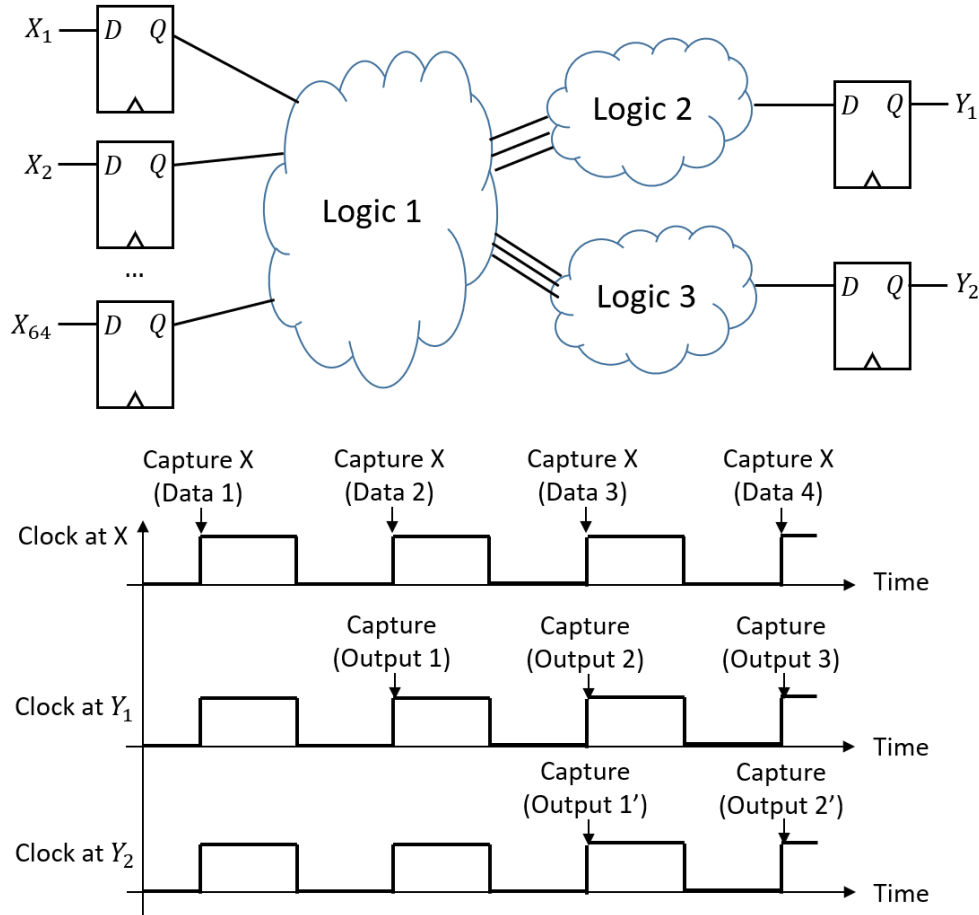
## Problem #2 (20 points)

The following figure shows a pipeline stage.  $X$  is the input and  $Y$  is the output.  $Y$  has two output signals,  $Y_1$  and  $Y_2$ . The system spec is as follows:



- Data is fed into the system every cycle (captured by the FFs on the left).
- Each data set "Data #" generates two outputs, "Output #" and "Output #'".
  - Output # is generated by Logic 1 and Logic 2. This is captured by  $Y_1$ .
  - Output #' is generated by Logic 1 and Logic 3. This is captured by  $Y_2$ .
- $X - Y_1$  is a single-cycle path as shown in the waveform above.
- $X - Y_2$  is a multi-cycle path (two cycles) as shown in the waveform above.

Parameters:

- $L_{i-k}$ : the logic delay from input  $X_i$  to output  $Y_k$  (e.g.,  $L_{64-2}$  means the logic delay from input  $X_{64}$  to output  $Y_2$ )
- $s$ : setup time of a flip-flop
- $h$ : hold time of a flip-flop
- $x$ : delay from the clock source to the clock pin of a flip-flop

- $c$ : clk-to-Q delay of a flip-flop
- $T_{CLK}$ : clock period
- $MIN, MAX$ : MIN, MAX operators

(1) Show all the setup time inequalities for the design (5 points). (Use the MIN, MAX operators.)

$$x + c + MAX(L_{1-1}, \dots, L_{64-1}) \leq x + T_{CLK} - s$$

$$x + c + MAX(L_{1-2}, \dots, L_{64-2}) \leq x + 2 \cdot T_{CLK} - s$$

(2) Show all the hold time inequalities for the design (5 points). (Use the MIN, MAX operators.)

$$x + c + MIN(L_{1-1}, \dots, L_{64-1}) \geq x + h$$

$$x + c + MIN(L_{1-2}, \dots, L_{64-2}) \geq x + 2 \cdot T_{CLK} + h$$

Answer the following questions for the figure above. Correct: +2 points, Wrong: -2 points, No answer: 0. Min: 0 points.

(3) Assume  $WNS < 0$ . In this case, if  $s$  goes up, WNS goes down. (True / False)

(4) Assume  $WNS < 0$ . In this case, if the delay of Logic 1 goes up, WNS goes down. (True / False)

(5) Assume  $WNS < 0$ . In this case, if the delay of Logic 3 goes up, WNS goes down. (True / False)

Answer the following questions for the figure above. Correct: +2 points, Wrong: -2 points, No answer: 0. Min: 0 points.

(6) Assume  $TNS < 0$ . In this case, if  $s$  goes up, TNS goes down. (True / False)

(7) Assume  $TNS < 0$ . In this case, if the delay of Logic 1 goes up, TNS goes down. (True / False)

(8) Assume  $TNS < 0$ . In this case, if the delay of Logic 2 goes up, TNS goes down. (True / False)

### Problem #3 (Static CMOS, 10 points)

Design the following function (draw a transistor-level schematic) using the static CMOS logic design methodology. Available input:  $A, B, C, D$ . Try to minimize the # TRs.

$$Y = A \cdot \overline{B \oplus (C + D)}$$

10 points if # TRs  $\leq 20$ . 7 points if  $20 < \# \text{ TRs} \leq 22$ . 5 points if # TRs  $> 22$ .

$$Y = \overline{\overline{A} + \{B \oplus (C + D)\}} = \overline{\overline{A} + \{B \cdot \overline{C} + \overline{D} + \overline{B} \cdot (C + D)\}} = \overline{\overline{A} + B \cdot \overline{C} \cdot \overline{D} + \overline{B} \cdot (C + D)}$$

This uses 7 NFETs and 7 PFETs (and 4 NFETs and 4 PFETs for the four inverters), which is a total of 11 NFETs and 11 PFETs.

$$\overline{\overline{A} + \{B \cdot \overline{C} + \overline{D} + \overline{B} \cdot (C + D)\}} = \overline{\overline{A} + B \cdot X + \overline{B} \cdot \overline{X}} \text{ (where } X = \overline{C + D}\text{)}$$


In this case, we design  $X$  and use an inverter to generate  $\overline{X}$  (3 NFETs + 3 PFETs).

Then, design the above expression, which requires 5 NFETs and 5 PFETs (and 2 NFETs and 2 PFETs for the two inverters to generate  $\overline{A}$  and  $\overline{B}$ ), which is a total of 10 NFETs and 10 PFETs.
 
## Problem #4 (TR Sizing, 10 points)

$R_n$  is the resistance of a 1X NFET (whose width is  $w_{min}$ ). “ $h \times$ ” for a TR means that the width of the TR is  $h \cdot w_{min}$ .

The following figure shows the NFET network of a static CMOS logic gate.



Notice that  $L, M, N$  are positive integer constants.

Timing constraint:  $\tau_f \leq R_n C$  ( $\tau_f$  is the worst-case fall delay).

Find the optimal sizes of the TRs that minimize the total transistor width. (Just saying “3X for all the TRs” will get 0 points. You should optimize the total width.)

$$a_1 = \dots = a_L = aX. b_1 = \dots = b_M = bX. c_1 = \dots = c_N = cX.$$

Constraints:  $\frac{1}{a} + \frac{1}{b} + \frac{1}{c} = 1$ . Minimize  $f = L \cdot a + M \cdot b + N \cdot c$ .

Let  $\frac{1}{a} = x, \frac{1}{b} = y, \frac{1}{c} = z$ . Then,  $x + y + z = 1$ . Minimize  $g = \frac{L}{x} + \frac{M}{y} + \frac{N}{z}$ .

$$\frac{\partial g}{\partial x} = -\frac{L}{x^2} + \frac{N}{z^2} = 0. \quad \frac{\partial g}{\partial y} = -\frac{M}{y^2} + \frac{N}{z^2} = 0. \quad \text{Thus, } x = \sqrt{\frac{L}{N}} \cdot z. \quad y = \sqrt{\frac{M}{N}} \cdot z.$$


From the constraint,  $z \left( \sqrt{\frac{L}{N}} + \sqrt{\frac{M}{N}} + 1 \right) = 1$ , so

$$z = \frac{\sqrt{N}}{\sqrt{L} + \sqrt{M} + \sqrt{N}}. \quad x = \frac{\sqrt{L}}{\sqrt{L} + \sqrt{M} + \sqrt{N}}. \quad y = \frac{\sqrt{M}}{\sqrt{L} + \sqrt{M} + \sqrt{N}}.$$

$$a_1 = \dots = a_L = \frac{\sqrt{L} + \sqrt{M} + \sqrt{N}}{\sqrt{L}} \times. \quad b_1 = \dots = b_M = \frac{\sqrt{L} + \sqrt{M} + \sqrt{N}}{\sqrt{M}} \times. \quad c_1 = \dots = c_N = \frac{\sqrt{L} + \sqrt{M} + \sqrt{N}}{\sqrt{N}} \times.$$
 
### Problem #5 (Analysis, 10 points)

Express the output  $Y$  as a Boolean function of the input signals (A, B, C, D, E, F, G, H).



$$\bar{Y} = A \cdot (B \cdot D + B \cdot F \cdot G \cdot H + C \cdot H + C \cdot G \cdot F \cdot D) + E \cdot (G \cdot H + G \cdot C \cdot B \cdot D + F \cdot D + F \cdot B \cdot C \cdot H)$$

## Problem #6 (STA, 10 points)

For the setup-time analysis, we use the slack = required time – arrival time. We can define a similar metric for the hold-time analysis as follows:

$$\text{slack (for hold time)} = \text{arrival time} - \text{required time}.$$

Notice that a hold-time violation occurs when the delay (arrival time) of a signal is too small. Thus, if we use the definition above, a positive slack means no hold-time violation and a negative slack means a hold-time violation. We can define WNS and TNS in the same way.

Answer the following questions for the hold-time analysis of a pipeline stage (between two flip-flop stages). Correct: +2 points. Wrong: -2 points. No answer: 0 points.

Minimum: 0 points.

(1) Assume  $WNS < 0$  and  $TNS < 0$ . If you increase the delay of a net in the critical path, WNS goes up. (True / False)

(2) Assume  $WNS < 0$  and  $TNS < 0$ . If you increase the delay of a gate in the critical path, TNS goes up. (True / False)

(3) Assume  $WNS < 0$ . In this case, can “ $WNS = TNS$ ” happen? (i.e., can WNS be equal to TNS?) (Yes / No)

(4) Assume  $TNS < 0$ . In this case, can “ $TNS < WNS$ ” happen? (Yes / No)

(5) Suppose  $T_{CLK} > 2 \cdot (T_S + T_H)$  where  $T_{CLK}$  is the clock period,  $T_S$  is the setup time of a FF, and  $T_H$  is the hold time of a FF. In this case, can a path have both setup-time and hold-time violations? (Yes / No)




## Problem #7 (TR Sizing, 10 points, Bonus)

$R_n$  is the resistance of a 1X NFET (whose width is  $w_{min}$ ). “ $h \times$ ” for a TR means that the width of the TR is  $h \cdot w_{min}$ .

The following figure shows the NFET network of a static CMOS logic gate  $Y =$
 
$$\overline{(x_{1,1} + \dots + x_{1,n_1}) \cdot (x_{2,1} + \dots + x_{2,n_2}) \cdot \dots \cdot (x_{p,1} + \dots + x_{p,n_p})}.$$



Notice that  $p, n_1, n_2, \dots, n_p$  are all positive integer constants. For example,  $p = 3, n_1 = L, n_2 = M, n_3 = N$  for Problem #4. This problem is a generalization of Problem #4.

Timing constraint:  $\tau_f \leq R_n C$  ( $\tau_f$  is the worst-case fall delay).

Find the optimal sizes of the TRs that minimize the total transistor width. (Just saying “ $n_p \times$  for all the TRs” will get 0 points. You should optimize the total width.)

$$x_{1,1} = \dots = x_{1,n_1} = a_1 X.$$

$$x_{2,1} = \dots = x_{2,n_2} = a_2 X.$$

...

$$x_{p,1} = \dots = x_{p,n_p} = a_p X.$$

Constraints:  $\frac{1}{a_1} + \frac{1}{a_2} + \dots + \frac{1}{a_p} = 1$ . Minimize  $f = n_1 \cdot a_1 + n_2 \cdot a_2 + \dots + n_p \cdot a_p$ .

Let  $\frac{1}{a_1} = c_1, \frac{1}{a_2} = c_2, \dots, \frac{1}{a_p} = c_p$ . Then,  $c_1 + c_2 + \dots + c_p = 1$ . Minimize  $g = \frac{n_1}{c_1} + \frac{n_2}{c_2} + \dots + \frac{n_p}{c_p}$ .

$$\frac{\partial g}{\partial c_k} = -\frac{n_k}{c_k^2} + \frac{n_p}{c_p^2} = 0 \text{ (for } k = 1, 2, \dots, p-1).$$

Thus,  $c_k = \sqrt{\frac{n_k}{n_p}} \cdot c_p$ .

From the constraint,  $\left( \sqrt{\frac{n_1}{n_p}} + \sqrt{\frac{n_2}{n_p}} + \dots + \sqrt{\frac{n_p}{n_p}} \right) \cdot c_p = 1$ .

Thus,  $c_p = \frac{\sqrt{n_p}}{\sqrt{n_1} + \sqrt{n_2} + \dots + \sqrt{n_p}}$ . Similarly,  $c_k = \frac{\sqrt{n_k}}{\sqrt{n_1} + \sqrt{n_2} + \dots + \sqrt{n_p}}$ .

Answer:

$$x_{1,1} = \dots = x_{1,n_1} = \frac{\sqrt{n_1} + \sqrt{n_2} + \dots + \sqrt{n_p}}{\sqrt{n_1}} \times$$

$$x_{2,1} = \dots = x_{2,n_2} = \frac{\sqrt{n_1} + \sqrt{n_2} + \dots + \sqrt{n_p}}{\sqrt{n_2}} \times$$

...

$$x_{p,1} = \dots = x_{p,n_p} = \frac{\sqrt{n_1} + \sqrt{n_2} + \dots + \sqrt{n_p}}{\sqrt{n_p}} \times$$