

EE434

ASIC and Digital Systems

Midterm Exam

Mar. 6, 2024. (2:10pm – 3pm)

Instructor: Dae Hyun Kim

Name:

WSU ID:

Problem	Points	
1	10	
2	20	
3	10	
4	10	
5	10	
6	10	
7 (Bonus)	10	
Total	80	

Problem #1 (10 points)

Answer the following questions for a digital system that has multiple pipeline stages.
Correct: +2 points. Wrong: -2 points. No answer: 0 points. Minimum: 0 points.

(Notice: Suppose a problem says, "If A happens, then B happens. (True / False)". In this case, if B can happen in some cases and cannot happen in some other cases, the answer is False. In other words, the answer is True only if B always happens when A happens.

For example, "If $x > 0$ and $y > 10$, then $y > x$." This is false because $y < x$ can also happen (e.g., $x=20$, $y=15$).

On the other hand, "If $x*y > 0$ and $y > 0$, then $x > 0$." This is true because if $y > 0$, then dividing both sides of $x*y > 0$ by y leads to $x > 0$.

(1) Assume $WNS < 0$ and $TNS < 0$. If you reduce the delay of a net in the system, WNS goes up. (True / False)

(2) Assume $WNS < 0$ and $TNS < 0$. If you reduce the delay of a net in the system, TNS goes up. (True / False)


(3) Assume $WNS = 0$. If the delay of a gate goes up, then WNS goes down. (True / False)

(4) Suppose all the paths in the pipeline stages have setup time violations. If the delay of a gate goes down, then WNS goes up. (True / False)

(5) Suppose all the paths in the pipeline stages have setup time violations. If the delay of a gate goes down, then TNS goes up. (True / False)

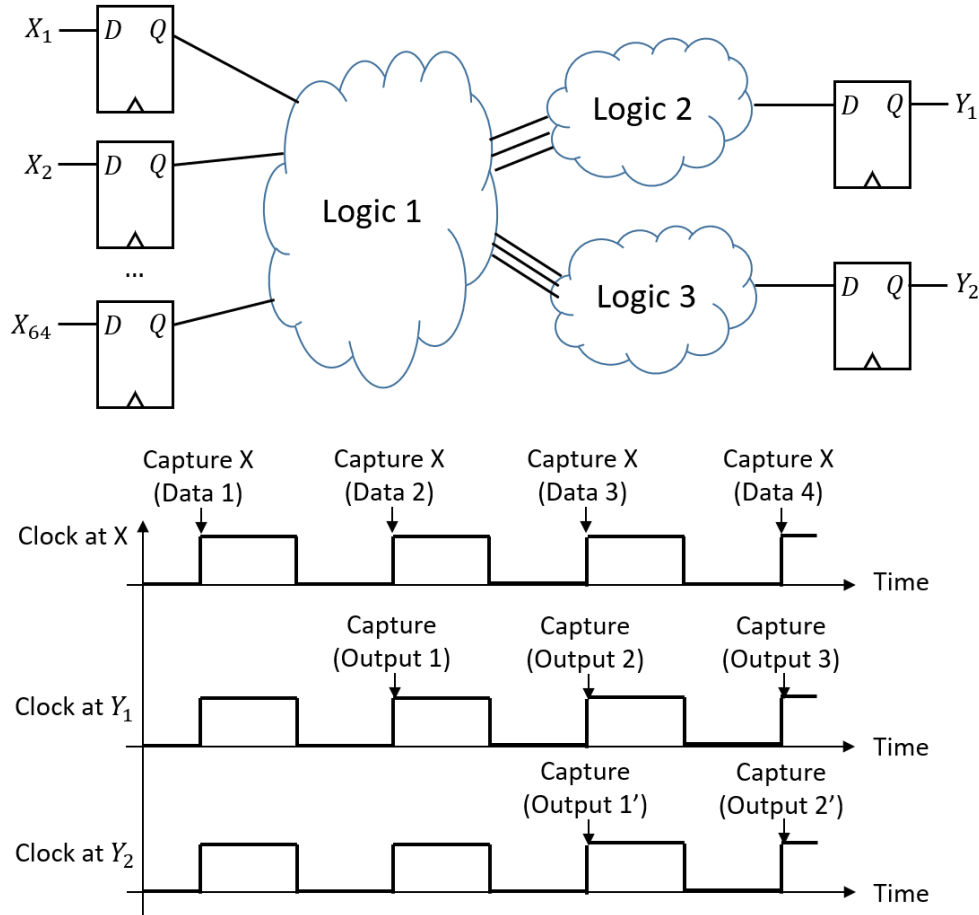Problem #2 (20 points)

The following figure shows a pipeline stage. X is the input and Y is the output. Y has two output signals, Y_1 and Y_2 . The system spec is as follows:



- Data is fed into the system every cycle (captured by the FFs on the left).
- Each data set "Data #" generates two outputs, "Output #" and "Output #'".
 - Output # is generated by Logic 1 and Logic 2. This is captured by Y_1 .
 - Output #' is generated by Logic 1 and Logic 3. This is captured by Y_2 .
- $X - Y_1$ is a single-cycle path as shown in the waveform above.
- $X - Y_2$ is a multi-cycle path (two cycles) as shown in the waveform above.

Parameters:

- L_{i-k} : the logic delay from input X_i to output Y_k (e.g., L_{64-2} means the logic delay from input X_{64} to output Y_2)
- s : setup time of a flip-flop
- h : hold time of a flip-flop
- x : delay from the clock source to the clock pin of a flip-flop

- c : clk-to-Q delay of a flip-flop
- T_{CLK} : clock period
- MIN, MAX : MIN, MAX operators

(1) Show all the setup time inequalities for the design (4 points). (Use the MIN, MAX operators.)

(2) Show all the hold time inequalities for the design (4 points). (Use the MIN, MAX operators.)

Answer the following questions for the figure above. Correct: +2 points, Wrong: -2 points, No answer: 0. Min: 0 points.

(3) Assume $WNS < 0$. In this case, if s goes up, WNS goes down. (True / False)

(4) Assume $WNS < 0$. In this case, if the delay of Logic 1 goes up, WNS goes down. (True / False)

(5) Assume $WNS < 0$. In this case, if the delay of Logic 3 goes up, WNS goes down. (True / False)

Answer the following questions for the figure above. Correct: +2 points, Wrong: -2 points, No answer: 0. Min: 0 points.

(6) Assume $TNS < 0$. In this case, if s goes up, TNS goes down. (True / False)

(7) Assume $TNS < 0$. In this case, if the delay of Logic 1 goes up, TNS goes down. (True / False)

(8) Assume $TNS < 0$. In this case, if the delay of Logic 2 goes up, TNS goes down. (True / False)

Problem #3 (Static CMOS, 10 points)

Design the following function (draw a transistor-level schematic) using the static CMOS logic design methodology. Available input: A, B, C, D . Try to minimize the # TRs.


$$Y = A \cdot \overline{\{B \oplus (C + D)\}}$$

10 points if # TRs ≤ 20 . 7 points if $20 < \text{\# TRs} \leq 22$. 5 points if # TRs > 22 .

 Problem #4 (TR Sizing, 10 points)

R_n is the resistance of a 1X NFET (whose width is w_{min}). “ $h \times$ ” for a TR means that the width of the TR is $h \cdot w_{min}$.

The following figure shows the NFET network of a static CMOS logic gate.



Notice that L, M, N are positive integer constants.

Timing constraint: $\tau_f \leq R_n C$ (τ_f is the worst-case fall delay).

Find the optimal sizes of the TRs that minimize the total transistor width. (Just saying “3X for all the TRs” will get 0 points. You should optimize the total width.)

Problem #6 (STA, 10 points)

For the setup-time analysis, we use the slack = required time – arrival time. We can define a similar metric for the hold-time analysis as follows:

$$\text{slack (for hold time)} = \text{arrival time} - \text{required time}.$$

Notice that a hold-time violation occurs when the delay (arrival time) of a signal is too small. Thus, if we use the definition above, a positive slack means no hold-time violation and a negative slack means a hold-time violation. We can define WNS and TNS in the same way.

Answer the following questions for the hold-time analysis of a pipeline stage (between two flip-flop stages). Correct: +2 points. Wrong: -2 points. No answer: 0 points.

Minimum: 0 points.

(1) Assume $WNS < 0$ and $TNS < 0$. If you increase the delay of a net in the critical path, WNS goes up. (True / False)

(2) Assume $WNS < 0$ and $TNS < 0$. If you increase the delay of a gate in the critical path, TNS goes up. (True / False)

(3) Assume $WNS < 0$. In this case, can “ $WNS = TNS$ ” happen? (i.e., can WNS be equal to TNS?) (Yes / No)

(4) Assume $TNS < 0$. In this case, can “ $TNS < WNS$ ” happen? (Yes / No)


(5) Suppose $T_{CLK} > 2 \cdot (T_S + T_H)$ where T_{CLK} is the clock period, T_S is the setup time of a FF, and T_H is the hold time of a FF. In this case, can a path have both setup-time and hold-time violations? (Yes / No)

Problem #7 (TR Sizing, 10 points, Bonus)

R_n is the resistance of a 1X NFET (whose width is w_{min}). “ $h \times$ ” for a TR means that the width of the TR is $h \cdot w_{min}$.

The following figure shows the NFET network of a static CMOS logic gate $Y =$
 
$$\overline{(x_{1,1} + \dots + x_{1,n_1}) \cdot (x_{2,1} + \dots + x_{2,n_2}) \cdot \dots \cdot (x_{p,1} + \dots + x_{p,n_p})}.$$



Notice that p, n_1, n_2, \dots, n_p are all positive integer constants. For example, $p = 3, n_1 = L, n_2 = M, n_3 = N$ for Problem #4. This problem is a generalization of Problem #4.

Timing constraint: $\tau_f \leq R_n C$ (τ_f is the worst-case fall delay).

Find the optimal sizes of the TRs that minimize the total transistor width. (Just saying “ $n_p \times$ for all the TRs” will get 0 points. You should optimize the total width.)