

**EE466**

**VLSI System Design**

**Final Exam**

**Dec. 13, 2021. (7:30pm – 9:30pm)**

**Instructor: Dae Hyun Kim ([daehyun@eecs.wsu.edu](mailto:daehyun@eecs.wsu.edu))**

**Name:**

**WSU ID:**

Problem	Points	
1	30	
2	20	
3	80	
4	20	
5	20	
6	30	
Total	200	


\* Allowed: Textbooks, cheat sheets, class notes, notebooks, calculators, watches

\* Not allowed: Electronic devices (smart phones, tablet PCs, laptops, etc.) except calculators and watches


### Problem #1 (DC Analysis, 30 points)

We will compare the following two buffers, BUF1 and BUF2.


BUF1: (composed of two inverters,  $G_1$  and  $G_2$ . Their DC curves are shown below.)

 

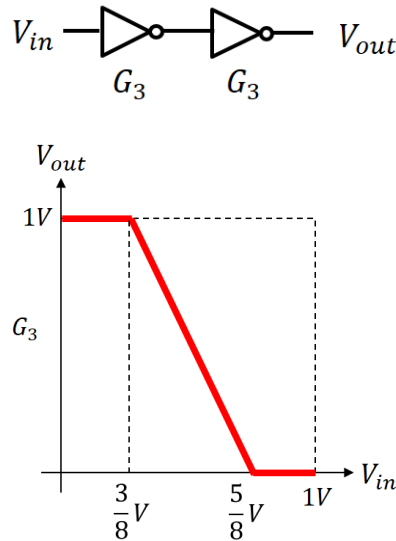BUF2: (composed of two identical inverters,  $G_3$ . Its DC curve is shown below.)



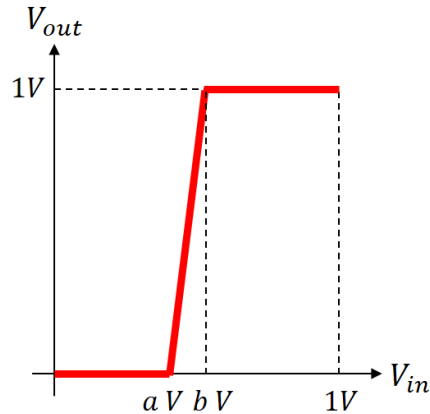Notice that the DC curves of the buffers will look like this:




Answer the following questions.

(1) Find  $a$  (V) and  $b$  (V) for BUF1. (10 points)

(2) Find  $a$  (V) and  $b$  (V) for BUF2. (10 points)

 (3) The following figure shows two configurations of two cascaded buffers.  $n(t)$  is a noise source. Answer the following questions (Correct: +2 points, Wrong: -2 points, no answer: 0 points, minimum: 0 points, maximum: 10 points).



(3-a) If  $n(t)$  is +0.4V, configuration (a) has a signal inversion problem for  $V_{in} = 0V$ . (True / False)

(3-b) If  $n(t)$  is +0.4V, configuration (b) has a signal inversion problem for  $V_{in} = 0V$ . (True / False)


(3-c) If  $n(t)$  is +0.6V, configuration (a) has a signal inversion problem for  $V_{in} = 0V$ . (True / False)

(3-d) If  $n(t)$  is +0.6V, configuration (b) has a signal inversion problem for  $V_{in} = 0V$ . (True / False)

(3-e) If  $n(t)$  is -0.4V, configuration (b) has a signal inversion problem for  $V_{in} = 1V$ . (True / False)
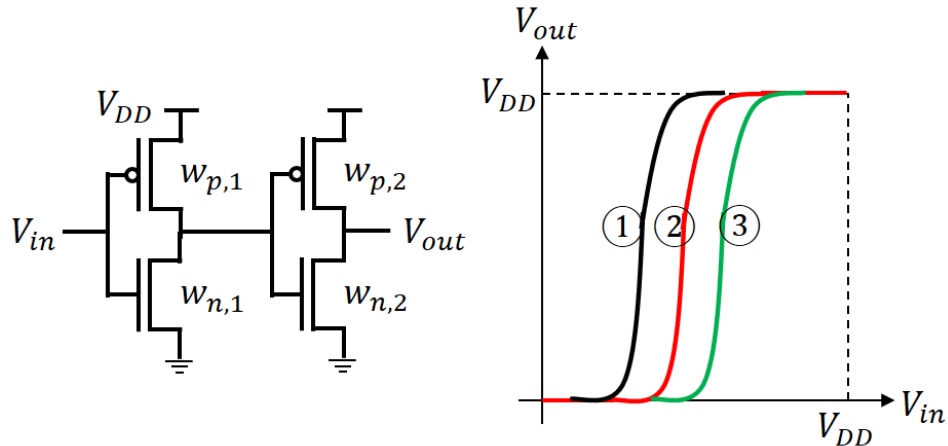
## Problem #2 (DC Analysis, 20 points)

The following figure shows a buffer composed of two inverters (left) and its DC characteristic curve (② in the right figure) for  $w_{n,1} = w_{n,2} = w_1$  and  $w_{p,1} = w_{p,2} = w_2$ .




Answer the following questions (Correct: +5 points, Wrong: -2 points, no answer: 0 points, minimum: 0 points, maximum: 20 points).

- (1) If we increase  $w_{n,1}$ , the DC curve is shifted from ② to ①. (True / False)
- (2) If we increase  $w_{n,2}$ , the DC curve is shifted from ② to ①. (True / False)
- (3) If we increase  $w_{p,1}$ , the DC curve is shifted from ② to ①. (True / False)
- (4) If we increase  $w_{p,2}$ , the DC curve is shifted from ② to ①. (True / False)
 
### Problem #3 (D Flip Flop, 80 points)

The following schematic implements a D FF. Answer the following questions. Assume that all the setup and hold times are positive ( $\geq 0$ ). You can also assume that  $T_{CLK}$  is the clock period and the duty cycle is 50% (i.e., the clock is high for  $\frac{T_{CLK}}{2}$  and low for  $\frac{T_{CLK}}{2}$ .)



- (1) Is it positive-edge-triggered or negative-edge-triggered or dual-edge-triggered or positive-level-sensitive or negative-level-sensitive? (5 points)
  
- (2) What does signal  $A$  do? Describe its function in detail. (5 points)
  
- (3) Estimate the setup time of the FF for  $D = 0$ . (10 points)
  
- (4) Estimate the setup time of the FF for  $D = 1$ . (10 points)
  
- (5) Estimate the hold time of the FF for  $D = 0$ . (10 points)
  
- (6) Estimate the hold time of the FF for  $D = 1$ . (10 points)

(7) True/False questions. Correct: +5 points, Wrong: -5 points, no answer: 0 points, minimum: 0 points.

(a) If the width of  $N_1$  goes up, the fall delay of the FF goes down. (True / False)

(b) If the width of  $N_2$  goes up, the fall delay of the FF goes down. (True / False)

(c) If the width of  $N_3$  goes up, the fall delay of the FF goes down. (True / False)

(d) If the width of  $N_4$  goes up, the fall delay of the FF goes down. (True / False)

(e) If the width of  $P_1$  goes up, the rise delay of the FF goes down. (True / False)

(f) If the width of  $P_2$  goes up, the rise delay of the FF goes down. (True / False)

#### **Problem #4 (Logic Design, 20 points)**

Design the following logic gate using NFETs and PFETs. Try to minimize the # TRs.  
Available input signals:  $A, B, C$

$$Y = A \cdot B + (A \oplus C)$$


≤18 TRs: 20 points. ≤20 TRs: 16 points. ≤22 TRs: 12 points. Otherwise: 10 points.

### Problem #5 (Transmission Gates, 20 points).

Design the following logic gate using transmission gates (TGs).

$$Y = A \cdot B + D \cdot (E \oplus F)$$

 
Available inputs:  $A, B, D, E, F$  (and 0 and 1). Use the following symbols for the TGs.



$\leq 10$  TGs: 20 points.  $\leq 12$  TGs: 17 points.  $\leq 14$  TGs: 15 points. Otherwise: 12 points.


 
## Problem #6 (Ring Oscillator, 30 points)



The figure shown above implements a ring oscillator. It consists of five inverters and two ideal switches. First,  $S_1$  is closed and  $S_2$  is open so that  $c_1 = 0, c_2 = 1, c_3 = 0, c_4 = 1$ , and  $c_5 = 0$ . Then, we open  $S_1$  and close  $S_2$  so that we can initiate the oscillation. In this case,  $c_5 = 0$  is fed into  $X_1$ , so  $c_1$  becomes 1,  $c_2 = 0, \dots, c_5 = 1$ . This can be used for a clock source as shown above.

Parameters/Constants:

- $p_k$ : The delay of the PFET of Inverter  $X_k$ . For example,  $p_2$  is the delay of the PFET of  $X_2$ , which is actually the time spent to charge node  $c_2$  to  $V_{DD}$ .
- $n_k$ : The delay of the NFET of Inverter  $X_k$ . For example,  $n_4$  is the delay of the NFET of  $X_4$ , which is actually the time spent to discharge node  $c_4$  to 0.
- Ignore all the parasitic RC.

Answer the following questions.

(1) Express the period ( $T_{CLK}$ ) of the CLK signal as a function of  $p_1, p_2, \dots, p_5, n_1, \dots, n_5$ . (10 points)

(2) The duty cycle of a clock signal is defined as the time it is high (logical value 1) divided by its period. For example, if a clock signal is high for 0.25ns and low for 0.75ns, the duty cycle is  $0.25\text{ns} / (0.25\text{ns} + 0.75\text{ns}) = 0.25$  (or 25%).

Find the duty cycle of the clock signal generated by the ring oscillator (Express the duty cycle using the constants). (10 points)

(3) If net  $c_4$  (instead of net  $c_5$ ) is used for the clock source, what is the duty cycle of the new clock signal? Express it as a function of the given constants. (10 points)

