

**EE466**  
**VLSI System Design**

**Final Exam**

**Oct. 17, 2024. (4:20pm – 5:35pm)**

**Instructor: Dae Hyun Kim ([daehyun.kim@wsu.edu](mailto:daehyun.kim@wsu.edu))**

**Name:**

**WSU ID:**

Problem	Points	
1	110	
2	10	
3	100	
Total	220	

\* Allowed: Textbooks, cheat sheets, class notes, notebooks, calculators, watches

\* Not allowed: Electronic devices (smart phones, tablet PCs, laptops, etc.) except calculators and watches


## Problem #1 (DFF, 110 points)

The following schematic shows a D flip flop. Answer the following questions.

- Assume that all the setup and hold times are positive ( $\geq 0$ ).
- If a net (node) does not have  $C_{\#}$ , then you can ignore its capacitance.
- Use  $R_{\#}$  for the resistance of the corresponding NFET, PFET, or TG.



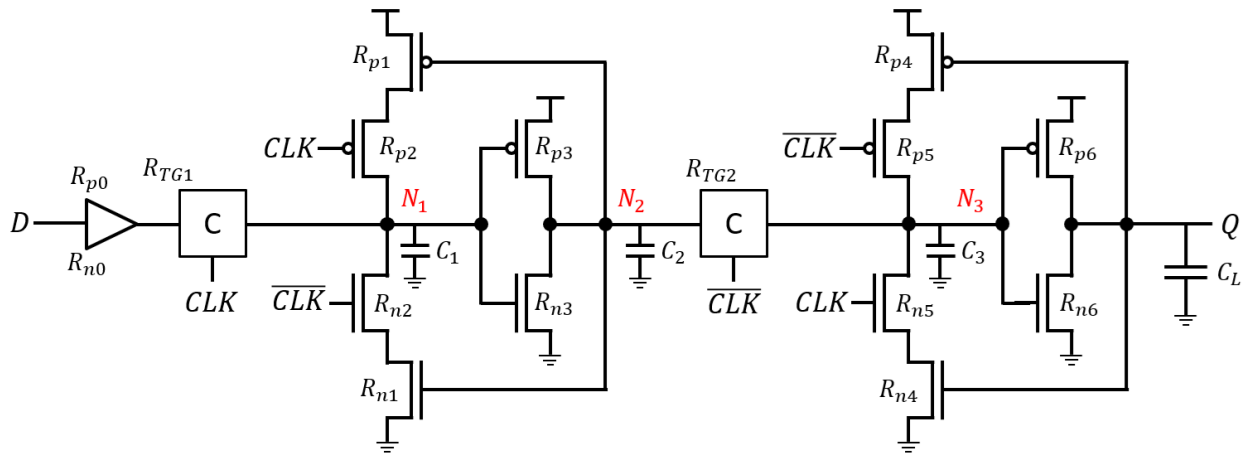- $M$  is a transmission gate (TG) and turned on when  $M$  is high (1).
- For the input buffer, you can think of it as a circuit having a PFET network (whose resistance is  $R_{p0}$ ) and an NFET network (resistance:  $R_{n0}$ ).



(1) Is it positive-edge-triggered or negative-edge-triggered? (10 points)

When  $CLK=1$ ,  $N_1 = D$  and  $N_2 = \bar{D}$ . When  $CLK$  goes low,  $TG2$  is turned on and  $N_3 = N_2 = \bar{D}$ , so  $Q = D$ . Thus, this is a negative-edge-triggered D FF.

(2) Estimate the fall delay of the FF. (10 points)


Suppose  $D=0$ ,  $Q=1$ , and  $CLK=1$ .  $N_1 = 0$ .  $N_2 = 1$ .  $N_3 = 0$ . When  $CLK$  goes low,  $TG2$  is turned on and  $N_3$  is pulled up by  $R_{p3}$  (delay =  $(R_{p3} + R_{TG2}) \cdot C_3$ ). Then,  $Q$  is discharged by  $R_{n6}$  (delay =  $R_{n6} \cdot C_L$ ).

Answer:  $(R_{p3} + R_{TG2}) \cdot C_3 + R_{n6} \cdot C_L$ .

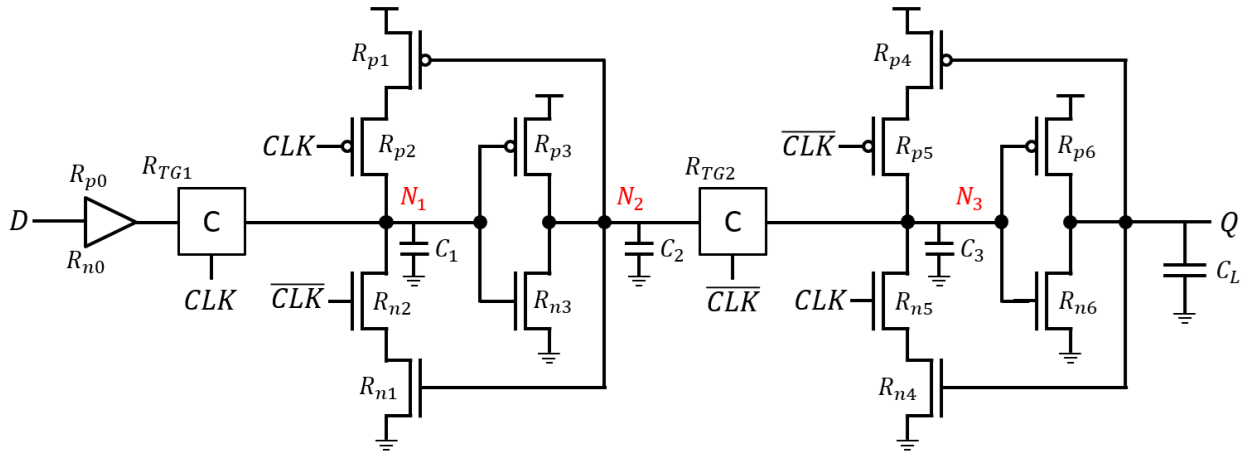(3) Estimate the rise delay of the FF. (10 points)

$D=1$ ,  $Q=0$ ,  $CLK=1$ .  $N_1 = 1$ .  $N_2 = 0$ .  $N_3 = 1$ . When  $CLK$  goes low,  $TG2$  is turned on and  $N_3$  is discharged by  $R_{n3}$  (delay =  $(R_{n3} + R_{TG2}) \cdot C_3$ ). Then,  $Q$  is charged by  $R_{p6}$  (delay =  $R_{p6} \cdot C_L$ ).

Answer:  $(R_{n3} + R_{TG2}) \cdot C_3 + R_{p6} \cdot C_L$ .



(4) Estimate the setup time of the FF for  $D = 0$ . (10 points)

$D=1, Q=1, CLK=1. N_1 = 1, N_2 = 0, N_3 = 0$ . If  $D$  becomes 0, then  $N_1 = 0$ , then  $N_2 = 1$ .  $CLK$  can go low only after  $N_2 = 1$ . The discharging time for  $N_1$  is  $(R_{n0} + R_{TG1}) \cdot C_1$ . The charging time for  $N_2$  is  $R_{p3} \cdot C_2$ .

Answer:  $(R_{n0} + R_{TG1}) \cdot C_1 + R_{p3} \cdot C_2$ .

(5) Estimate the setup time of the FF for  $D = 1$ . (10 points)

$D=0, Q=0, CLK=1. N_1 = 0, N_2 = 1, N_3 = 1$ . If  $D$  becomes 1, then  $N_1 = 1$ , then  $N_2 = 0$ .  $CLK$  can go low only after  $N_2 = 0$ . The charging time for  $N_1$  is  $(R_{p0} + R_{TG1}) \cdot C_1$ . The discharging time for  $N_2$  is  $R_{n3} \cdot C_2$ .

Answer:  $(R_{p0} + R_{TG1}) \cdot C_1 + R_{n3} \cdot C_2$ .


(6) Estimate the hold time of the FF for  $D = 0$ . (10 points)

$D=0, Q=1, CLK=1. N_1 = 0, N_2 = 1, N_3 = 0$ . If  $CLK$  goes low, then  $TG1$  is turned off. Then, even if  $D$  changes,  $Q$  is not affected by that. Thus, the hold time is zero (or just to be safe, some small value.)

Answer: 0 or delta.

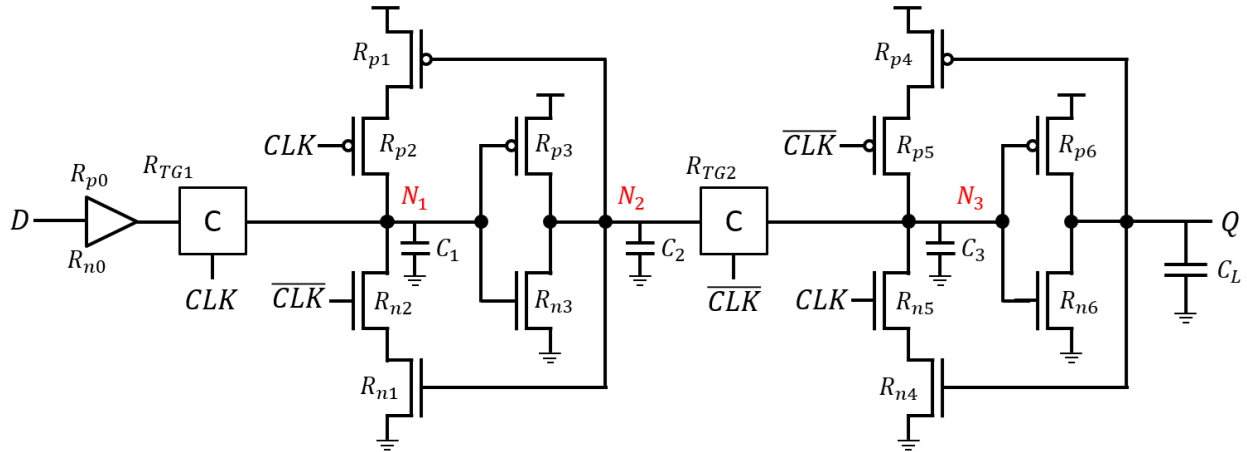
(7) Estimate the hold time of the FF for  $D = 1$ . (10 points)

Answer: 0 or delta (for the same reason as in (6)).



 (8) Estimate the followings. Assume that  $Q=0$  at time  $t_1$ . (20 points)

- Energy delivered from the DC source to the FF between  $t_1$  and  $t_2$ .
- Energy dissipated in the FF between  $t_1$  and  $t_2$ .



$D=0, Q=0. N_1 = 0, N_2 = 1, N_3 = 1.$

First, D goes high, so  $N_1$  is charged and  $N_2$  is discharged.

When CLK goes low,  $N_3$  is discharged and Q is charged.


When CLK goes high, nothing happens.

Answer:

- Energy delivered from the DC source to the FF:  $(C_1 + C_L) \cdot V_{DD}^2.$
- Energy dissipated in the FF:  $\frac{1}{2}(C_1 + C_2 + C_3 + C_L) \cdot V_{DD}^2$

 (9) Estimate the followings. Assume that  $Q=1$  at time  $t_3$ . (20 points)

- Energy delivered from the DC source to the FF between  $t_3$  and  $t_4$ .
- Energy dissipated in the FF between  $t_3$  and  $t_4$ .



$D=1, Q=1. N_1 = 1, N_2 = 0, N_3 = 0.$

First,  $D$  goes low, so  $N_1$  is discharged and  $N_2$  is charged.

When  $CLK$  goes low,  $N_3$  is charged and  $Q$  is discharged.

When  $CLK$  goes high, nothing happens.

Answer:


a) Energy delivered from the DC source to the FF:  $(C_2 + C_3) \cdot V_{DD}^2.$

b) Energy dissipated in the FF:  $\frac{1}{2}(C_1 + C_2 + C_3 + C_L) \cdot V_{DD}^2$
 
## Problem #2 (Logic Design, 10 points)


Design  $Y = \bar{A} + \bar{B} \cdot (C + \bar{D})$ . Available input:  $A, B, C, D$ . Use the static CMOS design methodology (draw a schematic). (10 points)


$$Y = \overline{A \cdot \{B + \bar{C} \cdot D\}}$$



### Problem #3 (DFF, 100 points)

The following schematic shows a positive-edge-triggered D flip flop. Answer the following questions.

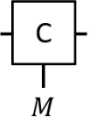
- Assume that all the setup and hold times are positive ( $\geq 0$ ).
  - If a net (node) does not have  $C_{\#}$ , then you can ignore its capacitance.
  - Use  $R_{\#}$  for the resistance of the corresponding NFET, PFET, or TG.
- 
- $M$  is a transmission gate (TG) and turned on when M is high (1).
  - For the input buffer, you can think of it as a circuit having a PFET network (whose resistance is  $R_{p0}$ ) and an NFET network (resistance:  $R_{n0}$ ).
  - When you analyze the delay/setup/hold times, ignore the R and C of the cross-coupled inverters.

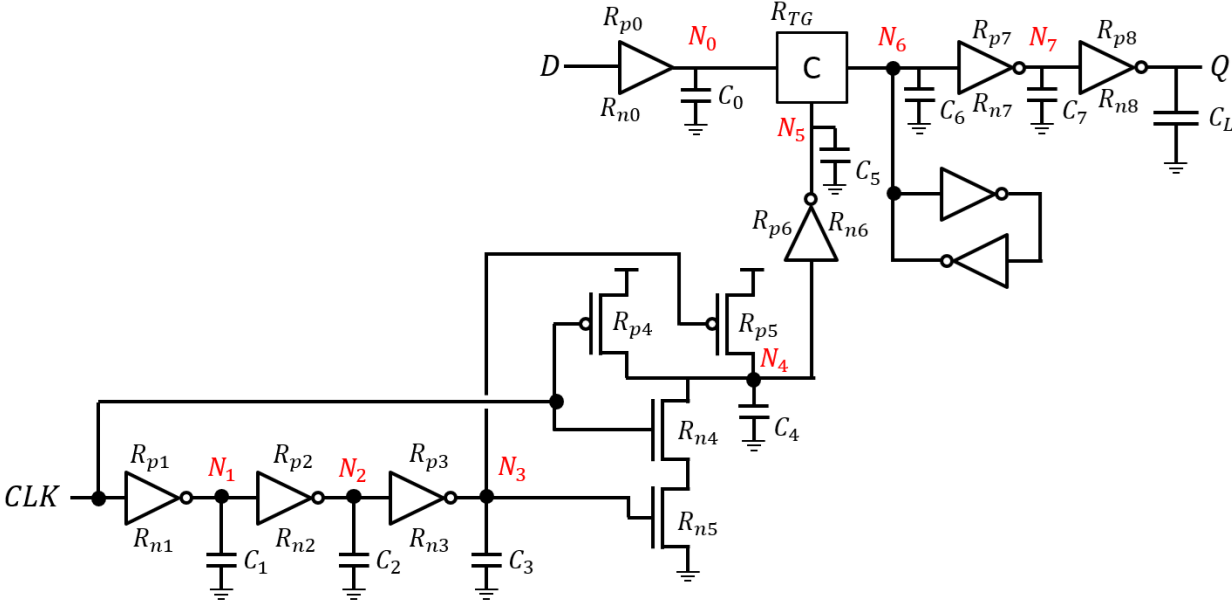

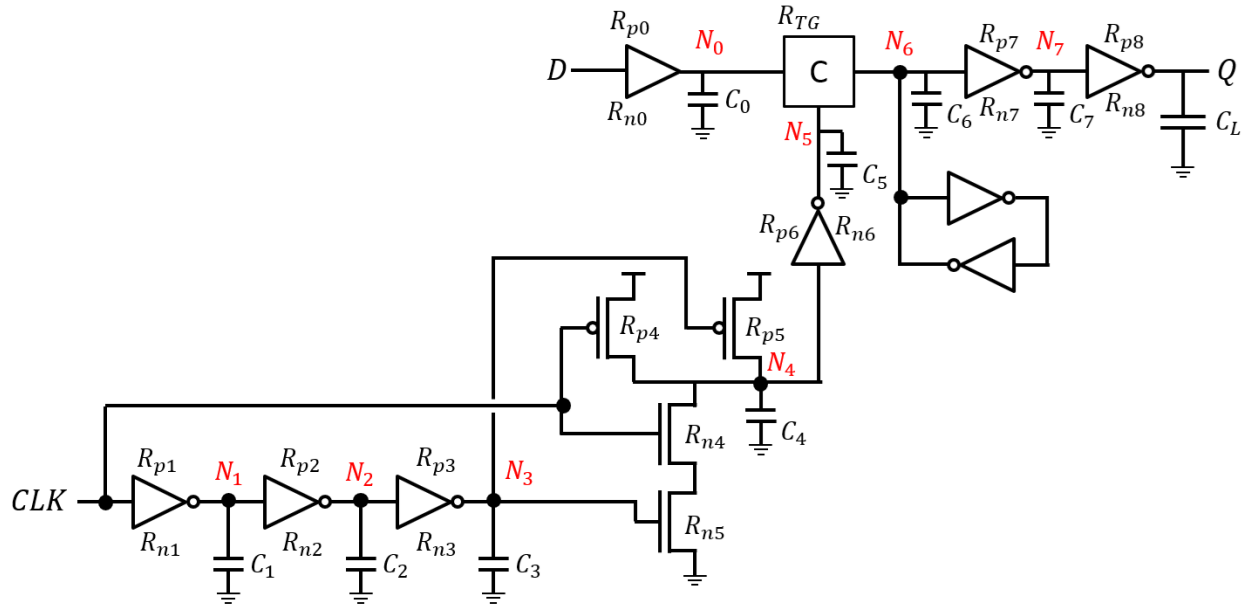(1) Estimate the fall delay of the FF. (10 points)

Suppose  $D=0$ ,  $Q=1$ , and  $CLK=0$ .  $N_1 = 1$ .  $N_2 = 0$ .  $N_3 = 1$ . When CLK goes high,  $N_4$  is discharged and  $N_5 = 1$ , so the TG is turned on. Then,  $N_6$  is discharged,  $N_7$  is charged, and Q is discharged.

Answer:  $(R_{n4} + R_{n5})C_4 + R_{p6} \cdot C_5 + (R_{n0} + R_{TG})C_6 + R_{p7} \cdot C_7 + R_{n8} \cdot C_L$ .



(2) Estimate the rise delay of the FF. (10 points)

Suppose  $D=1$ ,  $Q=0$ , and  $CLK=0$ .  $N_1 = 1$ .  $N_2 = 0$ .  $N_3 = 1$ . When  $CLK$  goes high,  $N_4$  is discharged and  $N_5 = 1$ , so the TG is turned on. Then,  $N_6$  is charged,  $N_7$  is discharged, and  $Q$  is charged.

Answer:  $(R_{n4} + R_{n5})C_4 + R_{p6} \cdot C_5 + (R_{p0} + R_{TG})C_6 + R_{n7} \cdot C_7 + R_{p8} \cdot C_L$ .

(3) Estimate the setup time of the FF for  $D = 0$ . (10 points)

Suppose  $D=1$ ,  $Q=1$ , and  $CLK=0$ .  $N_1 = 1$ .  $N_2 = 0$ .  $N_3 = 1$ . When  $CLK$  goes high,  $N_4$  is discharged and  $N_5 = 1$ , so the TG is turned on.  $N_0$  must be 0 before the TG is turned on (otherwise it might not be possible to discharge  $N_6$  in time). Discharging  $N_0$  takes  $R_{n0}C_0$ . If this is shorter than the time taken to turn on the TG, then the setup time is 0.

However, if it is longer than the time taken to turn on the TG, the difference between the two is the setup time.

Answer:  $\text{Max}(0, R_{n0} \cdot C_0 - (R_{n4} + R_{n5})C_4 + R_{p6} \cdot C_5)$ .

(4) Estimate the setup time of the FF for  $D = 1$ . (10 points)


Answer:  $\text{Max}(0, R_{p0} \cdot C_0 - (R_{n4} + R_{n5})C_4 + R_{p6} \cdot C_5)$ .

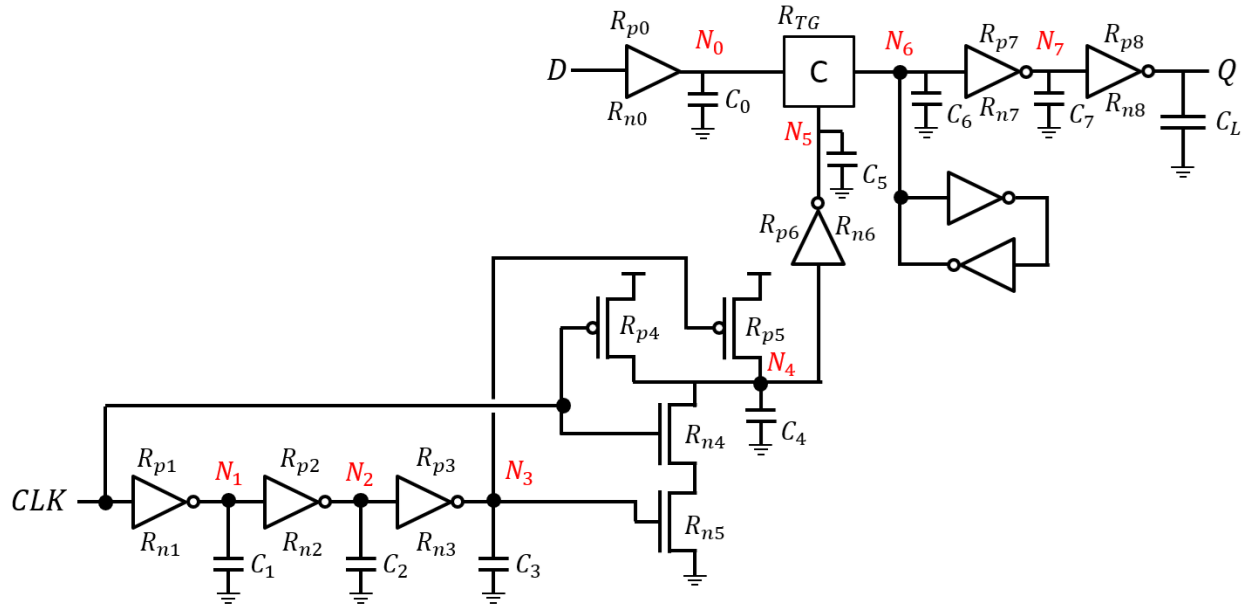(5) Estimate the hold time of the FF for  $D = 0$ . (10 points)

$D$  is allowed to change arbitrarily after the TG is turned off.

Answer:  $R_{n1} \cdot C_1 + R_{p2} \cdot C_2 + R_{n3} \cdot C_3 + R_{p5} \cdot C_4 + R_{n6} \cdot C_5$






(6) Estimate the hold time of the FF for  $D = 1$ . (10 points)

Answer:  $R_{n1} \cdot C_1 + R_{p2} \cdot C_2 + R_{n3} \cdot C_3 + R_{p5} \cdot C_4 + R_{n6} \cdot C_5$

(7) Estimate the followings. Assume that  $Q=0$  at time  $t_1$ . (20 points)

 - c) Energy delivered from the DC source to the FF between  $t_1$  and  $t_2$ .
- d) Energy dissipated in the FF between  $t_1$  and  $t_2$ .



$D=0, Q=0. N_1 = 1, N_2 = 0, N_3 = 1, N_4 = 1, N_5 = 0, N_0 = 0, N_6 = 0, N_7 = 1$ .

First, D goes high, so  $N_0$  is charged.

When CLK goes high,  $N_4$  is discharged,  $N_5$  is charged,  $N_6$  is charged,  $N_7$  is discharged, and Q is charged. At the same time,  $N_1$  is discharged,  $N_2$  is charged, and  $N_3$  is discharged, so  $N_4$  is charged,  $N_5$  is discharged.

When CLK goes low,  $N_1 = 1, N_2 = 0$ , and  $N_3 = 1$ .

Answer:


- a) Energy delivered from the DC source to the FF:

$$(C_0 + C_5 + C_6 + C_L + C_2 + C_4 + C_1 + C_3) \cdot V_{DD}^2 = (C_0 + C_1 + C_2 + C_3 + C_4 + C_5 + C_6 + C_L) \cdot V_{DD}^2.$$

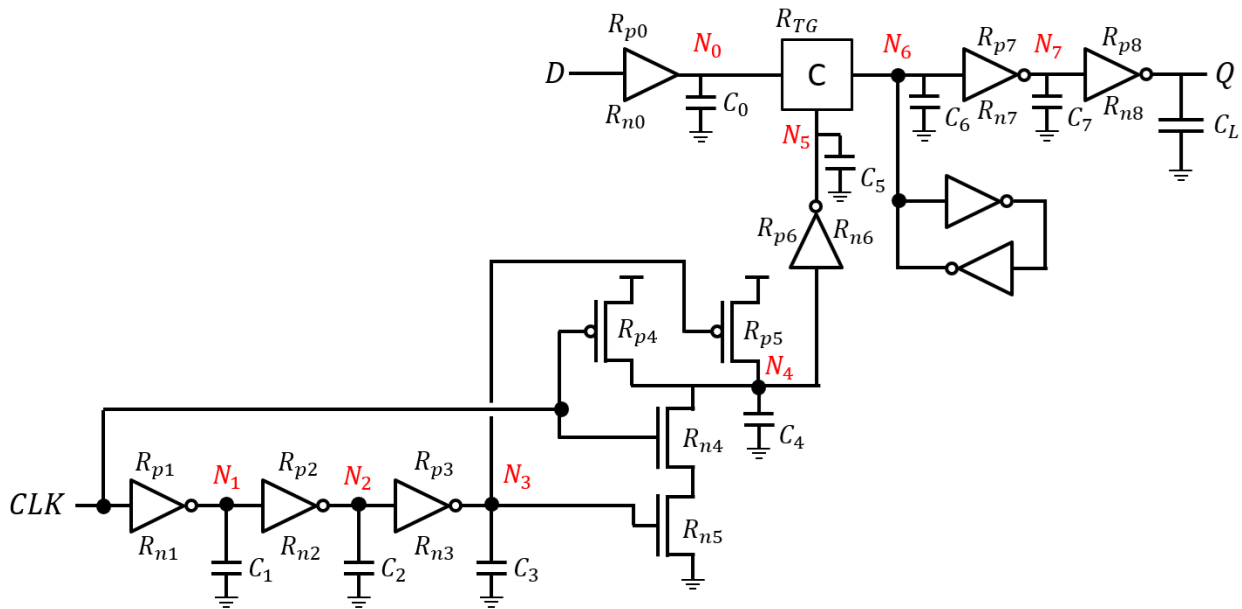b) Energy dissipated in the FF:


$$\frac{1}{2} (C_0 + C_4 + C_5 + C_6 + C_7 + C_L + C_1 + C_2 + C_3 + C_4 + C_5 + C_1 + C_2 + C_3) \cdot V_{DD}^2$$

$$= \frac{1}{2} (C_0 + 2C_1 + 2C_2 + 2C_3 + 2C_4 + 2C_5 + C_6 + C_7 + C_L) \cdot V_{DD}^2$$



(8) Estimate the followings. Assume that  $Q=1$  at time  $t_3$ . (20 points)

 - c) Energy delivered from the DC source to the FF between  $t_3$  and  $t_4$ .
- d) Energy dissipated in the FF between  $t_3$  and  $t_4$ .



$D=1, Q=1. N_1 = 1, N_2 = 0, N_3 = 1, N_4 = 1, N_5 = 0, N_0 = 1, N_6 = 1, N_7 = 0.$

First, D goes low, so  $N_0$  is discharged.

When CLK goes high,  $N_4$  is discharged,  $N_5$  is charged,  $N_6$  is discharged,  $N_7$  is charged, and Q is discharged. At the same time,  $N_1$  is discharged,  $N_2$  is charged, and  $N_3$  is discharged, so  $N_4$  is charged,  $N_5$  is discharged.

When CLK goes low,  $N_1 = 1$ ,  $N_2 = 0$ , and  $N_3 = 1$ .

Answer:

a) Energy delivered from the DC source to the FF:

$$(C_5 + C_7 + C_2 + C_4 + C_1 + C_3) \cdot V_{DD}^2 = (C_1 + C_2 + C_3 + C_4 + C_5 + C_7) \cdot V_{DD}^2.$$

b) Energy dissipated in the FF:

$$\begin{aligned} \frac{1}{2}(C_0 + C_4 + C_5 + C_6 + C_7 + C_L + C_1 + C_2 + C_3 + C_4 + C_5 + C_1 + C_2 + C_3) \cdot V_{DD}^2 \\ = \frac{1}{2}(C_0 + 2C_1 + 2C_2 + 2C_3 + 2C_4 + 2C_5 + C_6 + C_7 + C_L) \cdot V_{DD}^2 \end{aligned}$$