



Review – Logic Circuits

Dae Hyun Kim

EECS
Washington State University

Boolean Logic/Algebra

- Deals with two values (0, 1)
- NOT (one input, one output)
 - NOT 0 = 1
 - NOT 1 = 0
- AND (two inputs, one output)
 - 0 AND 0 = 0
 - 0 AND 1 = 0
 - 1 AND 0 = 0
 - 1 AND 1 = 1
- OR (two inputs, one output)
 - 0 OR 0 = 0
 - 0 OR 1 = 1
 - 1 OR 0 = 1
 - 1 OR 1 = 1

Boolean Logic/Algebra

- Laws

$$A \cdot B = B \cdot A$$

$$A \cdot A = A$$

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A + B = B + A$$

$$A + A = A$$

$$A + 0 = A$$

$$A + 1 = 1$$

$$A \cdot (B + C) = (A \cdot B) + (A \cdot C) = A \cdot B + A \cdot C$$

$$A + (B \cdot C) = (A + B) \cdot (A + C)$$

$$A \cdot \bar{A} = 0$$

$$A + \bar{A} = 1$$

$$\bar{\bar{A}} = A$$

Boolean Logic/Algebra

- De Morgan's Law

$$\overline{F(x_1, \dots, x_n, AND, OR)} = F(\overline{x_1}, \dots, \overline{x_n}, OR, AND)$$

$$\begin{aligned}\overline{A \cdot B} &= \bar{A} + \bar{B} \\ \overline{A + B} &= \bar{A} \cdot \bar{B}\end{aligned}$$

$$\overline{A \cdot (B + C + D \cdot E \cdot (F + G))} = \bar{A} + (\bar{B} \cdot \bar{C} \cdot (\bar{D} + \bar{E} + (\bar{F} \cdot \bar{G})))$$


- XOR, XNOR

$$Y = A \oplus B = A \cdot \bar{B} + \bar{A} \cdot B$$

$$Y = \overline{A \oplus B} = A \cdot B + \bar{A} \cdot \bar{B}$$

$$A \oplus B = B \oplus A$$


Systems

 

Basic Gates (Cells) and Signals

- We can categorize gates based on
 - (# inputs, # outputs)
 - Logic types (combinational, sequential)
 - ...
- Signals
 - 0, 1, Z (high-impedance), X (don't-care), U (unknown)
 - In general, 0 and 1 are always available as primary inputs (PIs).

Gates – (1, 1)

 

A	Y
0	0
1	0

Constant 0

$$0 \rightarrow Y$$

$$Y = 0$$

A	Y
0	0
1	1

Buffer

$$A \rightarrowtail Y$$

$$Y = A$$

A	Y
0	1
1	0

Inverter

$$A \rightarrowtail \circ Y$$

$$Y = \bar{A}$$


A	Y
0	1
1	1

Constant 1

$$1 \rightarrowtail Y$$

$$Y = 1$$

How to Derive the Boolean Equations

 

A	Y
0	0
1	0

$$Y = \bar{A} \cdot 0 + A \cdot 0 = 0$$



$$Y = 0$$

A	Y
0	0
1	1


$$Y = \bar{A} \cdot 0 + A \cdot 1 = A$$



$$Y = A$$

A	Y
0	1
1	0
 
$$Y = \bar{A} \cdot 1 + A \cdot 0 = \bar{A}$$



$$Y = \bar{A}$$


A	Y
0	1
1	1

$$Y = \bar{A} \cdot 1 + A \cdot 1 = 1$$




$$Y = 1$$

Gates – (2, 1)

 


A	B	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	1


Gates – (2, 1)

 

A	B	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	1	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

 


Gates – (n, 1)

 

- n -input AND: $Y = A_1 \cdot A_2 \cdot \dots \cdot A_n$
- n -input NAND: $Y = \overline{A_1 \cdot A_2 \cdot \dots \cdot A_n}$
- n -input OR: $Y = A_1 + A_2 + \dots + A_n$
- n -input NOR: $Y = \overline{A_1 + A_2 + \dots + A_n}$
- n -input XOR: $Y = A_1 \oplus A_2 \oplus \dots \oplus A_n$ (1 if #1's is odd)
- n -input XNOR: $Y = \overline{A_1 \oplus A_2 \oplus \dots \oplus A_n}$ (1 if #1's is even)


Gates – (2, 2)

 

- Half-adder

A	B	S	CO
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Gates – (3, 2)

 


- Full-adder

A	B	CI	S	CO
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Gates – (n, 1)

- Multiplexer (MUX)

 


- 4:1 MUX

$$Y = \bar{S}_1 \cdot \bar{S}_0 \cdot A_0 + \bar{S}_1 \cdot S_0 \cdot A_1 + S_1 \cdot \bar{S}_0 \cdot A_2 + S_1 \cdot S_0 \cdot A_3$$

- k -bit $n:1$ MUX

Gates – (n, m)

- Demultiplexer (DEMUX)

 

- 1:4 DEMUX


S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	A
0	1	0	0	A	0
1	0	0	A	0	0
1	1	A	0	0	0

Gates – (0, 0), (0, 1), (1, 0)

- (0, 0)
 - Fill cells (used for filling white space in a layout)
 - Decap cells
 - Tap cells
 - ...
- (0, 1)
 - Constant-output cells (used to connect a signal to ground, power)
 - ...
- (1, 0)
 - Antenna cells (used to fix antenna rule violations)
 - ...


Synchronization

- Timing diagram

 


Synchronization

 - Signal path
 - A traversal
 - from a primary input to a primary output
 - from a primary input to a flip-flop
 - from a flip-flop to a primary output
 - from a flip-flop to a flip-flop
- Different signal paths have different delays.
- Signal delays are data-dependent.



Synchronization

- Timing diagram

 

Synchronization

- Timing diagram

