
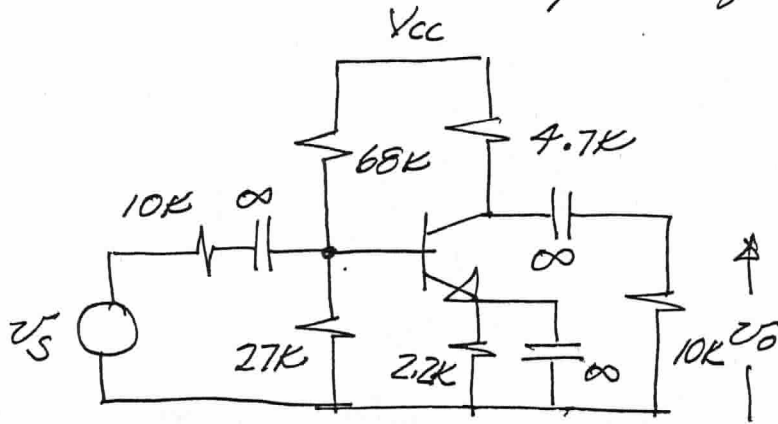


Consider the following voltage amplifier

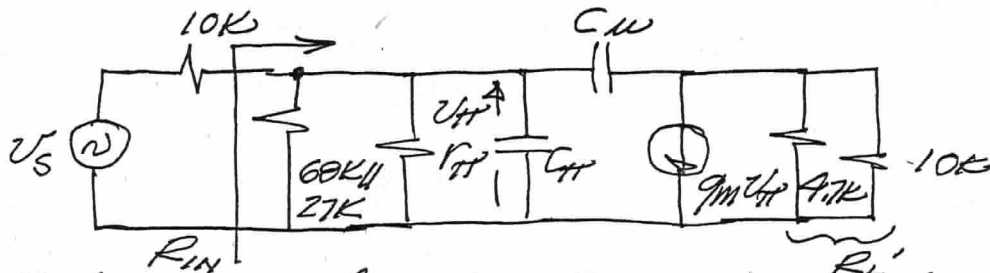

For the above circuit assume $I_C = 0.8 \text{ mA}$, $\beta = 200$, $f_T = 1 \text{ GHz}$, $C_{\mu} = 0.8 \text{ pF}$. Assume $r_o \rightarrow \infty$ and $r_x = 0$.

Draw the small-signal equivalent circuit -



Determine values for C_{μ} , C_{π} , g_m and r_{π}

$$g_m = \frac{I_C}{V_T} = \frac{0.8 \text{ mA}}{0.025 \text{ V}} = 0.032 \text{ S}, \quad r_{\pi} = \frac{\beta}{g_m} = \frac{200}{0.032} = 6.25 \text{ k}\Omega$$

$$2\pi f_T = \omega_T = \frac{g_m}{C_{\pi} + C_{\mu}}; \quad (C_{\pi} + C_{\mu}) = \frac{2\pi(10^9)}{0.032};$$

$$C_{\pi} + C_{\mu} = 5.09 \times 10^{-12}$$

If $C_{\mu} = 0.8 \text{ pF}$, then $C_{\pi} = 5.09 - 0.8 = 4.29 \text{ pF}$


Calculate R_{in}

$$R_{in} = 68 \text{ k}\Omega \parallel 27 \text{ k}\Omega \parallel 6.25 \text{ k}\Omega$$

$$R_{in} = 4.72 \text{ k}\Omega$$

$$R_{L'} = 10 \text{ k}\Omega \parallel 4.7 \text{ k}\Omega = 3.2 \text{ k}\Omega$$


Now the circuit becomes

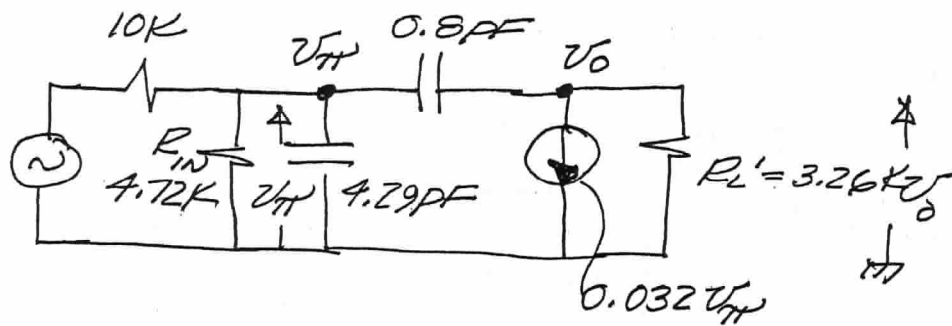

Now let $\frac{v_O}{v_H} \equiv K$ and use Miller's Theorem to reflect $C_M = 0.8 \text{ pF}$ across the input & output.

$$Z'_{IN} = \frac{Z}{1-K} \quad Z''_{OUT} = Z \left(\frac{K}{K-1} \right) \quad \text{where } Z = \frac{1}{j\omega C_M}$$
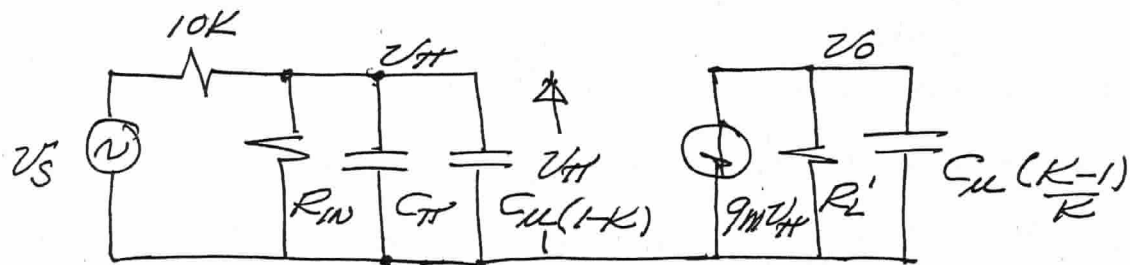
$$\therefore Z'_{IN} = \frac{1}{j\omega C_M (1-K)} \quad \text{and } Z''_{OUT} = \frac{1}{j\omega C_M} \left(\frac{K}{K-1} \right)$$



If $K \gg 1$ the $C_M \frac{K-1}{R} \ll C_M$ assume $\frac{1}{\omega C_M} \gg R_L'$ where ω is maybe 10 rad/sec . If we make this assumption and find it is valid. then $v_O = g_m v_H R_L'$.


$$\text{NOTE: for } \frac{1}{\omega C_M} = R_L' \Rightarrow \omega = \frac{1}{R_L' C_M} = \frac{1}{3.26 \times 10^3 (0.8) \times 10^{-12}}$$

$$= \frac{10^9}{2.6} = 0.38 \times 10^9 \text{ rad/sec}$$

$$f = 6 \times 10^7 \text{ Hz.}$$


With the assumption we can ignore the effects of C_u on the output, then the circuit simplifies as follows.
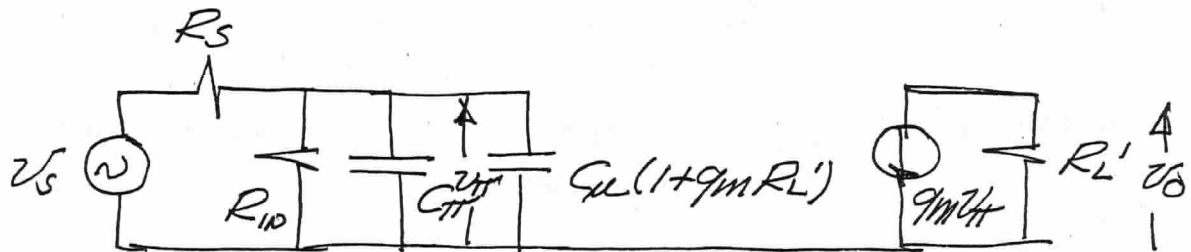
$$K = \frac{V_o}{V_{in}} = \frac{-g_m R_L' V_{in}}{V_{in}} = -g_m R_L'$$



$$\begin{aligned} \frac{V_o}{V_S} &= \frac{V_o}{V_{Th}} \cdot \frac{V_{Th}}{V_S} \\ &= \frac{-g_m R_L' V_{Th}}{V_{Th}} \cdot \frac{V_{Th}}{V_S} \end{aligned}$$

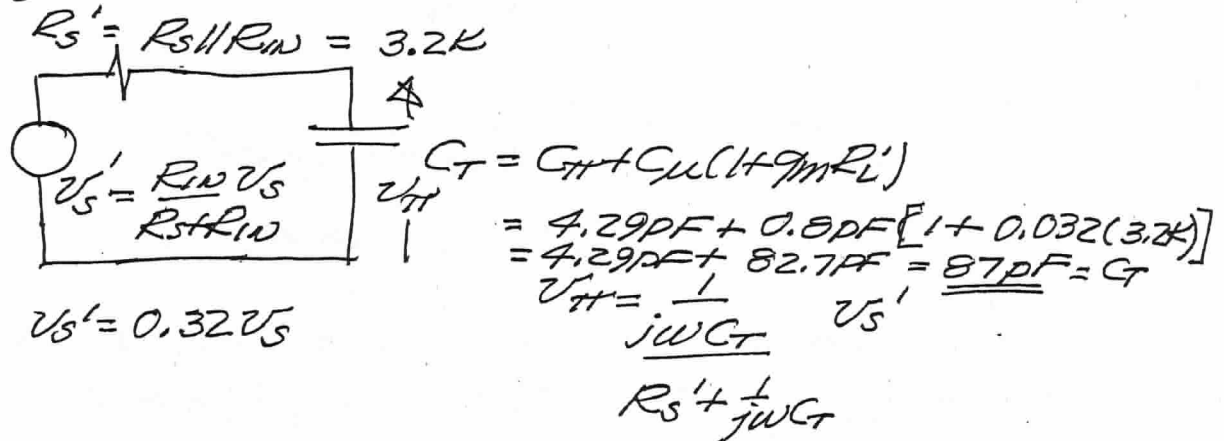For $\frac{V_{Th}}{V_S}$ use Thevenin equiv.



$$V_{Th} = \frac{1}{1 + j\omega R_S' C_T} \cdot 0.32 V_S$$

$$\frac{V_{Th}}{V_S} = \frac{0.32}{1 + j\omega R_S' C_T}$$

$$\text{Thus } \frac{V_o}{V_S} = \frac{-g_m R_L' (0.32)}{1 + j\omega R_S' C_T}$$

For $\omega=0$, the midband gain (low freq gain) is $-g_m R_L' (0.32)$

$$= -0.032 (3.2K)(0.32) = -32.8 \text{ V/V}$$

The ω_{3db} for this amp is $\frac{1}{R_S' C_T}$ as seen by

inspection of $\frac{V_o}{V_i} = \frac{-32.8}{1+j\omega R_S' C_T}$. ie that value of

ω where $\omega R_S' C_T = 1$

$$\text{Hence } \omega_{3db} = \frac{1}{R_S' C_T} = \frac{1}{3.2K \cdot 87pF}$$

$$\omega_{3db} = \frac{10^9}{278.4}$$

$$\omega_{3db} = 3.59 \times 10^6 \text{ rad/sec}$$

OR

$$f_{3db} = 5.71 \times 10^5 \text{ Hz}$$

$$\text{NOTE: } \left. \frac{1}{\omega C_{M1}} \right|_{\text{at } f_{3db}} = \frac{1}{3.59 \times 10^6 (0.8) 10^{+12}} = \frac{1}{\omega C_{M1}}$$
$$\approx \frac{10^6}{2.87} = 348 \text{ K}\Omega$$

Thus $348K \gg R_L'$ and our assumption to ignore effects of C_M on the output is a good one.

Also note: Due to the Miller effect, $C_M(1+g_m R_L') =$ which is much larger than C_T . 82.7pF

Hence \odot a small capacitor C_M affects the 3db freq. in a big way if the voltage gain (K) is high.

To conclude:

To estimate the 3dB radian frequency.
determine the effective input resistance R_s' ,
using Thevenin equivalents, determine the
total capacitance, C_T , using Miller's Theorem,
and then

$$\omega_{3db} = \frac{1}{R_s' C_T}$$