

# EE 311

Quiz1 (10pts)

August 21, 2013

Name \_\_\_\_\_

ID \_\_\_\_\_

1. A transresistance amplifier with  $R_i = 500\Omega$ ,  $R_m = 1000\frac{V}{A}$ , and  $R_o = 100\Omega$  is fed with a signal current-source,  $i_s$ , having a resistance  $R_s = 4.5K$  and is connected to a load resistance,  $R_L = 900\Omega$ .

- (5pts) a) Draw the complete circuit for the amplifier, the source and load and label all elements.

- (5pts) b) Determine the transresistance gain,  $R = \frac{v_L}{i}$  where  $v_L$  is the voltage across the  $900\Omega$  load resistor.