


EE 311

Quiz 11 (10pts)

Name _____

November 22, 2013

ID _____

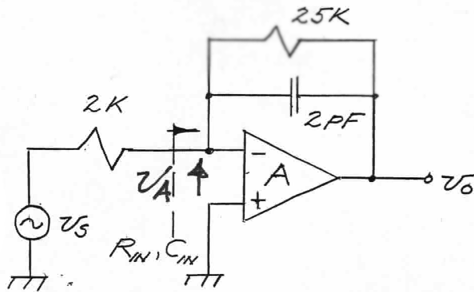

1. Consider the voltage amplifier in the circuit above to be ideal except that it has a finite gain $A = 49$. Using Miller's theorem, determine the input resistance, R_{IN} , and input capacitance, C_{IN} , at the input to the amplifier.

$R_{IN} = \text{_____} (5 \text{ pts})$

$C_{IN} = \text{_____} (5 \text{ pts})$

EXTRA CREDIT:

To find the 3_{dB} frequency for v_o/v_s , we need to know the RC time constant seen by the source, v_s . What is the value of R in the RC time constant?

$R = \text{_____} (5 \text{ pts})$