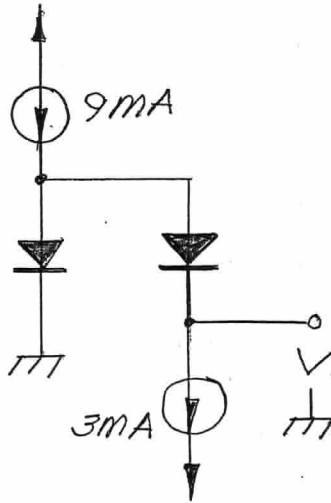


- (10pts) 1. In the circuit shown, diode,  $D_2$ , has twice the junction area of diode,  $D_1$ . Determine the value of  $V$ .



$V =$  \_\_\_\_\_